CS-200 Computer Architecture

Part 4b. Instruction Level Parallelism
Basic Pipelining

Paolo lenne <paolo.ienne@epfl.ch>

Circuit Timing and Performance


- Most of the time so far we have mainly discussed circuits at a higher level of timing abstraction: what happens every cycle
 - Finite State Machines: state <= next_state</pre>
 - Functional units and memory elements perform one operation over a small number of cycles: e.g., a combinational ALU performs an addition per cycle
- To make faster circuits, we need to zoom-in briefly and understand more of signal propagation and timing limitations

Signal Propagation


- The edge of the clock signal indicates:
 - 1. When new data can be applied to the combinational part of the circuit
 - 2. When old input data have crossed the combinational part of the circuit, the result is ready, and it can be stored at the output

 To operate circuits "as fast as we can", we apply a clock signal whose period is equal to the critical path delay (that is, the longest delay) of the circuit

Propagation Time

 


Propagation Time

 

For this circuit to operate properly, it must be


$$T_{CLK,\;comb} \geq T_{critical\;path}$$

Combinational Circuit

 

Only a small number of transistors are active (= changing state) at a given time


Adding Intermediate Registers

 

For this circuit to operate properly, it must be

$$T_{CLK, pipe} \ge T_{newcritical\ path} \cong T_{critical\ path}/3$$

 Combinatorial Circuit with Interspersed Registers



What Has Changed?


- Functionally: absolutely no change!
 - We just have a fine grain control of the propagation through the intermediate registers

- Clock can run faster
 - If we have introduced N stages of intermediate registers evenly, roughly our critical path is N times smaller
 - Clock can run N times faster!

- Great?!
 - Not really: we now need N cycles to get the result...

Multiple Operations in a Pipeline

 Inactive areas for one operation can be used for **other operations!**



Pipeline

Any Advantage Now?

- Time to compute a single operation is **roughly the same** as in the original circuit
- New results are available:
 - In the original circuit, every original period T
 - In the circuit with the registers used for a single calculation, every N cycles of period $T/N \rightarrow$ every T
 - In the circuit with the registers where we inject a new computation every cycle, we get

a new result every T/N!

We can generate arbitrarily more results (N large)?!...

Latency and Throughput


Latency

- Time between a computation begins and result is available
 - Original circuit: T
 - Pipelined circuit: T/N × N = T

Throughput

- Number of results available in the unit time
 - Original circuit: 1/T = f
 - Pipelined circuit: 1/(T/N) = N/T = N × f
- Above values only in theory...


Practical Pipelining

 


• Latency
$$\lambda_{pipe} = N \cdot \max_{i=0..N-1} (T_i + T_{FF}) = N \cdot T_{CLK, pipe} = N / f_{pipe} > \lambda_{orig}$$

• Throughput
$$\phi_{pipe} = 1/\max_{i=0..N-1} (T_i + T_{FF}) = f_{pipe}$$

 Useful Representation of the Pipeline Activity



 Pipeline Schedule Describes What Is in the Pipeline at Each Cycle



Summary

- Pipelining consists in splitting a task in smaller "subtasks", and in performing in parallel each "subtask" on a different piece of data
- **Pipelining** is an extremely general technique to **increase the throughput** of a system (circuit, processor, computer,...)
- Pipelining does not improve latency (actually worsens it!)
- Therefore, pipelining is only effective when one has to repeat a job on many pieces of data (signal processing, communication packets,... and processor instructions!)

References

- Patterson & Hennessy, COD RISC-V Edition
 - Beginning of Section 4.6