 


Timing Issues in Multi-level Logic Optimization

Giovanni De Micheli
Integrated Systems Laboratory



This presentation can be used for non-commercial purposes as long as this note and the copyright footers are not removed

© Giovanni De Micheli – All rights reserved

Module 1

◆ Objectives:

- ▲ Timing verification:
- ▲ Delay modeling
- ▲ Critical paths
- ▲ The false path problem

Timing verification and optimization

◆ Verification:

▲ Check that a circuit runs at speed

- ▼ Satisfies I/O delay constraints
- ▼ Satisfies cycle-time constraints

◆ Optimization:

▲ Minimum *delay*

- ▼ (subject to *area* constraints)

▲ Minimum *area*

- ▼ Subject to *delay* constraints

Delay modeling

◆ Gate delay modeling:

▲ Straightforward for bound networks

- ▼ Cell library models: $d = a + b \text{ Cap}$
- ▼ Cap due to fanout and wiring

▲ Approximations for unbound networks

- ▼ Virtual gates

◆ Network delay modeling:


▲ Compute signal propagation

- ▼ Topological methods
- ▼ Logic/topological methods (false paths)

Network delay modeling

- ◆ For each vertex v_i
- ◆ Propagation delay d_i :
 - ▲ I/O propagation delays are usually zero
- ◆ *Data-ready time* t_i :
 - ▲ Input data-ready time denote when inputs are available
 - ▲ Computed elsewhere by *forward traversal*
 - ▲ $t_i = d_i + \max_j t_j \quad \text{s.t. } (v_j, v_i) \in E$

Example

 

◆ Propagation delays:

▲ $d_g = 3$; $d_h = 8$; $d_m = 1$; $d_k = 10$; $d_l = 3$

▲ $d_n = 5$; $d_p = 2$; $d_p = 2$; $d_x = 2$; $d_y = 3$

Network delay modeling

◆ For each vertex v_i :

◆ Required *data-ready time* $\underline{t}_i$:

▲ Specified at the primary outputs

▲ Computed elsewhere by *backward traversal*


▲ $\underline{t}_i = \min_j \underline{t}_j - d_j \text{ s.t. } (v_i, v_j) \in E$

◆ Slack s_i :

▲ Difference between required and actual data-ready times

$$s_i = \underline{t}_j - t_i$$

Example

 

$d_n=5; d_i=3; d_k=10; d_h=8; d_g=3;$
 $d_x=2; d_y=3; d_q=2; d_m=1; d_p=2;$

◆ Required data-ready times:

▲ $\underline{t}_x = 25$ and $\underline{t}_y = 25$

Example

◆ $s_x = 2; s_y = 0$

◆ $\underline{t}_m = 25 - 2 = 23; s_m = 23 - 21 = 2$

◆ $\underline{t}_q = 25 - 3 = 22; s_q = 22 - 22 = 0$

◆ $\underline{t}_l = \min \{23 - 1; 22 - 2\} = 20; s_l = 20 - 20 = 0$

◆ $\underline{t}_h = 23 - 1 = 22; s_h = 22 - 11 = 11$

◆ $\underline{t}_k = 20 - 3 = 17; s_k = 17 - 13 = 4$

◆ $\underline{t}_p = 20 - 3 = 17; s_p = 17 - 17 = 0$


◆ $\underline{t}_n = 17 - 2 = 15; s_n = 15 - 15 = 0$

◆ $\underline{t}_b = 15 - 5 = 10; s_b = 10 - 10 = 0$


◆ $\underline{t}_g = \min \{22 - 11; 17 - 10; 17 - 2\} = 7; s_g = 7 - 3 = 4$

◆ $\underline{t}_a = 7 - 3 = 4; s_a = 4 - 0 = 4$

 $d_x=2; d_y=3; d_q=2; d_m=1; d_p=2;$
 $d_n=5; d_l=3; d_k=10; d_h=8; d_g=3;$



Example

 

Topological critical path

- ◆ Assume topologic computation of :

- ▲ *Data-ready* by forward traversal
- ▲ *Required data-ready* by backward traversal


- ◆ *Topological critical path* :

- ▲ Input/output path with zero slacks
- ▲ Any increase in the vertex propagation delay affects the output data-ready time

- ◆ A topological critical path may be *false*:

- ▲ No event can propagate along that path
- ▲ **Because of interaction of logic and topology**

Example

 

- ◆ All gates have unit delay
- ◆ All inputs ready at time 0
- ◆ Longest topological path : $(V_a, V_c, V_d, V_y, V_z)$:
 - ▲ Path delay: 4 units
- ◆ Critical true path: (V_a, V_c, V_d, V_y) :
 - ▲ Path delay: 3 units

Sensitizable paths

- ◆ A path in a logic network is *sensitizable* if an event can propagate from its tail to its head
- ◆ A critical *path* is a sensitizable path of maximum weight
- ◆ Only sensitizable paths should be considered
- ◆ Non-sensitizable paths are *false* and can be discarded

Sensitizable paths

- ◆ **Path:**

- ▲ Ordered set of vertices

- ◆ **Inputs to a vertex:**

- ▲ Direct predecessors

- ◆ **Side-inputs of a vertex:**

- ▲ Inputs not on the path

Sensitization condition

◆ Path: $P = (v_{x0}, v_{x1}, \dots, v_{xm})$


◆ An event propagates along P if :

$$\partial f_{x_i} / \partial x_{i-1} = 1, i = 1, 2, \dots, m$$

◆ Remarks :

- ▲ Boolean differences are function of the side-inputs and values on the side-inputs may change
- ▲ Boolean differences must be true *at the time that the event propagates*

Example

 

◆ Path: $(v_a, v_c, v_d, v_y, v_z)$

▲ $\partial f_y / \partial d = e = 1$ at time 2

▲ $\partial f_z / \partial y = e' = 1$ at time 3

◆ Not dynamically sensitizable because **e** settles at time 1

Modes for delay computation

◆ Transition *mode*:

- ▲ Variables assumed to hold previous values
 - ▼ Model circuit node capacitances
- ▲ *Two test vectors* are needed

◆ Floating *mode*:

- ▲ Circuit is assumed to be memoryless
 - ▼ Variables have unknown value until set by input test vector
- ▲ Need *only one* test vector

Static co-sensitization

◆ Assumption:

- ▲ Circuit modeled by *AND*, *OR*, *INV* gates
- ▲ *INV* are irrelevant to the analysis
- ▲ Floating mode

◆ Controlling values:

- ▲ 0 for *AND* gate
- ▲ 1 for *OR* gate

◆ Gate is *controlled* when controlling value is present

Static co-sensitization

- ◆ Path: $P = (v_{x0}, v_{x1}, \dots, v_{xm})$
- ◆ A vector *statically co-sensitizes* a path to 1 (or to 0) if :
 - ▲ $x_m = 1$ (or 0) and
 - ▲ v_{xi-1} has a controlling value whenever v_{xi} has a controlled value
- ◆ Necessary condition for a path to be true
- ◆ Sufficient conditions are based on the *timing* of the signal

False path detection test

◆ For all input vectors, one of the following is true:

▲ (1) A gate is controlled and

- ▼ the path provides a non-controlling value
- ▼ a side-input provides a controlling value


▲ (2) A gate is controlled and

- ▼ The path and a side-input have controlling values
- ▼ The side-input presents the controlling value first

▲ (3) A gate is not controlled and

- ▼ A side-input presents the non-controlling value last

Example

 

◆ Path: $(v_a, v_c, v_d, v_y, v_z)$

◆ For $a = 0, b = 0$:

▲ Condition (1) occurs at the OR gate

◆ For $a = 0, b = 1$:

▲ Condition (2) occurs at the AND gate

◆ For $a = 1, b = 0$:

▲ Condition (2) occurs at the OR gate

◆ For $a = 1, b = 1$:

▲ Condition (1) occurs at the AND gate

Important problems

- ◆ Check if circuit works at speed $\underline{t}$:
 - ▲ Verify that all true paths are faster than $\underline{t}$
 - ▲ Show that all paths slower than $\underline{t}$ are false
- ◆ Compute groups of false paths
- ◆ Compute critical true path:
 - ▲ Binary search for values of $\underline{t}$
 - ▲ Show that all paths slower than $\underline{t}$ are false

Summary

- ◆ **Timing optimization is crucial for achieving competitive logic design**
- ◆ **Timing optimization problems are hard:**
 - ▲ **Detection of critical paths**
 - ▼ **Elimination of false paths**
 - ▲ **Network transformations**