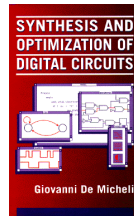


Libraries and Mapping

Giovanni De Micheli
Integrated Systems Laboratory



This presentation can be used for non-commercial purposes as long as this note and the copyright footers are not removed

© Giovanni De Micheli – All rights reserved

Module 1

◆ Objective

▲ Libraries

▲ Problem formulation and analysis

▲ Algorithms for library binding based on structural methods

Library binding

- ◆ **Given an unbound logic network and a set of library cells**
 - ▲ **Transform into an interconnection of instances of library cells**
 - ▲ **Optimize delay**
 - ▼ (under area or power constraints)
 - ▲ **Optimize area**
 - ▼ Under delay and/or power constraints
 - ▲ **Optimize power**
 - ▼ Under delay and/or area constraints
- ◆ **Library binding is called also technology mapping**
 - ▲ **Redesigning circuits in different technologies**

Major approaches

◆ Rule-based systems

- ▲ Generic, handle all types of cells and situations
- ▲ Hard to obtain circuit with specific properties
- ▲ Data base:
 - ▼ Set of pattern pairs
 - ▼ Local search: detect pattern, implement its best realization


◆ Heuristics

▲ 1

▲ L

◆ Motivation

▲ F

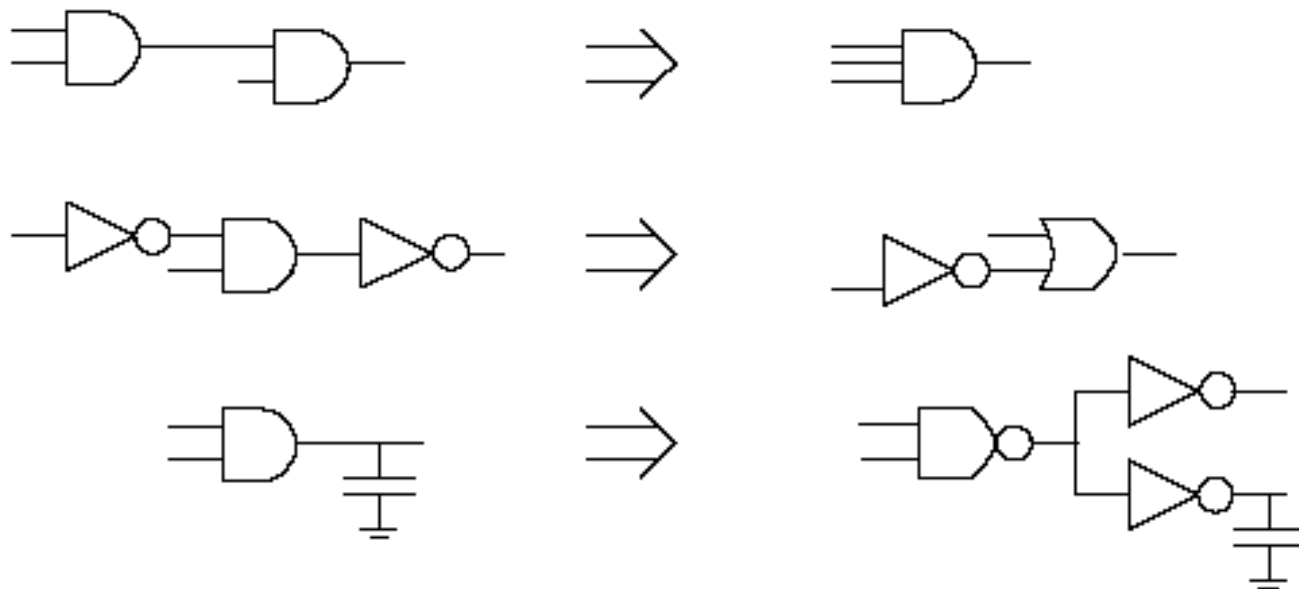

Library binding: issues

◆ Matching:

- ▲ A cell matches a sub-network when their terminal behavior is the same
- ▲ Tautology problem
- ▲ *Input-variable* assignment problem

◆ Covering:

- ▲ A cover of an unbound network is a partition into sub-networks which can be replaced by library cells
- ▲ Binate covering problem

Assumptions

- ◆ **Network granularity is fine**

- ▲ **Decomposition into base functions:**

- ▲ 2-input **AND, OR, NAND, NOR**


- ◆ **Trivial binding**

- ▲ **Use base cells to realize decomposed network**


- ▲ **There exists always a trivial binding:**

- ▼ **Base-cost solution...**


Example

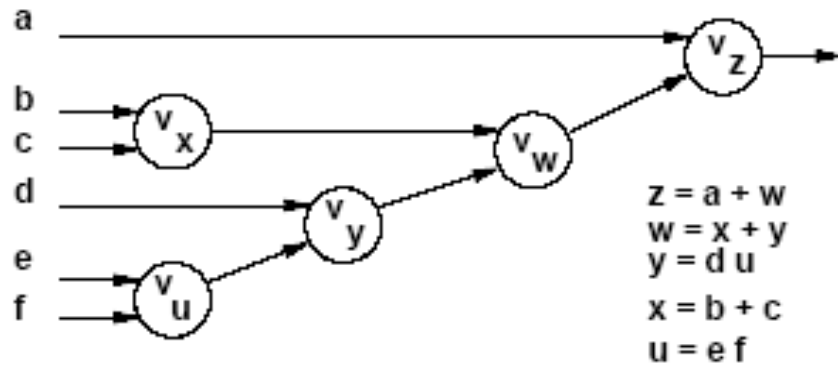


(a)

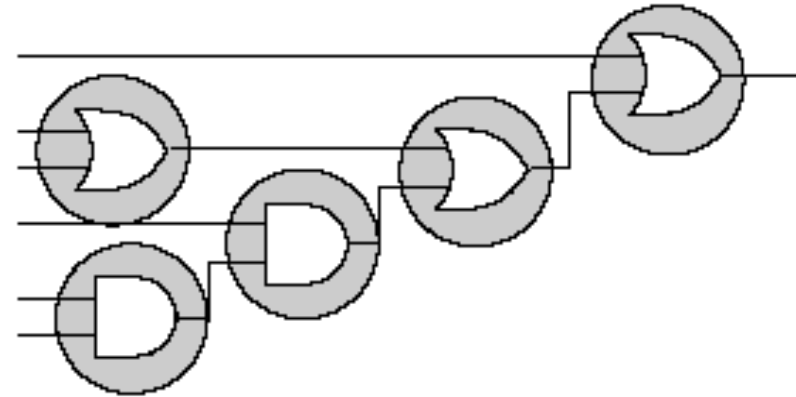

(b)


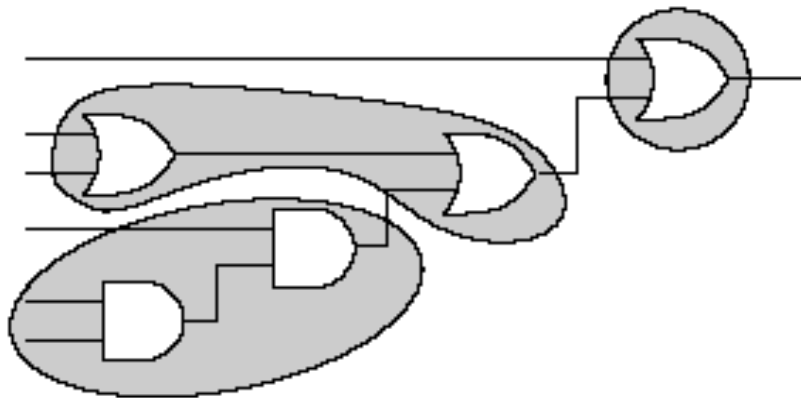


(c)

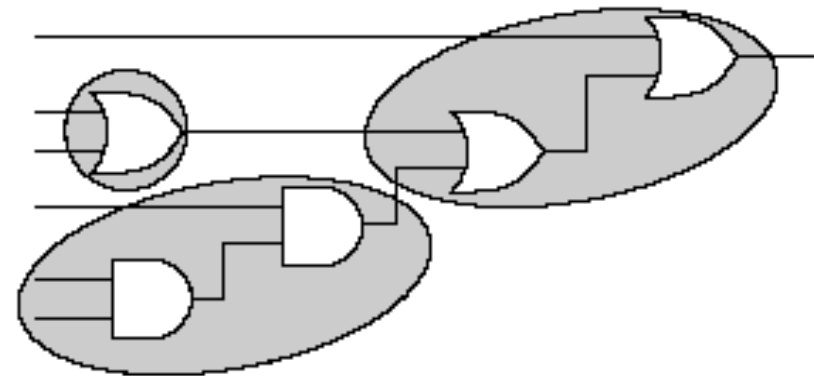

(d)



Example

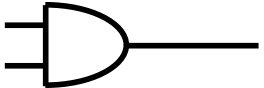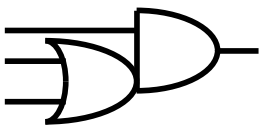Library	Cost
 AND2	4
 OR2	4
 OA21	5

$$x = b + c$$

$$y = ax$$

$$z = xd$$

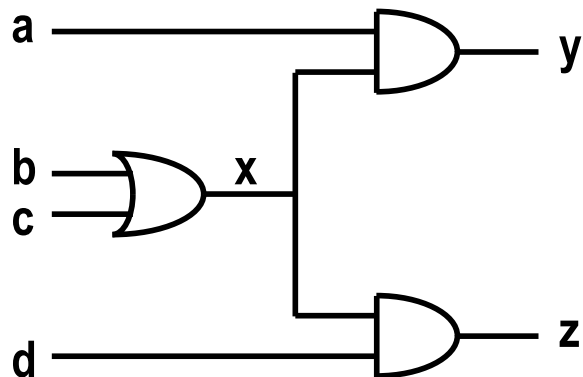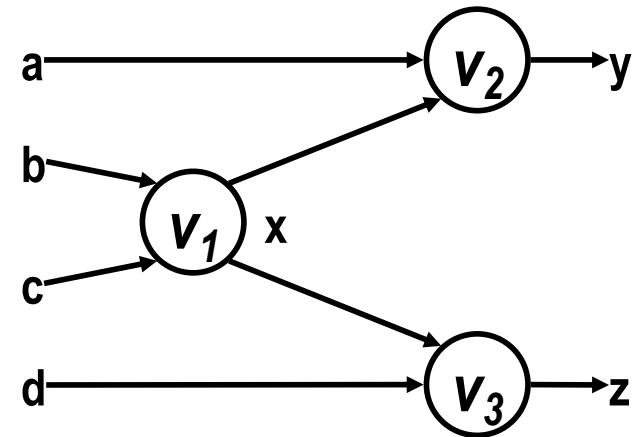


$m_1: \{v_1, \text{OR2}\}$

$m_2: \{v_2, \text{AND2}\}$

$m_3: \{v_3, \text{AND2}\}$

$m_4: \{v_1, v_2, \text{OA21}\}$

$m_5: \{v_1, v_3, \text{OA21}\}$

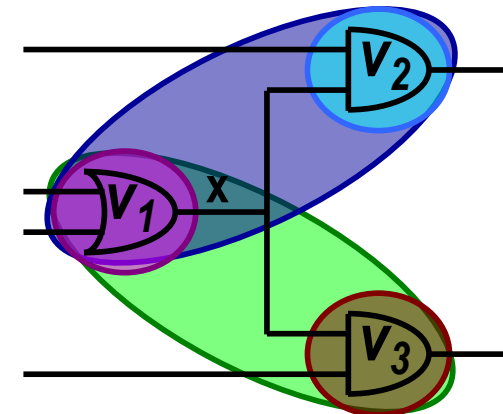

Heuristic approach to library binding

◆ Split problem into various stages:

▲ Decomposition

- ▼ Cast network and library in standard form
- ▼ Decompose into base functions
- ▼ Example, **NAND2** and **INV**

▲ Partitioning

- ▼ Break network into cones
- ▼ Reduce to many **multi-input, single-output** networks


▲ Covering

- ▼ Cover each sub-network by library cells


◆ Most tools use this strategy

▲ Sometimes stages are merged


Decomposition

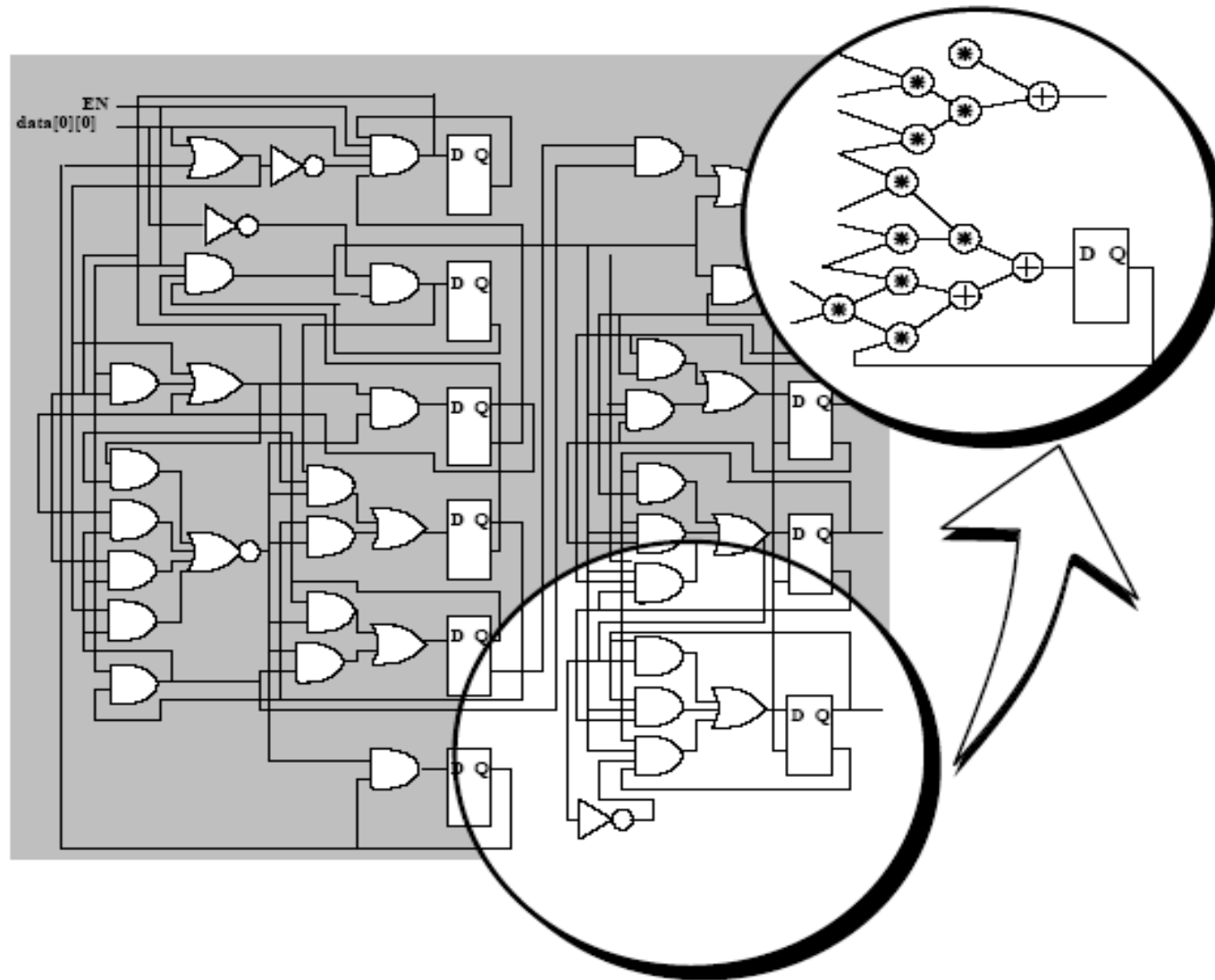

Partitioning

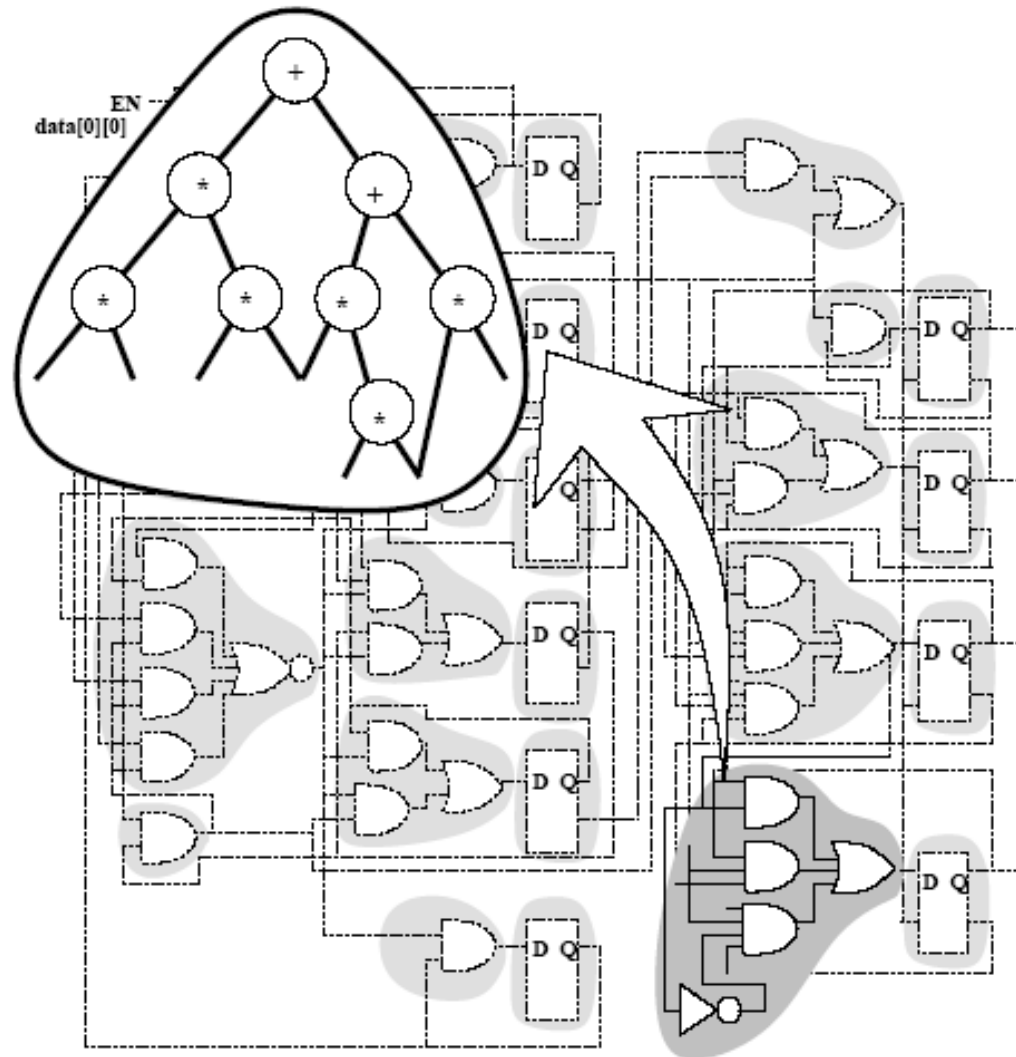

Covering

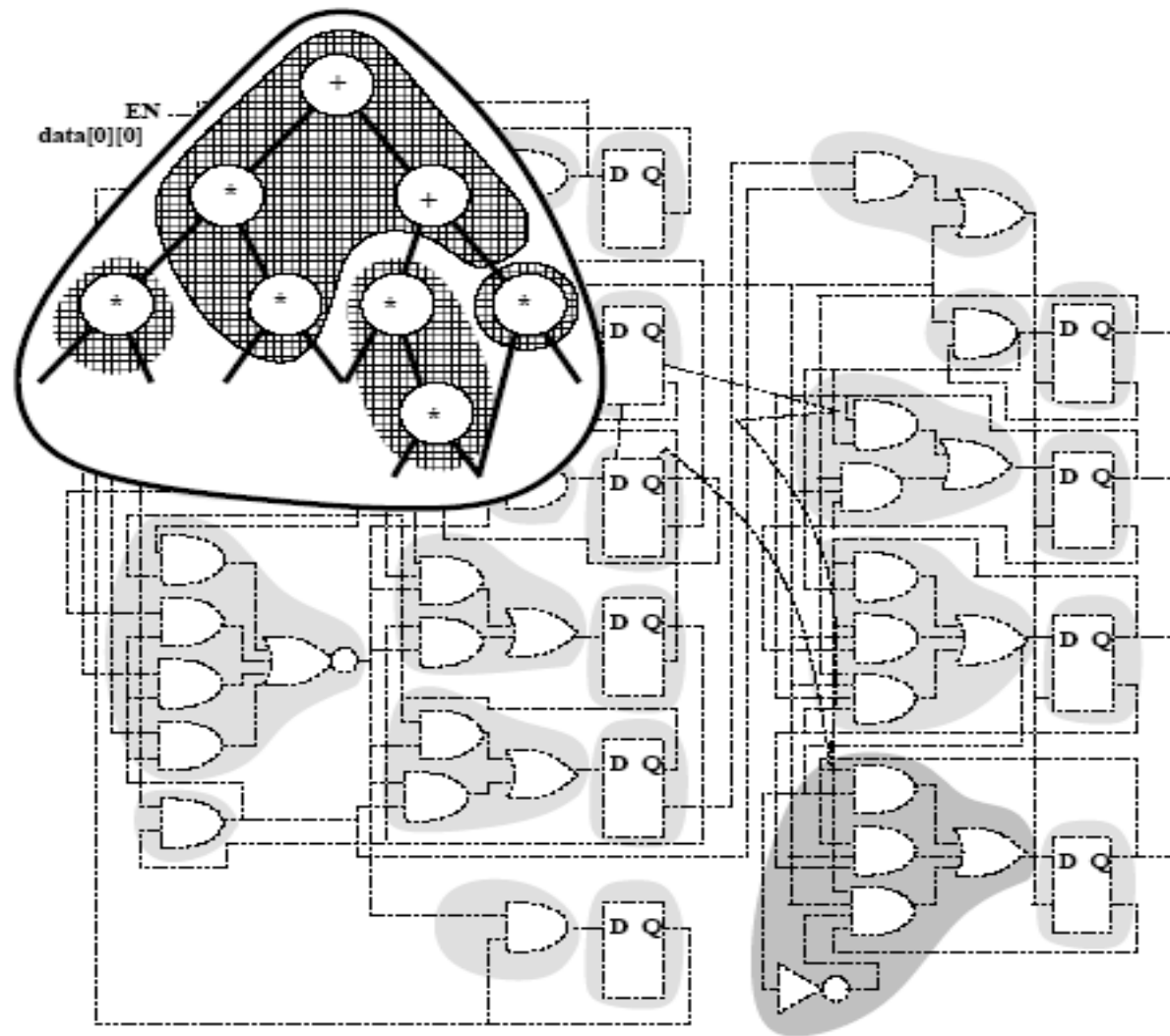

Heuristic algorithms

◆ Structural approach

▲ Model functions by patterns

▼ Example: tree, dags

▲ Rely on pattern matching techniques

◆ Boolean approach

▲ Use Boolean models

▲ Solve the tautology problem

▼ Use BDD technology

▲ More powerful

Example

◆ Boolean vs. structural matching

◆ $f = xy + x'y' + y'z$



◆ $g = xy + x'y' + xz$

◆ Function equality is a tautology





▲ Boolean match

◆ Patterns may be different

▲ Structural match may not exist

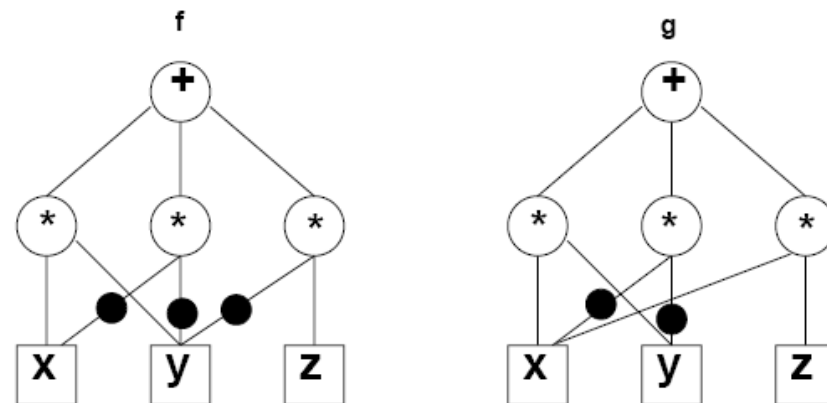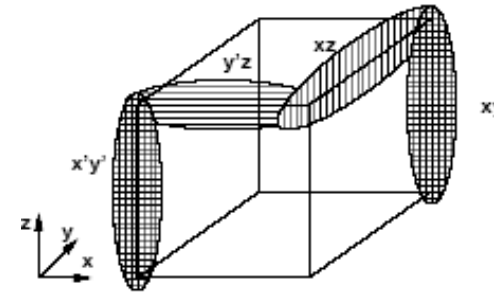


Example

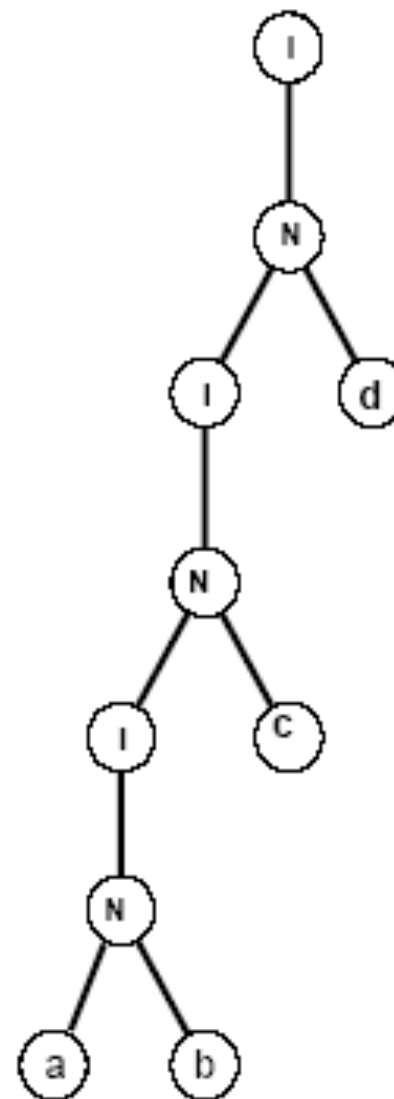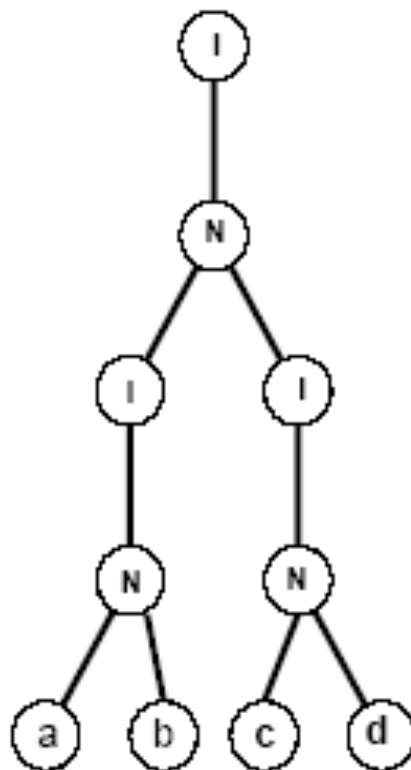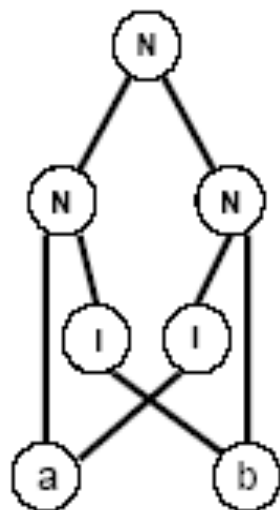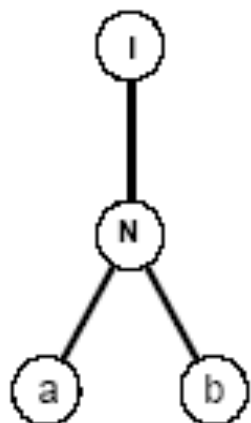

Example


SUBJECT TREE

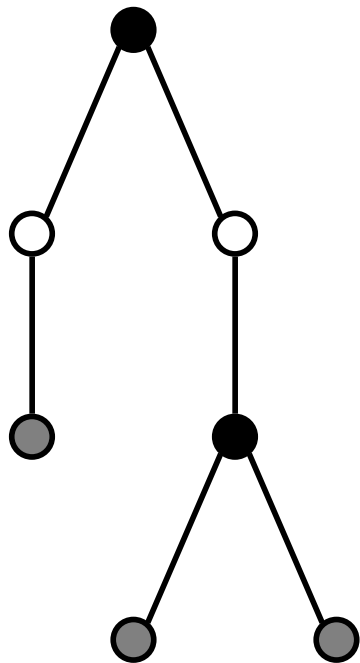


PATTERN TREES




cost = 2
INV

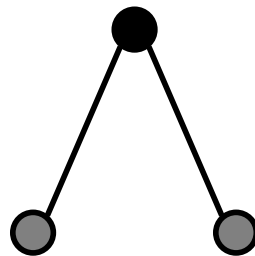

cost = 3
NAND

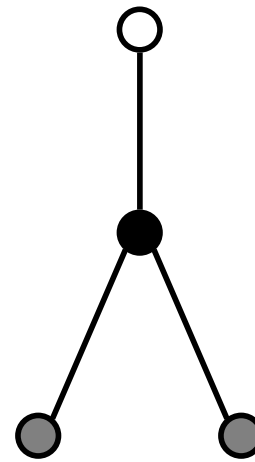


cost = 4
AND

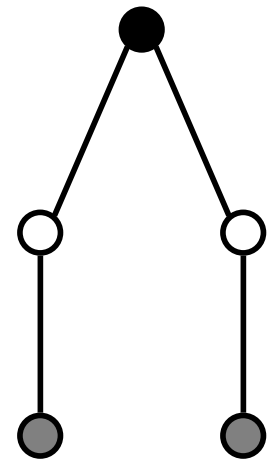

cost = 5
OR

Example: Lib

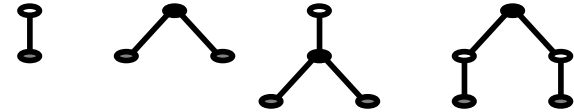

Match of s: t1
cost = 2






Match of t: t1
cost = 2+3 = 5

Match of t: t3
cost = 4

Match of r: t2
cost = 3+2+4 = 9

Match of r: t4
cost = 5+3 = 8

Match of u: t2
cost = 3

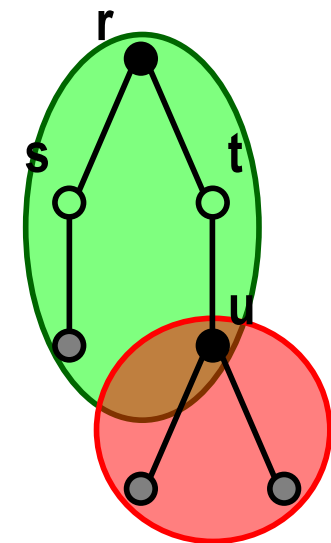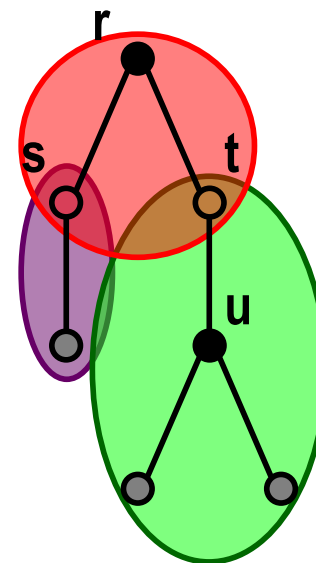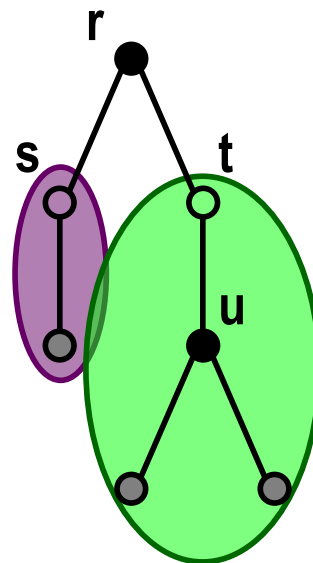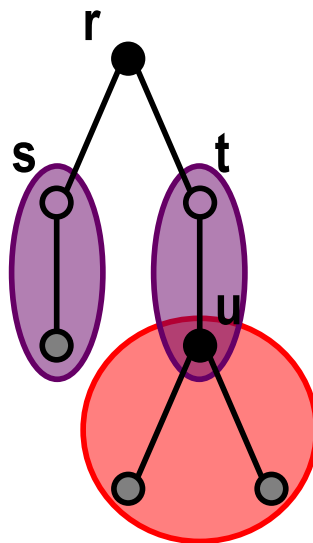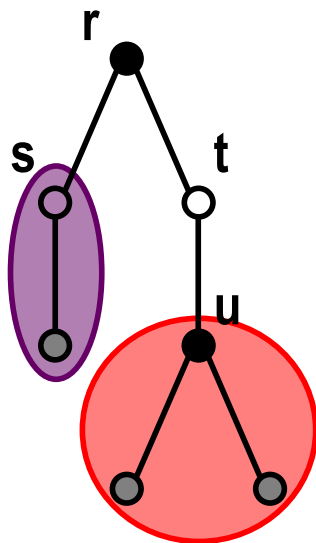

Tree covering

- ◆ **Dynamic programming**

- ▲ Visit subject tree bottom up

- ◆ **At each vertex**

- ▲ **Attempt to match:**

- ▼ Locally rooted subtree to all library cell
 - ▼ Find best match and record

- ▲ There is always a match when the base cells are in the library

- ◆ **Bottom-up search yields and optimum cover**

- ◆ **Caveat:**

- ▲ Mapping into trees is a distortion for some cells
 - ▲ Overall optimality is weakened by the overall strategy of splitting into several stages

Different covering problems

◆ Covering for minimum area:

- ▲ Each cell has a fixed area cost (label)

- ▲ Area is additive:

 - ▼ Add area of match to cost of sub-trees

◆ Covering for minimum delay:

- ▲ Delay is fanout independent


 - ▼ Delay computed with (max, +) rules

 - ▼ Add delay of match to highest cost of sub-trees

- ▲ Delay is fanout dependent



 - ▼ Look-ahead scheme is required

Simple library

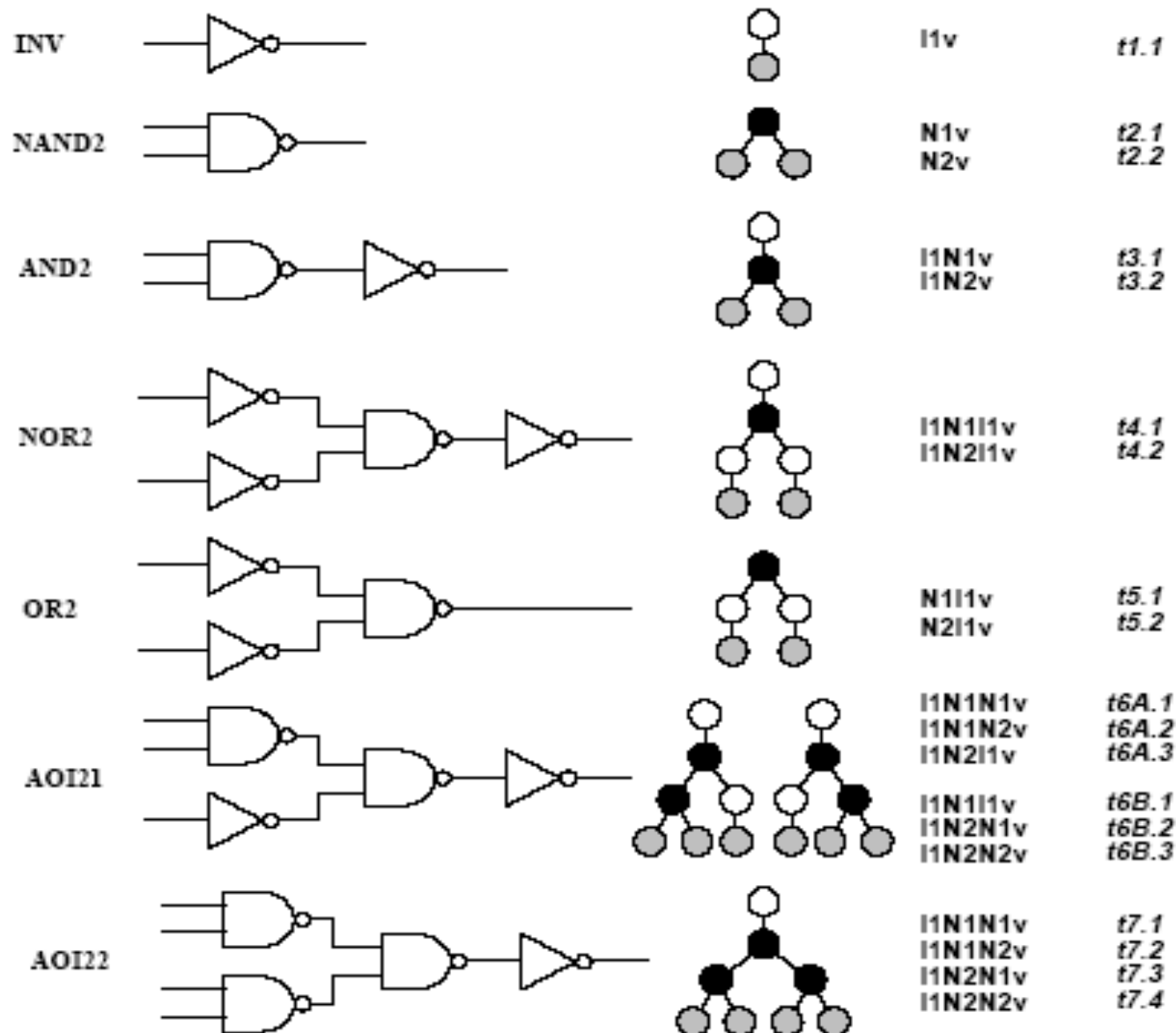

Example – minimum area cover

◆ Area cost: INV:2 NAND2:3 AND2: 4 AOI21: 6

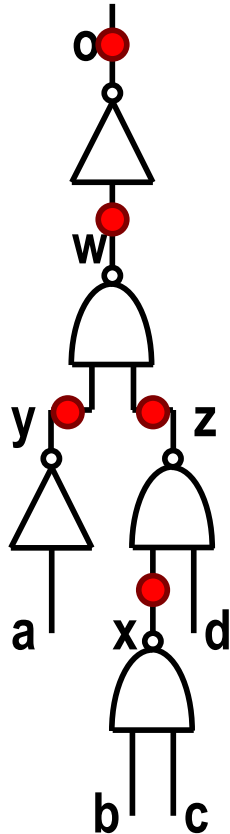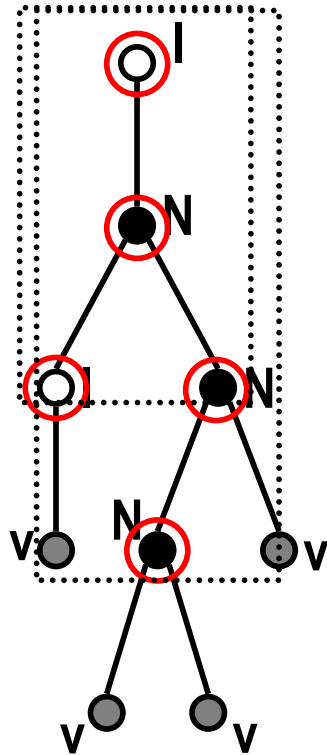Network	Subject graph	Vertex	Match	Gate	Cost
		x	t2	NAND2(b,c)	3
		y	t1	INV(a)	2
		z	t2	NAND2(x,d)	$3+3 = 6$
		w	t2	NAND2(y,z)	$3+6+ 2 = 11$
		o	t1	INV(w)	$2+11 = 13$
			t3	AND2(y,z)	$6 + 4 + 2 = 12$
			t6B	AOI21(x,d,a)	$6 + 3 = 9$

Example – minimum delay cover

- ◆ Fixed delays: **INV:2** **NAND2:4** **AND2: 5** **AOI21: 10**
- ◆ All inputs are stable at time 0, except for $t_d = 6$

Network	Subject graph	Vertex	Match	Gate	Cost
		x	t2	NAND2(b,c)	4
		y	t1	INV(a)	2
		z	t2	NAND2(x,d)	6+4 = 10
		w	t2	NAND2(y,z)	10 + 4 = 14
		o	t1	INV(w)	14 + 2 = 16
			t3	AND2(y,z)	10 + 5 = 15
			t6B	AOI21(x,d,a)	10 + 6 = 16

Minimum-delay cover for load-dependent delays

◆ Model

- ▲ Gate delay is $d = \alpha + \beta \text{ cap_load}$
- ▲ Capacitive load depends on the driven cells (fanout cone)
- ▲ There is a finite (possibly small) set of capacitive loads

◆ Algorithm

- ▲ Visit subject tree bottom up
- ▲ Compute an array of solutions for each possible load
- ▲ For each input to a matching cell, the best match for the corresponding load is selected



◆ Optimality

- ▲ Optimum solution when all possible loads are considered
- ▲ Heuristic: group loads into bins

Example – minimum delay cover

- ◆ Delays: **INV**:1+load **NAND2**: 3+load **AND2**: 4+load **AOI21**: 9+load
- ◆ All inputs are stable at time 0, except for $t_d = 6$
- ◆ All loads are 1



Same as before !

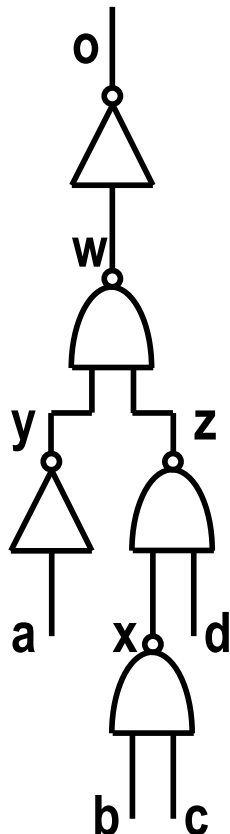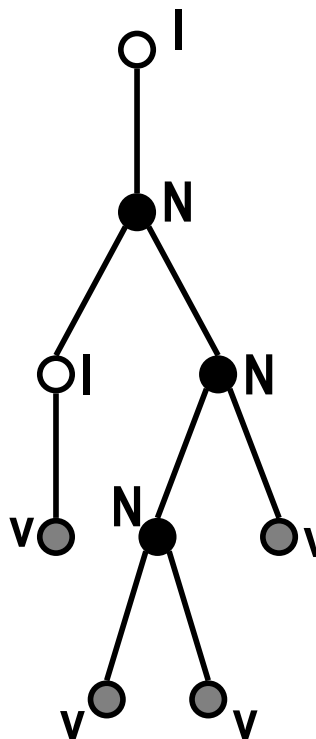Network	Subject graph	Vertex	Match	Gate	Cost
		x	t2	NAND2(b,c)	4
		y	t1	INV(a)	2
		z	t2	NAND2(x,d)	6+4 = 10
		w	t2	NAND2(y,z)	10 + 4 = 14
		o	t1	INV(w)	14 + 2 = 16
			t3	AND2(y,z)	10 + 5 = 15
			t6B	AOI21(x,d,a)	10 + 6 = 16

Example – minimum delay cover

- ◆ Delays: **INV**: $1 + \text{load}$ **NAND2**: $3 + \text{load}$ **AND2**: $4 + \text{load}$ **AOI21**: $9 + \text{load}$
- ◆ All inputs are stable at time 0, except for $t_d = 6$
- ◆ All loads are 1 (for cells seen so far)
- ◆ Add new cell **SINV** with delay $1 + \frac{1}{2} \text{load}$ and load 2
- ◆ The sub-network drives a load of 5

Example – minimum delay cover

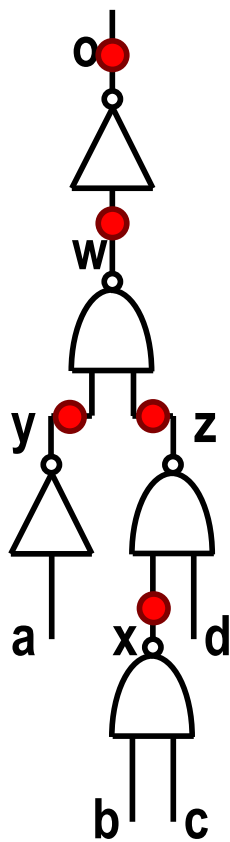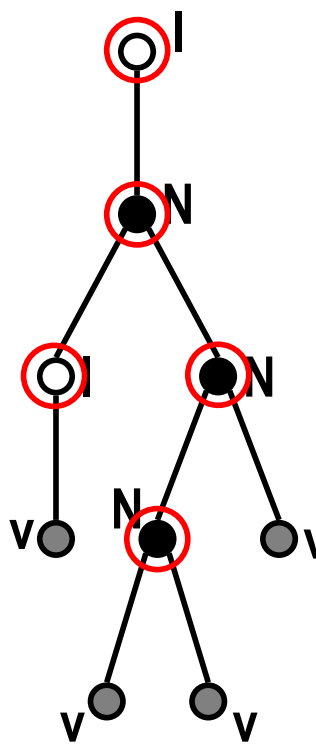Network	Subject graph	Vertex	Match	Gate	Cost		
					Load=1	Load=2	Load=5
		x	t2	NAND2(b,c)	4	5	8
		y	t1	INV(a)	2	3	6
		z	t2	NAND2(x,d)	10	11	14
		w	t2	NAND2(y,z)	14	15	18
		o	t1	INV(w)			20
			t3	AND2(y,z)			19
			t6B	AOI21(x,d,a) SINV(w)			20 18.5


Module 2

◆ Objectives

- ▲ Boolean covering
- ▲ Boolean matching
- ▲ Simultaneous optimization and binding
- ▲ Extensions to Boolean methods

Boolean covering

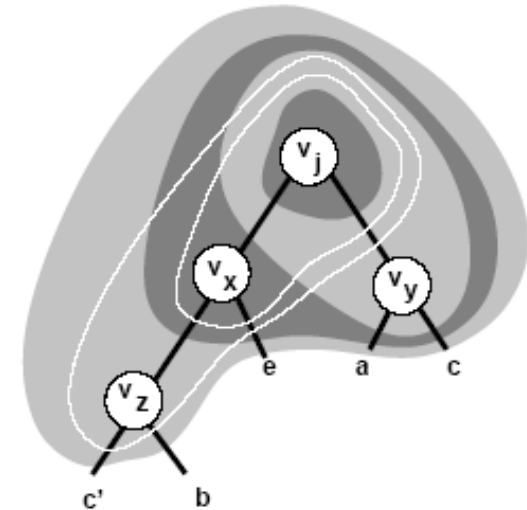- ◆ Decompose network into base functions
- ◆ Partition network into cones
- ◆ Apply bottom-up covering to each cone
 - ▲ When considering vertex v :
 - ▼ Construct clusters by local elimination
 - ▼ Limit the depth of the cluster by limiting the support of the function
 - ▼ Associate several functions with vertex v
 - ▼ Apply matching and record cost



$$\begin{aligned}f_{j,1} &= xy; \\f_{j,2} &= x(a + c); \\f_{j,3} &= (e + z)y; \\f_{j,4} &= (e + z)(a + c); \\f_{j,5} &= (e + c' + d)y; \\f_{j,6} &= (e + c' + d)(a + c); \end{aligned}$$

Boolean matching

P -equivalence

◆ Cluster function $f(x)$

- ▲ Sub-network behavior

◆ Pattern function $g(y)$

- ▲ Cell behavior

◆ P -equivalence

- ▲ Is there a permutation operator P , such that $f(x) = g(Px)$ is a tautology?

◆ Approaches:

- ▲ Tautology check over all input permutations
- ▲ Multi-rooted pattern ROBDD capturing all permutations

Input/output polarity assignment

- ◆ ***NPN*** classification of logic functions

- ◆ ***NPN***-equivalence

- ▲ There exist a permutation operator ***P*** and complementation operators ***N_i*** and ***N_o***, such that $f(x) = N_o g (P N_i x)$ is a tautology

- ◆ **Variations:**

- ▲ ***N***-equivalence


- ▲ ***PN***-equivalence

Boolean matching

◆ Pin assignment problem:


▲ Map cluster variables x to pattern variables y

▲ Characteristic equation: $A(x,y) = 1$

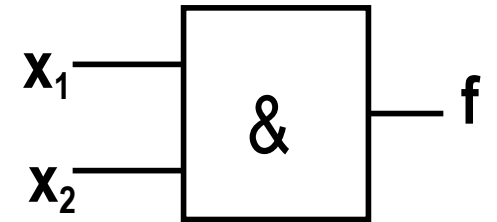

◆ Pattern function under variable assignment:

▲ $g_A(x) = S_y (A(x,y) g(y))$

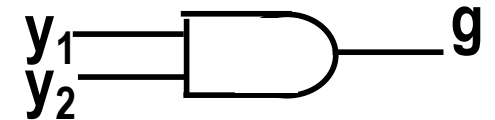

◆ Tautology problem

▲ $f(x) = g_A(x)$

▲ $\forall_x f(x) = S_y (A(x,y) g(y))$

Example

◆ Cluster terminals: x -- cell terminals: y

◆ Assign x_1 to y'_2 and x_2 to y_1

◆ Characteristic equation


$$\blacktriangle A(x_1, x_2, y_1, y_2) = (x_1 \oplus y_2) (x_2 \overline{\oplus} y_1)$$

◆ AND pattern function

$$\blacktriangle g = y_1 y_2$$

◆ Pattern function under assignment
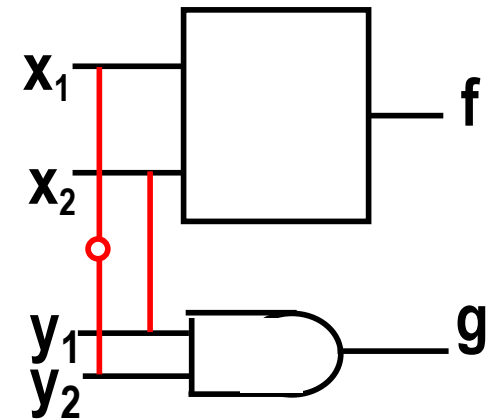
$$\blacktriangle S_{y_1 y_2} A g = S_{y_1 y_2} ((x_1 \oplus y_2) (x_2 \overline{\oplus} y_1) y_1 y_2) = x_2 x'_1$$



Signatures and filters

- ◆ Capture some properties of Boolean functions
- ◆ If signatures do not match, there is no match
- ◆ Signatures are used as filters to reduce computation
- ◆ Signatures:
 - ▲ Unateness
 - ▲ Symmetries
 - ▲ Co-factor sizes
 - ▲ Spectra

Filters based on unateness and symmetries

- ◆ Any pin assignment must associate:

- ▲ Unate variables in $f(x)$ with unate variables in $g(y)$

- ▲ Binate variables in $f(x)$ with binate variables in $g(y)$

- ◆ Variables or group of variables:

- ▲ That are interchangeable in $f(x)$ must be interchangeable in $g(y)$

Example

◆ Cluster function: $f = abc$

- ▲ Symmetries $\{ \{ a,b,c \} \}$

- ▲ Unate

◆ Pattern functions

- ▲ $g_1 = a + b + c$

 - ▼ Symmetries $\{ \{ a,b,c \} \}$

 - ▼ Unate

- ▲ $g_2 = ab + c$

 - ▼ Symmetries $\{ \{ a,b \}, \{ c \} \}$

 - ▼ Unate

- ▲ $g_3 = abc' + a' b' c$

 - ▼ Symmetries $\{ \{ a,b,c \} \}$

 - ▼ Binate

Concurrent optimization and library binding


◆ Motivation

- ▲ Logic simplification is usually done prior to binding
- ▲ Logic simplification and substitution can be combined with binding

◆ Mechanism

- ▲ Binding induces some *don't care* conditions
- ▲ Exploit *don't cares* as degrees of freedom in matching

Example

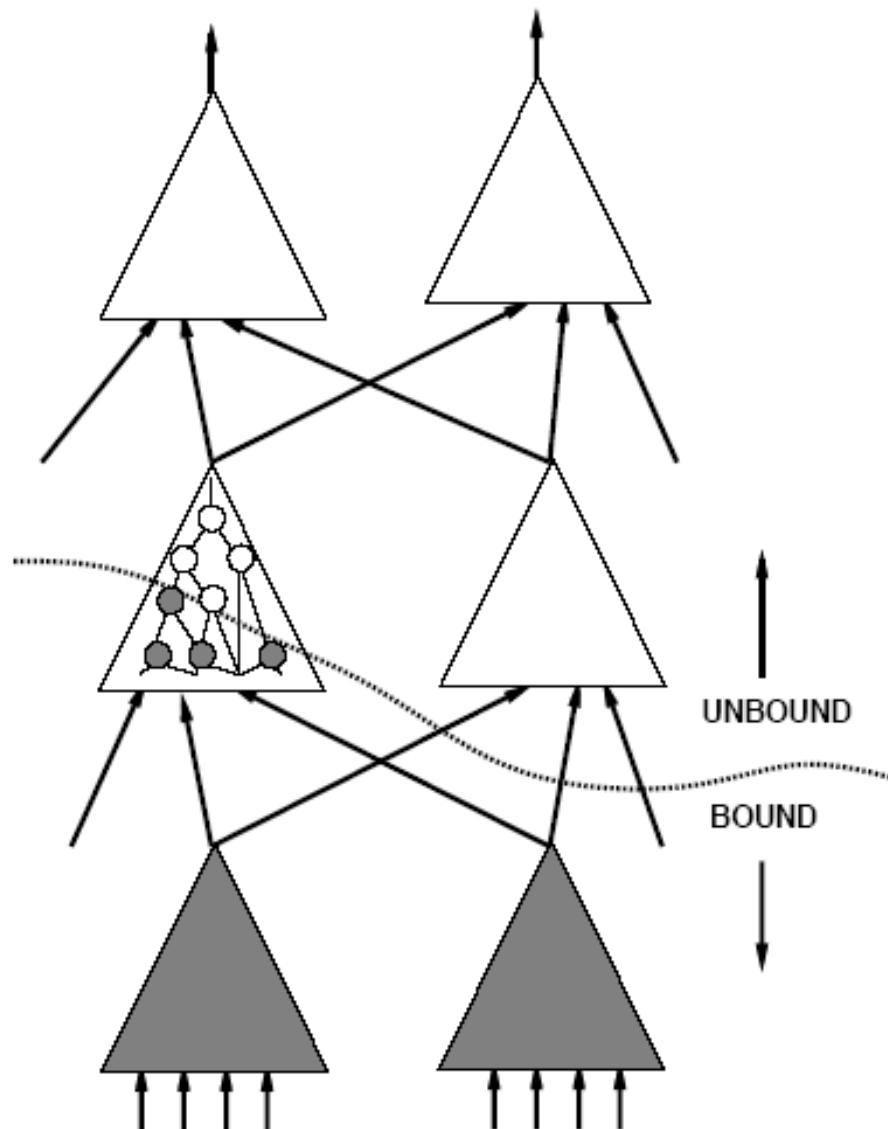

Boolean matching with *don't care* conditions

◆ Given $f(x)$, $f_{DC}(x)$ and $g(y)$

▲ g matches f , if g is equivalent to h , where:




$$f \oplus f_{DC} \leq h \leq f + f_{DC}$$

◆ Matching condition:



$$\forall_x (f_{DC}(x) + f(x) \oplus S_y (A(x,y) g(y)))$$

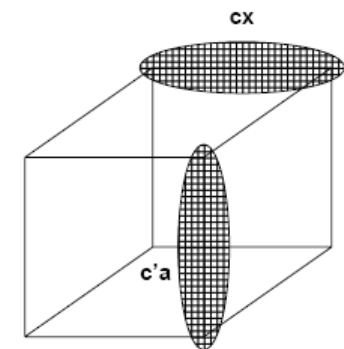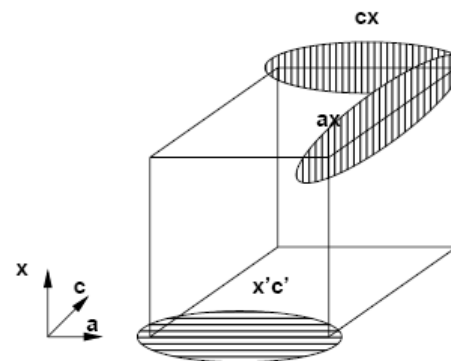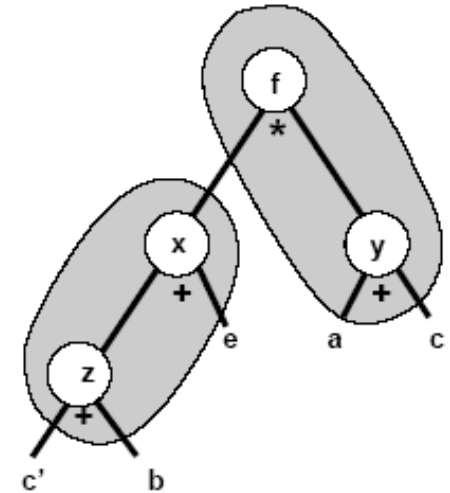Example

- ◆ Assume v_x is bound to an $OR3(c', b, e)$
- ◆ Don't care set includes $x \oplus (c' + b + e)$
- ◆ Consider $f_j = x(a + c)$ with $CDC = x'c'$
- ◆ No simplification.
 - ▲ Mapping into AOI gate.
- ◆ Matching with DCs.
 - ▲ Map to a MUX gate.



Example

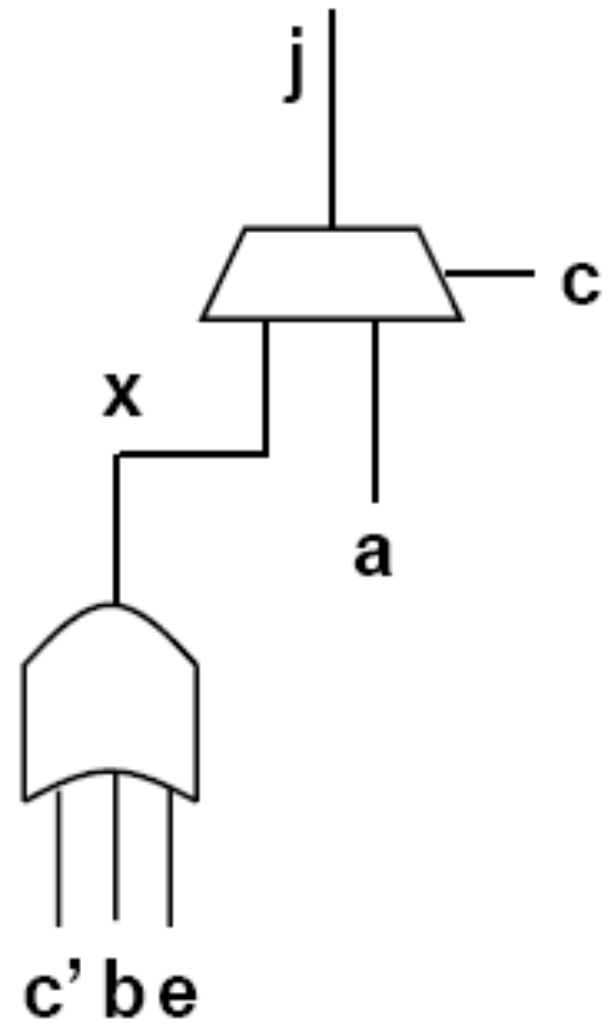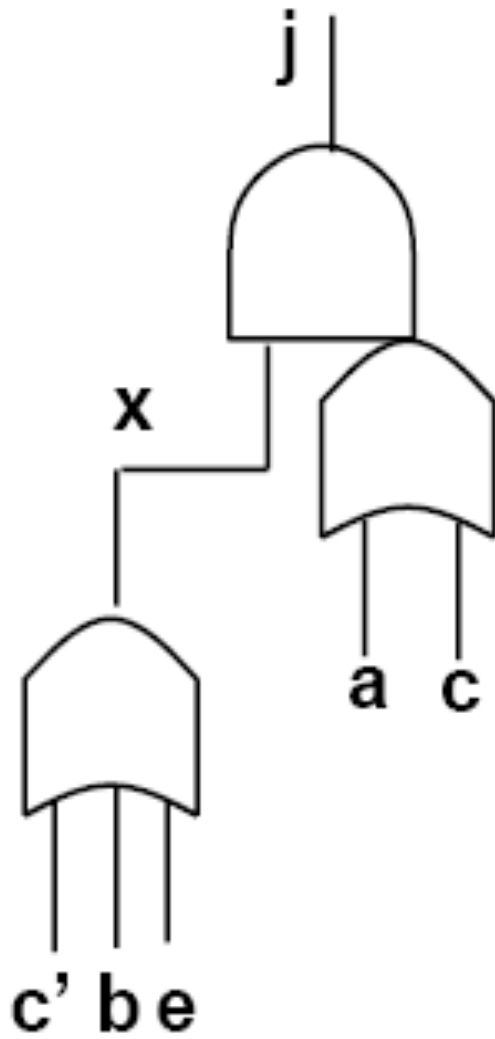

Extended matching

◆ Motivation:

- ▲ Search implicitly for best pin assignment
- ▲ Make a single test, determining matching and assignment

◆ Technique:

- ▲ Construct BDD model of cell and assignments

◆ Visual intuition:

- ▲ Imagine to place **MUX** function at cell inputs
- ▲ Each cell input can be routed to any cluster input (or voltage rail)
- ▲ Input polarity can be changed:
 - ▼ NP-equivalence (extensible to NPN)
- ▲ Cell and cluster may differ in size

◆ Cell and multiplexers are described by a composite function **$G(x,c)$**

- ▲ Pin assignment is determining **c**


Example

◆ $g = y_1 + y_2 y'_3$

◆ $y_1(c,x) = (c_0 c_1 x_1 + c_0 c'_1 x_2 + c'_0 c_1 x_3) \oplus c_2$

◆ $G = y_1(c,x) + y_2(c,x) y_3(c,x)'$

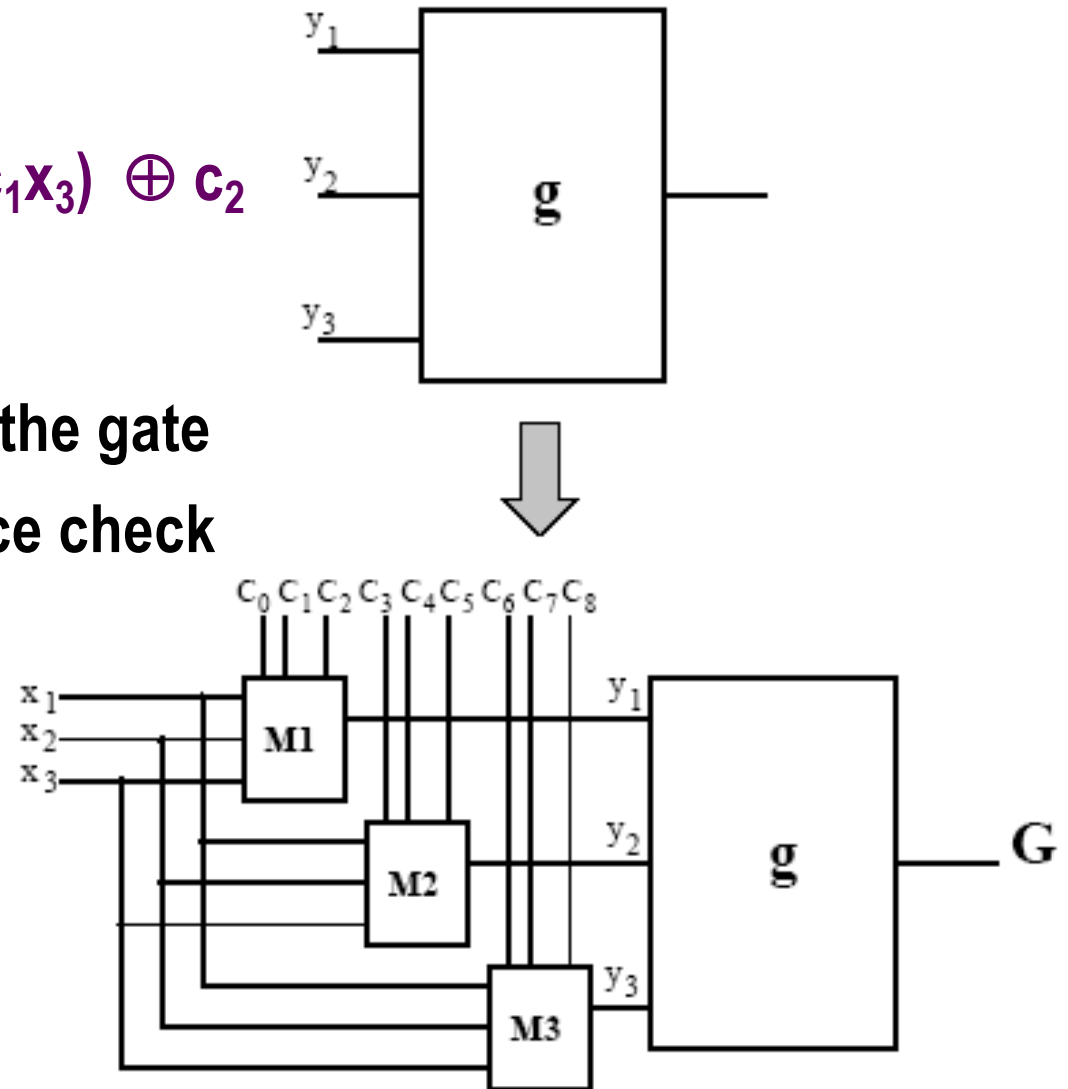◆ An EXOR gate can be placed at the gate output to support NPN-equivalence check



Extended matching modeling

◆ Model composite functions with ROBDDs

- ▲ Assume n -input cluster and m -input cell

- ▲ For each cell input:

 - ▼ $\lceil \log_2 n \rceil$ variables for pin permutation

 - ▼ One variable for input polarity

- ▲ Total size of c : $m(\lceil \log_2 n \rceil + 1)$

- ▲ One additional variable for output polarity


◆ A match exists if there is at least one value of c satisfying

$$M(c) = \forall_x [G(x,c) \oplus f(x)]$$

Example

◆Cell: $g = x' y$


◆Cluster: $f = wz'$

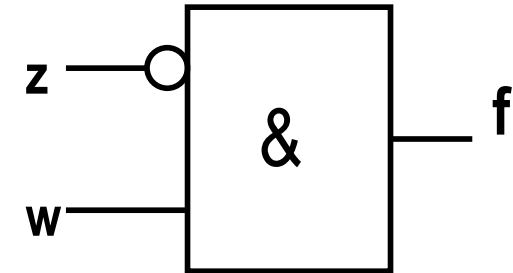

◆ $G(a,b,c,d) = (c \oplus (za + wa'))' (d \oplus (zb + wb'))$

◆ $F \oplus G = (wz) \oplus (c \oplus (za + wa'))' (d \oplus (zb + wb'))$

◆ $M(c) = ab'c'd' + a'bcd$

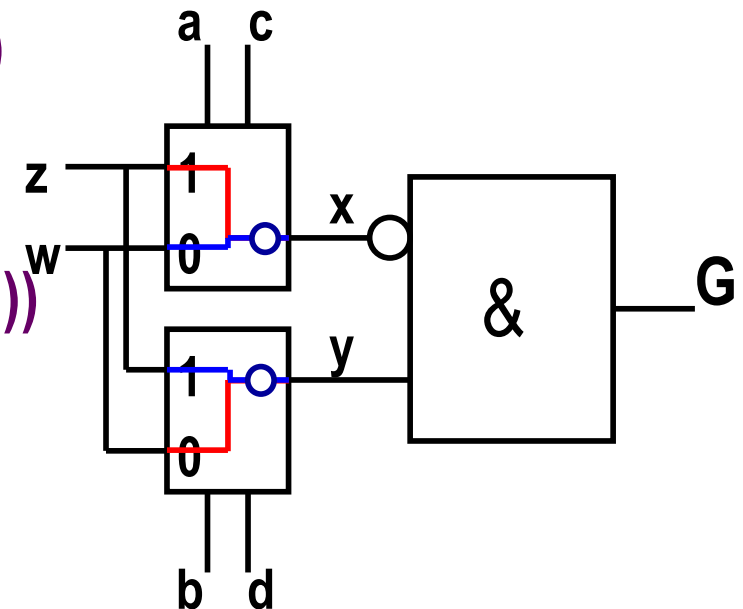

Extended matching

- ◆ Extended matching captures implicitly all possible matches
- ◆ No extra burden when exploiting *don't care* sets
- ◆ $M(c) = \forall_x [G(x,c) \oplus f(x) + f_{DC}(x)]$
- ◆ Efficient BDD representation
- ◆ Extensions:
 - ▲ Support multiple-output matching
 - ▲ Full library representation

Full library model

- ◆ Represent full library with $L(x,c)$

- ▲ One single (large) BDD

- ◆ Visual intuition


- ▲ All composite cells connected to a MUX

- ◆ Compare cluster to library $L(x,c)$

- ▲ $M(c) = \forall_x [L(x,c) \oplus f(x) + f_{DC}(x)]$

- ▲ Vector c determines:

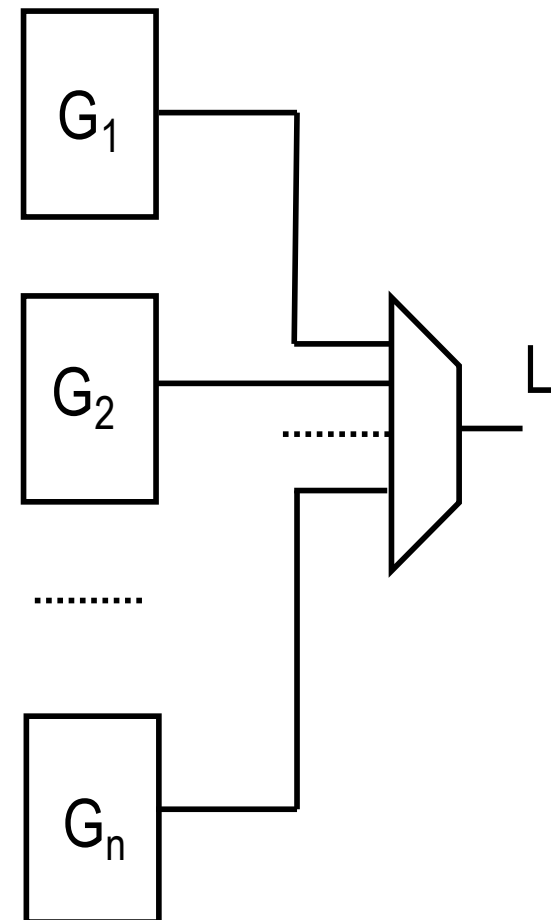- ▼ Feasible cell matches
 - ▼ Feasible pin assignments
 - ▼ Feasible output polarity



Summary

- ◆ **Library binding is a key step in synthesis**
- ◆ **Most systems use some rules together with heuristic algorithms that concentrate on combinational logic**
 - ▲ **Best results are obtained with Boolean matching**
 - ▲ **Sometimes structural matching is used for speed**
- ◆ **Library binding is tightly linked to buffering and to physical design**