

CS-472: Design Technologies for Integrated Systems

Exercise Problem Set 10 Solution

Date: 28/11/2024

Topic: Boolean methods (cf. slide set 12)

Problem 1

Consider the logic network where inputs are $\{a, b, c, d\}$ and output is $\{f\}$ defined as:

$$k = ad$$

$$n = c + k$$

$$m = \overline{ab}$$

$$f = m + n$$

Assuming $CDC_{in} = ab$, compute CDC_{out} .

cf: Algorithm in textbook p.385

Ans:

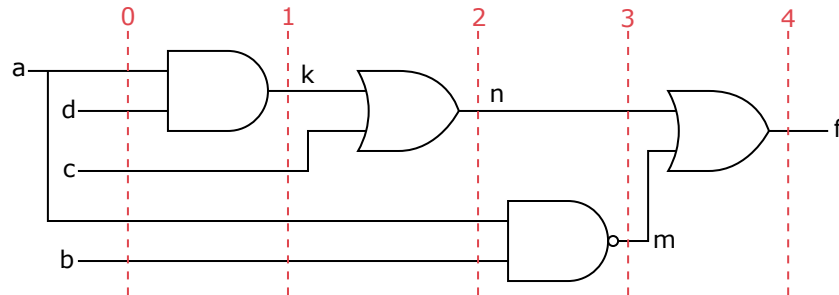


Figure 1: Cuts in the logic circuit during CDC computation

Figure ?? shows some possible successive *cuts* of the network that we will use to compute the CDC_{out} by network traversal. The CDC computation for each cut proceeds as follows:

0. $CDC_{in} = ab$

1. $CDC_{cut} = ab + (ad \oplus k)$

drop d: $(ab + (a \oplus k)) \cdot (ab + k) = ab + \bar{a}k$ ($\{a = 1, b = 1\}$ and $\{a = 0, k = 1\}$ will not happen)

2. $CDC_{cut} = ab + \bar{a}k + ((c + k) \oplus n)$

drop k: $(ab + \bar{a} + \bar{n}) \cdot (ab + (c \oplus n)) = ab + c\bar{n} + \bar{a}\bar{c}n$

drop c: $(ab + \bar{n}) \cdot (ab + \bar{a}n) = ab$

3. $CDC_{cut} = ab + (\overline{ab}) \oplus m$
 drop a : $(b + (\bar{b} \oplus m)) \cdot \bar{m} = \bar{m}$
 drop b : $\bar{m}$
4. $CDC_{cut} = \bar{m} + ((m + n) \oplus f)$
 drop m : $\bar{f}$
 drop n : $\bar{f}$
 $CDC_{cut} = \bar{f}$

Output f is always 1 since m can never be 0.

Problem 2

Consider the logic network from Problem 1. Compute the ODC sets for all internal and input vertices assuming that the output is fully observable.

cf: Algorithm in textbook p.390

Ans:

$$\begin{array}{ll}
 \frac{\partial(m+n)}{\partial m} = n \oplus 1 = \bar{n}, & ODC_m = n = ad + c \\
 \frac{\partial(m+n)}{\partial n} = m \oplus 1 = \bar{m}, & ODC_n = m = \bar{a}\bar{b} \\
 \frac{\partial(c+k)}{\partial k} = c \oplus 1 = \bar{c}, & ODC_k = c + m = c + \bar{a}\bar{b} \\
 \frac{\partial(c+k)}{\partial c} = k \oplus 1 = \bar{k}, & ODC_c = k + m = ad + \bar{a}\bar{b} \\
 \frac{\partial(ad)}{\partial d} = 0 \oplus a = a, & ODC_d = \bar{a} + c + m = \bar{a} + \bar{b} + c \\
 \frac{\partial(\overline{ab})}{\partial b} = 1 \oplus \bar{a} = \bar{a}, & ODC_b = \bar{a} + n = \bar{a} + ad + c
 \end{array}$$

Signal a has two fanouts: $\{k, m\}$ cf: p. 392

$$\begin{array}{ll}
 \frac{\partial(ad)}{\partial a} = 0 \oplus d = d, & ODC_{a,k} = \bar{d} + c + m = \bar{a} + \bar{b} + c + \bar{d} \\
 \frac{\partial(\overline{ab})}{\partial a} = 1 \oplus \bar{b} = \bar{b}, & ODC_{a,m} = \bar{b} + n = ad + \bar{b} + c
 \end{array}$$

$$\begin{aligned}
 ODC_a &= ODC_{a,k}|_{a=\bar{a}} \oplus ODC_{a,m} \\
 &= (a + \bar{b} + c + \bar{d}) \oplus (ad + \bar{b} + c) \\
 &= (\bar{a}\bar{b}\bar{c}d) \oplus (ad + \bar{b} + c) \\
 &= \bar{b} + c + d
 \end{aligned}$$