

CS-472: Design Technologies for Integrated Systems

Exercise Problem Set 10

Date: 21/11/2024

Topic: Boolean methods for multi-level logic synthesis (cf. slide set 12)

Problem 1

Consider the logic network where inputs are $\{a, b, c, d\}$ and output is $\{f\}$ defined as:

$$k = ad$$

$$n = c + k$$

$$m = \overline{(ab)}$$

$$f = m + n$$

Assuming $CDC_{in} = ab$, compute CDC_{out} .

Problem 2

Consider the logic network from Problem 1. Compute the ODC sets for all internal and input vertices assuming that the output is fully observable.