

CS-472: Design Technologies for Integrated Systems

Exercise Problem Set 11

Date: 5/12/2024

Topics: Timing analysis & retiming (cf. slide sets 13 & 14)

Problem 1

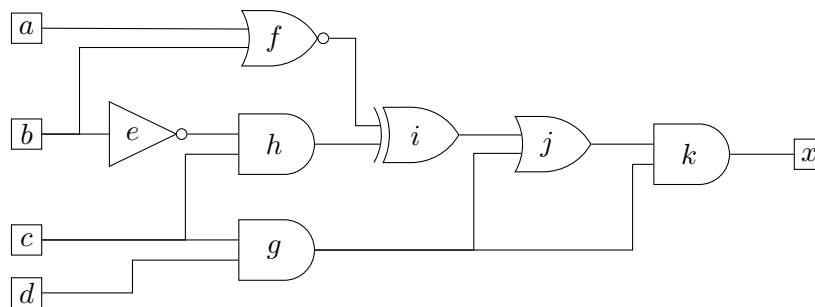


Figure 1: Combinational logic network.

Consider the network in Fig. 1: The inputs are $\{a, b, c, d\}$ and the output is x . The data ready time for all the inputs is 0, and the inputs are stable after time 0. Assume the following delays for logic gates:

INV gate: $t_d = 1$ ns;
AND gate: $t_d = 1$ ns;
OR/NOR/XOR gate: $t_d = 2$ ns.

- (a) The data required time for the output x is 7 ns. Find all the topological critical paths.
- (b) Is the path (b, e, h, i, j, k, x) a true critical path?

Problem 2

 


Figure 2: Sequential logic network.

Consider the network in Fig. 2, where the rectangles are registers. Assume the following delays for logic gates:

AND gate: $t_d = 3$ ns;

OR gate: $t_d = 4$ ns;

XOR gate: $t_d = 5$ ns.

- Draw the synchronous network graph, where weights of vertices are the combinational delays of the logic gates, and weights of the edges are the numbers of registers between two vertices.
- What is the minimum cycle time currently (before retiming)?
- Draw the constraint graph modeling to search for a legal retiming with a cycle time of 12 ns.
- To find a retiming solution, apply the Bellman-Ford Algorithm on the constraint graph using r_a as the source (compute the longest distance from r_a to each vertex).
- Redraw the retimed synchronous network graph using the retiming vector $\vec{r}$ obtained in (d). Verify that the targeted cycle time 12 ns is met.