

Constructive Computer Architecture:


# Non-Pipelined Processors

Thomas Bourgeat – EPFL

Slides Prepared with Arvind – 6.1920 spring  
2023
 
# Single-Cycle RISC Processor

As an illustrative example, we use a subset of RISC-V 32-bit ISA.



Datapath (arrows in this diagram) are conceptual; the real datapaths are derived automatically from the Bluespec description

# RISC-V Register States

## ◆ 32 general purpose registers (GPR)

- x0, x1, ..., x31
- 32-bit wide integer registers
- x0 is hard-wired to zero

## ◆ Program counter (PC)

- 32-bit wide

## ◆ CSR (Control and Status Registers)

- mcycle
- minstret
- mhartid
- mtohost
- ...

We will not  
deal with  
CSRs in this  
subject

# Single-Cycle Implementation

```
module mkProcessor(Empty);
  Reg#(Word)  pc <- mkReg(0);
  RFile2R1W   rf <- mkRFile2R1W;
  MagicMemory iMem <- mkMagicMemory;
  MagicMemory dMem <- mkMagicMemory;
  rule doProcessor;
    let inst <- iMem.req(MemReq{op:Ld, addr:pc, data:dwv});
    let dInst = decode(inst);
    // dInst fields: iType, aluFunc, brFunc, dst, src1, src2, imm
    let rVal1 = rf.rd1(dInst.src1);
    let rVal2 = rf.rd2(dInst.src2);
    let eInst = execute(dInst, rVal1, rVal2, pc);
    // eInst fields: iType, dst, data, addr, nextPC
    updateState(eInst, pc, rf, dMem);
  endrule
endmodule
```

instantiate the state

extracts the fields

read the register file


computes values needed to update the processor state

actions to update the processor state

# Every BSV program serves two purposes

- ◆ It is a description from which a compiler can synthesize a hardware circuit
- ◆ Like any program, it is a description which can be executed to produce an answer
  - For example, the Single-cycle implementation can be simulated in software to execute any RISC-V program
 
# Understanding generated hardware (the real datapath)



```
let rVal1 = rf.rd1(dInst.src1);  
let rVal2 = rf.rd2(dInst.src2);
```

- ◆ Not all instructions have both `src1` and `src2` fields but there is no harm/cost in reading unused registers; we never use results of undefined fields
- ◆ When the same function is called with two different arguments, a mux is generated automatically

# Understanding generated hardware - *continued*

```
case (iType)
  OP: data = alu(rVal1, rVal2, aluFunc);
  OPIMM: data = alu(rVal1, imm, aluFunc);
  ...
  LOAD: begin addr = rVal1+imm; nextPc = pc+4; end
  STORE: begin addr = rVal1+imm; data = rVal2;
          nextPc = pc+4; end ...
```

- ◆ How many alu circuits?
  - The two uses of alu are mutually exclusive, so the BSV compiler/backend tools should share the same alu circuit;
  - Can address calculation use the same alu?
- ◆ Reuse is not necessarily a good idea because it prevents specialization
  - The circuit for pc+4 has a lot fewer gates than the circuit for pc+imm

*Generally, we don't concern ourselves with the sharing of combinational circuits*


# Instruction Decoding

- ◆ An instruction can be executed only after each of its fields has been extracted
  - Fields are needed to access the register file, compute address to access memory, supply the proper opcode to ALU, set the pc, ...
- ◆ Some 32-bit values may not represent an instruction or may represent an instruction not supported by our implementation
- ◆ Many instructions differ only slightly from each other in both decoding and execution

Unlike RISC-V, some instruction sets are extremely complicated to decode, e.g., Intel X86

# Decoding instructions

## An Example

 

- ◆ What RISC-V instruction is represented by these 32 bits?
- ◆ Reference manual specifies the fields as follows:
  - opcode = 0110011    => opCode Op, R-type encoding
  - funct3 = 000        => ADD
  - rd = 00011         => x3
  - rs1 = 00010        => x2
  - rs2 = 00001        => x1
- ◆ What is the meaning of executing this instruction?

```
rf.wr(3, alu(rf.rd1(2), rf.rd2(1), Add)); pc<=pc+4;
```


# Decoding Instructions:

extract fields needed for execution

Maybe type  
allows marking  
as valid or  
invalid

instruction  
Bit#(32)

 pure combinational  
logic: derived  
automatically from  
the high-level  
description



# Decoded Instruction Type

```
typedef struct {  
    IType  
    AluFunc  
    BrFunc  
    Maybe#(RIndx) dst;  
    Maybe#(RIndx) src1;  
    Maybe#(RIndx) src2;  
    Maybe#(Data) imm;  
} DecodedInst deriving(Bits, Eq);
```

Destination  
register 0 behaves  
like an Invalid  
destination

Instruction groups  
with similar  
executions paths

```
typedef enum {Unsupported, Alu, Ld, St, J, Jr, Br, Auipc}
```

```
IType deriving(Bits, Eq);
```

```
typedef enum {Add, Sub, And, Or, Xor, Slt, Sltu, Sll, Sra,  
Srl} AluFunc deriving(Bits, Eq);
```

```
typedef enum {Eq, Neq, Lt, Ltu, Ge, Geu, AT, NT} BrFunc  
deriving(Bits, Eq);
```

# Internal names for various opcode and funct3 patterns

// opcode

Bit#(7) opOpImm = 7'b0010011; // OP-IMM

Bit#(7) opOp = 7'b0110011; // OP

Bit#(7) opLui = 7'b0110111; // LUI

Bit#(7) opAuipc = 7'b0010111; // AUIPC

Bit#(7) opJal = 7'b1101111; // JAL

Bit#(7) opJalr = 7'b1100111; // JALR

Bit#(7) opBranch = 7'b1100011; // BRANCH

Bit#(7) opLoad = 7'b0000011; // LOAD

Bit#(7) opStore = 7'b0100011; // STORE

// funct3

Bit#(3) fnADD = 3'b000; // ADD

Bit#(3) fnSLL = 3'b001; // SLL

Bit#(3) fnSLT = 3'b010; // SLT .....

names given by us

Names and associated values are specified in the RISC-V ISA

# Decode Function

```

function DecodedInst decode(Bit#(32) inst);
  let opcode = inst[ 6 : 0 ];
  let rd      = inst[ 11 : 7 ];
  let funct3  = inst[ 14 : 12 ];
  let rs1     = inst[ 19 : 15 ];
  let rs2     = inst[ 24 : 20 ];
  let aluSel  = inst[ 30 ]; // Add/Sub, Srl/Sra
  Bit#(32)immI=...; Bit#(32)immS=...; Bit#(32)immB=...;
  Bit#(32)immU=...; Bit#(32)immJ=...; // I/S/B/U/J-imm
  DecodedInst dInst = ?;
  case (opcode)
    opOp
    ...
  endcase
  return dInst;
endfunction

```

initially  
undefined



# Decoding Instructions

```
case (opcode)
  opOpImm: ...
  opOp: ...
  opLui: ...
  opAuipc: ...
  opJal: ...
  opJalr: ...
  opBranch: ...
  opLoad: ...
  opStore: ...
  default: ... // Unsupported
endcase
```

```
// opcode
Bit#(7) opOpImm = 7'b0010011;
Bit#(7) opOp    = 7'b0110011;
Bit#(7) opLui   = 7'b0110111;
Bit#(7) opAuipc = 7'b0010111;
Bit#(7) opJal   = 7'b1101111;
Bit#(7) opJalr  = 7'b1100111;
Bit#(7) opBranch = 7'b1100011;
Bit#(7) opLoad  = 7'b0000011;
Bit#(7) opStore = 7'b0100011;
```

# Decoding Instructions: Computational Instructions

```
opOpImm: begin
    dInst.iType = Alu;
    dInst.aluFunc = case (funct3)
        fnAND: And;
        fnSLTU: Sltu;
        ...
        fnADD: Add;
        fnSR: aluSel == 0 ? Srl : Sra;
    endcase;
    dInst.brFunc = NT;
    dInst.dst = Valid rd;
    dInst.src1 = Valid rs1;
    dInst.src2 = Invalid;
    dInst.imm = Valid ImmI;
end
```

Decoding instructions  
with immediate operand  
(i.e., opcode = OP-IMM)  
is similar

# Decoding Instructions: Unconditional Jumps

opJal: begin

```
dInst.iType = J;  
dInst.aluFunc = ?;  
dInst.brFunc = AT;  
dInst.dst = Valid rd;  
dInst.src1 = Invalid;  
dInst.src2 = Invalid;  
dInst.imm = Valid immJ;
```

Jump to pc+offset

end

opJalr: begin

```
dInst.iType = Jr;  
dInst.aluFunc = ?;  
dInst.brFunc = AT;  
dInst.dst = Valid rd;  
dInst.src1 = Valid rs1;  
dInst.src2 = Invalid;  
dInst.imm = Valid immI;
```

Jump indirect through  
register

end

# Decoding Instructions: Conditional Branch

```
opBranch: begin
  Maybe#(BrFunc) brF =
    case(func3)
    fnBEQ: Valid Eq;
    ...
    fnBGEU: Valid Geu;
    default: Invalid;
  endcase;
  dInst.iType = isValid(brF) ? Br : Unsupported;
  dInst.aluFunc = ?;
  dInst.brFunc = fromMaybe(?, brF);
  dInst.dst = Invalid;
  dInst.src1 = Valid rs1;
  dInst.src2 = Valid rs2;
  dInst.imm = Valid immB;
end
```


# Decoding Instructions: Load & Store

```
opLoad: begin // only support LW
    dInst.iType = funct3 == fnLW ? Ld : Unsupported;
    dInst.aluFunc = Add; // calc effective addr
    dInst.brFunc = NT;
    dInst.dst = Valid rd;
    dInst.src1 = Valid rs1;
    dInst.src2 = Invalid;
    dInst.imm = Valid immI;
end
opStore: begin // only support SW
    dInst.iType = funct3 == fnSW ? St : Unsupported;
    dInst.aluFunc = Add; // calc effective addr
    dInst.brFunc = NT;
    dInst.dst = Invalid;
    dInst.src1 = Valid rs1;
    dInst.src2 = Valid rs2;
    dInst.imm = Valid immS;
end
```

# Decoding instructions: Unsupported

```
default: begin
    dInst.iType = Unsupported;
    dInst.aluFunc = ?;
    dInst.brFunc = NT;
    dInst.dst = Invalid;
    dInst.src1 = Invalid;
    dInst.src2 = Invalid;
    dInst.imm = Invalid;
end
```
 
# Reading Registers and Executing Instructions



# Output type of exec function

```
typedef struct {  
    IType          iType;  
    Maybe#(RIndx)  dst;  
    Data           data;  
    Addr           addr;  
    Bool           brTaken;  
} ExecInst deriving(Bits, Eq);
```

# Execute Function

```
function ExecInst exec(DecodedInst dInst, Data rVal1, Data rVal2,
                      Addr pc);

  ExecInst eInst = ?;
  Data aluVal2 = fromMaybe(rVal2, dInst.imm);

  let aluRes = alu(rVal1, aluVal2, dInst.aluFunc);
  eInst.iType = dInst.iType;
  eInst.data = dInst.iType==St? rVal2 :
               (dInst.iType==J || dInst.iType==Jr)? (pc+4):
               dInst.iType==Auipc ?
               (pc+fromMaybe(?, dInst.imm)) : aluRes;

  eInst.brTaken = aluBr(rVal1, rVal2, dInst.brFunc);
  let brAddr = brAddrCalc(pc, rVal1, dInst.iType,
                          fromMaybe(?, dInst.imm));
  eInst.addr = (dInst.iType==Ld || dInst.iType==St)?
               aluRes : brAddr;
  eInst.dst = dInst.dst;
  return eInst;
endfunction
```

# Branch Address Calculation

```
function Addr brAddrCalc(Addr pc, Data val,  
                        IType iType, Data imm);  
    Addr targetAddr = case (iType)  
        J   : {pc + imm};  
        Jr  : {truncateLSB(val + imm), 1'b0};  
        Br  : pc + imm;  
        default: error; //32'hAAAAAAAA  
    endcase;  
    return targetAddr;  
endfunction
```

Half word aligned;  
Maybe needed to support  
compressed instruction format

# Single-Cycle RISC-V

## *atomic state updates*

```
if(eInst.iType == Ld)
  eInst.data <- dMem.req(MemReq{op: Ld,
                               addr: eInst.addr, data: ?});
else if (eInst.iType == St)
  let dummy <- dMem.req(MemReq{op: St,
                               addr: eInst.addr, data: data});


if(isValid(eInst.dst))
  rf.wr(fromMaybe(? , eInst.dst), eInst.data);
let nextPC = eInst.brTaken ? eInst.addr: pc + 4;
pc <= nextPC;
```

endrule

endmodule


state updates

 The whole processor is described using one rule;  
lots of big combinational functions


 
# Variations on non-pipelined microarchitectures


An exercise in construction and deconstruction


 
# Princeton Architecture

instructions and data reside in the same memory


Memory instructions can't be executed in one cycle!



- ◆ We can't do instruction fetch and LD/ST at the same time because there is only one memory
- ◆ Such resource conflicts are known as *structural hazards* and require multicycle implementation
- ◆ Extra registers are required to hold values between cycles

# Princeton Architecture

introduce intermediate state

 

- ◆ Every instruction takes two cycles: Fetch followed by Execute
- ◆ Insert f2d register to hold the fetched instruction
- ◆ A one bit register to record the state of the instruction

```
typedef enum {Fetch, Execute} State deriving (Bits, Eq);
```

# Princeton Architecture

## Two-cycle

```
module mkProcPrincetonTwoCycle(Empty);  
  Code to instantiate pc, rf, magic mem  
  Reg#(Word)  f2d <- mkRegU;  
  Reg#(State) state <- mkReg(Fetch);  
  
  rule doFetch if (state == Fetch);  
    Code to fetch the instruction at pc  
    f2d <= inst;  
    state <= Execute;  
  endrule  
  
  rule doExecute if (state == Execute);  
    Code to decode the instruction in f2d, execute,  
    updateState  
    state <= Fetch;  
  endrule  
endmodule
```

If state is Fetch then fetch the instruction and put it in f2d, and change the state to Execute

If state is Execute then execute the instruction in f2d, and change the state to Fetch

# doExecute rule reexamined

```
rule doExecute if (state == Execute);
```

```
  let inst = f2d;
```

```
  let dInst = decode(inst);
```

```
  let rVal1 = rf.rd1(dInst.src1);
```

```
  let rVal2 = rf.rd2(dInst.src2);
```

```
  let eInst = execute(dInst, rVal1, rVal2, pc);
```

```
  //Extract fields of eInst: data, addr, dst;
```

```
  // memory access
```

```
  if (eInst.iType == LOAD) begin
```

```
    data <- dMem.req(MemReq{op:Ld, addr:addr, data: dwv});
```

```
  end else if (eInst.iType == STORE) begin
```

```
    let dummy <- dMem.req(MemReq{op:St, addr:addr,  
data:data});
```


```
  end
```

```
  // register file write
```

```
  if (dst.valid) rf.wr(dst.index, data);
```

```
  // pc update
```

 
```
  pc <= eInst.nextPc; state <= Fetch;
```



Execution of all instructions except LD/ST can be completed in the Fetch cycle

updateState(eInst.pc, rf, dMem)  
expanded
 
# Another Princeton Architecture: where non-memory instructions take one cycle



- ◆ Do fetch, decode, and execute in one cycle for all non-memory instructions; no need for **f2d**
- ◆ For a memory instruction:
  - after fetch, decode and execute, put the partially executed instruction in a register (**e2m**)
  - In the next cycle, do the memory operation, update the register file and pc

# Princeton Architecture

where non-memory instructions take one cycle

```

rule doFetch if (state == FetchExecute);
  let inst <- mem.req(MemReq{op: Ld, addr: pc, data: dwv});
  let dInst = decode(inst);
  let rVal1 = rf.rd1(dInst.src1); //similarly rVal2
  let eInst = execute(dInst, rVal1, rVal2, pc);
  if (eInst.iType==Ld) || (eInst.iType==St) begin
    e2m <= eInst;
    state <= MemoryAccess;
  end else begin
    if (eInst.dst.valid) rf.wr(eInst.dst.index, eInst.data);
    pc <= eInst.nextPc;
    state <= FetchExecute;
  end
endrule

rule doMemoryAccess if (state == MemoryAccess);
  updateState(e2m, pc, rf, mem);
  state <= FetchExecute;
endrule

```

Save the executed instruction state in e2m register



# Performance implications

- ◆ Suppose fraction  $f$  of  $N$  executed instructions are memory access instructions
  - Two-cycle Princeton architecture will take  $2N$  cycles
  - How many cycles will the variable-cycle Princeton architecture take?


$$\begin{aligned} &f*2*N + (1-f)*N \\ &= (1+f)*N \end{aligned}$$

As far as the performance is concerned, cycle counts in not the whole story; one needs to compare the cycle times of the two designs as well

More to come later

# Realistic Memory Interface

## Request/Response methods

 

No response for Stores;  
Load responses come back in the requested order


```
interface Memory;
  method Action req(MemReq req);
  method ActionValue#(Word) resp();
endinterface

typedef struct {MemOp op; Word addr; Word data;}
MemReq deriving(Bits, Eq);

typedef enum {Ld, St} MemOp deriving(Bits, Eq);

m.req(MemReq{op:Ld, addr:a, data:dwv});
m.req(MemReq{op:St, addr:a, data:v});
let data <- m.resp();
```
 
# Princeton architecture with a realistic memory




- ◆ With request/response memory even instruction fetch cannot be completed in one cycle
  - Instruction fetch must be split into two rules – send request and receive response
  - Need registers to hold the state of a partially executed instructions

# Processor with realistic memory

```
module mkProcPrincetonMulticycle(Empty);  
  Code to instantiate pc, rf, mem, and registers that hold  
  the state of a partially executed instruction  
  rule doFetch if (state == Fetch);  
    Code to initiate instruction fetch; go to Execute  
  rule doExecute if (state == Execute);  
    let inst <- mem.resp;  
    Code to 1. execute all instructions except memory  
    instructions; go to Fetch  
    Or 2. initiate memory access;  
    go to Fetch (Store) OR go to LoadWait (Load)  
  rule doLoadWait if (state == LoadWait);  
    Code to wait for the load value, update rf, go to Fetch  
endmodule
```
 
# Multicycle ALU's

multicycle or floating point ALU operations



- ◆ Multicycle ALU's can be viewed as request/response modules
- ◆ Instructions can be further classified after decoding as simple 1 cycle, multicycle (e.g., multiply) or memory access

# Processor with realistic memory and multicycle ALUs

```
module mkProcMulticycle(Empty);
```

```
    Code to instantiate pc, rf, mem, and registers to hold the  
    state of a partially executed instruction
```

```
    rule doFetch if (state == Fetch);
```

```
        Code to initiate instruction fetch; go to Execute
```

```
    rule doExecute if (state == Execute);
```

```
        let inst <- mem.resp;
```

```
        Code to 1. execute all instructions except  
                    memory and multicycle instructions; go to Fetch
```

```
        Or 2. initiate memory access
```

```
            go to Fetch (Store) OR go to LoadWait (Load)
```

```
        Or 3. initiate multicycle instruction; go to MCWait
```


```
    rule doLoadWait if (state == LoadWait);
```

```
        Code to wait for the load value, update rf, go to Fetch
```

```
    rule doMCWait if (state == MCWait);
```

```
        Code to wait for MC value, update rf, go to Fetch
```

```
endmodule
```

 

- ❖ Clock speed depends upon the longest combinational path between two state elements. Thus, in a single cycle implementation

$$t_{\text{Clock}} > t_M + t_{\text{DEC}} + t_{\text{RF}} + t_{\text{ALU}} + t_M + t_{\text{WB}}$$

- ◆ Clock in a two-cycle implementation may be faster

$$t_{\text{Clock}} > \max \{t_M, (t_{\text{DEC}} + t_{\text{RF}} + t_{\text{ALU}} + t_M + t_{\text{WB}})\}$$

However, this may not improve the performance because now some instructions will take two cycles to execute

# Cycle counts

- ◆ Different instructions take different number of cycles in our designs
  - Depending upon the type of opcode, an instruction has to go through 1 to 3 processor-rule firings
  - The number of cycles between processor-rule firings depends on how quickly the memory responds or a multicycle functional unit completes its work for the input data

Next, we will study pipelining

# Processor Interface




```
module mkProcessor(Empty);  
    ...  
endmodule
```

- ◆ For testing, processor is connected to a host computer\* which can read and write the memory of the processor directly
- ◆ The processor's memory is preloaded with program and data; it always starts at pc=0
- ◆ When the program terminates it writes a 0 in a predetermined location and stops the simulation
  - If the program hits an illegal or unsupported instruction, it dumps the processor state and stops the simulation

Consequently, the processor interface has no methods, ie, its interface is Empty!

 \*In the simulation environment the host computer is the same computer on which the simulator runs



# Extras



# Instruction Formats

## ◆ R-type instruction



## ◆ I-type instruction & I-immediate (32 bits)



I-imm = signExtend(inst[31:20])

## ◆ S-type instruction & S-immediate (32 bits)



S-imm = signExtend({inst[31:25], inst[11:7]})

# Instruction Formats *cont.*

## ◆ SB-type instruction & B-immediate (32 bits)




B-imm = signExtend({inst[31], inst[7], inst[30:25], inst[11:8], 1'b0})

## ◆ U-type instruction & U-immediate (32 bits)



U-imm = signExtend({inst[31:12], 12'b0})
 
## ◆ UJ-type instruction & J-immediate (32 bits)



J-imm = signExtend({inst[31], inst[19:12], inst[20], inst[30:21], 1'b0})

# Computational Instructions *cont.*


## ◆ Register-immediate instructions (U-type)



- opcode = LUI :  $rd \leftarrow \text{U-imm}$
- opcode = AUIPC :  $rd \leftarrow pc + \text{U-imm}$
- U-imm = {inst[31:12], 12'b0}

# Computational Instructions
 
## ◆ Register-Register instructions (R-type)



- opcode=OP:  $rd \leftarrow rs1 \text{ (funct3, funct7) } rs2$
- funct3 = SLT/SLTU/AND/OR/XOR/SLL
- funct3= ADD
  - ◆ funct7 = 0000000:  $rs1 + rs2$
  - ◆ funct7 = 0100000:  $rs1 - rs2$
- funct3 = SRL
  - ◆ funct7 = 0000000: logical shift right
  - ◆ funct7 = 0100000: arithmetic shift right

# Computational Instructions *cont*

## ◆ Register-immediate instructions (I-type)




- opcode = OP-IMM:  $rd \leftarrow rs1$  (funct3) I-imm
- I-imm = signExtend(inst[31:20])
- funct3 = ADDI/SLTI/SLTIU/ANDI/ORI/XORI

## ◆ A slight variant in coding for shift instructions - SLLI / SRLI / SRAI

- $rd \leftarrow rs1$  (funct3, inst[30]) I-imm[4:0]

# Control Instructions
 
## ◆ Unconditional jump and link (UJ-type)



- opcode = JAL:  $rd \leftarrow pc + 4$ ;  $pc \leftarrow pc + J-imm$
- J-imm =  $signExtend(\{inst[31], inst[19:12], inst[20], inst[30:21], 1'b0\})$
- Jump  $\pm 1MB$  range


## ◆ Unconditional jump via register and link (I-type)



- opcode = JALR:  $rd \leftarrow pc + 4$ ;  $pc \leftarrow (rs1 + I-imm) \& \sim 0x01$
- I-imm =  $signExtend(inst[31:20])$

# Control Instructions *cont.*

## ◆ Conditional branches (SB-type)

 

- opcode = BRANCH:  $pc \leftarrow \text{compare}(\text{funct3}, rs1, rs2) ? pc + B\text{-imm} : pc + 4$
- B-imm =  $\text{signExtend}(\{inst[31], inst[7], inst[30:25], inst[11:8], 1'b0\})$
- Jump  $\pm 4\text{KB}$  range
- funct3 = BEQ/BNE/BLT/BLTU/BGE/BGEU

# Load & Store Instructions

## ◆ Load (I-type)



- opcode = LOAD:  $rd \leftarrow \text{mem}[rs1 + \text{I-imm}]$
- I-imm =  $\text{signExtend}(\text{inst}[31:20])$
- funct3 = LW/LB/LBU/LH/LHU

## ◆ Store (S-type)



- opcode = STORE:  $\text{mem}[rs1 + \text{S-imm}] \leftarrow rs2$
- S-imm =  $\text{signExtend}(\{\text{inst}[31:25], \text{inst}[11:7]\})$
- funct3 = SW/SB/SH