

EE-320 Exercise 2

1. For $W = 50 \mu\text{m}$, $L_{\text{drawn}} = 0.5 \mu\text{m}$, $L_D = 0.08 \mu\text{m}$, plot the drain current of an NFET as a function of V_{GS} as V_{GS} varies from 0 to 3 V. Assume that $V_{DS} = 3 \text{ V}$, $\mu_n C_{ox} = 50 \mu\text{A/V}^2$, $\lambda = 0.1 \text{ V}^{-1}$, and $V_{TH} = 0.7 \text{ V}$.

2. Find an expression for the I_X and the transconductance of M_1 as a function of V_X as V_X varies from 0 to 1 V. Assume $V_{DD} = 3 \text{ V}$, $V_B = 0$, $\lambda = 0.1 \text{ V}^{-1}$, $\gamma = 0.45 \text{ V}^{1/2}$, $2\Phi_F = 0.9 \text{ V}$, $V_{TH0} = 0.7 \text{ V}$.

