


EE-320 Exercise 7

1. Design a common-source amplifier with a resistive load (schematic shown below) with the following design specifications. Assume $\lambda=0$, $\gamma=0$, $V_{DD}=3V$, $V_{TH}=0.5V$, $\mu_n C_{ox}=1mA/V^2$.

- M_1 is in saturation
- The minimum output voltage to keep M_1 in saturation is 0.2V
- The total power consumption of the amplifier is 3mW
- The absolute value of gain is 15
- $L=0.5\mu m$ for the transistor

Find the following:

 - a) DC level of the input
- b) The width (W) of M_1
- c) R_D
- d) DC (bias) level of the output



2. Assuming transistors are in saturation, calculate the small-signal voltage gain of the following circuits ($\lambda \neq 0$, $\gamma=0$).

