

Analog IC design (EE-320), Lecture 4

Prof. Mahsa Shoaran

Institute of Electrical and Micro Engineering, School of Engineering, EPFL


Review: Small-signal model

Saturation

$$I_D \approx \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}}$$
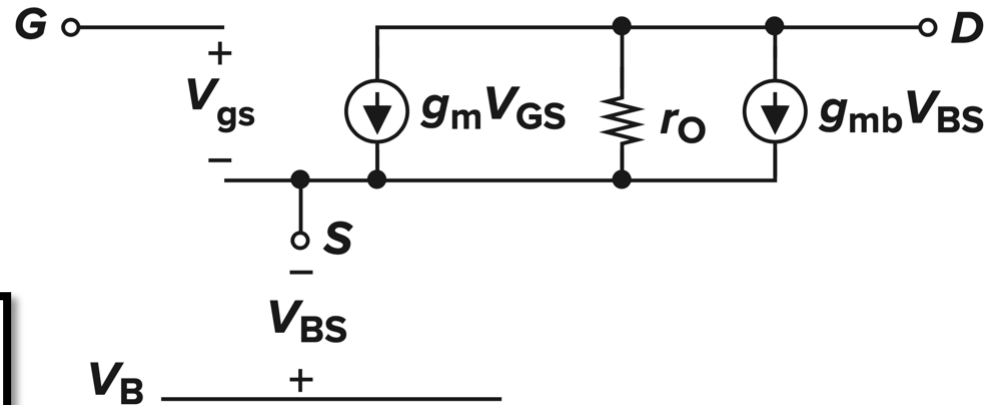
$$\begin{aligned} g_m &= \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D} \\ &= \frac{2 I_D}{V_{GS} - V_{TH}} \end{aligned}$$



Review: Small-signal model

Saturation

$$I_D \approx \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}}$$

$$g_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D}$$



$$= \frac{2I_D}{V_{GS} - V_{TH}}$$

$$r_O \approx \frac{1}{\lambda I_D}$$




$$g_{mb} = \frac{\partial I_D}{\partial V_{BS}}$$

$$= g_m \frac{\gamma}{2\sqrt{2\Phi_F + V_{SB}}}$$

$$= \eta g_m$$

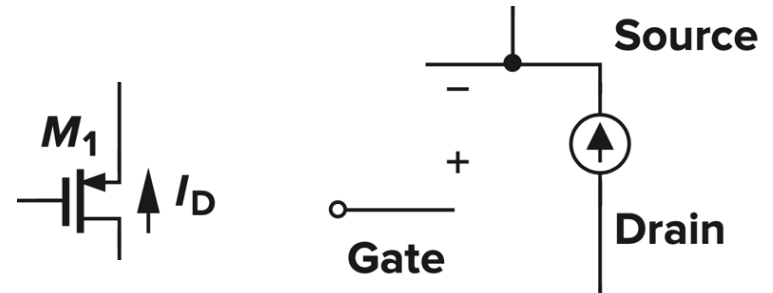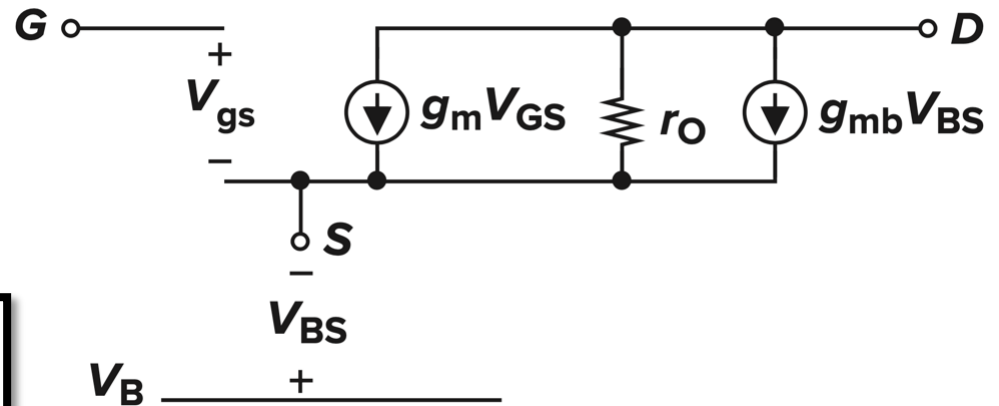


Review: MOS Device Capacitances, layout

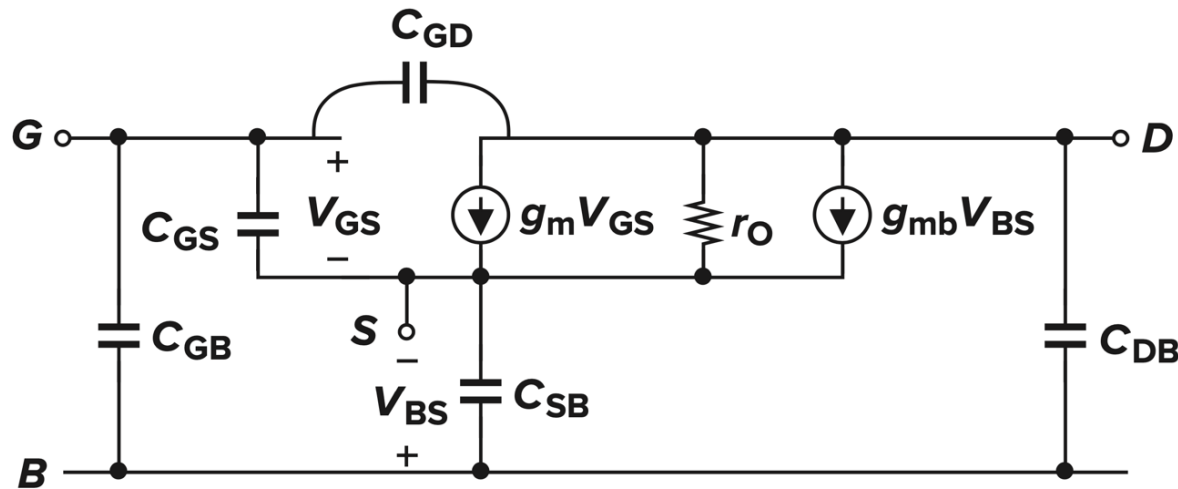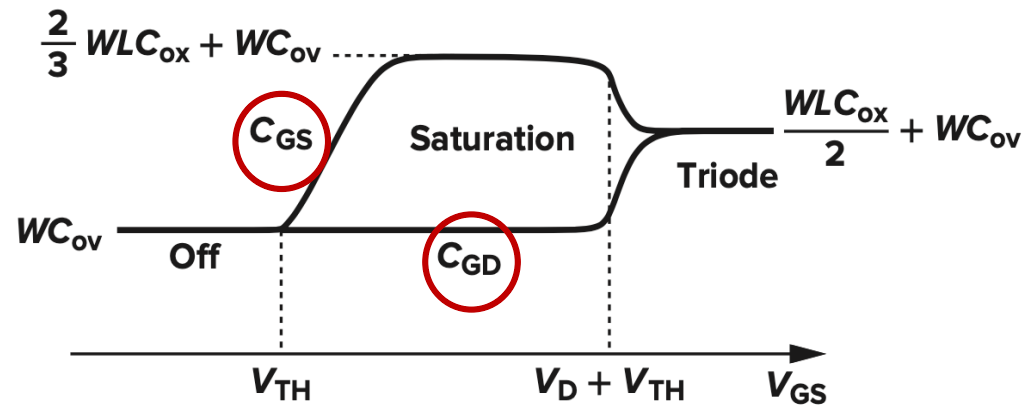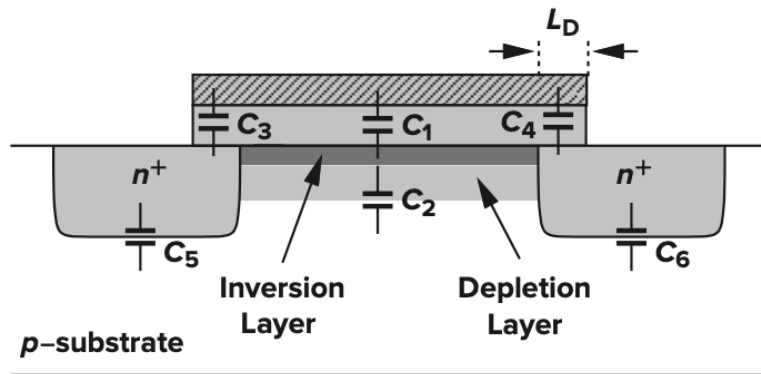

Common-Source Stage - with **Resistive** Load

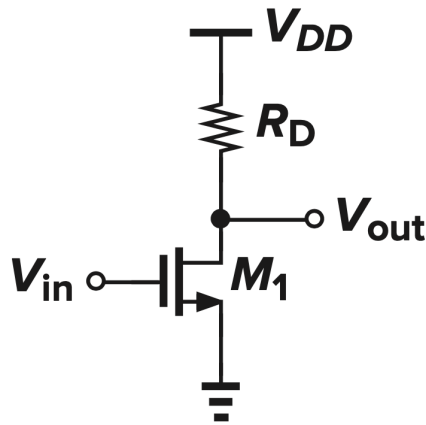- The **common-source** topology: receives the input at the **gate** and produces the output at the **drain**




$$V_{out} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2 \quad (\text{saturation})$$

$$V_{in1} - V_{TH} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{TH})^2$$


↓ (triode)
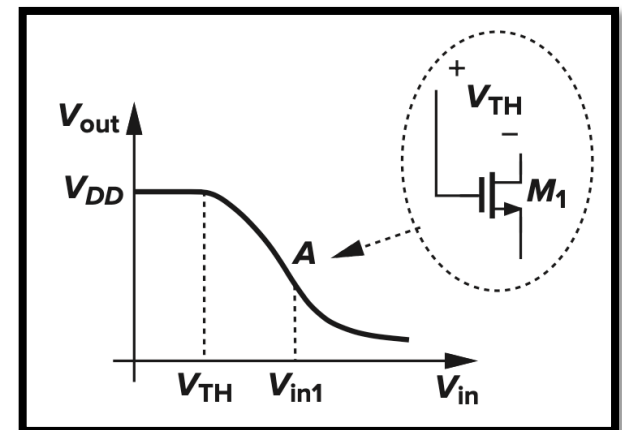
$$V_{out} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [2(V_{in} - V_{TH})V_{out} - V_{out}^2]$$



Common-Source Stage - with Resistive Load

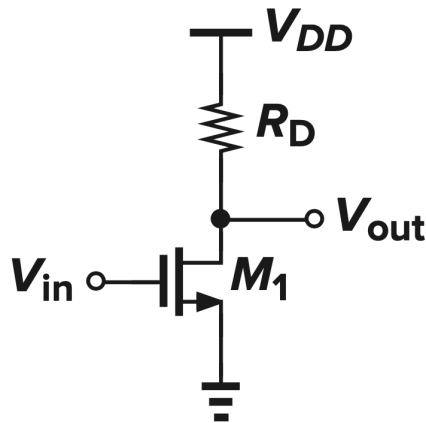- The **common-source** topology: receives the input at the **gate** and produces the output at the **drain**



$$V_{out} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2 \quad (\text{saturation})$$



$$V_{in1} - V_{TH} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{TH})^2$$

↓ (triode)


$$V_{out} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [2(V_{in} - V_{TH})V_{out} - V_{out}^2]$$

$$V_{out} \ll 2(V_{in} - V_{TH})$$
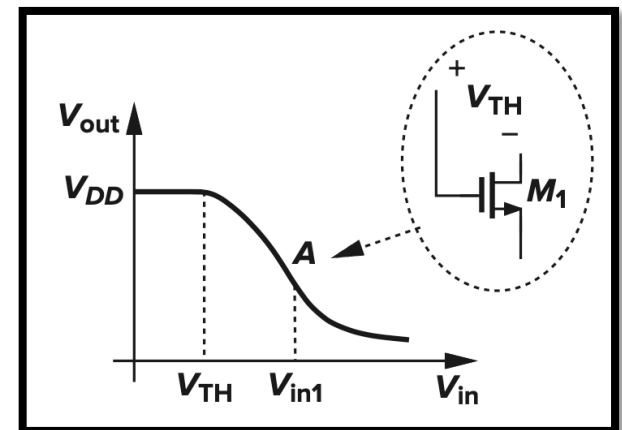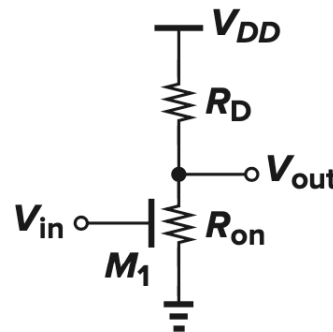
$$\begin{aligned} V_{out} &= V_{DD} \frac{R_{on}}{R_{on} + R_D} \\ &= \frac{V_{DD}}{1 + \mu_n C_{ox} \frac{W}{L} R_D (V_{in} - V_{TH})} \end{aligned}$$



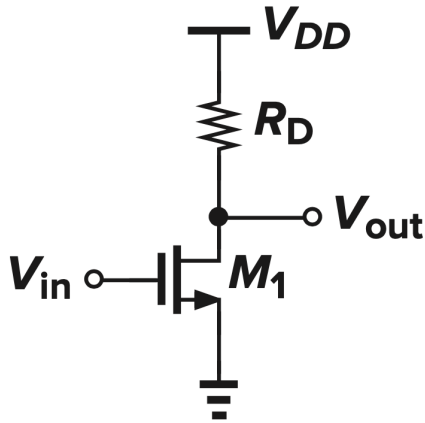Common-Source Stage - with Resistive Load



$$V_{out} > V_{in} - V_{TH}$$


$$V_{out} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2$$

$$A_v = \frac{\partial V_{out}}{\partial V_{in}}$$

$$= -R_D \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})$$

$$= -g_m R_D$$

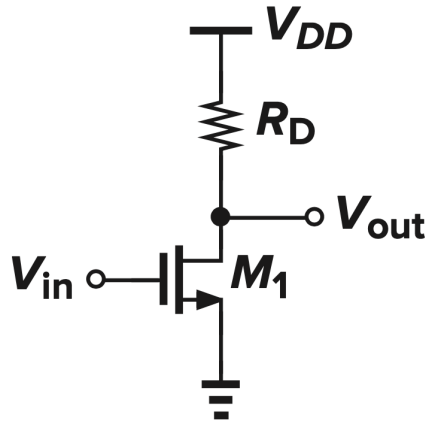Common-Source Stage - with Resistive Load



$$V_{out} > V_{in} - V_{TH}$$


$$V_{out} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2$$

$$A_v = \frac{\partial V_{out}}{\partial V_{in}}$$


$$= -R_D \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})$$

$$= -g_m R_D$$

small-signal model:

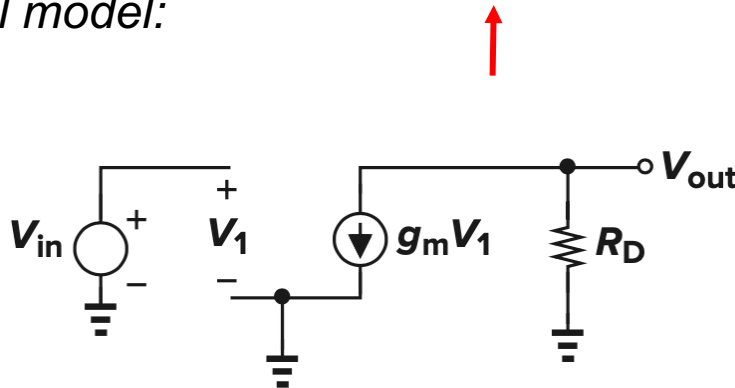

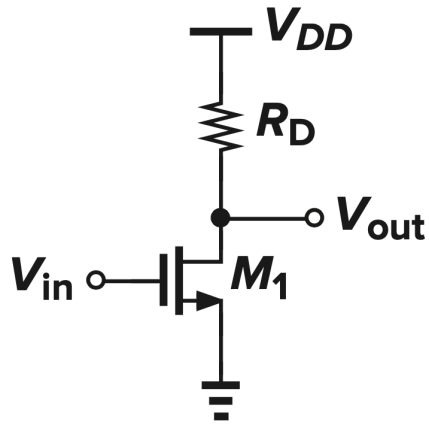Common-Source Stage - with Resistive Load



$$V_{out} > V_{in} - V_{TH}$$


$$V_{out} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2$$

$$A_v = \frac{\partial V_{out}}{\partial V_{in}}$$

$$= -R_D \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})$$

$$= -g_m R_D$$


small-signal model:

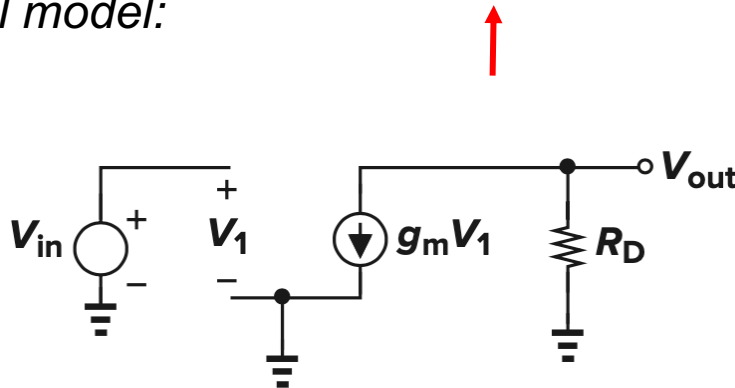



$$A_v = -\sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} \frac{V_{RD}}{I_D}$$

$$A_v = -\sqrt{2\mu_n C_{ox} \frac{W}{L} \frac{V_{RD}}{\sqrt{I_D}}}$$

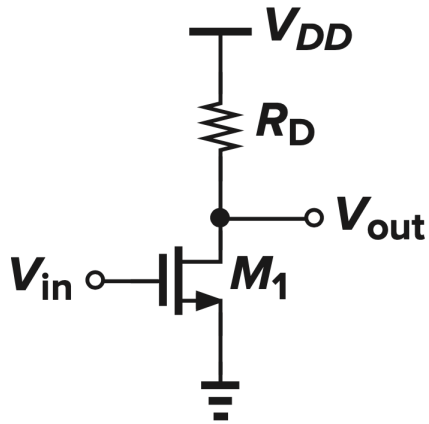Example: I_D and g_m as a function of V_{in} ?




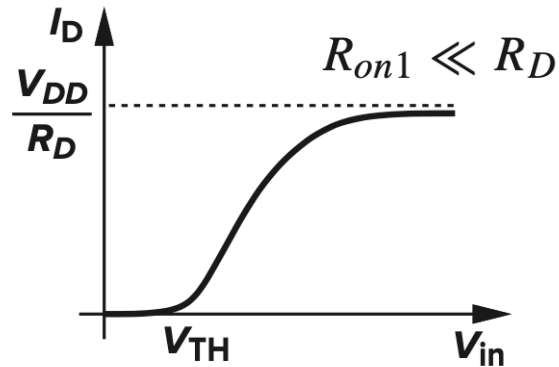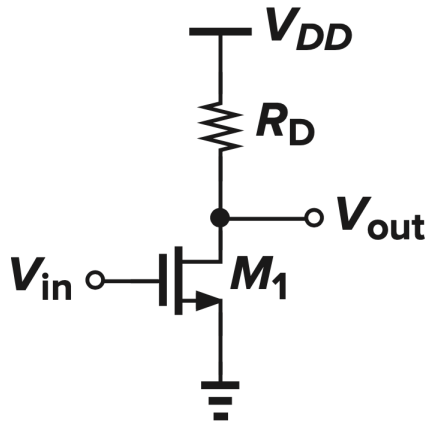Example: I_D and g_m as a function of V_{in} ?




(saturation)
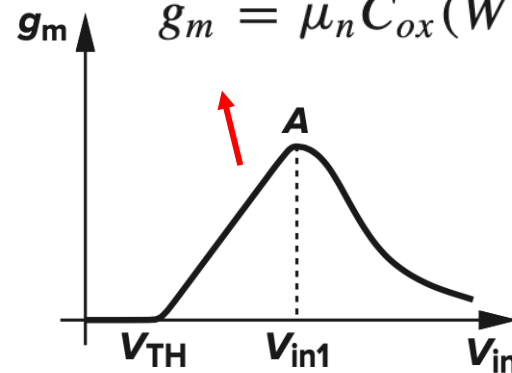
$$g_m = \mu_n C_{ox} (W/L) (V_{GS} - V_{TH})$$



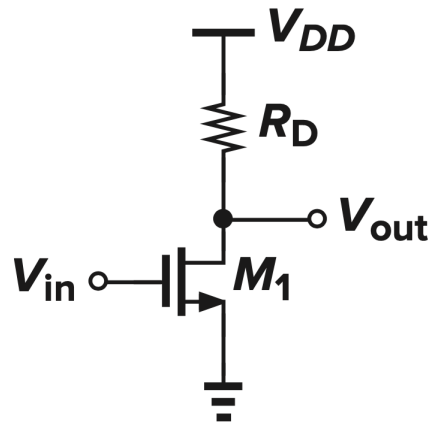Example: I_D and g_m as a function of V_{in} ?



(triode)

$$g_m = \mu_n C_{ox} (W/L) V_{DS}$$



$$V_{out} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [2(V_{in} - V_{TH}) V_{out} - V_{out}^2]$$

$$A_v = \frac{\partial V_{out}}{\partial V_{in}} = \frac{-\mu_n C_{ox} (W/L) R_D V_{out}}{1 + \underbrace{\mu_n C_{ox} (W/L) R_D (V_{in} - V_{TH} - V_{out})}_{\text{(point A)}}}$$


(point A)

(saturation)
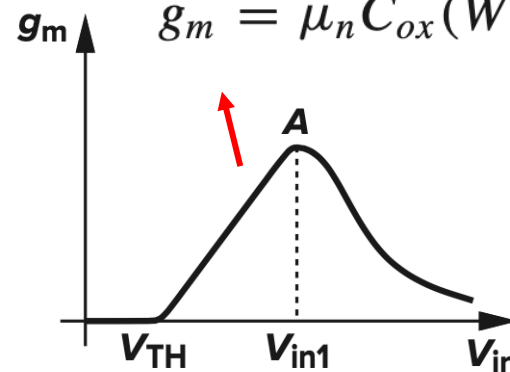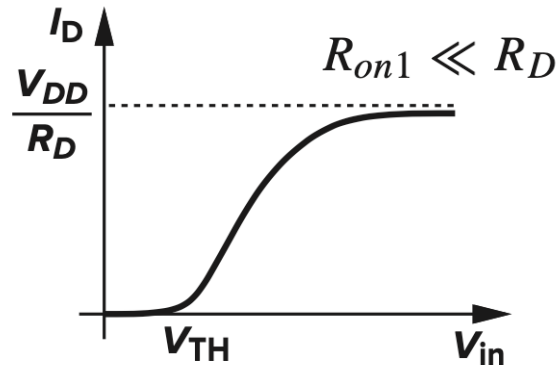
$$g_m = \mu_n C_{ox} (W/L) (V_{GS} - V_{TH})$$



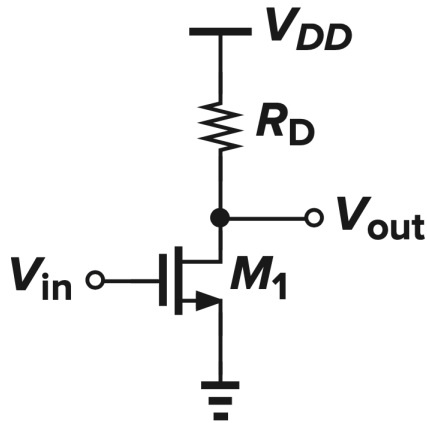CS stage including channel-length modulation




$$V_{out} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2 (1 + \lambda V_{out})$$

$$\begin{aligned} \frac{\partial V_{out}}{\partial V_{in}} &= -R_D \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH}) (1 + \lambda V_{out}) \\ &\quad - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2 \lambda \frac{\partial V_{out}}{\partial V_{in}} \end{aligned}$$

$$\begin{aligned} A_v &= -R_D g_m - \frac{R_D}{r_O} A_v \\ &= -g_m \frac{r_O R_D}{r_O + R_D} \end{aligned}$$

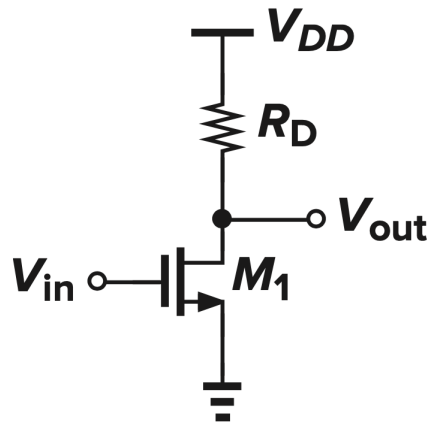CS stage including channel-length modulation




$$V_{out} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2 (1 + \lambda V_{out})$$

$$\frac{\partial V_{out}}{\partial V_{in}} = -R_D \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH}) (1 + \lambda V_{out}) - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2 \lambda \frac{\partial V_{out}}{\partial V_{in}}$$

$$A_v = -R_D g_m - \frac{R_D}{r_o} A_v$$


$$= -g_m \frac{r_o R_D}{r_o + R_D}$$

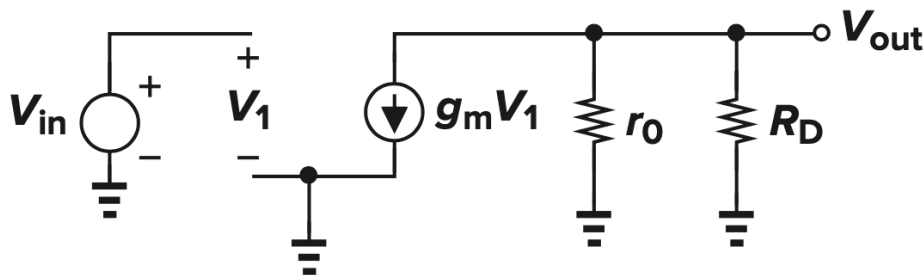


$$g_m V_1 (r_o \parallel R_D) = -V_{out}$$

$$V_{out} / V_{in} = -g_m (r_o \parallel R_D)$$

Example: Voltage gain?

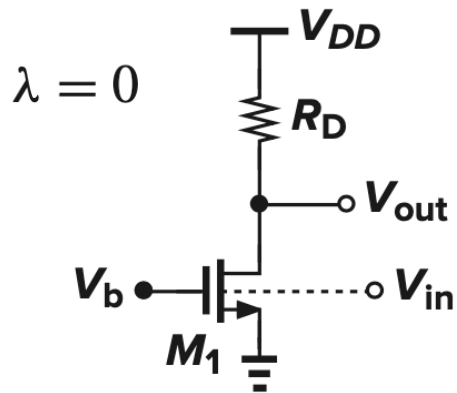


$$A_v = -g_{mb} R_D$$

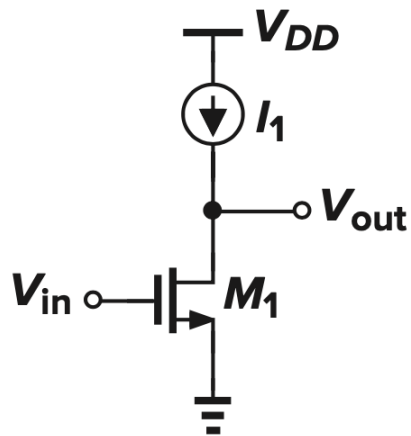


$$A_v = -g_m r_O$$

CS Stage - with Diode-Connected Load

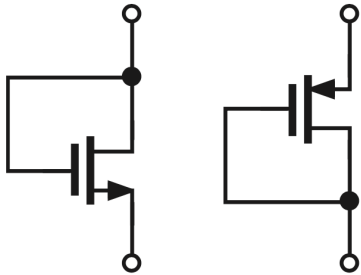- It is difficult to fabricate resistors with controlled values or a reasonable physical size
 - use transistors with **gain** and **drain** shorted



Diode-Connected Device

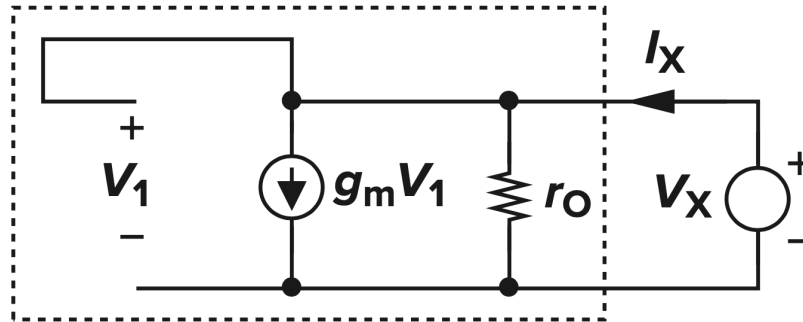


$$V_X/I_X = (1/g_m) \parallel r_o \approx 1/g_m$$



CS Stage - with Diode-Connected Load

- It is difficult to fabricate resistors with controlled values or a reasonable physical size
 - use transistors with **gain** and **drain** shorted

Diode-Connected Device

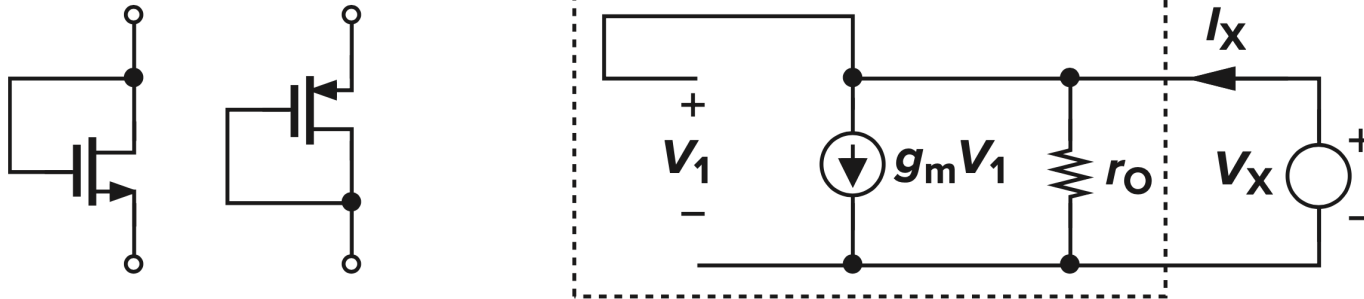

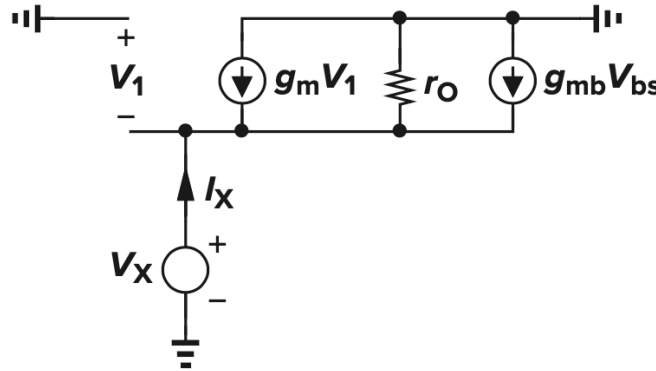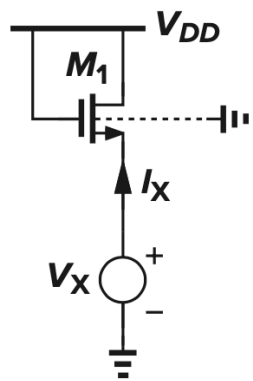
$$V_X / I_X = (1/g_m) \parallel r_o \approx 1/g_m$$



$$\begin{aligned} (g_m + g_{mb}) V_X + \frac{V_X}{r_o} &= I_X \\ \frac{V_X}{I_X} &= \frac{1}{g_m + g_{mb} + r_o^{-1}} \\ &= \frac{1}{g_m + g_{mb}} \parallel r_o \\ &\approx \frac{1}{g_m + g_{mb}} \end{aligned}$$

CS Stage - with Diode-Connected Load

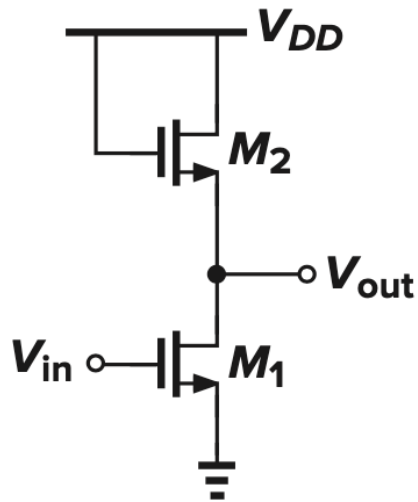


$$A_v = -g_{m1} \frac{1}{g_{m2} + g_{mb2}}$$

$$= -\frac{g_{m1}}{g_{m2}} \frac{1}{1 + \eta}$$

$$A_v = -\frac{\sqrt{2\mu_n C_{ox}(W/L)_1 I_{D1}}}{\sqrt{2\mu_n C_{ox}(W/L)_2 I_{D2}}} \frac{1}{1 + \eta}$$

$$= -\sqrt{\frac{(W/L)_1}{(W/L)_2}} \frac{1}{1 + \eta}$$

CS Stage - with Diode-Connected Load

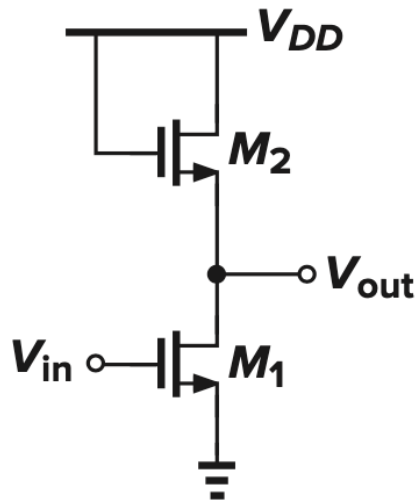

$$A_v = -g_{m1} \frac{1}{g_{m2} + g_{mb2}}$$

$$= -\frac{g_{m1}}{g_{m2}} \frac{1}{1 + \eta}$$


$$A_v = -\frac{\sqrt{2\mu_n C_{ox} (W/L)_1 I_{D1}}}{\sqrt{2\mu_n C_{ox} (W/L)_2 I_{D2}}} \frac{1}{1 + \eta}$$

$$= -\sqrt{\frac{(W/L)_1}{(W/L)_2}} \frac{1}{1 + \eta}$$

✓ The input-output characteristic is relatively linear

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{in} - V_{TH1})^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - V_{out} - V_{TH2})^2$$

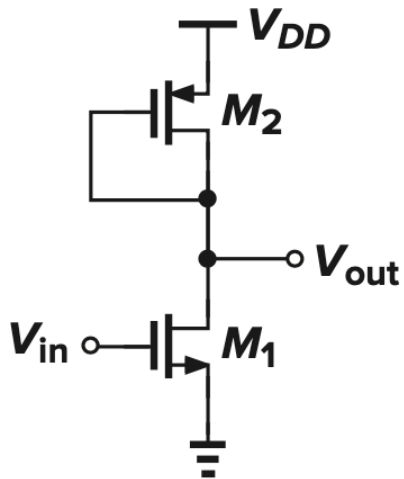
CS Stage - with PMOS Diode-Connected Load



(assuming no r_o)

$$A_v = -\sqrt{\frac{\mu_n(W/L)_1}{\mu_p(W/L)_2}}$$

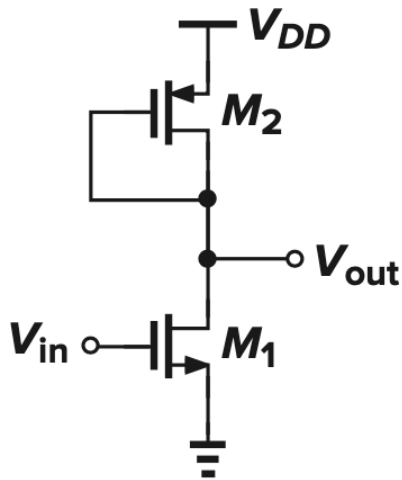CS Stage - with PMOS Diode-Connected Load




(assuming no r_o)

$$A_v = -\sqrt{\frac{\mu_n(W/L)_1}{\mu_p(W/L)_2}}$$

- A **high gain** requires a “**strong**” input device and a “**weak**” load device
 - disproportionately wide or long transistors $\gg$ large input or load cap
 - another limitation: reduction in allowable voltage swings

$$\mu_n \left(\frac{W}{L} \right)_1 (V_{GS1} - V_{TH1})^2 = \mu_p \left(\frac{W}{L} \right)_2 (V_{GS2} - V_{TH2})^2 \rightarrow \boxed{\frac{|V_{GS2} - V_{TH2}|}{V_{GS1} - V_{TH1}} = A_v}$$

CS Stage - with Diode-Connected Load

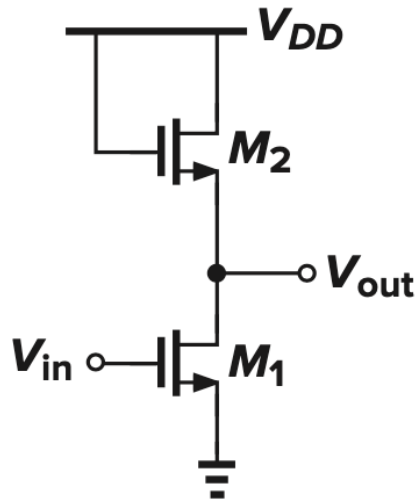


- Including channel-length modulation:


$$A_v = -g_{m1} \left(\frac{1}{g_{m2}} \parallel r_{O1} \parallel r_{O2} \right)$$

CS Stage with **Current-Source** Load

- To achieve a large voltage gain in a single stage, $A_v = -g_m R_D$ suggests that we should increase the **load impedance** of the CS stage
- With a resistor or diode-connected load, increasing the load resistance translates to a large dc drop across the load, limiting the output voltage **swing**
- A more practical approach is to replace the load with a device that does not obey Ohm's law, such as a **current source**

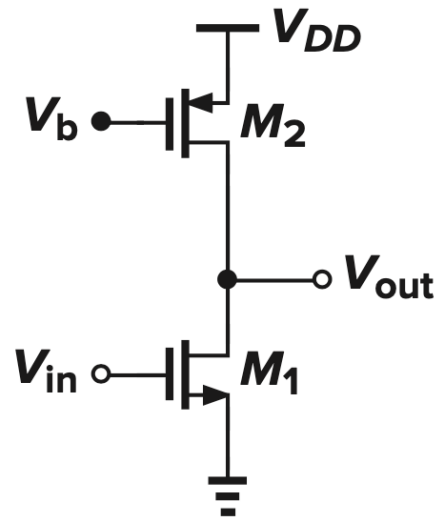

CS Stage with Current-Source Load

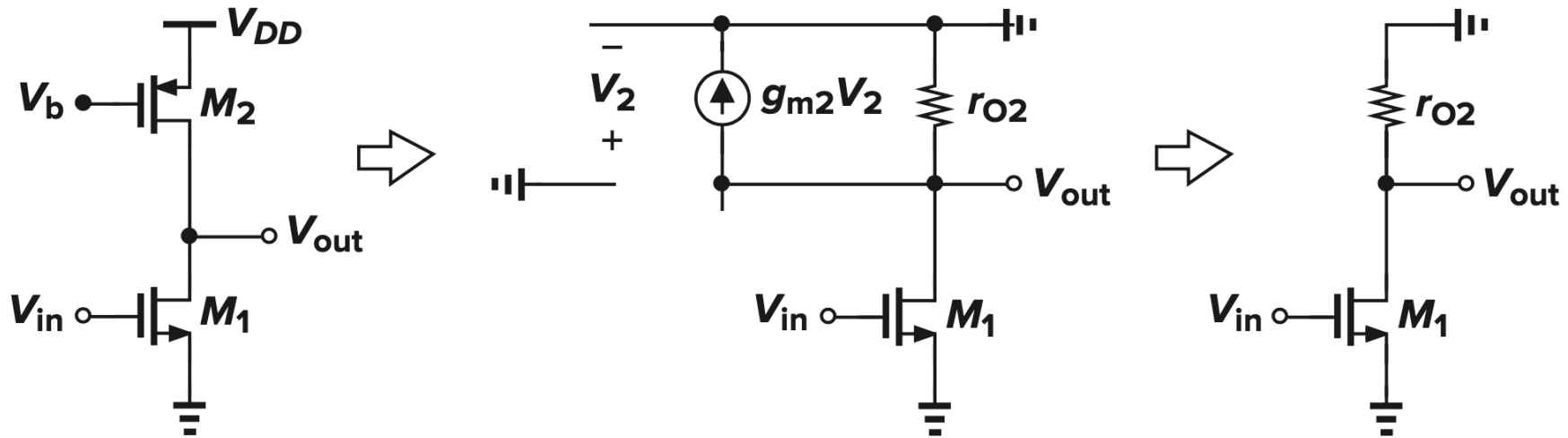

$$A_v = -g_{m1}(r_{o1} \parallel r_{o2})$$


- The output impedance and minimum required $|V_{DS}|$ of M_2 less strongly coupled than the value and voltage drop of a resistor

$$|V_{DS2,min}| = |V_{GS2} - V_{TH2}|$$

- If r_{o2} is not sufficiently high, the length and width of M_2 can be increased while maintaining the same overdrive voltage
 - penalty: the larger capacitance introduced by M_2 at the output node


CS Stage with **Active** Load

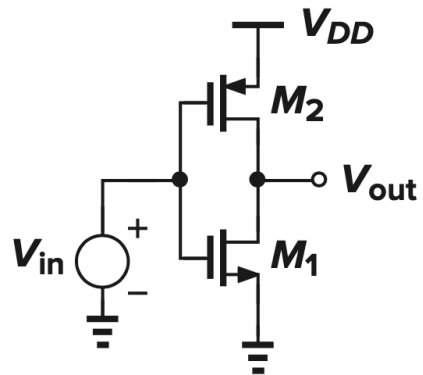- Replace the constant current source with an amplifying device



CS Stage with **Active** Load

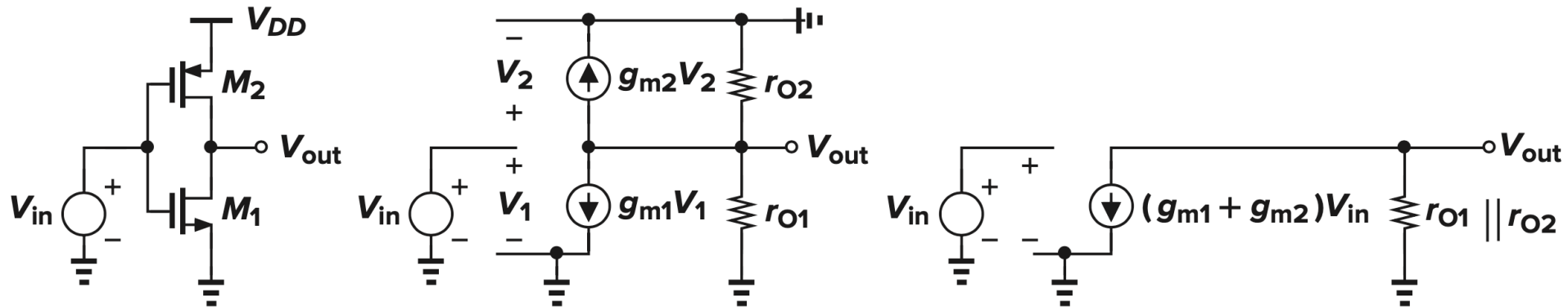
- Replace the constant current source with an amplifying device



$$A_v = -(g_{m1} + g_{m2})(r_{O1} || r_{O2})$$

CS Stage with **Active** Load

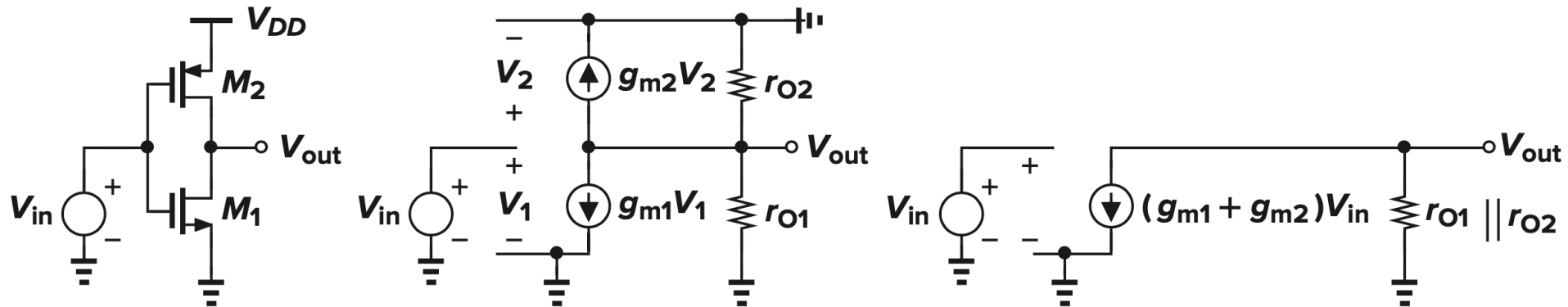- Replace the constant current source with an amplifying device



$$A_v = -(g_{m1} + g_{m2})(r_{O1} || r_{O2})$$

- a “**complementary CS stage**”


× the bias current of the two transistors is a strong function of PVT

$$V_{GS1} + |V_{GS2}| = V_{DD}$$

× it amplifies supply voltage variations (“supply noise”)

CS Stage with Triode Load

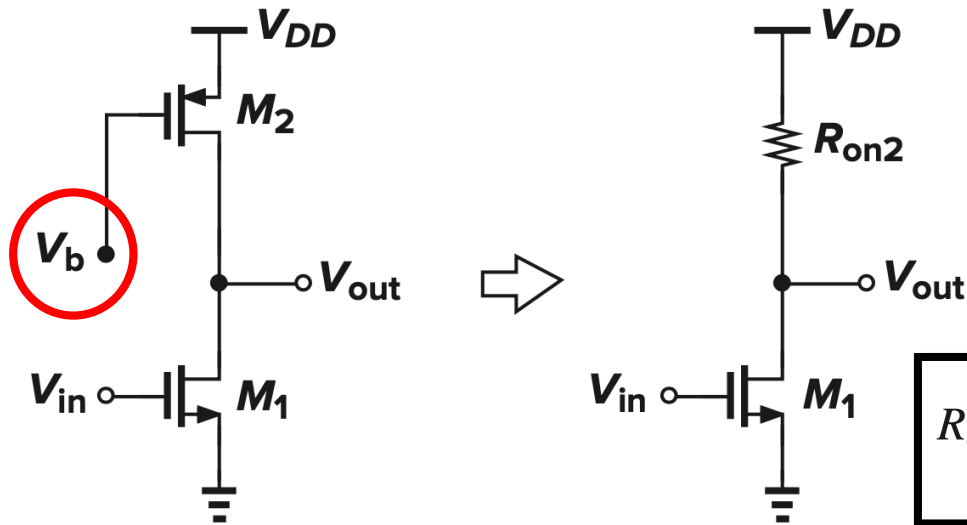
- A MOS device operating in the deep triode region behaves as a resistor



$$R_{on2} = \frac{1}{\mu_p C_{ox} (W/L)_2 (V_{DD} - V_b - |V_{THP}|)}$$

CS Stage with Triode Load

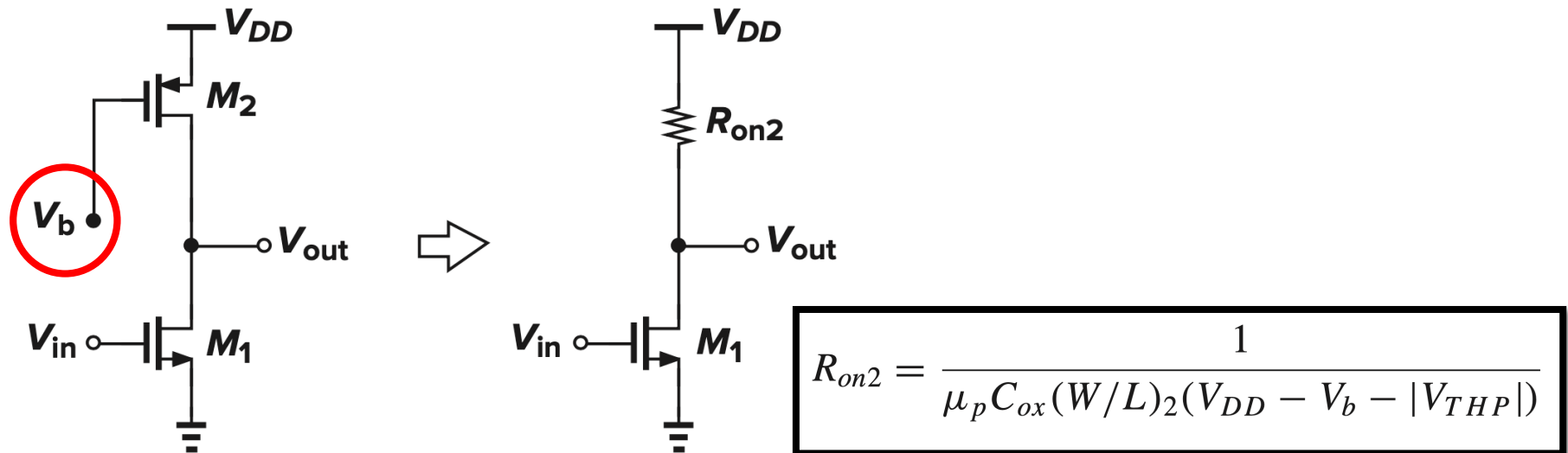
- A MOS device operating in the deep triode region behaves as a resistor



- × Dependence of R_{on2} on $\mu_p C_{ox}$, V_b , and V_{THP}
 - × $\mu_p C_{ox}$ and V_{THP} vary with process and temperature
 - × generating a precise V_b requires additional complexity
- ✓ Triode loads consume less voltage headroom than diode-connected

CS Stage with Source Degeneration


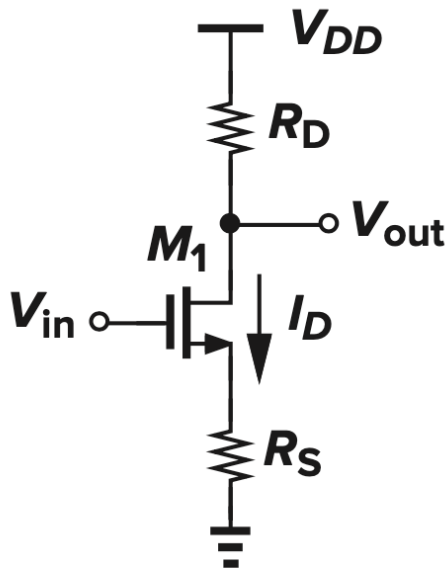
- The nonlinear dependence of the drain current upon overdrive: nonlinearity
- Placing a “**degeneration**” resistor in series with the **source** terminal makes the input device more **linear** (i.e., make the gain a weaker function of g_m)



$$G_m = \partial I_D / \partial V_{in} \quad \rightarrow \quad G_m = \frac{g_m}{1 + g_m R_S}$$
$$V_{GS} = V_{in} - I_D R_S$$

CS Stage with Source Degeneration

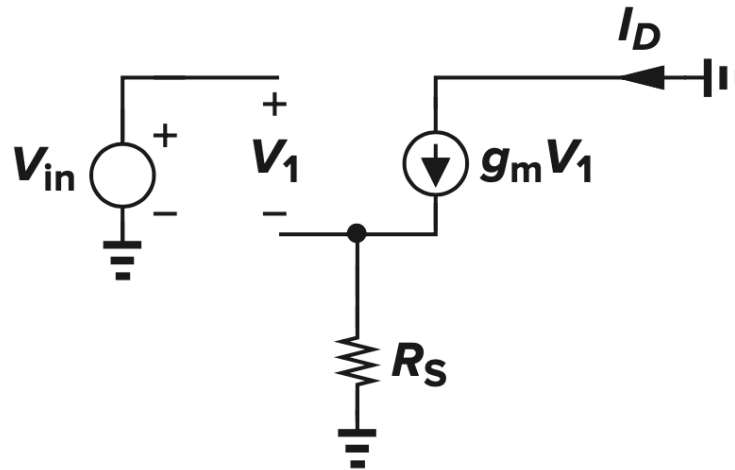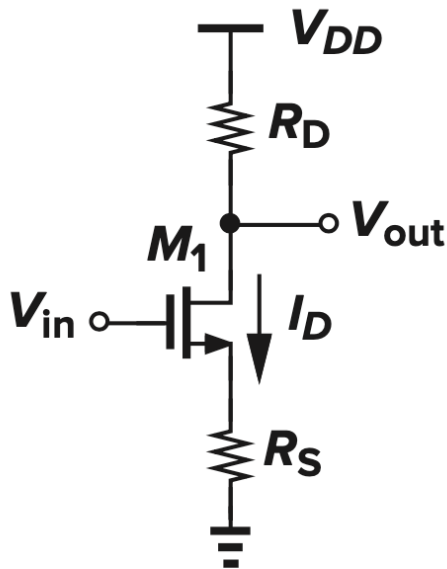- The nonlinear dependence of the drain current upon overdrive: nonlinearity
- Placing a “**degeneration**” resistor in series with the **source** terminal makes the input device more **linear** (i.e., make the gain a weaker function of g_m)



$$G_m = \partial I_D / \partial V_{in}$$

$$V_{GS} = V_{in} - I_D R_S$$




$$G_m = \frac{g_m}{1 + g_m R_S}$$



$$\begin{aligned} A_v &= -G_m R_D \\ &= \frac{-g_m R_D}{1 + g_m R_S} \end{aligned}$$

CS Stage with Source Degeneration


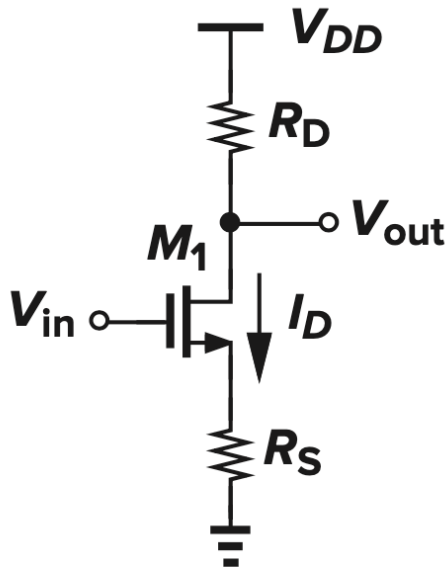


$$G_m = \frac{g_m}{1 + g_m R_S}$$



$$A_v = -G_m R_D$$
$$= \frac{-g_m R_D}{1 + g_m R_S}$$

- As R_S increases, G_m becomes a weaker function of g_m and hence the drain current
- For $R_S \gg 1/g_m$, we have $G_m \approx 1/R_S$, i.e., $I_D \approx V_{in}/R_S$: most of the change in V_{in} appears across R_S and the drain current is a “**linearized**” function of the input voltage
- The linearization is obtained at the cost of lower gain

G_m in the presence of g_{mb} and r_o

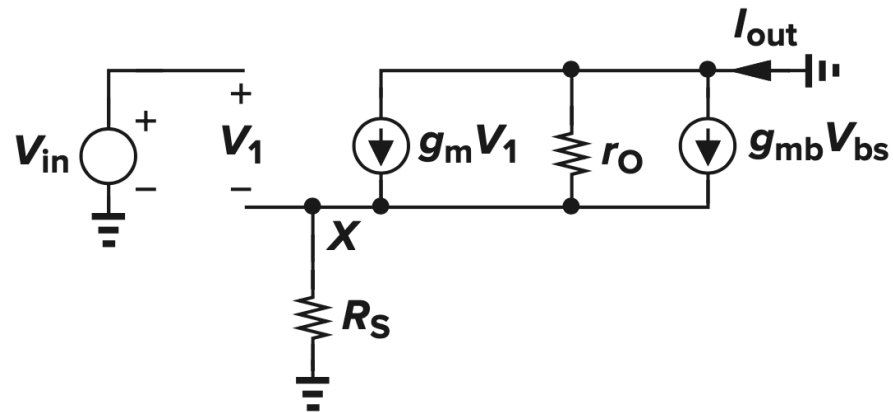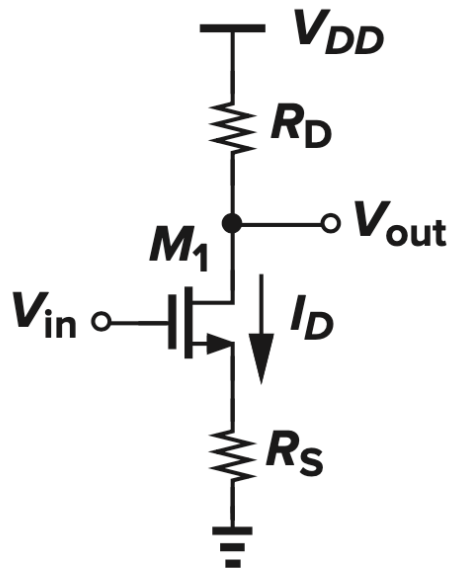

G_m in the presence of g_{mb} and r_o

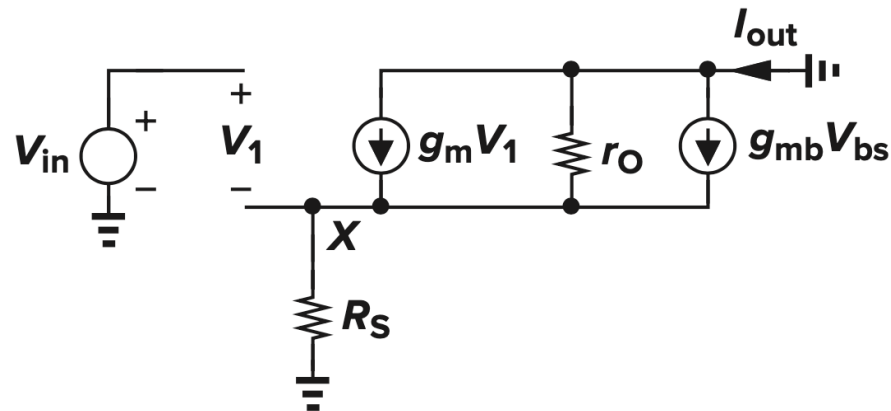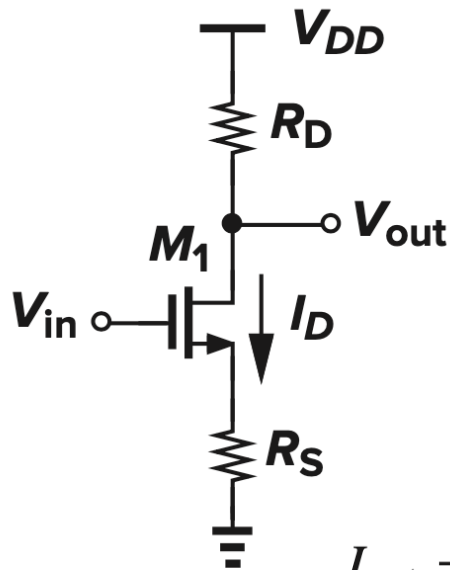


$$I_{out} = g_m V_1 - g_{mb} V_X - \frac{I_{out} R_S}{r_o}$$

$$= g_m (V_{in} - I_{out} R_S) + g_{mb} (-I_{out} R_S) - \frac{I_{out} R_S}{r_o}$$

$$G_m = \frac{I_{out}}{V_{in}}$$

$$= \frac{g_m r_o}{R_S + [1 + (g_m + g_{mb}) R_S] r_o}$$


Gain by Inspection

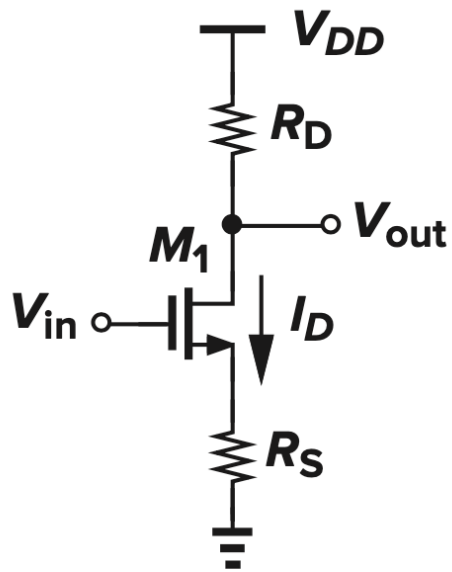

$$A_v = \frac{-g_m R_D}{1 + g_m R_S}$$



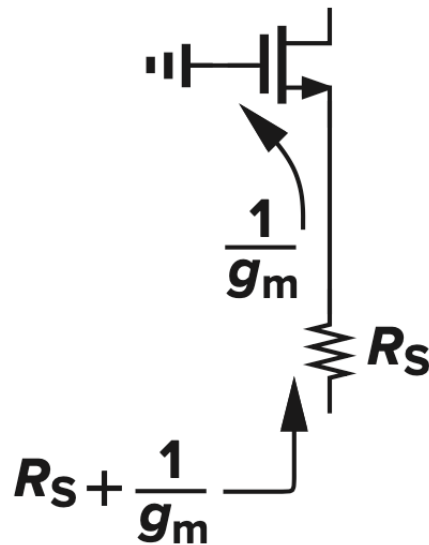
$$A_v = - \frac{R_D}{\frac{1}{g_m} + R_S}$$




Resistance seen in the source path

Example: Calculate the small-signal gain

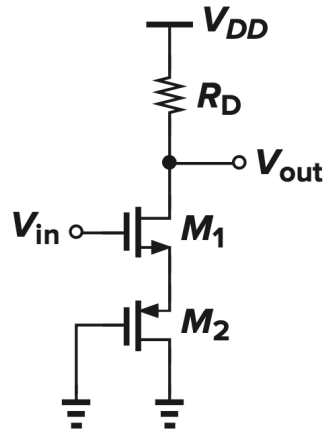


$$\lambda = \gamma = 0$$

Example: Calculate the small-signal gain

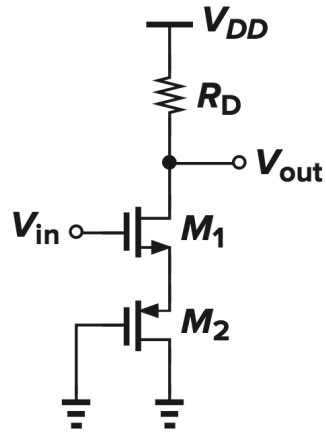

$$\lambda = \gamma = 0$$

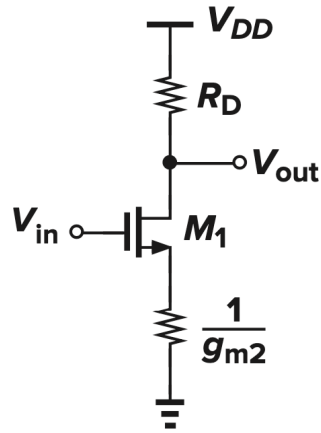

$$A_v = - \frac{R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$