

Analog IC design (EE-320), Lecture 6

Prof. Mahsa Shoaran



Institute of Electrical and Micro Engineering, School of Engineering, EPFL

Homework 1, TP Schedule

- **Homework 1 assignment** will be posted this week
- EDADK document to be signed and uploaded via moodle, please complete the assignment **by Nov 6**
- **First TP session on Nov 11 in BC07-08 from 3:15pm to 6pm**

Week	Subject by week – EE-320: Analog IC design – Fall 2024	Suggested Chapters
Week 1: 09/09 – 15/09	Introduction, organization, review of BJT and MOS transistors + Exercise1	Ch 1, Ch 2.1-2.4, Slides on Moodle
Week 2: 16/09 – 22/09	Holiday - No class	
Week 3: 23/09 – 29/09	MOS large and small-signal models, regimes of operations + Exercise2	Ch 2.1-2.4
Week 4: 30/09 – 06/10	MOS parasitic effects, layout basic, single-stage amplifiers + Exercise3	Ch 2.1-2.4, Ch 3.1
Week 5: 07/10 – 13/10	Single-stage amplifiers + Exercise4	Ch 3.1-3.7
Week 6: 14/10 – 20/10	Single-stage amplifiers + Exercise5	Ch 3.1-3.7
Week 7: 21/10 – 27/10	Holiday – No class	
Week 8: 28/10 – 03/11	Single-stage amplifiers + Cascode + Exercise6 + Homework1	Ch 4.1-4.4
Week 9: 04/11 – 10/11	Differential amplifiers + Exercise7	Ch 4.1-4.4
Week 10: 11/11 – 17/11	TP1 Practical exercise session on Cadence	Tutorial on Moodle
Week 11: 18/11 – 24/11	TP2 Practical exercise session on Cadence	Tutorial on Moodle
Week 12: 25/11 – 01/12	TP3 Practical exercise session on Cadence + Homework2	Tutorial on Moodle
Week 13: 02/12 – 08/12	TP4 Practical exercise session on Cadence	Tutorial on Moodle
Week 14: 09/12 – 15/12	Differential amplifiers, current mirrors + Exercise8	Ch 4.1-4.4, Ch 5.1-5.3
Week 15: 16/12 – 22/12	Current mirrors + Exercise9	Ch 5.1-5.3

Review: Common-Source

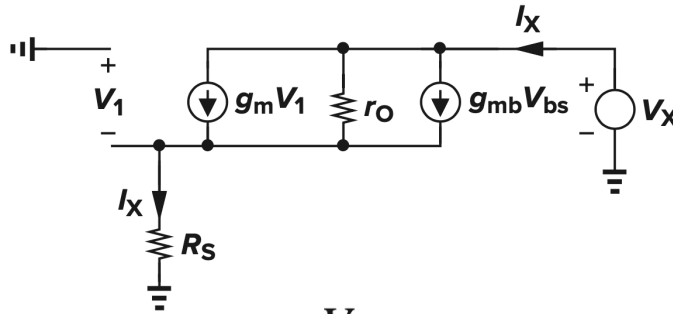
 


$$R_{out} = [1 + (g_m + g_{mb})R_S]r_O + R_S$$

$$= [1 + (g_m + g_{mb})r_O]R_S + r_O$$

$$\frac{V_{out}}{V_{in}} = \frac{-g_m r_O R_D}{R_D + R_S + r_O + (g_m + g_{mb})R_S r_O}$$

Review: Common-Source, Source-Follower


 
 


$$R_{out} = [1 + (g_m + g_{mb})R_S]r_O + R_S$$



$$= [1 + (g_m + g_{mb})r_O]R_S + r_O$$

$$\frac{V_{out}}{V_{in}} = \frac{-g_m r_O R_D}{R_D + R_S + r_O + (g_m + g_{mb})R_S r_O}$$


 
 
 
Source follower: common-drain or voltage buffer




Review: Source-Follower

  

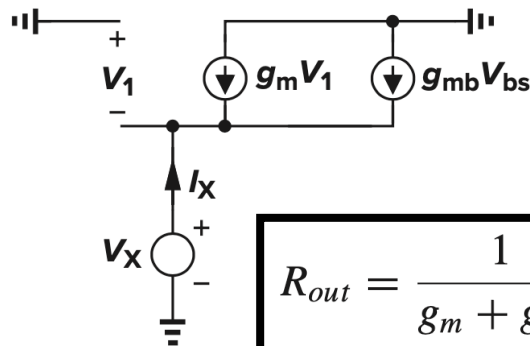  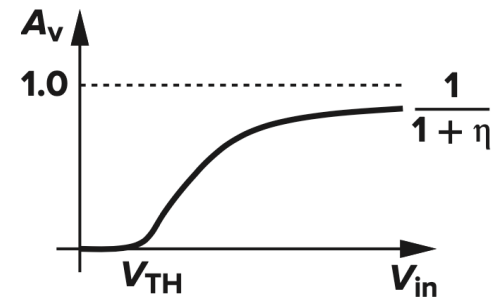
$$A_v = \frac{g_m R_S}{1 + (g_m + g_{mb}) R_S}$$



$$R_{out} = \frac{1}{g_m + g_{mb}}$$

 

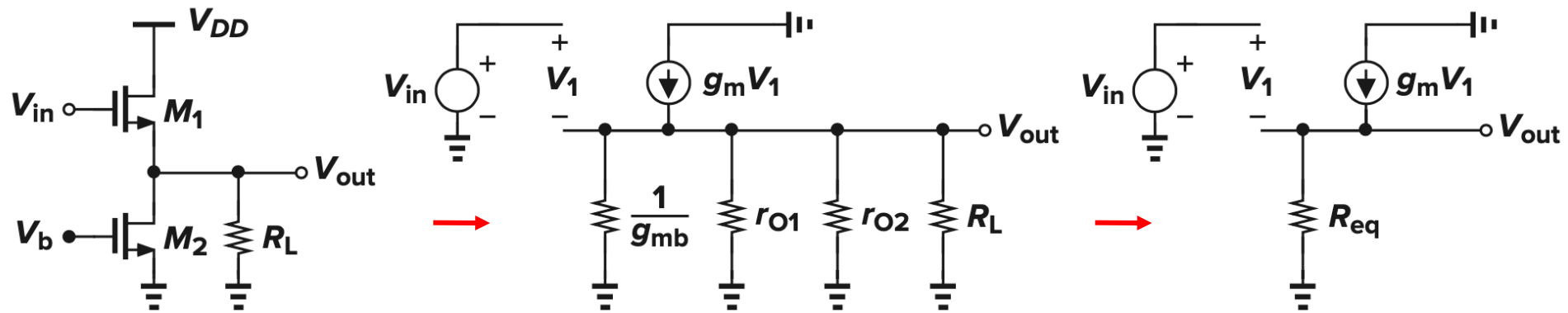
Review: Source Follower with a finite load resistance




$$A_v = \frac{R_{eq}}{R_{eq} + \frac{1}{g_m}}$$

$$R_{eq} = (1/g_{mb}) || r_{O1} || r_{O2} || R_L$$

Example: Calculate the voltage gain

 

Example: Calculate the voltage gain

 



$$A_v = \frac{\frac{1}{g_{m2} + g_{mb2}} \parallel r_{O2} \parallel r_{O1} \parallel \frac{1}{g_{mb1}}}{\frac{1}{g_{m2} + g_{mb2}} \parallel r_{O2} \parallel r_{O1} \parallel \frac{1}{g_{mb1}} + \frac{1}{g_{m1}}}$$

PMOS Source Follower with no body effect


- Source follower drawbacks:
 - **nonlinearity**
 - **voltage headroom limitation**
- Even if biased by an ideal current source, some nonlinearity exists due to the **nonlinear** dependence of V_{TH} upon the **source** potential

PMOS Source Follower with no body effect

  - Source follower drawbacks:
 - **nonlinearity**
 - **voltage headroom limitation**
- Even if biased by an ideal current source, some nonlinearity exists due to the **nonlinear** dependence of V_{TH} upon the **source** potential
- The nonlinearity due to body effect can be eliminated if the bulk is tied to source



Source Follower: a level shifter

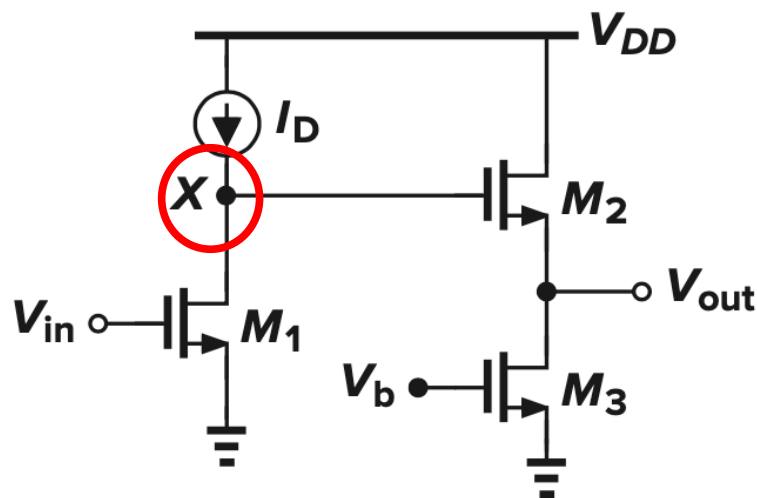


$$V_{GS1} - V_{TH1} \quad \rightarrow \quad V_{GS2} + (V_{GS3} - V_{TH3})$$

- Source followers shift the dc level by V_{GS} , thereby consuming voltage headroom and limiting the swings
- One application of source followers is in performing **voltage-level shift**


Common-Gate Stage

 - A common-gate (CG) stage senses the input at the **source** and produces the output at the **drain**




Common-Gate Stage

 - A common-gate (CG) stage senses the input at the **source** and produces the output at the **drain**



Common-Gate Stage: large signal analysis

 

in saturation


$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_{TH})^2$$

$$V_{out} = V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_{TH})^2 R_D$$

driving M_1 into the triode region if:

$$V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_{TH})^2 R_D = V_b - V_{TH}$$

Common-Gate Stage: large signal analysis

 

in saturation

$$V_{out} = V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_{TH})^2 R_D$$


$$\frac{\partial V_{out}}{\partial V_{in}} = -\mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_{TH}) \left(-1 - \frac{\partial V_{TH}}{\partial V_{in}} \right) R_D$$

$$\boxed{\partial V_{TH} / \partial V_{in} = \partial V_{TH} / \partial V_{SB} = \eta}$$

$$= \mu_n C_{ox} \frac{W}{L} R_D (V_b - V_{in} - V_{TH}) (1 + \eta)$$

$$\boxed{= g_m (1 + \eta) R_D}$$

Common-Gate Stage: large signal analysis

 

in saturation

$$V_{out} = V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_{TH})^2 R_D$$

$$\frac{\partial V_{out}}{\partial V_{in}} = -\mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_{TH}) \left(-1 - \frac{\partial V_{TH}}{\partial V_{in}} \right) R_D$$

$$\boxed{\partial V_{TH} / \partial V_{in} = \partial V_{TH} / \partial V_{SB} = \eta}$$


$$= \mu_n C_{ox} \frac{W}{L} R_D (V_b - V_{in} - V_{TH}) (1 + \eta)$$

$$\boxed{= g_m (1 + \eta) R_D}$$


- for $\lambda = 0$, the **input impedance** (seen at the source of M_1): $\boxed{1 / (g_m + g_{mb})}$

$$\boxed{1 / [g_m (1 + \eta)]}$$


Common-Gate Stage: general case

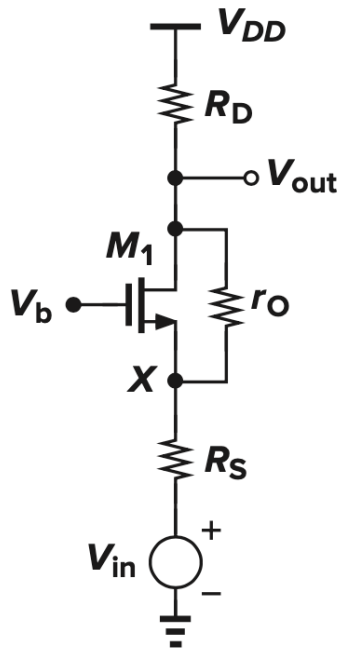


Common-Gate Stage: general case

 

Common-Gate Stage: general case

 


Common-Gate Stage: general case

 

$$V_1 - \frac{V_{out}}{R_D} R_S + V_{in} = 0$$

$$r_O \left(\frac{-V_{out}}{R_D} - g_m V_1 - g_{mb} V_1 \right) - \frac{V_{out}}{R_D} R_S + V_{in} = V_{out}$$

Common-Gate Stage: general case

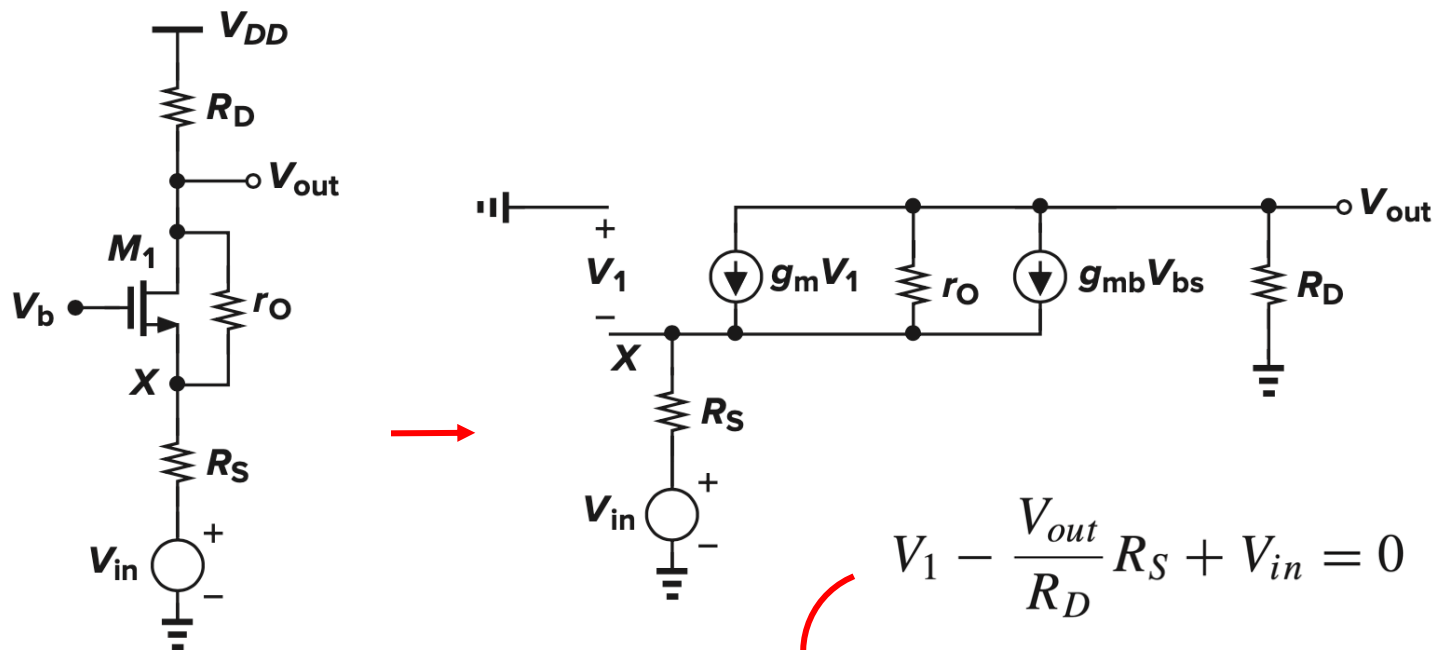


$$V_1 - \frac{V_{out}}{R_D} R_S + V_{in} = 0$$

$$r_O \left(\frac{-V_{out}}{R_D} - g_m V_1 - g_{mb} V_1 \right) - \frac{V_{out}}{R_D} R_S + V_{in} = V_{out}$$


$$r_O \left[\frac{-V_{out}}{R_D} - (g_m + g_{mb}) \left(V_{out} \frac{R_S}{R_D} - V_{in} \right) \right] - \frac{V_{out} R_S}{R_D} + V_{in} = V_{out}$$

Common-Gate Stage: general case

 

$$\frac{V_{out}}{V_{in}} = \frac{(g_m + g_{mb})r_O + 1}{r_O + (g_m + g_{mb})r_O R_S + R_S + R_D} R_D$$

Common-Gate Stage: general case


 


$$\frac{V_{out}}{V_{in}} = \frac{(g_m + g_{mb})r_O + 1}{r_O + (g_m + g_{mb})r_O R_S + R_S + R_D} R_D$$



Gain of a
degenerated CS stage

$$\frac{V_{out}}{V_{in}} = \frac{-g_m r_O R_D}{R_D + R_S + r_O + (g_m + g_{mb})R_S r_O}$$

Input resistance of a CG stage

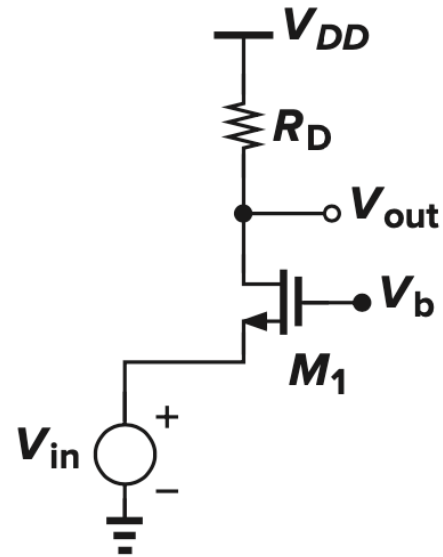 

Input resistance of a CG stage

 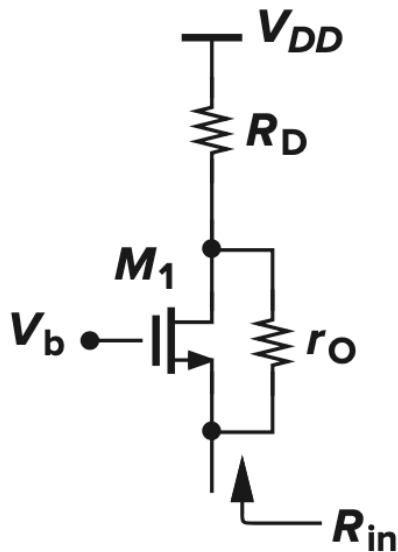


$$R_D I_X + r_O [I_X - (g_m + g_{mb}) V_X] = V_X$$



$$\begin{aligned} \frac{V_X}{I_X} &= \frac{R_D + r_O}{1 + (g_m + g_{mb}) r_O} \\ &\approx \frac{R_D}{(g_m + g_{mb}) r_O} + \frac{1}{g_m + g_{mb}} \end{aligned}$$


Input resistance of a CG stage

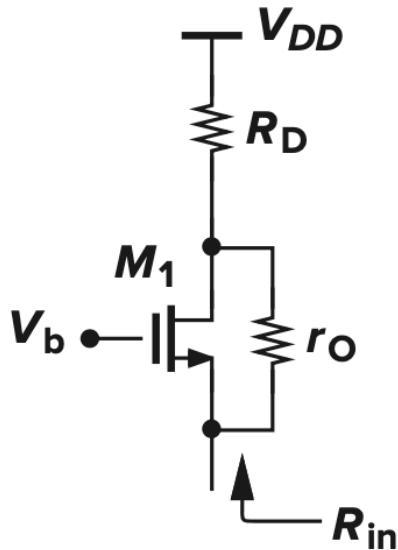

$$\frac{V_X}{I_X} = \frac{R_D + r_O}{1 + (g_m + g_{mb})r_O}$$
$$\approx \frac{R_D}{(g_m + g_{mb})r_O} + \frac{1}{g_m + g_{mb}}$$

- ✓ the **drain impedance** is **divided** by $(g_m + g_{mb})r_O$ when seen at the **source**

Input resistance of a CG stage

 


$$\frac{V_X}{I_X} = \frac{R_D + r_O}{1 + (g_m + g_{mb})r_O}$$
$$\approx \frac{R_D}{(g_m + g_{mb})r_O} + \frac{1}{g_m + g_{mb}}$$

✓ the **drain impedance** is **divided** by $(g_m + g_{mb})r_O$ when seen at the **source**

$$R_D = 0 \quad \rightarrow \quad \frac{V_X}{I_X} = \frac{r_O}{1 + (g_m + g_{mb})r_O}$$
$$= \frac{1}{\frac{1}{r_O} + g_m + g_{mb}}$$

Input resistance of a CG stage

 


$$\frac{V_X}{I_X} = \frac{R_D + r_O}{1 + (g_m + g_{mb})r_O}$$
$$\approx \frac{R_D}{(g_m + g_{mb})r_O} + \frac{1}{g_m + g_{mb}}$$



the input impedance approaches infinity


Output resistance of a CG stage

 

$$R_{out} = \{[1 + (g_m + g_{mb})r_O]R_S + r_O\} \parallel R_D$$

Recall: Output resistance of a degenerated CS

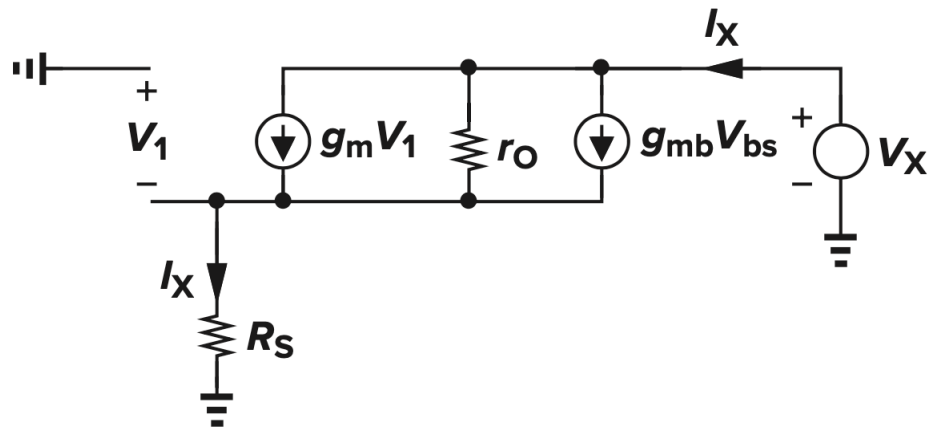- Source degeneration **increases** the output resistance




$$r_O[I_X + (g_m + g_{mb})R_S I_X] + I_X R_S = V_X$$

$$R_{out} = [1 + (g_m + g_{mb})R_S]r_O + R_S$$

$$= [1 + (g_m + g_{mb})r_O]R_S + r_O$$


$$\approx (g_m + g_{mb})r_O R_S + r_O$$

$$= [1 + (g_m + g_{mb})R_S]r_O$$

 


- The overall output resistance is the parallel combination of R_{out} and R_D

Example: Calculate the voltage gain

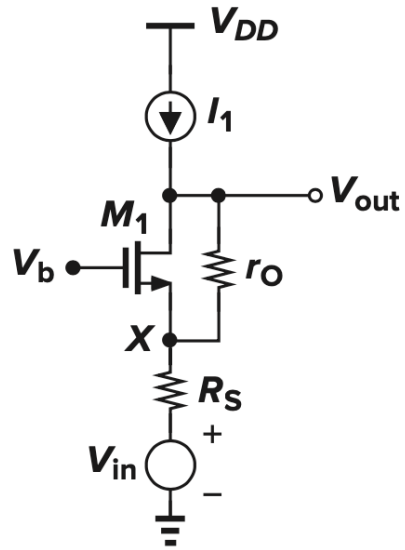

- A common-gate stage with a **current-source load**

Example: Calculate the voltage gain

 

- A common-gate stage with a current-source load

$$\frac{V_{out}}{V_{in}} = \frac{(g_m + g_{mb})r_O + 1}{r_O + (g_m + g_{mb})r_O R_S + R_S + R_D} R_D$$


$$R_D \rightarrow \infty$$




$$A_v = (g_m + g_{mb})r_O + 1$$

Cascode stage

 - The cascade of a **CS stage** and a **CG stage** is called a “cascode” topology, providing many useful properties.



Cascode: bias condition

 

$$V_b - V_{GS2} \geq V_{in} - V_{TH1}$$

$$V_{out} \geq V_b - V_{TH2}$$



$$\begin{aligned} V_{out} &\geq V_{in} - V_{TH1} + V_{GS2} - V_{TH2} \\ &= (V_{GS1} - V_{TH1}) + (V_{GS2} - V_{TH2}) \end{aligned}$$

- ✓ the minimum output level for both transistors to operate in saturation is equal to the overdrive voltage of M_1 plus that of M_2

Cascode: large-signal behavior

