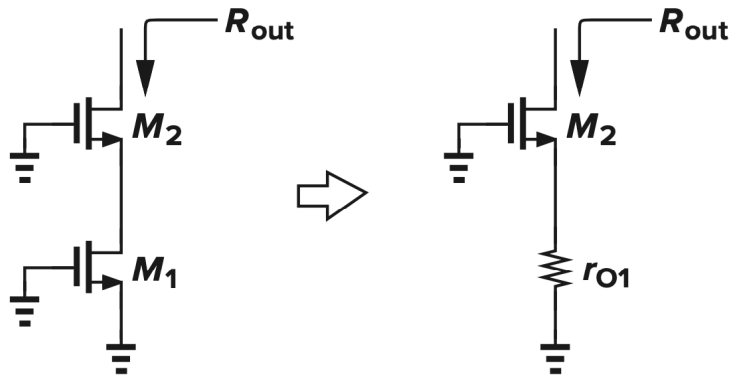


Analog IC design (EE-320), Lecture 8

Prof. Mahsa Shoaran


Institute of Electrical and Micro Engineering, School of Engineering, EPFL

Review: Cascode. Diff Pair



Cascode: high output impedance
 
$$R_{out} \approx (g_{m2} + g_{mb2})r_{O2}r_{O1}$$




$$G_m = I_{out} / V_{in}$$

$$A_v = -G_m R_{out}$$


- For G_m calculation: the output is ac shorted
- For R_{out} calculation: the input voltage is set to zero

Review: Cascode. Diff Pair

 

Cascode: high output impedance

 
$$R_{out} \approx (g_{m2} + g_{mb2})r_{o2}r_{o1}$$



$$G_m = I_{out} / V_{in}$$

$$A_v = -G_m R_{out}$$

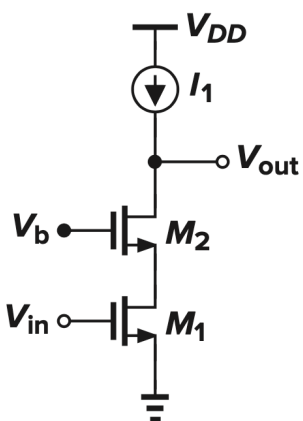
- For G_m calculation: the output is ac shorted
- For R_{out} calculation: the input voltage is set to zero



$$G_m \approx g_{m1}$$


$$R_{out} \approx (g_{m2} + g_{mb2})r_{o2}r_{o1}$$

$$|A_v| = (g_{m2} + g_{mb2})r_{o2}g_{m1}r_{o1}$$

 


Differential input-output characteristics

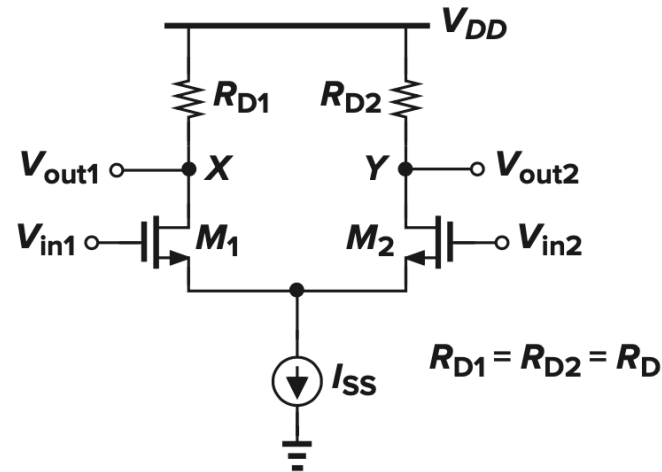(neglecting channel-length modulation and body effect):




 Differential input-output characteristics of a diff pair




Differential input-output characteristics


 
(neglecting channel-length modulation and body effect):




 
Differential input-output characteristics of a diff pair






Common-mode input-output characteristics

  


Common-mode input-output characteristics

  
  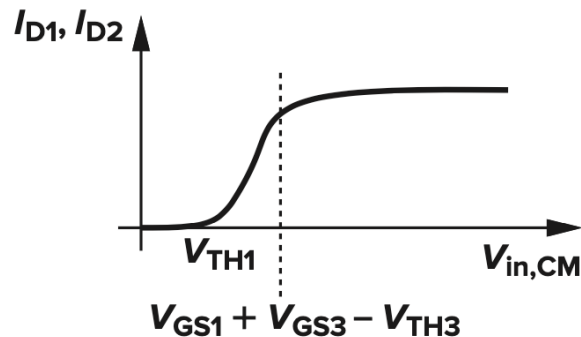
$$V_{GS1} + (V_{GS3} - V_{TH3}) \leq V_{in,CM} \leq \min \left[V_{DD} - R_D \frac{I_{SS}}{2} + V_{TH}, V_{DD} \right]$$






Maximum output swing

 


Single-ended peak-to-peak output swing:

$$V_{DD} - (V_{GS1} - V_{TH1}) - (V_{GS3} - V_{TH3})$$


Large signal analysis

   



Small-signal analysis: gain

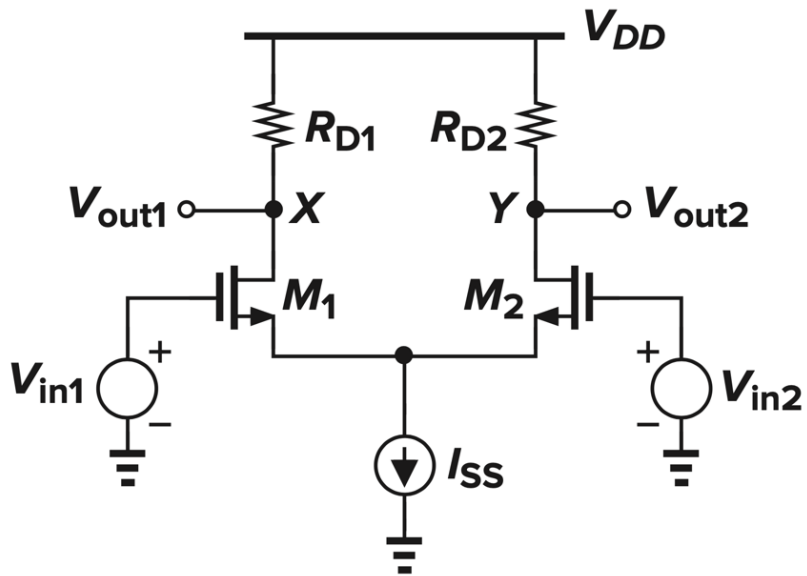

Small-signal analysis: gain (method 1)

 

Small-signal analysis: gain (method 1)

 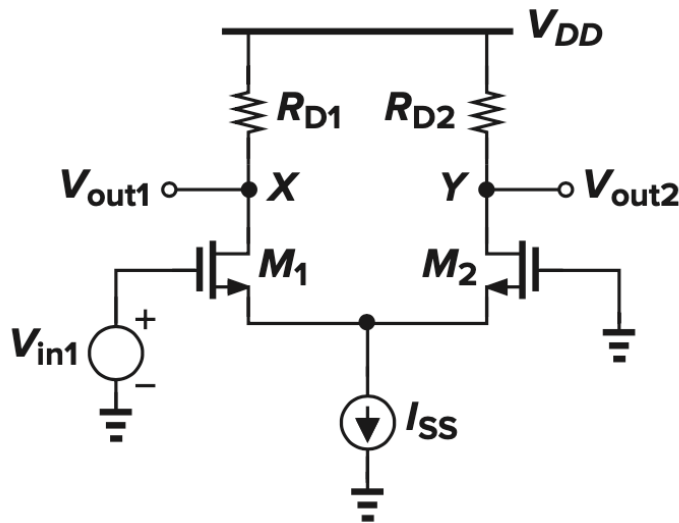


$$\frac{V_X}{V_{in1}} = \frac{-R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$

$$\frac{V_Y}{V_{in1}} = \frac{R_D}{\frac{1}{g_{m2}} + \frac{1}{g_{m1}}}$$



$$(V_X - V_Y)|_{\text{Due to } V_{in1}} = \frac{-2R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}} V_{in1}$$

Small-signal analysis: gain (method 1)

 


$$(V_X - V_Y)|_{\text{Due to } V_{in1}} = \frac{-2R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}} V_{in1}$$

$$g_{m1} = g_{m2} = g_m \quad \downarrow$$



$$(V_X - V_Y)|_{\text{Due to } V_{in1}} = -g_m R_D V_{in1}$$

$$(V_X - V_Y)|_{\text{Due to } V_{in2}} = g_m R_D V_{in2}$$

 

$$\boxed{\frac{(V_X - V_Y)_{tot}}{V_{in1} - V_{in2}} = -g_m R_D}$$

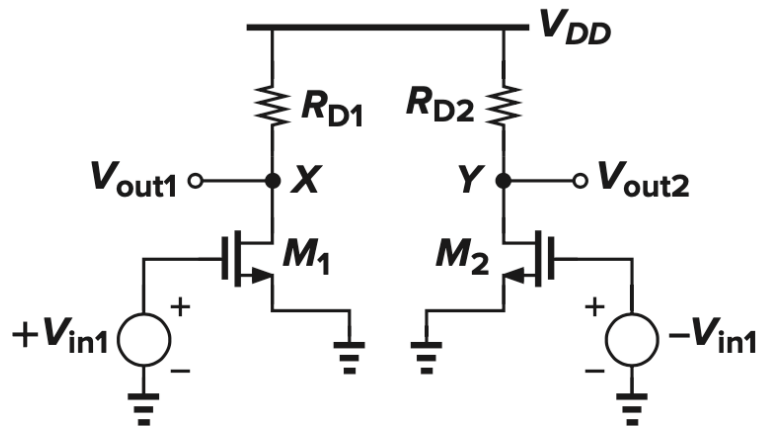 Small-signal gain with half-circuit model (method 2)



- ✓ If a **fully-symmetric differential pair** senses **differential inputs** (i.e., the two inputs change by equal and opposite amounts from the equilibrium condition), then the concept of “**half circuit**” can be applied



$$V_X / V_{in1} = -g_m R_D$$

$$V_Y / (-V_{in1}) = -g_m R_D$$




$$(V_X - V_Y) / (2V_{in1}) = -g_m R_D$$

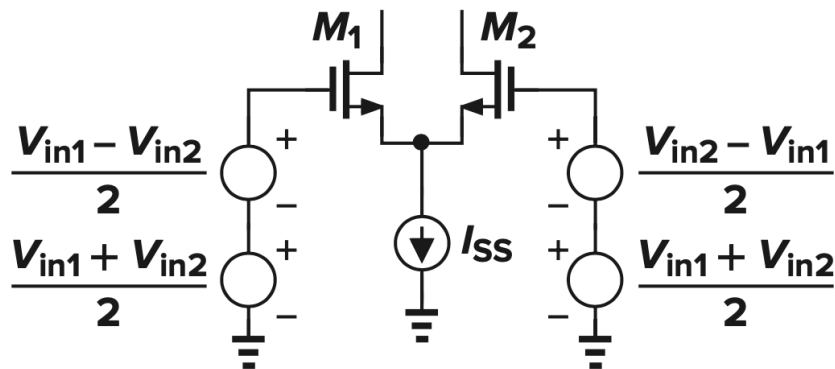 
Half-circuit model for non-differential inputs



 
Half-circuit model for non-differential inputs




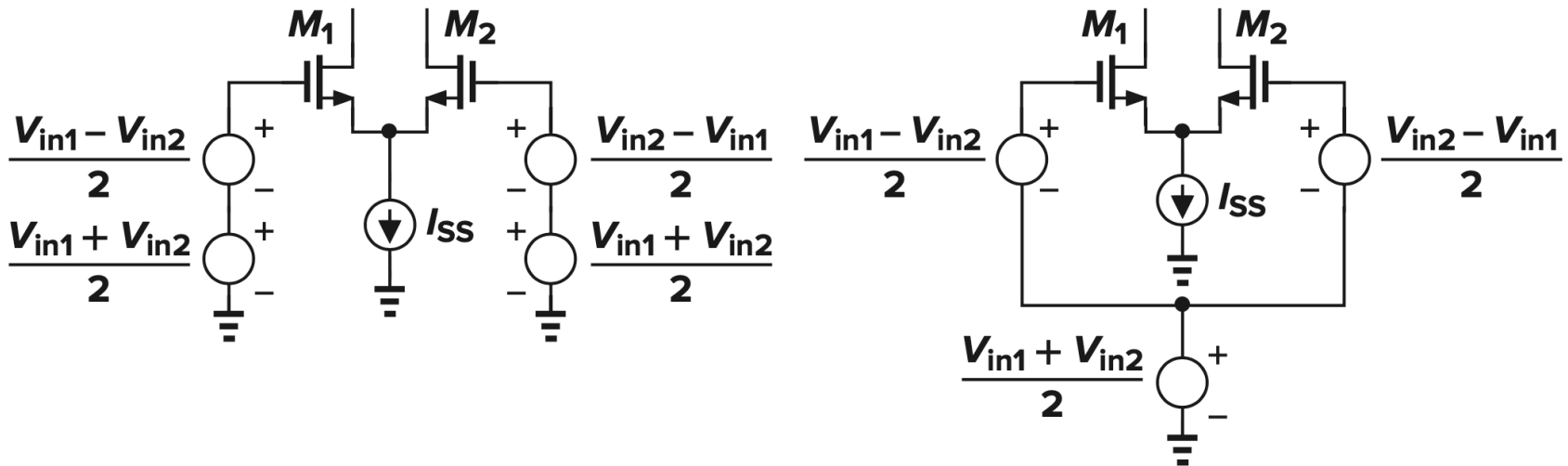
Conversion of arbitrary inputs to differential and common-mode components




 
Half-circuit model for non-differential inputs



 
 
Half-circuit model for non-differential inputs



 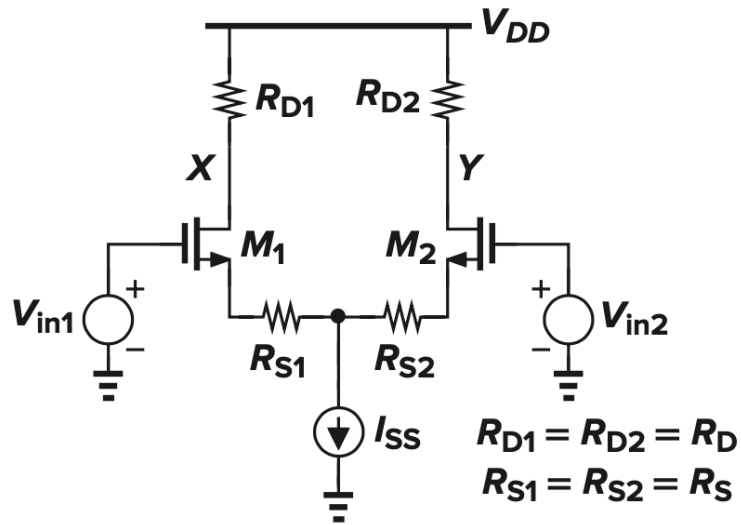Degenerated differential pair for improved linearity



 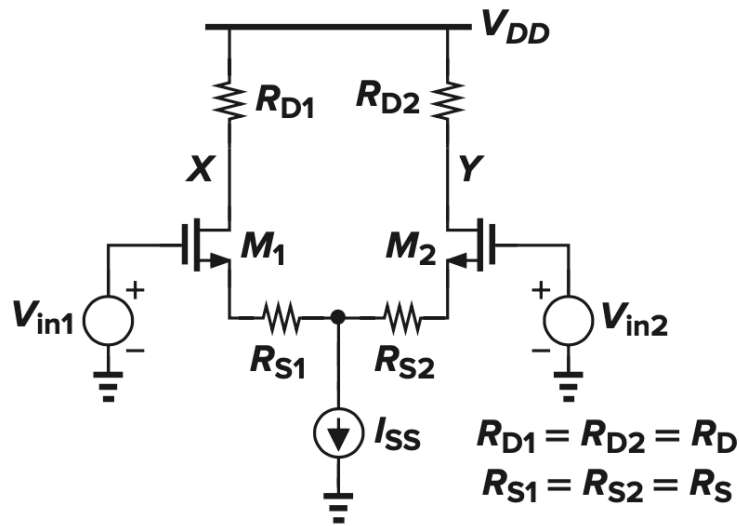Degenerated differential pair for improved linearity




half-circuit:

$$|A_v| = \frac{R_D}{\frac{1}{g_m} + R_S}$$

✓ the circuit trades **gain** for **linearity**


Common-mode response

 - An important advantage of differential amplifiers is their ability to **suppress the effect of common-mode** perturbations
 - In reality, the circuit is not fully symmetric nor does the current source exhibit an infinite output impedance
 - As a result, a fraction of the input CM variation appears at the output




Common-mode response

 - An important advantage of differential amplifiers is their ability to **suppress the effect of common-mode** perturbations
 - In reality, the circuit is not fully symmetric nor does the current source exhibit an infinite output impedance
 - As a result, a fraction of the input CM variation appears at the output



- ✓ In a symmetric circuit, input CM variations disturb the bias points, altering the **gain** and possibly limiting the swing


Example

 

Assume that $(W/L)_{1,2}=25/0.5$, $\mu_n C_{ox}=50\mu A/V^2$, $V_{TH}=0.6V$, $\lambda=\gamma=0$, and $V_{DD}=3V$.

- ❖ What is the required input CM voltage for which R_{SS} sustains 0.5V?
- ❖ Calculate R_D for a differential gain of 5.
- ❖ What happens at the output if the input CM level is 50 mV higher than the value calculated above?

Example

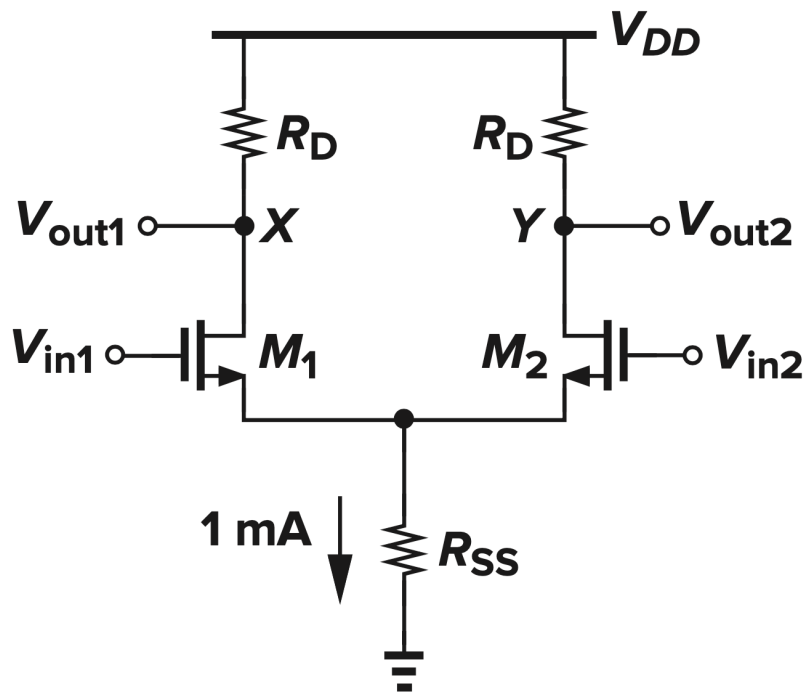

Assume that $(W/L)_{1,2}=25/0.5$, $\mu_n C_{ox}=50\mu A/V^2$, $V_{TH}=0.6V$, $\lambda=\gamma=0$, and $V_{DD}=3V$.

- ❖ What is the required input CM voltage for which R_{SS} sustains 0.5V?
- ❖ Calculate R_D for a differential gain of 5.
- ❖ What happens at the output if the input CM level is 50 mV higher than the value calculated above?


$$I_{D1} = I_{D2} = 0.5 \text{ mA}$$



$$V_{GS1} = V_{GS2} = \sqrt{\frac{2I_{D1}}{\mu_n C_{ox} \frac{W}{L}}} + V_{TH} = 1.23 \text{ V}$$

$$V_{in,CM} = V_{GS1} + 0.5 \text{ V} = 1.73 \text{ V}$$

Example

 


Assume that $(W/L)_{1,2}=25/0.5$, $\mu_n C_{ox}=50\mu A/V^2$, $V_{TH}=0.6V$, $\lambda=\gamma=0$, and $V_{DD}=3V$.

- ❖ What is the required input CM voltage for which R_{SS} sustains 0.5V?
- ❖ Calculate R_D for a differential gain of 5.
- ❖ What happens at the output if the input CM level is 50 mV higher than the value calculated above?

$$g_m = \sqrt{2\mu_n C_{ox} (W/L) I_{D1}} = 1/(632 \Omega) \quad \rightarrow \quad R_D = 3.16 \text{ k}\Omega$$


Example

 

Assume that $(W/L)_{1,2}=25/0.5$, $\mu_n C_{ox}=50\mu A/V^2$, $V_{TH}=0.6V$, $\lambda=\gamma=0$, and $V_{DD}=3V$.


- ❖ What is the required input CM voltage for which R_{SS} sustains 0.5V?
- ❖ Calculate R_D for a differential gain of 5.
- ❖ What happens at the output if the input CM level is 50 mV higher than the value calculated above?

$$\begin{aligned}
 |\Delta V_{X,Y}| &= \Delta V_{in,CM} \frac{R_D/2}{R_{SS} + 1/(2g_m)} \\
 &= 50 \text{ mV} \times 1.94 \\
 &= 96.8 \text{ mV}
 \end{aligned}$$

 


Common-mode response

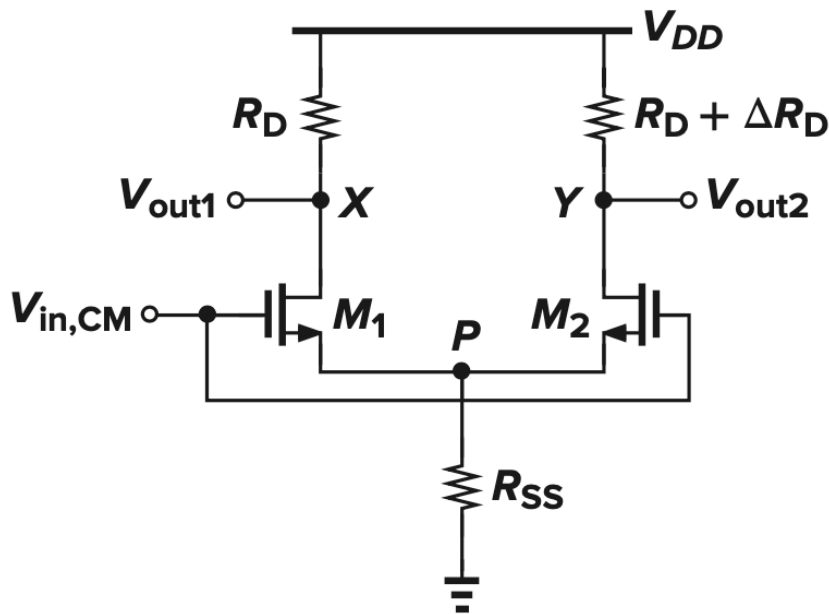- The **finite output impedance** of the tail current source results in some **CM gain** in a symmetric differential pair: usually a **minor** concern
- More troublesome: variation of **differential output** as a result of a change in **CM input**, due to **asymmetry (mismatches)** of two sides during manufacturing



Common-mode response

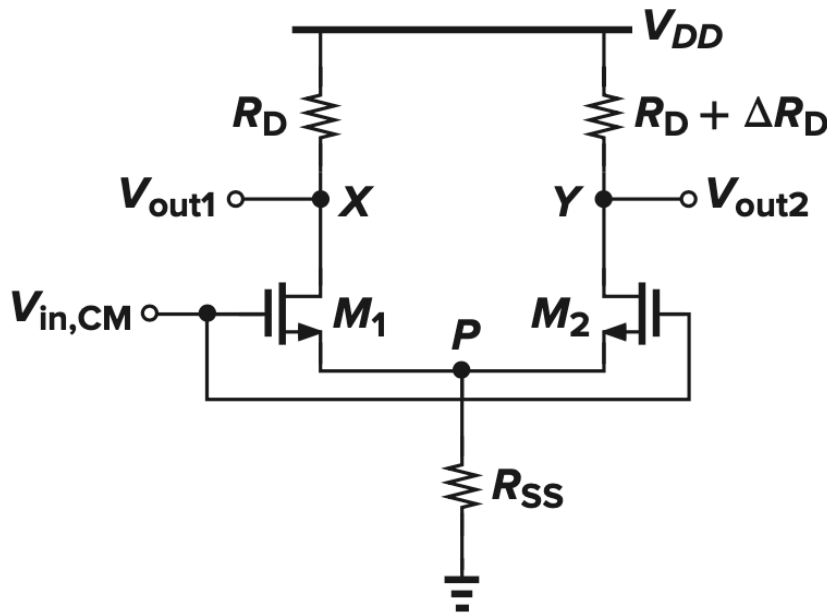
- The **finite output impedance** of the tail current source results in some **CM gain** in a symmetric differential pair: usually a **minor** concern
- More troublesome: variation of **differential output** as a result of a change in **CM input**, due to **asymmetry (mismatches)** of two sides during manufacturing



$$\Delta V_P = \frac{R_{SS}}{R_{SS} + \frac{1}{2g_m}} \Delta V_{in,CM}$$

Common-mode response

 - The **finite output impedance** of the tail current source results in some **CM gain** in a symmetric differential pair: usually a **minor** concern
- More troublesome: variation of **differential output** as a result of a change in **CM input**, due to **asymmetry (mismatches)** of two sides during manufacturing




$$\Delta V_P = \frac{R_{SS}}{R_{SS} + \frac{1}{2g_m}} \Delta V_{in,CM}$$

$$\Delta V_X = -\Delta V_{in,CM} \frac{g_m}{1 + 2g_m R_{SS}} R_D$$


$$\Delta V_Y = -\Delta V_{in,CM} \frac{g_m}{1 + 2g_m R_{SS}} (R_D + \Delta R_D)$$

 CM noise in the presence of resistor mismatch



- The common-mode response of differential pairs depends on the **output impedance** of the tail current source and **asymmetries** in the circuit
- Two effects: variation of the **output CM** level (in the absence of mismatch) and **conversion** of input CM variations to **differential** components at the output
- The latter effect is much more severe, so the CM response should be studied with **mismatches** taken into account


 
CM noise in the presence of resistor mismatch





- The common-mode response of differential pairs depends on the **output impedance** of the tail current source and **asymmetries** in the circuit
- Two effects: variation of the **output CM** level (in the absence of mismatch) and **conversion** of input CM variations to **differential** components at the output
- The latter effect is much more severe, so the CM response should be studied with **mismatches** taken into account

Common-mode response with input pair mismatch

  - The asymmetry in the circuit comes from both the **load resistors** and the **input transistors**, the latter contributing a typically **much greater mismatch**
- Due to **dimension** and **threshold** voltage mismatches, the two transistors carry slightly **different currents** and have **unequal g_m**



 
 
Common-mode response with input pair mismatch



$$(g_{m1} + g_{m2})(V_{in,CM} - V_P)R_{SS} = V_P$$

$$V_P = \frac{(g_{m1} + g_{m2})R_{SS}}{(g_{m1} + g_{m2})R_{SS} + 1} V_{in,CM}$$

  Common-mode response with input pair mismatch



$$(g_{m1} + g_{m2})(V_{in,CM} - V_P)R_{SS} = V_P$$

$$V_P = \frac{(g_{m1} + g_{m2})R_{SS}}{(g_{m1} + g_{m2})R_{SS} + 1} V_{in,CM}$$



$$\begin{aligned} V_X &= -g_{m1}(V_{in,CM} - V_P)R_D \\ &= \frac{-g_{m1}}{(g_{m1} + g_{m2})R_{SS} + 1} R_D V_{in,CM} \end{aligned}$$

$$V_Y = -g_{m2}(V_{in,CM} - V_P)R_D$$

$$= \frac{-g_{m2}}{(g_{m1} + g_{m2})R_{SS} + 1} R_D V_{in,CM}$$



$$V_X - V_Y = -\frac{g_{m1} - g_{m2}}{(g_{m1} + g_{m2})R_{SS} + 1} R_D V_{in,CM}$$

$$A_{CM-DM} = -\frac{\Delta g_m R_D}{(g_{m1} + g_{m2})R_{SS} + 1}$$


CMRR: common-mode rejection ratio

- For a meaningful comparison of differential circuits, the **undesirable differential component produced by CM variations** must be normalized to the **wanted differential output resulting from amplification**
 - “Common-mode rejection ratio” (**CMRR**) defined as the desired gain divided by the undesired gain




$$\text{CMRR} = \left| \frac{A_{DM}}{A_{CM-DM}} \right|$$

  

CMRR?

 


Recall: differential gain

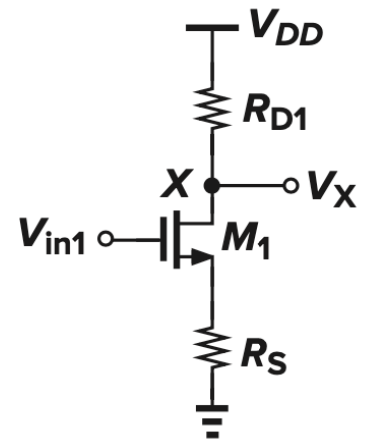 
 


$$\frac{V_X}{V_{in1}} = \frac{-R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}} \quad \frac{V_Y}{V_{in1}} = \frac{R_D}{\frac{1}{g_{m2}} + \frac{1}{g_{m1}}}$$

$$|A_{DM}| = \frac{R_D}{2} \frac{g_{m1} + g_{m2} + 4g_{m1}g_{m2}R_{SS}}{1 + (g_{m1} + g_{m2})R_{SS}}$$

 

Recall: common-mode gain

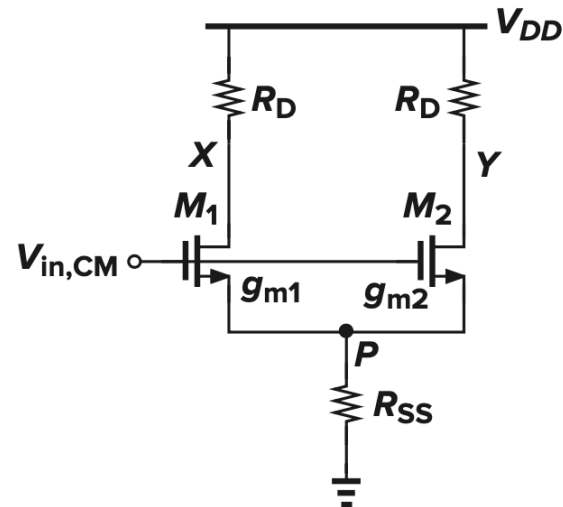 

$$A_{CM-DM} = - \frac{\Delta g_m R_D}{(g_{m1} + g_{m2}) R_{SS} + 1}$$

$$\text{CMRR} = \left| \frac{A_{DM}}{A_{CM-DM}} \right|$$

$$\begin{aligned} \text{CMRR} &= \frac{g_{m1} + g_{m2} + 4g_{m1}g_{m2}R_{SS}}{2\Delta g_m} \\ &\approx \frac{g_m}{\Delta g_m} (1 + 2g_m R_{SS}) \end{aligned}$$

$$2g_m R_{SS} \gg 1$$



$$\text{CMRR} \approx 2g_m^2 R_{SS} / \Delta g_m$$

$$g_m = (g_{m1} + g_{m2})/2 \quad \Delta g_m = g_{m1} - g_{m2}$$



$$= \frac{2g_m R_{SS}}{\left(\frac{\Delta g_m}{g_m} \right)}$$

$$\text{CMRR} = \left| \frac{A_{DM}}{A_{CM-DM}} \right|$$

$$\text{in dB: } \text{CMRR}(dB) \equiv 20 \log \left| \frac{A_{DM}}{A_{CM-DM}} \right|$$

CMRR should be as large as possible

Differential Pair with MOS Loads

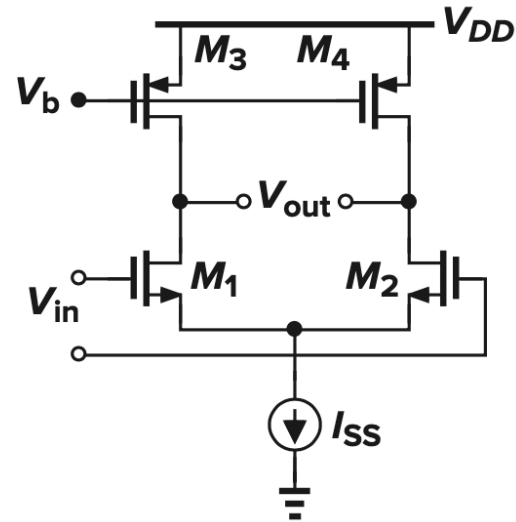 

$$A_v = -g_{mN} (g_{mP}^{-1} \parallel r_{ON} \parallel r_{OP})$$


$$\approx -\frac{g_{mN}}{g_{mP}}$$

$$A_v = -g_{mN}(r_{ON} \parallel r_{OP})$$

$$A_v \approx -\sqrt{\frac{\mu_n(W/L)_N}{\mu_p(W/L)_P}}$$



Cascode differential pair

 - The gain of the differential pair with current-source loads relatively low, in the range of 5 to 10 in nanometer technologies
 - increase the output impedance of both PMOS and NMOS by **cascoding**



Cascode differential pair

 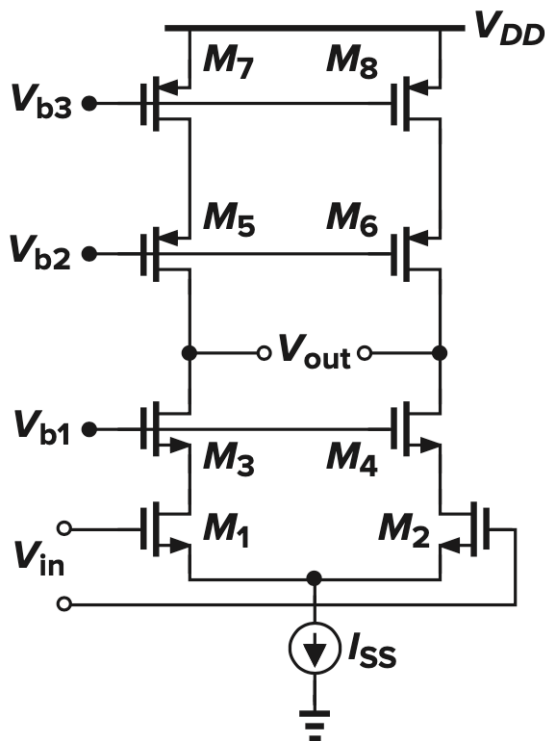- The gain of the differential pair with current-source loads relatively low, in the range of 5 to 10 in nanometer technologies
 - increase the output impedance of both PMOS and NMOS by **cascoding**
 - increases the differential **gain** at the cost of more **headroom**



$$|A_v| \approx g_{m1}[(g_{m3}r_{o3}r_{o1}) \parallel (g_{m5}r_{o5}r_{o7})]$$