

EE-334

Digital System Design

Discussion for Exercise 4
Key Lock FSM

Andreas Burg

FSM for Key Lock: Considerations

- Initial state: door closed (RLED on, GLED off)
- Once any key is pressed, both LEDs go off
- Each key need to be pressed and released
- Key combination 0,2,1 leads to an open door (1 cycle, GLED on) before returning to door closed
- Any other key combination still requires 3 key strokes to return to door closed
- Which states do we need?
 - Door closed
 - Door open
 - Track history of key presses & press/release
 - 2 states for each correct key (press and release, except last one where release is Open)
 - 2 states for incorrect keys (press and release, except last one where release is Closed)

FSM for Key Lock with Moore FSM


KeyValid $\in \{'0', '1'\}$

Key $\in \{0,1,2,3\}$

GLLED $\in \{'0', '1'\}$

RLED $\in \{'0', '1'\}$

	KeyValid	Key
P	'1'	-
R	'0'	-

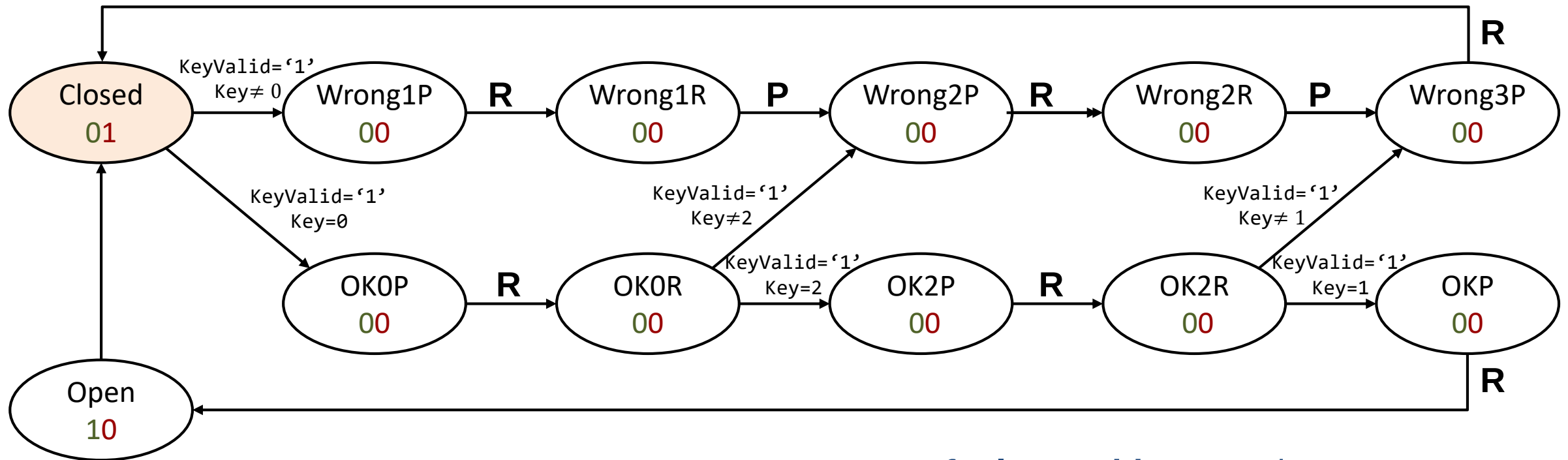

Default transition: stay in same state

FSM for Key Lock with Moore FSM

KeyValid $\in \{'0', '1'\}$

Key $\in \{0,1,2,3\}$

GLED $\in \{'0', '1'\}$

RLED $\in \{'0', '1'\}$

Counter

CountEN $\in \{'0', '1'\}$

CountClear $\in \{'0', '1'\}$

	KeyValid	Key
P	'1'	-
R	'0'	-

