

EE-334

Digital System Design

Custom Digital Circuits
Finite State Machines
and their description in VHDL

Andreas Burg

Purpose/Task of Finite State Machines


- **Finite state machines (FSMs)** are a mathematical model of computation
- FSMs describe discrete time systems
 - At each point in time the **FSM is in exactly one of its possible states**
 - **State changes** instantly and only **when proceeding from one time instant to the next**
 - Perfect match with synchronous design, where state changes only with clock edge
 - The **outputs and the next state** are **defined by** the **inputs and the present state**
- In digital system design, the FSM formalism is particularly useful for
 - **Functional specification** of control- and protocol-tasks
 - **Modeling** overall system behavior in an abstract way for simulation
 - **Formal verification** (with the help of Automata Theory)
 - **Describing sequential** circuits for synthesis

Purpose/Task of Finite State Machines


- **Every practical discrete-time system** with a finite number of states and inputs **can be described** completely (datapath and control) **as a finite-state-machine**
 - However, **for datapaths**, the number of states explodes and **FSMs are not a convenient description**.
- In practice, the **FSM formalism is mostly used for the control part**
 - **control** the operations and the flow of data in **datapaths**
 - generate sequences of control signals to orchestrate operation over time
 - internal results from a datapath and modify dataflow accordingly
 - **manage the communication between** system **components** through sequential protocols
 - react to inputs depending on the current state of the system
 - **keep track of the “relevant” history** of a system in compressed form (state)

Purpose/Task of Finite State Machines

- Some examples for use of FSMs

 

 Datapath of a dedicated DSP block (here: FIR filter)



Handshake protocol for connected chips/components



Control of traffic lights

Mealy FSM: Formal Specification



- **Mealy-FSMs are the most generic description of an FSM** (can, in principal fully describe any synchronous system on a functional level)
- **Inputs, outputs, and states are abstract quantities** chosen from finite sets
- **Formal specification of Mealy FSM:** Separate functions compute
 - the output from the present state and the input
 - the next state from the present state and the input

$$\begin{array}{ll} o(k) = g(i(k), s(k)) & \text{Output function} \\ s(k+1) = f(i(k), s(k)) & \text{Next state function} \end{array}$$

$$s(0) = s_0 \quad \text{Initial state}$$

$$\text{Latency} = 0$$
  
$$\begin{array}{ll} i(k) \in I & \text{Input} \\ o(k) \in O & \text{Output} \\ s(k) \in S & \text{State} \end{array}$$



State Diagram Representation

- Formal FSM definition describes the operation, but not the transfer functions
- **State diagrams** provide a graphical means to represent
 - the next state transfer function and
 - the output


- **State diagram formalism**

- State represented by vertices
- Transition represented by edges
- Input (condition) and output: annotated on edges $\langle \text{input/output} \rangle$

Default transition: no input annotation
Taken when the condition for no other transition is met

- **Initial (RESET) state** defines $s(0)$
 
$$I = \{a, b\}, S = \{p, q, r, t\}, O = \{0, 1\}$$




State Table Representation

- State diagrams become difficult to handle for complex FSMs
- **Table representation** of next-state and output functions is then **more convenient**
 - Specifies the next-state-function and the output-function in tabular form
 - Equivalent to the state diagram (except for not containing the reset state)

next-state-function

$i(k)$	a	b
$s(k)$	$s(k + 1)$	
p	r	t
q	p	q
r	q	r
t	r	p

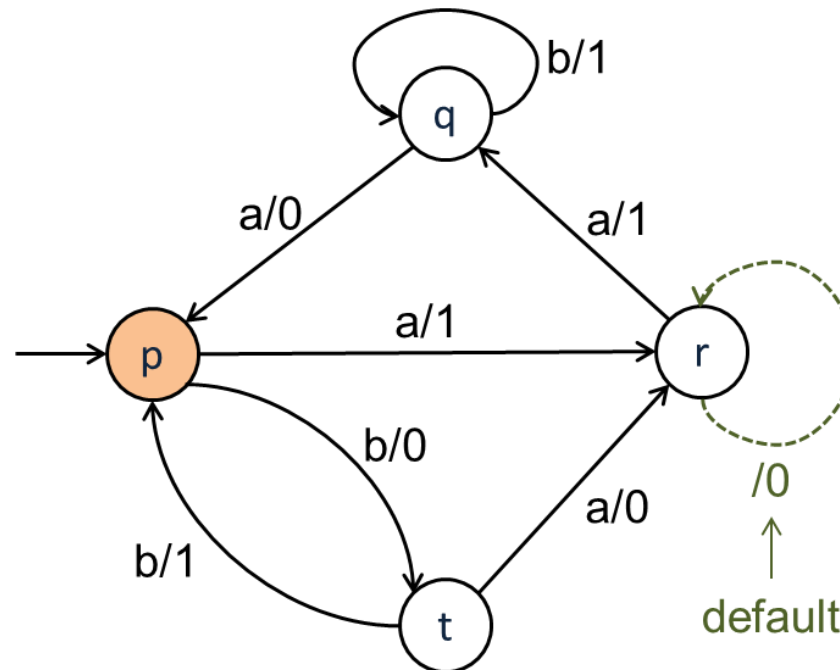

output-function

$i(k)$	a	b
$s(k)$	$o(k)$	
p	1	0
q	0	1
r	1	0
t	0	1

Moore FSM: Formal Specification



- **Moore-FSMs** are a less generic form of FSMs
 - Output is only a function of the present state

$$\begin{array}{ll} o(k) = g(s(k)) & \text{Output function} \\ s(k+1) = f(i(k), s(k)) & \text{Next state function} \end{array}$$

$$s(0) = s_0 \quad \text{Initial state}$$

$$\text{Latency} = \mathbf{1}$$
  
$$\begin{array}{ll} i(k) \in I & \text{Input} \\ o(k) \in O & \text{Output} \\ s(k) \in S & \text{State} \end{array}$$



- The **Moore structure** mainly **impacts latency**
 - Outputs can not react directly to an input in the same state (time step)
 - No direct combinational logic between input and output

Mealy FSM: Formal Specification and RTL Diagram

- **Mealy-FSMs are the most generic description of an FSM** (can, in principal fully describe any synchronous system on a functional level)

Formal specification

- Outputs and next state are defined based on separate transfer functions
- Initial state required to initialize the iteration


$$\begin{array}{ll} o(k) = g(i(k), s(k)) & \text{Output function} \\ s(k+1) = f(i(k), s(k)) & \text{Next state function} \end{array}$$

$$s(0) = s_0 \quad \text{Initial state}$$

$$\text{Latency} = 0$$

RTL diagram

 - Two blocks of **combinational logic** to
 - Compute the next state
 - Compute the output
- A **register** to store the present state




Descriptions of Moore FSM

- **Moore FSMs simplify the state diagram** and the table representation
 - **Outputs are associated (annotated) with states**
 - Transitions without annotation correspond to the default transitions (only one default transition per state!)





next-state- and output-function

$i(k)$	a	b	
$s(k)$	$s(k + 1)$		$o(k)$
u	z	w	1
v	z	w	0
w	x	u	0
x	y	x	0
y	v	y	1
z	z	x	1

 


Some Rules for Valid FSMs

- **Completeness:** Next-state-function and output-function must be specified for all states and for all possible inputs (Mealy)
 - Default transition collapses all so far unspecified transitions into one
 - Multiple identical transitions can be collapsed with OR, if they end up in the same state and produce the same output
- **Uniqueness:** Next-state-function and output-function must be unique
 - the same input/state combination can never result in two conflicting next-states and/or outputs

    


RTL Architecture of FSMs

- **Formal definition of FSMs provides** immediately the **RTL architecture diagram** for the digital implementation
- Required **hardware components**
 - A **combinational logic** block that computes the output $o(k)$ using the function g
 - A **combinational logic** block that computes the next state $s(k + 1)$ using the function f
 - A **register (Flip-Flop)** that stores the current state $s(k)$ and updates it to $s(k + 1)$ on each clock edge

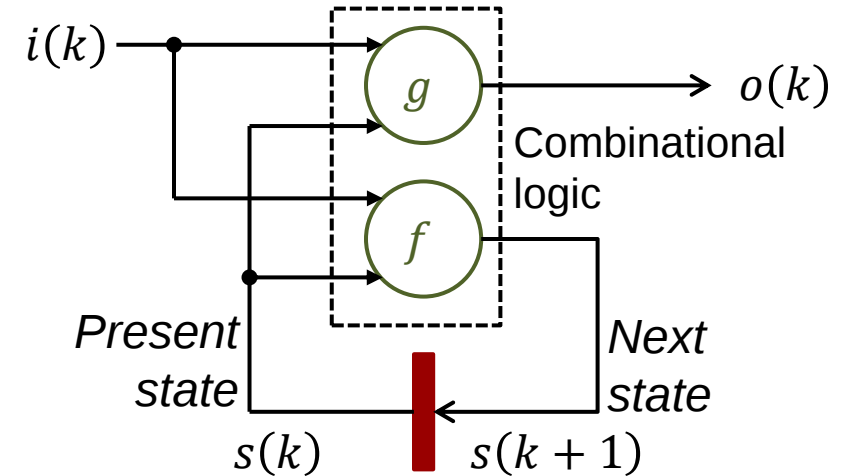

Specifying FSMs for Digital (RTL) Circuits


- Abstract **FSM specification** relies on **abstract** (finite) **sets for states, inputs, and outputs** which do not provide insight how these materialize in a real system
- **Impact of digital circuit implementation**
 - states, inputs, and outputs have a binary representation
 - FSMs typically have multiple inputs and multiple outputs
 - Each output has its own transfer function
 - State transitions (and outputs) are defined by the value of multiple inputs

 

Specifying FSMs for Digital Circuits


- Many transitions do not depend on all input signals

 - Example:** go through 6 states when an enable signal ($En='1'$) is set. In the last state, wait until $Clr='1'$ before returning to the first state, regardless of En



i	En	Clr
a	0	0
b	0	1
c	1	0
d	1	1

 - Boolean expressions and the use of “don’t cares” (‘-’) merge equivalent transitions



	En	Clr
A	1	-
B	-	1

$A : En == '1'$
 $B : Clr == '1'$

Specifying FSMs for Digital Circuits


- **Caveat: Implicit merging of state transitions**
 - Conditions based on boolean functions are not necessarily mutually exclusive
 - Incomplete conditions: using “don’t care” also leads to non-mutually-exclusive conditions
- Remember, next-state- and output-functions must be unambiguous

**Specifying state transitions with incomplete conditions
must be done with great care**

- **Risk of mismatch between formal specification and implementation:**
 - HDL descriptions often resolve ambiguities through sequential formulation of the conditions
 - Formal specification of FSMs does not imply precedence of multiple conditions!!

Specifying FSMs for Digital Circuits

 - Example for ambiguous state transition specifications, resolved “accidentally” in different VHDL specifications




```
case STATExDP is
  -- Initial state
when A =>
  if ENxS = '1' then
    STATExDN <= B;
  end if;
  if CLRxS = '1' then
    STATExDN <= C;
  end if;
```

```
case STATExDP is
  -- Initial state
when A =>
  if CLRxS = '1' then
    STATExDN <= C;
  end if;
  if ENxS = '1' then
    STATExDN <= B;
  end if;
```

What happens if $ENxS = '1'$ and $CLRxS = '1'$???

VHDL Implementation of FSMs

- To implement an FSM in VHDL we directly describe its RTL diagram components
 - The **state register** corresponds to a **clocked process** (register)
 - The two **transfer functions g and f** correspond Boolean logic that **can be realized as**
 - **Concurrent statements**: one for each output and for the next state
 - **Sequential process(es)**: different options
- **Implementation of transfer functions based on processes** is often preferred

 

State Register Description

- Clocked process **only assigns next state to the present state**
 - Next state defined in separate processes

```
-- Clocked Process, generating a FlipFlop behavior
p_seq: PROCESS (clock_signal, async_reset_signal) IS
BEGIN -- process name: p_seq
    IF async_reset_signal = '0|1' THEN
        present_state_signal <= constant;
    ELSIF clock_signal'EVENT AND clock_signal = '1' THEN
        present_state_signal <= next_state_signal;
    END IF;
END PROCESS p_seq;
```

Output and Next State Logic in a Single Process

- Logic with a **single combinational process** is often the **most readable**
 - Start with a **CASE** statement to **identify the present state**
 - **IF** statements for each state represent conditions for the **next state** and **outputs** as a function of the **FSM inputs**

```
-- FSM Logic Process (for next state and/or outputs)
process_name: PROCESS (present_state_signal,
                        FSM_input_signals) IS

BEGIN
    -- Default assignments
    next_state_signal    <= present_state_signal;
    FSM_output_signal_1 <= default_output_expression;

    CASE present_state_signal IS
        WHEN state_1 =>
            -- Conditional statements based on inputs
            IF condition_1_on_FSM_input_signals THEN
                next_state_signal <= next_state_specification;
                FSM_output_signal_1 <= output_expression;
            END IF;
            ...
        WHEN state_2 =>
            ...
        WHEN OTHERS =>
            ...
    END CASE;
END PROCESS process_name;
```

FSM State Encoding

- State representation is irrelevant from a functional perspective
- **For implementation:** abstract **states must be represented with multiple bits**

- Each state must be assigned a unique binary representation

- Minimum bit encoding

$$K \text{ states} \Rightarrow \lceil \log_2 k \rceil \text{ bits}$$

- More bits than necessary can be used to represent the state of a system
- For representing K states with B_K bits the number of possible state encodings is

$$\frac{(2^{B_K} - 1)!}{(2^{B_K} - K)! B_K!}$$


Parasitic States

- Consider an FSM with K states encoded with $B_K \geq \lceil \log_2 K \rceil$ bits

of physical states
 2^{B_K}

of logical states
 K

- In some cases, $2^{B_K} > K$
- Parasitic states:** unused physical states
 - For parasitic states, the *behavior of an FSM implementation is deterministic and defined by the circuit implementation, but **not specified***
 - Transition into a parasitic state is triggered by unspecified input => **State-transitions must be specified completely** (possibly using default transitions)
- Impact varies from *erroneous output* to *unspecified behavior for some cycles* to *complete lock-up*

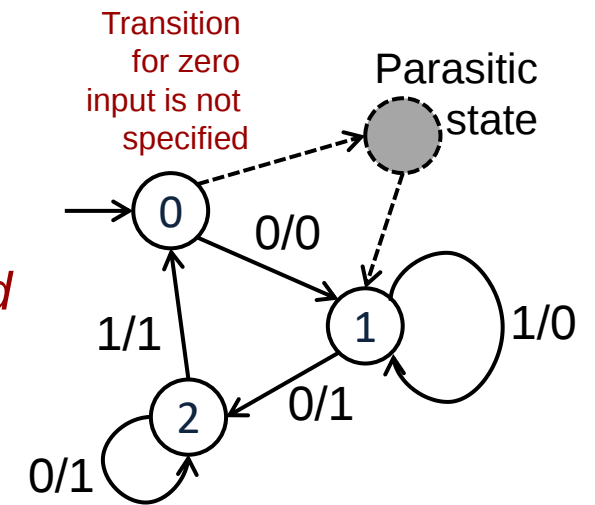

Defining States as Enumerated Types

- **Manually encoding states** to define state variables often
 - **is inconvenient** overhead during VHDL implementation
 - **limits readability** of the code: calling states by a name contributes to readability
 - **is inflexible** since state representation can not be optimized

- VHDL allows for **enumeration types** : ideal for state variables

- **Values can be arbitrary strings** (ideal for state names)

```
TYPE enum_type_name IS (value_1, value_2, ...);
```

```
SIGNAL signal_name : enum_type_name;
```

- Abstract type without pre-defined binary representation: chosen by the synthesis tool during optimization
- Every FSM requires its own type matched to the states required


```
ARCHITECTURE rtl OF my_fsm_states IS
    -- type declarations for FSM states
    TYPE state_type IS (StateA, StateB, StateC);

    -- signal declaration
    SIGNAL STATExDN, STATExDP : state_type;

BEGIN
    ...
END;
```

FSM Example

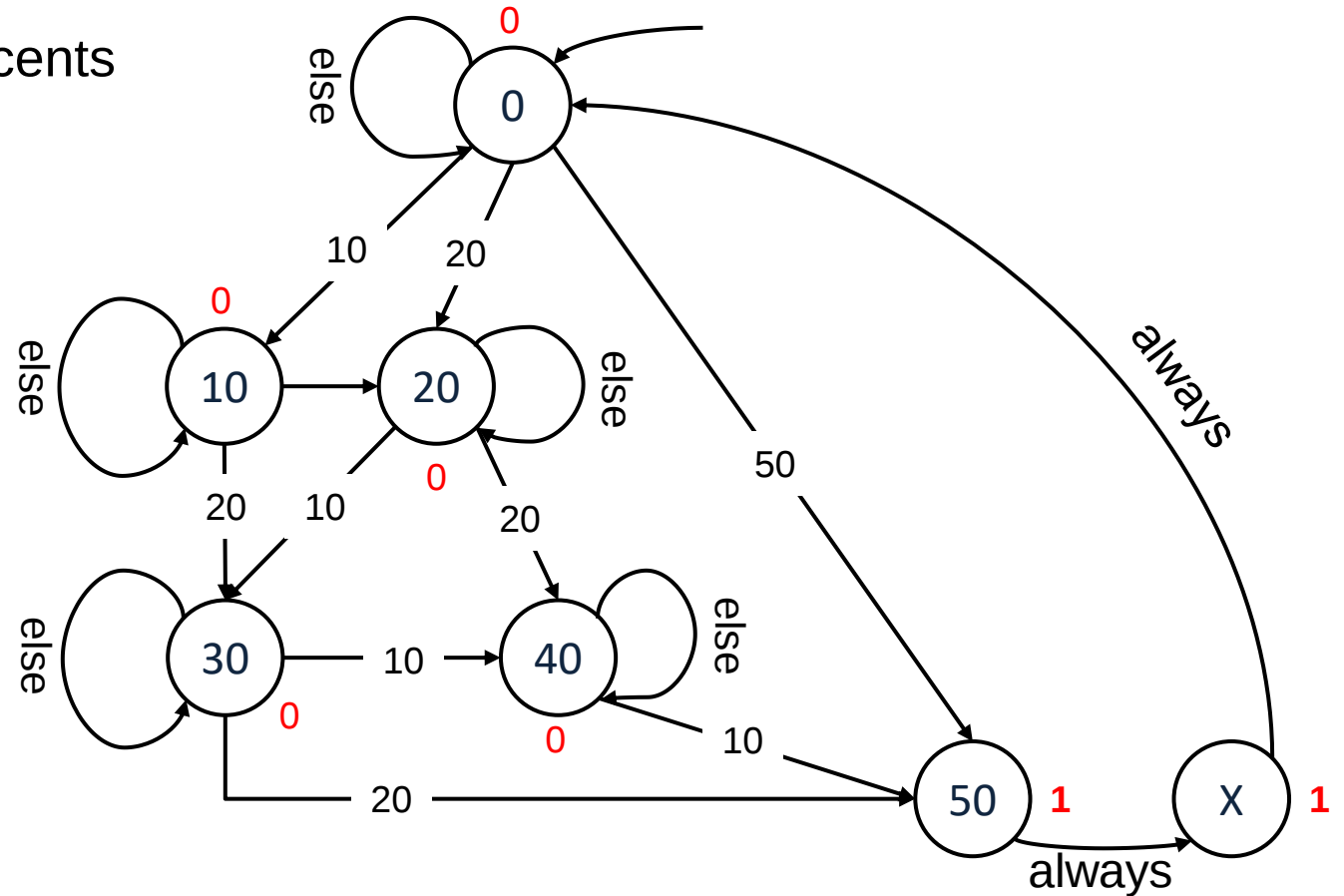- Vending machine waiting to enter 50 cents
 - Coins: 10, 20, 50 cents
 - Output = 1 for 2 entire cycles after 50 cents have been entered
 - Overflows are handled by returning the entered coin and remaining on the current amount




Timing Diagrams

- State diagrams provide a complete and unambiguous FSM specification
 - However, state diagrams do not illustrate the evolution of (input and output) signals over time
- **Timing diagrams show waveforms examples** produced by an FSM
- **Timing diagrams** are very useful to illustrate system behavior, but have also several issues:
 - **Complete specification requires enumeration of all possible input/state combinations**
 - **A single timing diagram is often incomplete**
 - **Causality** is often **not clearly visible** from a timing diagram
 - Often **no explicit definition of states**: must be reconstructed

Timing Diagrams

 - Timing diagrams often use a particular graphical notation to clarify causalities and dependencies



From Timing Diagrams to FSMs

- To reconstruct an FSM compatible with a given set of timing diagrams **check each clock cycle of all timing diagrams to identify**
 - **States:** assign separate states to each clock cycle in which
 - Outputs are different for the same input
 - Next state is different for the same input
 - **State-transitions:** for each state, find all the next states in the timing diagram
 - Annotate transitions with the inputs causing/triggering the transition
 - **Outputs:** distinguish between Moore and Mealy outputs
 - Moore: for each state, identify outputs that are independent of the inputs (i.e., change only on state transition)
 - Mealy: for each state and each input combination annotate a state transition with the corresponding input with the output (different transitions may have the same start- and end-point, but different outputs)

Example

- Specify a state machine that complies with the given timing diagram
 - Note: Specification is incomplete since $AxSI=1$ and $BxSI=0$ is not specified!!!

