

EE-334

Digital System Design


Custom Digital Circuits

Timing Analysis and Constraints in Synchronous Circuits

Andreas Burg

Reminder: Principle of Synchronous RTL Design


- Synchronous circuits are composed of
 - Registers that store the current state and
 - Combinational logic that defines the next state
- A **single global clock signal triggers all registers** at the same time
 - **Registers capture all outputs** of the combinational logic at the same time **when they are stable**
 - Inputs of all combinational circuits change at the same time
- **After the positive clock edge**
 - **the circuit enters a transient state** and
 - **stabilizes again after some time**, ready for the next clock edge

 

How can we verify that data is always captured safely?



Register Timing Requirements

 - Requirements for safely capturing the next state/data are set by the registers
- Input must be **stable during** the data **call window** around the active clock edge
- Formal register **timing requirements**:
 - Setup time t_{setup}^{FF} : time the data must be stable before the active clock edge
 - Hold time t_{hold}^{FF} : time the data must remain stable after the active clock edge



Static Timing Analysis (STA)

- **Static Timing Analysis** characterizes a digital circuit in terms of its timing parameters and **verifies the timing requirements** of a circuit and its registers
- Questions answered by static timing analysis
 - **How fast can we clock a circuit?**
 - **What is the time window in which we can safely**
 - **apply signals** to the input? (stimuli application)
 - **sample the output** of a circuit? (response acquisition)

 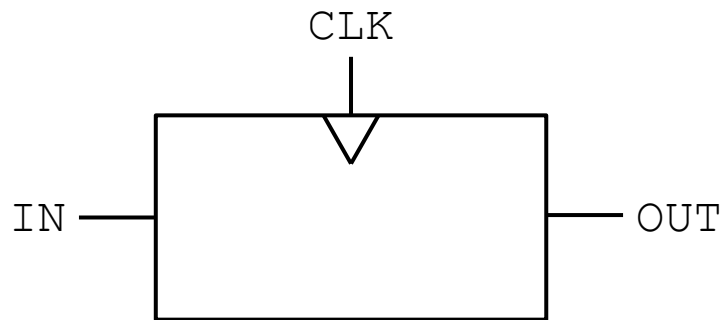

Δ . . . Stimuli application



T . . . Response acquisition

↑ . . . Active clock edge



Modelling the Delay of Combinational Circuits

- Combinational Circuits are composed of combinational logic gates

  - Logic gates have a **propagation delay**





- Delays of subsequent gates **add up**

 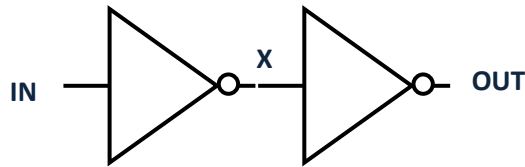

- To abstract transient effects it is convenient to **define a minimum and a maximum delay**


- Contamination delay (min):** t_{cd}

- Propagation delay (max):** t_{pd}

  

Characterizing the Delay of Combinational Circuits

- **Combinational circuits have multiple inputs and multiple outputs**
 - Different inputs may cause changes in the same output
 - The same input may cause changes in different outputs
- **Consider all paths from all inputs to all outputs and define**
 - **Contamination delay:** shortest path t_{cd}
 - Based on contamination delays of the gates
 - Earliest change of an output after a change on any input
 - **Propagation delay:** longest path t_{pd}
 - Based on propagation delays of the gates
 - Latest change of an output after a change on any input


 


Delays of Complex Gates and Sub-Circuits

- Contamination delay and propagation delay determine the time when the output of a combinational circuit is guaranteed to be **stable**


- Transition window** (transient time between contamination and propagation delay):
 - Outputs do not match Boolean equations
 - Must assume outputs are unknown

- Example**

  

Static Timing Analysis

 - STA is based on **delays of combinational logic and sequential elements**



Combinational logic


- Timing arc from input to output
 - Propagation delay t_{pd}^{logic}
 - Contamination delay t_{cd}^{logic}
 - Entire circuit (multiple paths)
 - Critical path $t_{crit}^{logic} = \max(t_{pd}^{logic})$

Sequential elements

- Timing arc **from clock to output** (between clock and data)
 - Propagation delay t_{pd}^{FF}
 - Contamination delay t_{cd}^{FF}

Static Timing Analysis: Path Groups

- STA considers **four path groups**, defined by the type of start- and end-points
 - **Input-to-Register** (t_{is}): from a primary input to a register data input
 - **Register-to-Register** (t_{ss}): from **clock input** of a register to the **data input** of a register
 - **Register-to-Output** (t_{so}): from clock input of a register to a primary output
 - **Input-to-Output** (t_{io}): direct path from a primary input to a primary output

 

STA: Checking Timing Conditions

- **Timing requirements for all register-to-register paths**
 - Path starts from the **clock pin** of a register and **ends on the data pin** of a register


- **Setup condition:** latest arrival

$$\underbrace{t_{pd}^{FF} + t_{pd}^{logic}}_{t_{ss}^{max}} < t_{clk} - t_{setup}^{FF}$$

**Determines
maximum
frequency**

- Hold condition: earliest arrival
 
$$\underbrace{t_{cd}^{FF} + t_{cd}^{logic}}_{t_{ss}^{min}} > t_{hold}^{FF}$$




Critical Path

- The **critical path** is the path within a circuit that **limits** its **clock frequency**
- The critical path contains
 - For reg->reg: the Clk->Q delay of the register from which it starts
 - The delay of the subsequent logic
- The critical path does not include:
 - For in->reg: the stimuli application delay (if known, otherwise 0)
 - For reg->out: the output sampling time (if known, otherwise 0)
 - The setup time of the register at the end

STA: Checking Timing Conditions

- **Timing requirements** for all **input-to-register** paths
 - Path starts from **primary input** and ends on the **data pin** of a register
 - **Setup condition**: latest arrival
 $t_{\Delta} + t_{pd}^{logic} < t_{clk} - t_{setup}^{FF}$
 - **Hold condition**: earliest arrival
 $t_{\Delta} + t_{cd}^{logic} > t_{hold}^{FF}$

 **Determine
setup window
for primary
inputs**




STA: Checking Timing Conditions

- **Timing requirements** for all **register-to-output** paths
 - Path starts from data pin of a register and ends on the sampling of the output
 - **Setup condition**: earliest (ideal) sampling
 - **Hold condition**: latest (ideal) sampling

$$t_{pd}^{FF} + t_{pd}^{logic} < t_T$$


Determine the sampling window for primary outputs

$$t_{cd}^{FF} + t_{cd}^{logic} > t_T$$

 


Static Timing Analysis on Gate Level

- The STA procedure identifies
 - the critical (longest) path t_{pd}^{logic} to verify setup
 - the shortest path t_{cd}^{logic} to verify hold
- Identify the shortest and the longest path for the data-input of each Flip-Flop
 - Annotate the circuit with the worst-case arrival times (delay) of the signal
 - Start from the clock input of the FFs
 - Keep only the longest (shortest) path (Add-Compare-Select)

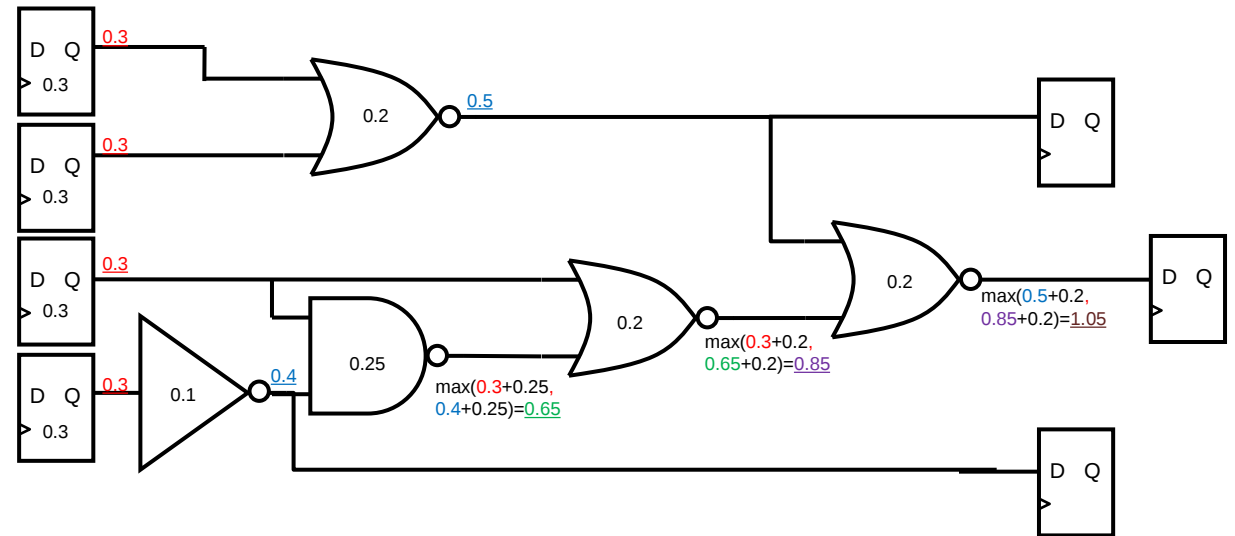


Static Timing Analysis of Datapath Components

- STA of gate level circuits is tedious and therefore carried out by automatic tools
- Designers often want to **have a quick estimate of complex circuits composed of arithmetic components** or other well-studied combinational circuits
- Combinational sub-circuits have multiple inputs and multiple outputs
 - **Critical paths** of sub-circuits **have different start and end-points**
 - Critical end-point in one sub-circuit is often NOT the critical starting point in the next sub-circuit
- **Accurate timing analysis is difficult**
 - Needs to be done at the gate level or with complex models of the individual sub-circuits.

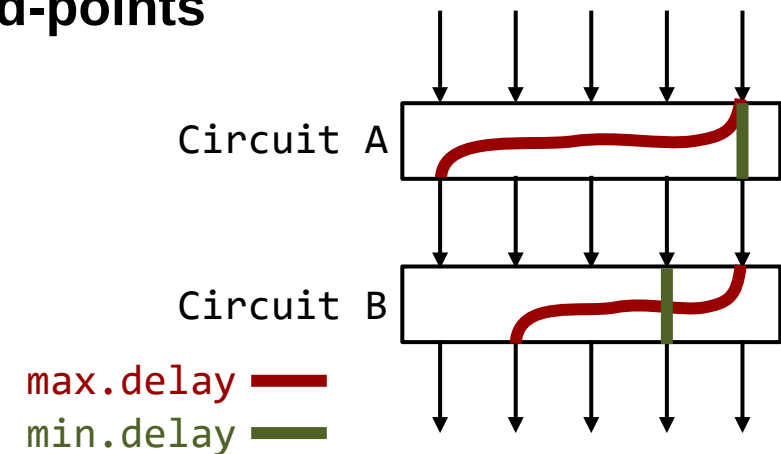

Static Timing Analysis of Datapath Components

 - In practice, we are often only **interested in a quick worst-case estimate**
 - Model** timing of **each** (combinational) **component** with its **min. and max delay** only
 - Worst case estimate** obtained by
 - Approximating the **longest path from the sum of the maximum delays**
 - Approximating the **shortest path from the sum of the minimum delays**



Timing in Hierarchical Designs

- Concatenate two blocks A and B (design entities or chips)
 - Register-to-output path of block A and the input-to-register path of block B merge into a new register-to-register path

$$t_{so}^{max}(A) + t_{is}^{max}(B) < t_{clk} - t_{setup}^{FF}$$

$$t_{so}^{min}(A) + t_{is}^{min}(B) > t_{hold}^{FF}$$

