

EE-334

Digital System Design

Discussion for Exercise 3
VHDL and Block Diagrams

Andreas Burg

Task 1: 2-to-1 Multiplexer

- Find the problems in the given code:
 - IF statement has no ELSE and no default assignment:
 - Code will not work as a multiplexer
 - A latch is produced since **OUTxDO** should only follow **In1xDI** if **Se1xSI** = '1'

```
process(all)
begin
    if SelxSI = '1' then
        OutxDO <= In1xDI;
    end if;
end process;
```



- Correct the code to fix the problem: Either default statement or else

```
process(all)
begin
    OutxDO <= In0xDI;

    if SelxSI = '1' then
        OutxDO <= In1xDI;
    end if;
end process;
```



```
process(all)
begin
    if SelxSI = '1' then
        OutxDO <= In1xDI;
    else
        OutxDO <= In0xDI;
    end if;
end process;
```



Task 2: Some Arbitrary Combinational Circuit


- Find and correct the errors in the code:
- Draw the schematic:

- Two **syntax errors**
 - Missing semicolon (;) in the last line
 - Missing **ELSE** statement
- One **semantic error**: clocked process assigns ResxDN instead of ResxDP in one branch of the **IF** statement

```
signal ResxDN, ResxDP : unsigned(8-1 downto 0);

begin

process(CLKxCI, RSTxRI)
begin
  if (RSTxRI = '1') then
    ResxDP <= (others => '0');
  elsif (CLKxCI'event and CLKxCI = '1') then
    ResxDN <= ResxDP;
  end if;
end process;
ResxDN <= AxDI + BxDI      when CxDI + DxDI > 1 else
          AxDI - BxDI - 1  when CxDI > DxDI and DxDI /= 0
          AxDI + 1;
ELSE
```

 

Task 3a: Another Arbitrary Combinational Circuit

- Find and correct the errors in the code:
 - Two **syntax errors**
 - 2x missing THEN keyword
 - Two **semantic errors**:
 - Clocked process is missing the RSTxRI signal in the sensitivity list
 - Combinatorial logic process is missing many signals in the sensitivity list: to avoid enumerating all signals we can use **ALL** instead

```
signal ResxDN, ResxDP : unsigned(8-1 downto 0);


begin
    process(CLKxCI) (CLKxCI, RSTxRI)
    begin
        if (RSTxRI = '1') then
            ResxDP <= (others => '0');
        elsif (CLKxCI'event and CLKxCI = '1') then
            ResxDP <= ResxDN;
        end if;
    end process;

    process() (ALL)
    begin
        if Sel0xSI = '1' THEN
            ResxDN <= AxDI + BxDI;
        elsif Sel1xSI = '1' THEN
            ResxDN <= AxDI + CxDI;
        else
            ResxDN <= DxDI + 1;
        end if;
    end process;
```



 Task 3a: Another Arbitrary Combinational Circuit

- Reconstruct the schematic of the circuit



```
signal ResxDN, ResxDP : unsigned(8-1 downto 0);

begin


process(CLKxCI, RSTxRI)
begin
    if (RSTxRI = '1') then
        ResxDP <= (others => '0');
    elsif (CLKxCI'event and CLKxCI = '1') then
        ResxDP <= ResxDN;
    end if;
end process;

process(all)
begin
    if Sel0xSI = '1' then
        ResxDN <= AxDI + BxDI;
    elsif Sel1xSI = '1' then
        ResxDN <= AxDI + CxDI;
    else
        ResxDN <= DxDI + 1;
    end if;
end process;
```



 Task 4: Counter indicating when it reaches its MAX

- A free-running counter CNTxDP that sets MaxPulsexS0='1' in the **same cycle** when it (CNTxDP) reaches its maximum value "1111"
- Find the issue(s) with the VHDL code:
 - **Serious synchronous design issue:**
MaxPulsexS0 has no reset and should only be clocked when RSTxRI is not '1'
➔ lead to logic that combines RSTxRI with CLKxCI
 - **Functional issue:**
 - MaxPulsexS0 is assigned inside a clocked process (IF clk'event statement) ➔ Signal is output of a register




```
signal CNTxDP : unsigned(4-1 downto 0);

begin

process(CLKxCI, RSTxRI)
begin
    if (RSTxRI = '1') then
        CNTxDP <= (others => '0');
    elsif (CLKxCI'event and CLKxCI = '1') then
        CNTxDP <= CNTxDP + 1;
        if CNTxDP = "1111" then
            MaxPulsexS0 <= '1';
        else
            MaxPulsexS0 <= '0';
        end if;
    end if;
end process;
```

 Task 5: Block Diagram to VHDL

- Arithmetic translates into corresponding logic blocks
- MUX: some form of conditional statement controlled by SelxSI



```
signal ResxDN, ResxDP : unsigned(8-1 downto 0);

begin


process(CLKxCI, RSTxRI)
begin
    if (RSTxRI = '1') then
        ResxDP <= (others => '0');
    elsif (CLKxCI'event and CLKxCI = '1') then
        ResxDP <= ResxDN;
    end if;
end process;

with SelxSI select
    ResxDN <= AxDI + 1           when "00",
              AxDI - BxDI - 1   when "01",
              AxDI + BxDI       when "10" | "11",
              (others => 'X')   when others;

OutxDO <= ResxDP;
```

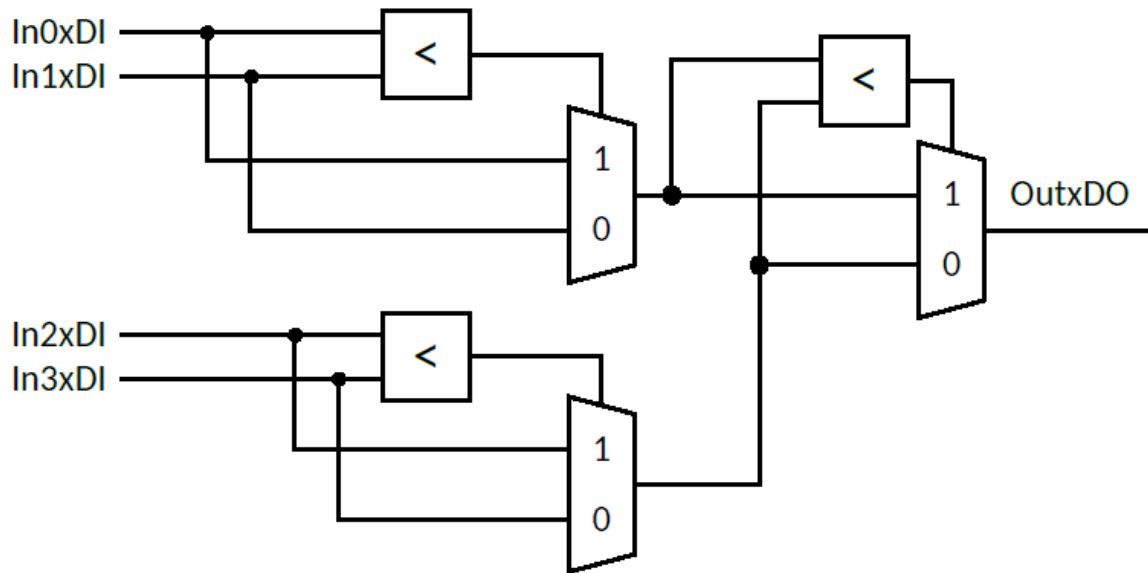Task 6: Block Diagram to VHDL

- Multiple MUXes: describe one-by one and connect
- Comparators that control the MUXes can be realized
 - **As combinational logic that generates explicit select signals controlling the MUX (i.e., conditional assignments in VHDL) OR**
 - Directly in the combinational statement



```
signal Res0xD, Res1xD, Res2xD : unsigned(8-1 downto 0);
signal Comp0xS, Comp1xS, Comp2xS : std_logic;


begin
  Comp0xS <= '1' when In0xDI < In1xDI else '0'; -- Comparators
  Comp1xS <= '1' when In2xDI < In3xDI else '0';
  Comp2xS <= '1' when Res0xD < Res1xD else '0';

  Res0xD <= In0xDI when Comp0xS = '1' else In1xDI; -- Mux
  Res1xD <= In2xDI when Comp1xS = '1' else In3xDI;
  Res2xD <= Res0xD when Comp2xS = '1' else Res1xD;

  OutxDI <= Res2xD;
```

 
Task 7: Block Diagram to VHDL

- Adder with multiple possible inputs (shared resource) with a register



```

signal Src0xD, Src1xD : unsigned(8-1 downto 0);
signal ResxDN, ResxDP : unsigned(8-1 downto 0);

begin

process(CLKxCI, RSTxRI)
begin
    if (RSTxRI = '1') then
        ResxDP <= (others => '0');
    elsif (CLKxCI'event and CLKxCI = '1') then
        ResxDP <= ResxDN;
    end if;
end process;

with SelxSI select
    Src0xD <= AxDI           when "00"|"01",
             DxDI           when "10"|"11",
             (others => 'X') when others;

with SelxSI select
    Src1xD <= BxDI           when "00",
             CxDI           when "01",
             "00000001"     when "10"|"11",
             (others => 'X') when others;

    ResxDN <= Src0xD + Src1xD;

    OutxD0 <= ResxDP;
end rtl;
    
```