


Plan du Cours

- Calcul de pertes
- Calcul de l'efficacité versus fréquence de commutation

References additionnelles:

Fundamentals of Power Electronics, Robert W. Erickson, Dragan Maksimović, SECOND EDITION University of Colorado Boulder, Colorado
Electronique de puissance, Philippe Barrade, presses polytechniques et universitaires romandes

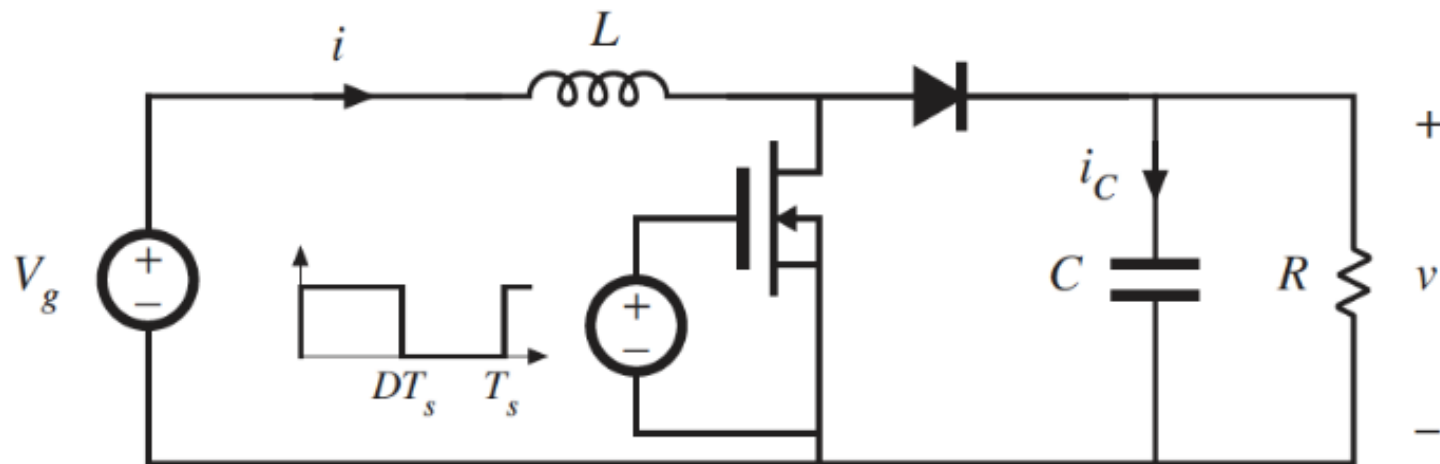What is the efficiency of the circuit that you simulated/calculated?




Introduction de pertes

1. Pertes en conduction: se passe pendant la conduction

- Semiconductor forward bias
- Parasitics: inductances, capacitances, resistances

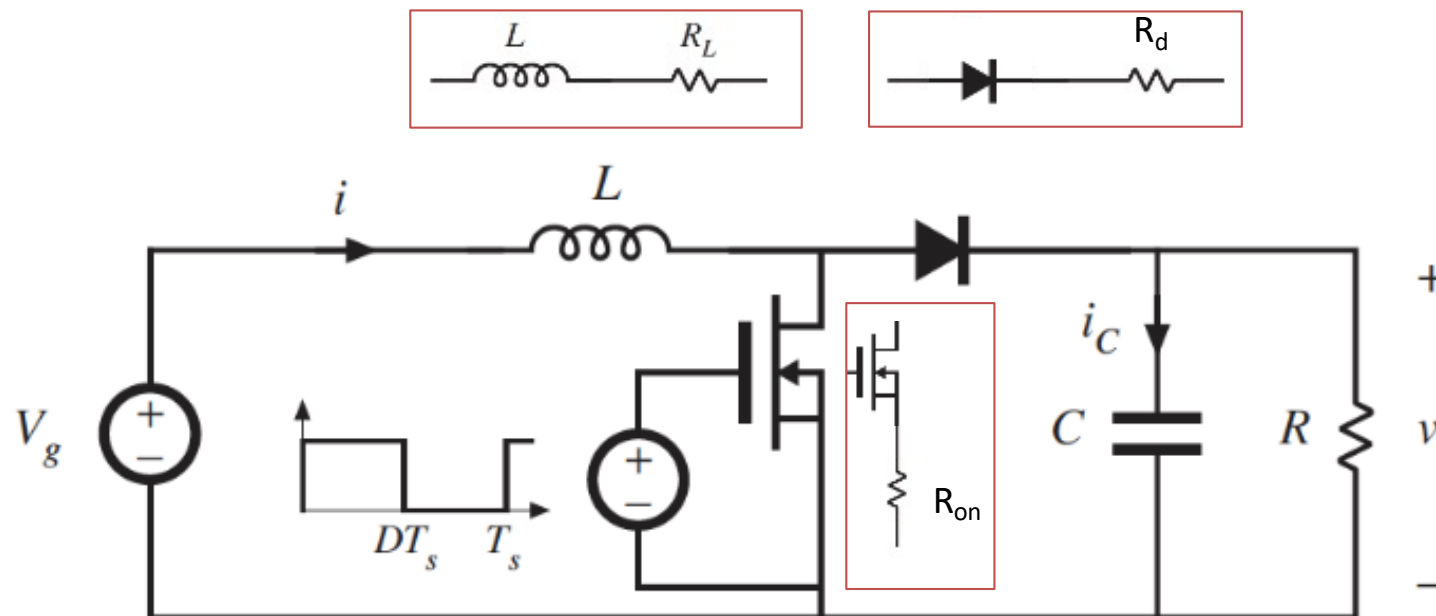
2. Pertes en commutation: se passe à chaque commutation



Pertes en conduction

Pertes en conduction

Power dissipated in the inductor

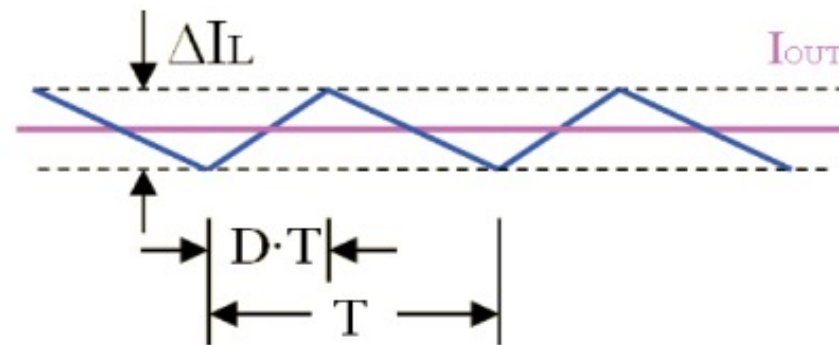

The inductor conduction loss is given by:

$$P_L = I_{RMS_L}^2 \times R_{DCR} \quad (1)$$

Where R_{DCR} is the DC-Resistance of the inductor.

The rms inductor current is given by:

$$I_{RMS_L}^2 = I_O^2 + \frac{\Delta I^2}{12} \quad (2)$$

Where ΔI = ripple current

Typically ΔI is about 30% of the output current. Therefore, the inductor current can be calculated to be:


$$I_{RMS_L} = I_O \times 1.00375 \quad (3)$$

Puissance dissipée (pertes): $P_L = I_{RMS}^2 \times R_{DC}$
 For small ripple: $P_L = I_{DC}^2 \times R_{DC}$

Pertes en conduction

Power dissipated in the transistor and diodes:

Boost converter example

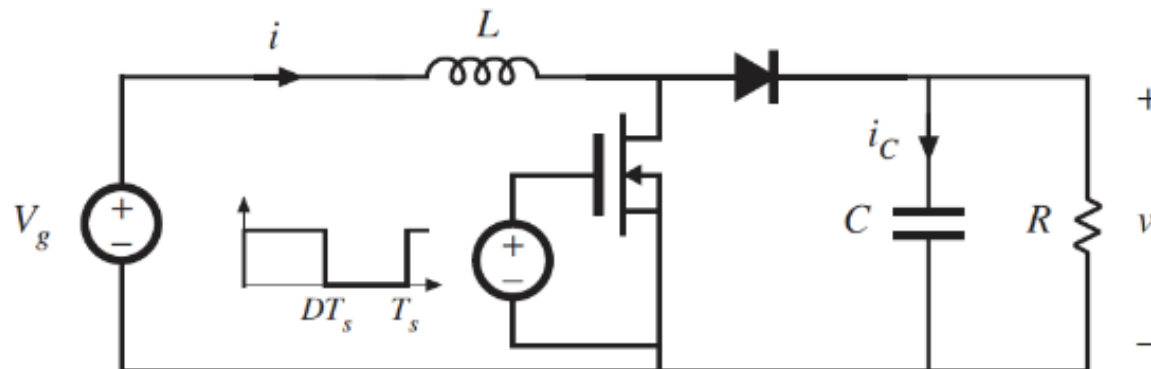

Models of on-state semiconductor devices:

MOSFET: on-resistance R_{on}

Diode: constant forward voltage V_D plus on-resistance R_D


Insert these models into subinterval circuits

Pertes en conduction

Power dissipated in the transistor:

- Model uses average currents and voltages
- To correctly predict power loss in a resistor, use rms values
- Result is the same, provided ripple is small

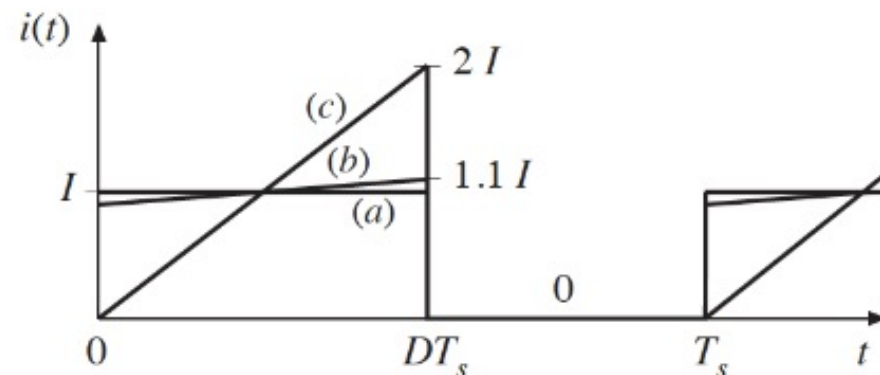MOSFET current waveforms, for various ripple magnitudes:




<i>Inductor current ripple</i>	<i>MOSFET rms current</i>	<i>Average power loss in R_{on}</i>
(a) $\Delta i = 0$	$I \sqrt{D}$	$D I^2 R_{on}$
(b) $\Delta i = 0.1 I$	$(1.00167) I \sqrt{D}$	$(1.0033) D I^2 R_{on}$
(c) $\Delta i = I$	$(1.155) I \sqrt{D}$	$(1.3333) D I^2 R_{on}$

- To predict the power loss in a resistor R, we must calculate the root-mean-square current I_{RMS} , rather than the average current. The average power loss is then given by $R I_{RMS}^2$
- If inductor current ripple is small: average model correctly predicts average power loss
- DC (average) model correctly predicts losses in the component non-idealities, provided that the inductor current ripple is small.

Pertes en conduction


Power dissipated in the transistor:

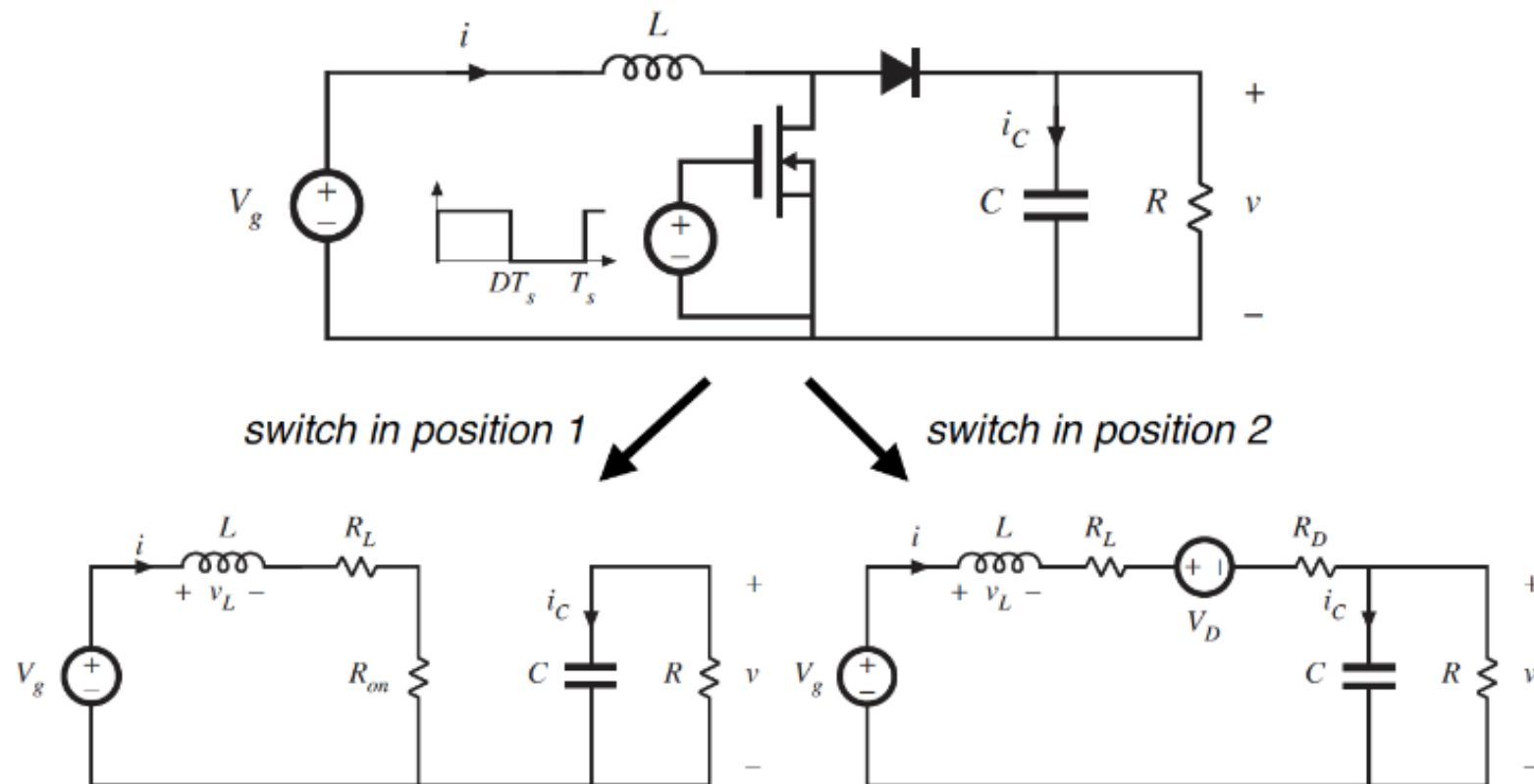

Pertes en conduction

Power dissipated in diodes:

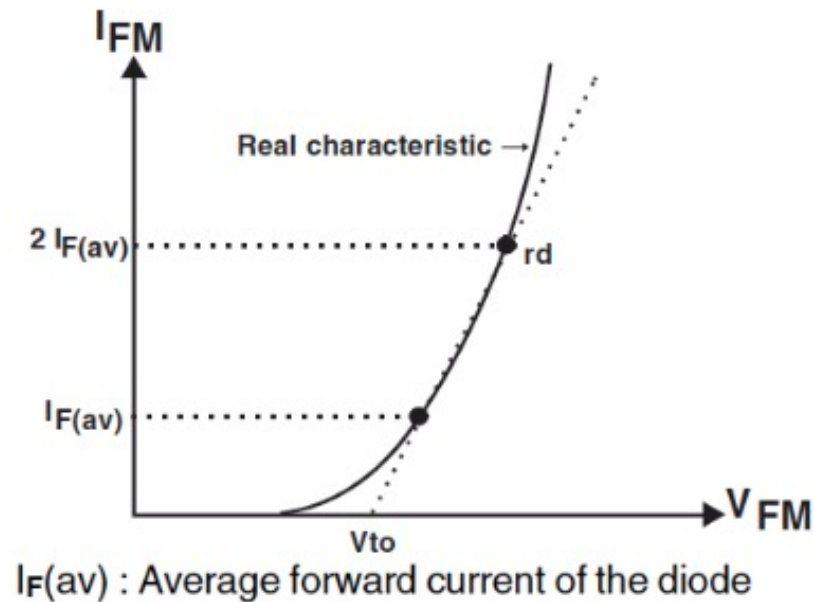In spite of the high operating frequency, the conduction losses remain the main cause of the junction's temperature increase in the majority of the applications. Therefore, it is important to accurately estimate these losses.



The forward voltage can be expressed by: $V_{FM} = V_{to} + r_d I_{FM}$
 V_{to} and r_d are given in the datasheet for each part


$$P_{cond} = V_{to} I_{F(av)} + r_d I_F(RMS)^2$$

$I_{F(av)}$: average forward current in the diode

$I_F(RMS)$: RMS forward current in the diode

Pertes en commutation

Pertes en commutation: MOSFET

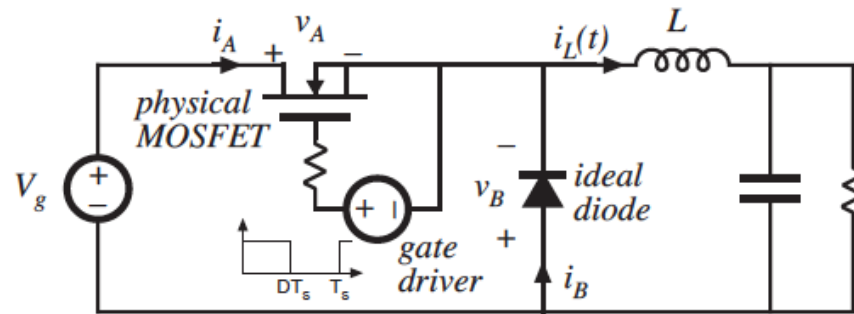


Buck converter example

$$v_B(t) = v_A(t) - V_g$$

$$i_A(t) + i_B(t) = i_L$$

transistor turn-off transition
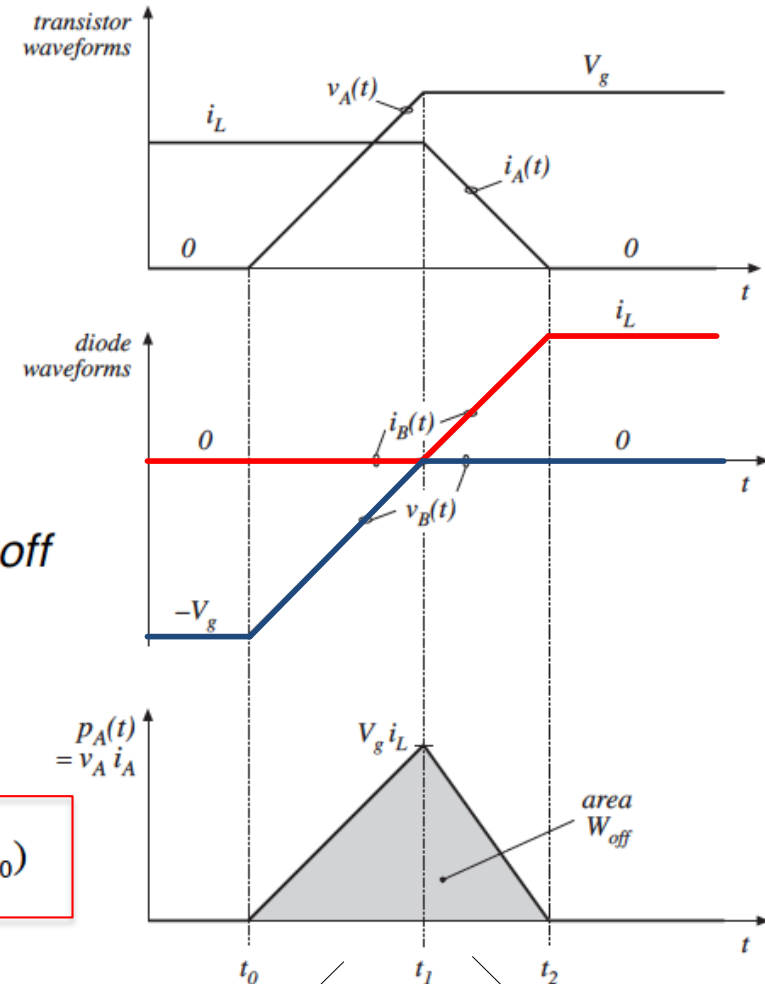
$$W_{off} = \frac{1}{2} V_g i_L (t_2 - t_0)$$



Temps pour charger
le C_{GD} du MOSFET

Temps pour décharger
le C_{gs} du MOSFET

Pertes en commutation: MOSFET

Energy lost during transistor turn-off transition:

$$W_{off} = \frac{1}{2} V_g i_L (t_2 - t_0)$$

Similar result during transistor turn-on transition.


Average power loss:

$$P_{sw} = \frac{1}{T_s} \int_{\text{switching transitions}} p_A(t) dt = (W_{on} + W_{off}) f_s$$

Perte en commutation: proportionnelle à la fréquence de commutation


Introduction: Pertes sur les diodes

Pertes en commutation: Diode

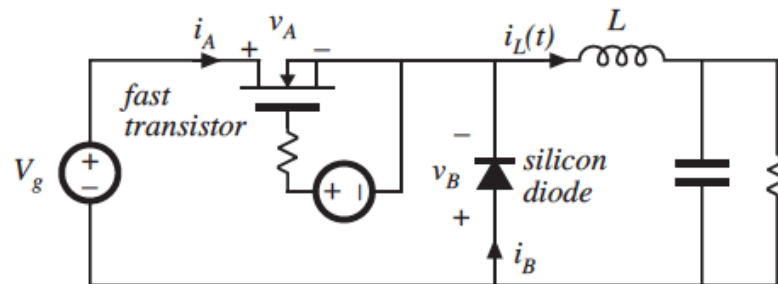


Under forward bias:

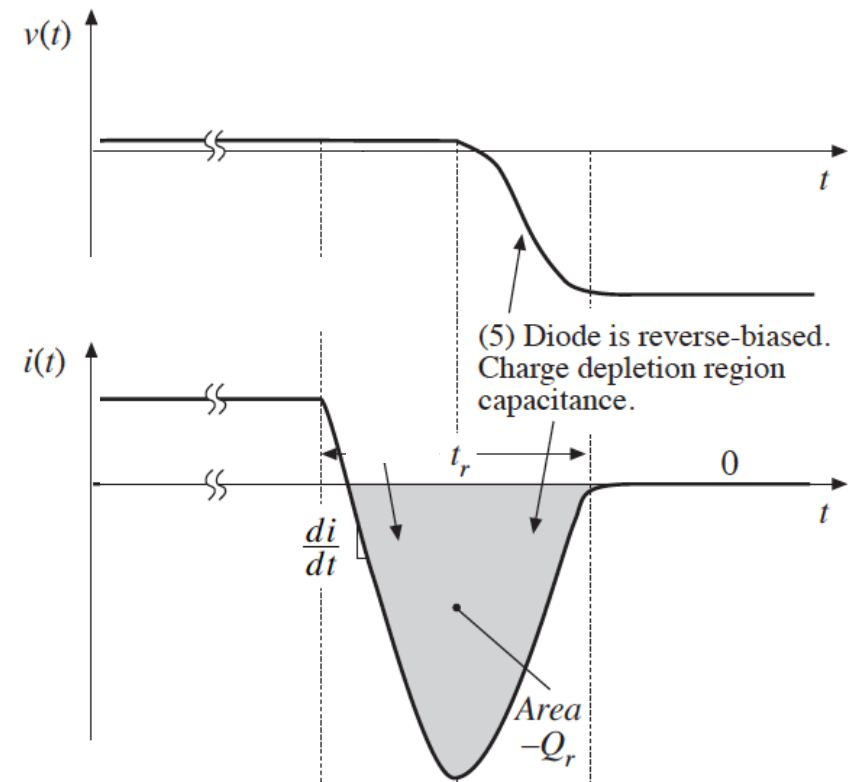
- substantial amount of charges is stored in the n^- region
- Increases conductivity
- Reduces R_{ON}



Pertes en commutation: Diode

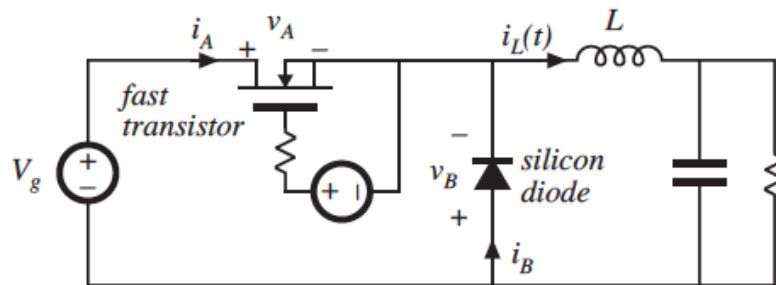

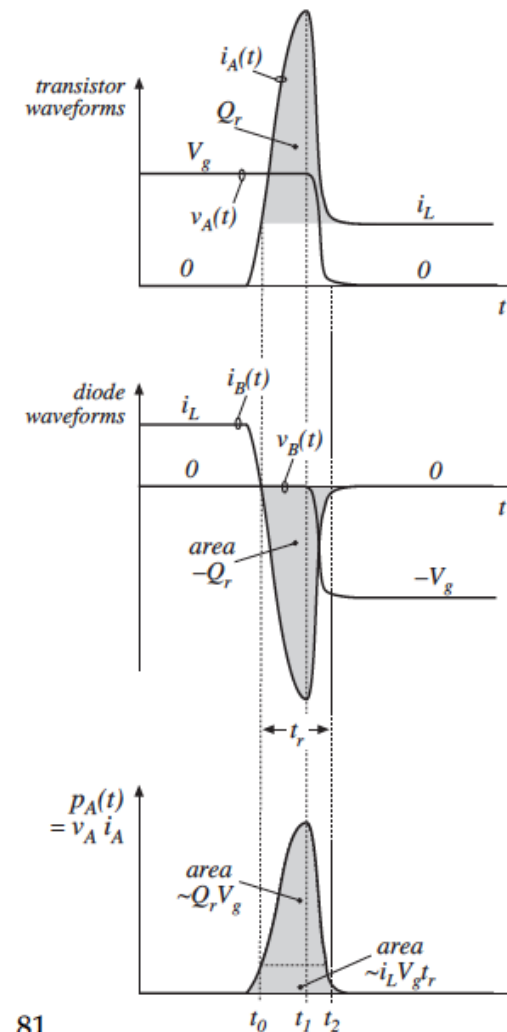- Diode recovered stored charge Q_r flows through transistor during transistor turn-on transition, inducing switching loss
- Q_r depends on diode on-state forward current, and on the rate-of-change of diode current during diode turn-off transition



Efficacité versus fréquence de commutation

Add up all of the energies lost during the switching transitions of one switching period:

$$W_{tot} = W_{on} + W_{off} + W_D + W_C + W_L + \dots$$

Average switching power loss is

$$P_{sw} = W_{tot} f_{sw}$$

Total converter loss can be expressed as


$$P_{loss} = P_{cond} + P_{fixed} + W_{tot} f_{sw}$$

where

P_{fixed} = fixed losses (independent of load and f_{sw})

P_{cond} = conduction losses

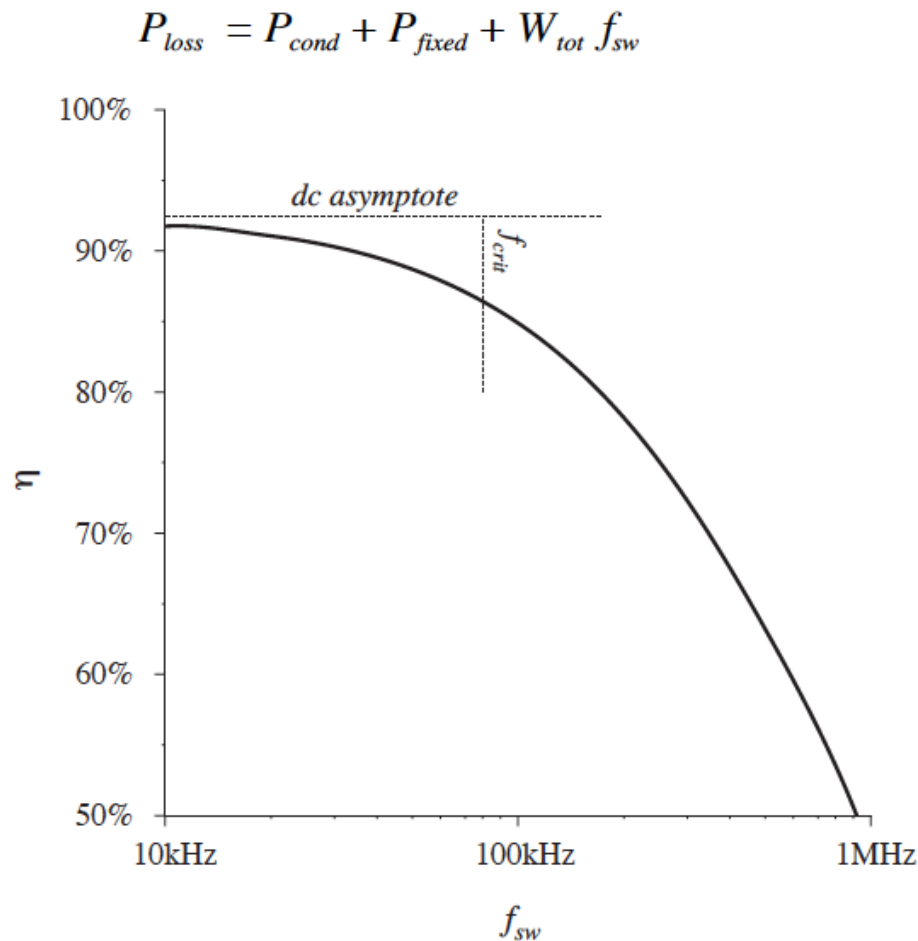Efficacité versus fréquence de commutation



Switching losses are equal to the other converter losses at the critical frequency

$$f_{crit} = \frac{P_{cond} + P_{fixed}}{W_{tot}}$$


This can be taken as a rough upper limit on the switching frequency of a practical converter. For $f_{sw} > f_{crit}$, the efficiency decreases rapidly with frequency.

Exemple: Effet des pertes en conduction sur le convertisseur boost

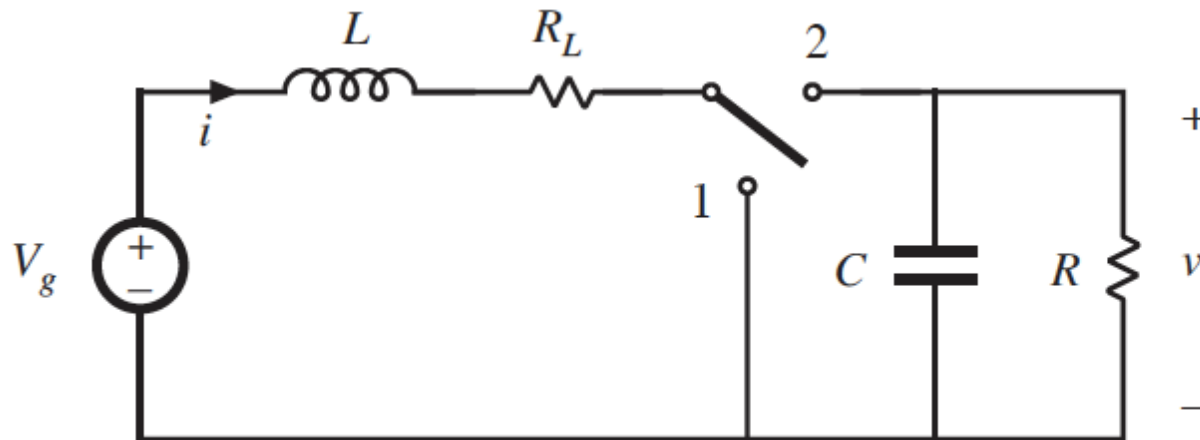
Example: inductor copper loss (resistance of winding):



Insert this inductor model into boost converter circuit:





Introduction de pertes

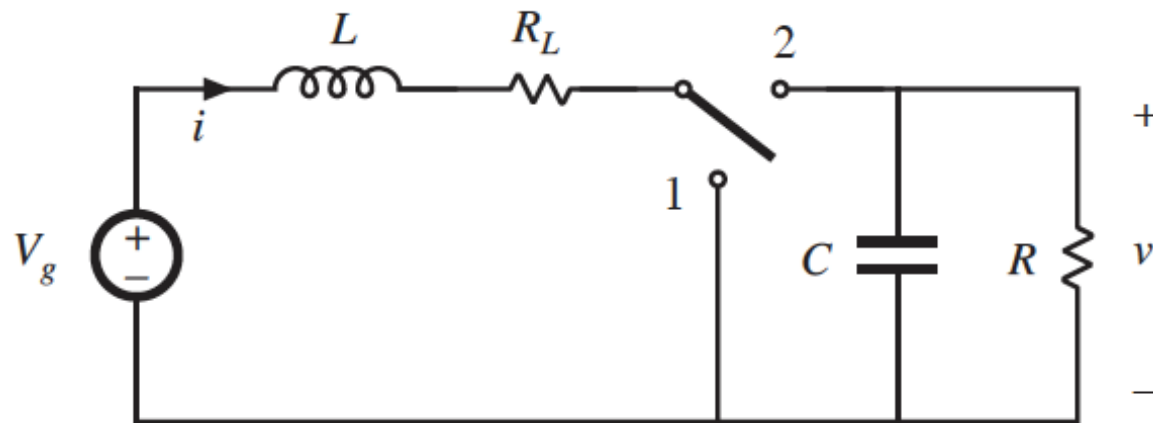

switch in position 1

switch in position 2

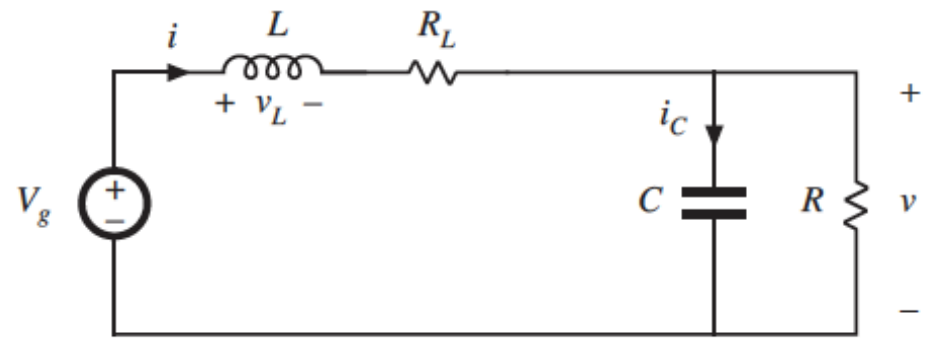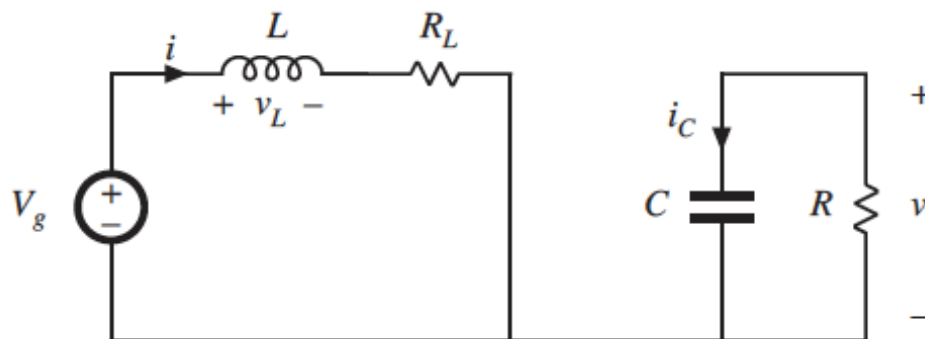


Introduction de pertes

Inductor current and capacitor voltage:

$$v_L(t) = V_g - i(t) R_L$$

$$i_C(t) = -v(t) / R$$

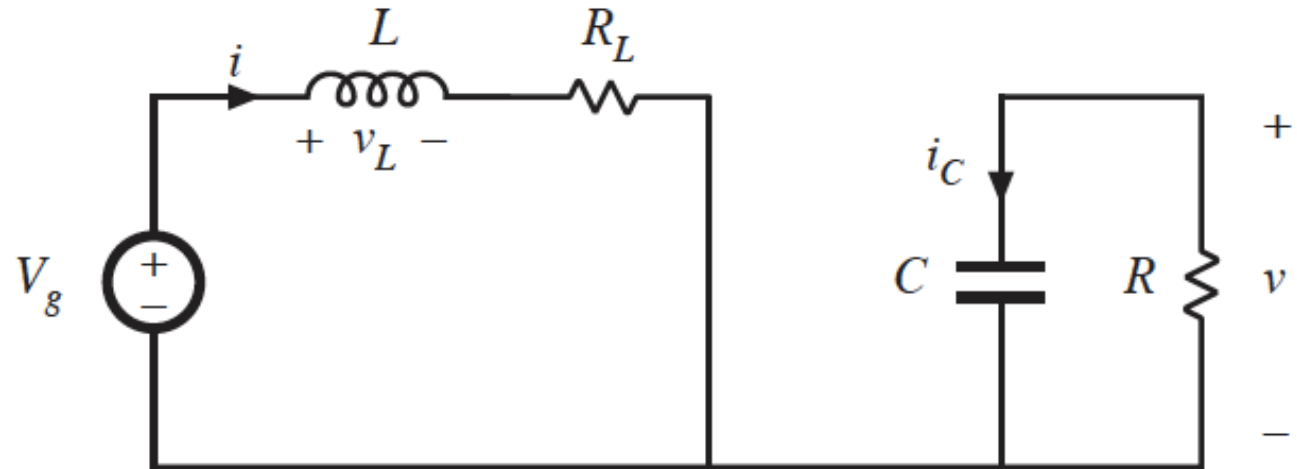


Small ripple approximation:

$$v_L(t) = V_g - I R_L$$

$$i_C(t) = -V / R$$

Introduction de pertes

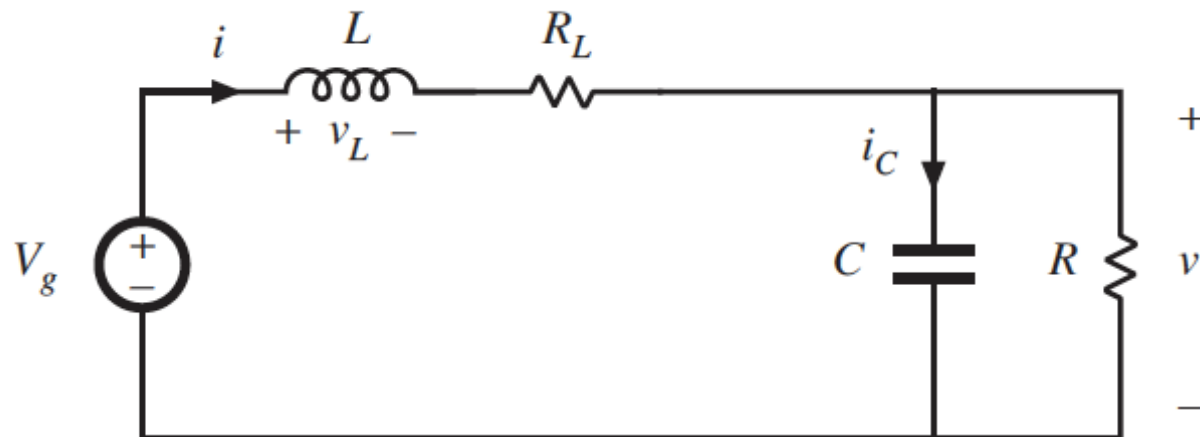

$$v_L(t) = V_g - i(t) R_L - v(t) \approx V_g - I R_L - V$$

$$i_C(t) = i(t) - v(t) / R \approx I - V / R$$

Introduction de pertes

Average inductor voltage:

$$\begin{aligned}\langle v_L(t) \rangle &= \frac{1}{T_s} \int_0^{T_s} v_L(t) dt \\ &= D(V_g - I R_L) + D'(V_g - I R_L - V)\end{aligned}$$

Inductor volt-second balance:


$$0 = V_g - I R_L - D'V$$

Average capacitor current:

$$\langle i_C(t) \rangle = D(-V/R) + D'(I - V/R)$$

Capacitor charge balance:

$$0 = D'I - V/R$$

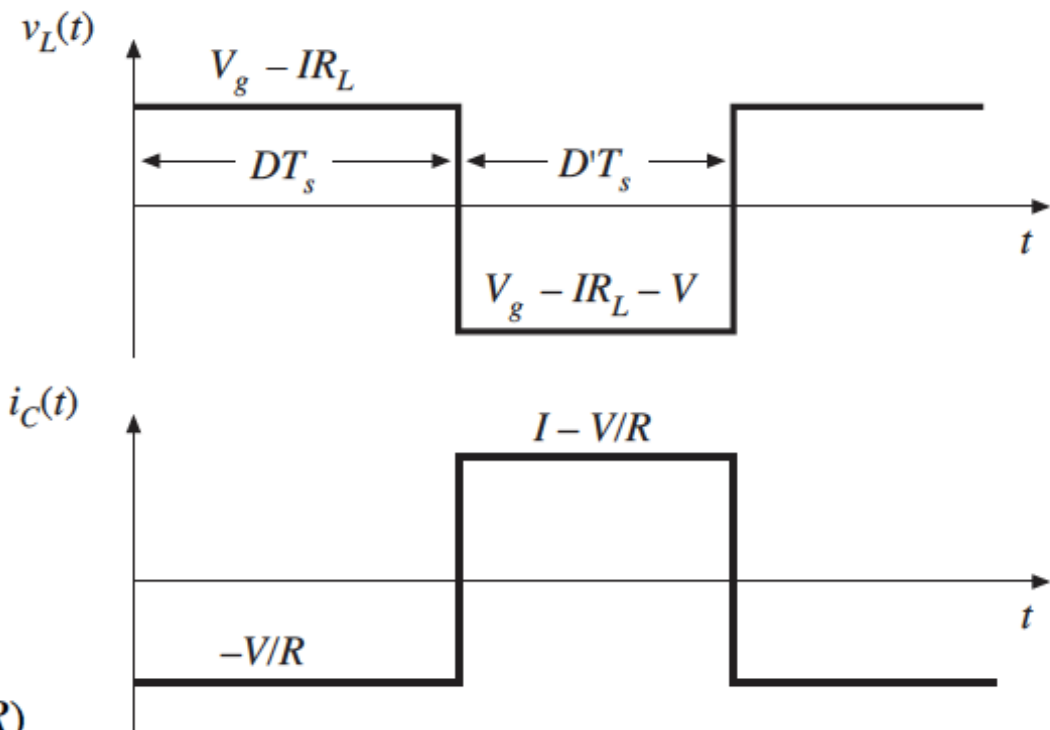

Introduction de pertes


We now have two equations and two unknowns:

$$0 = V_g - I R_L - D'V$$

$$0 = D'I - V / R$$

Eliminate I and solve for V :
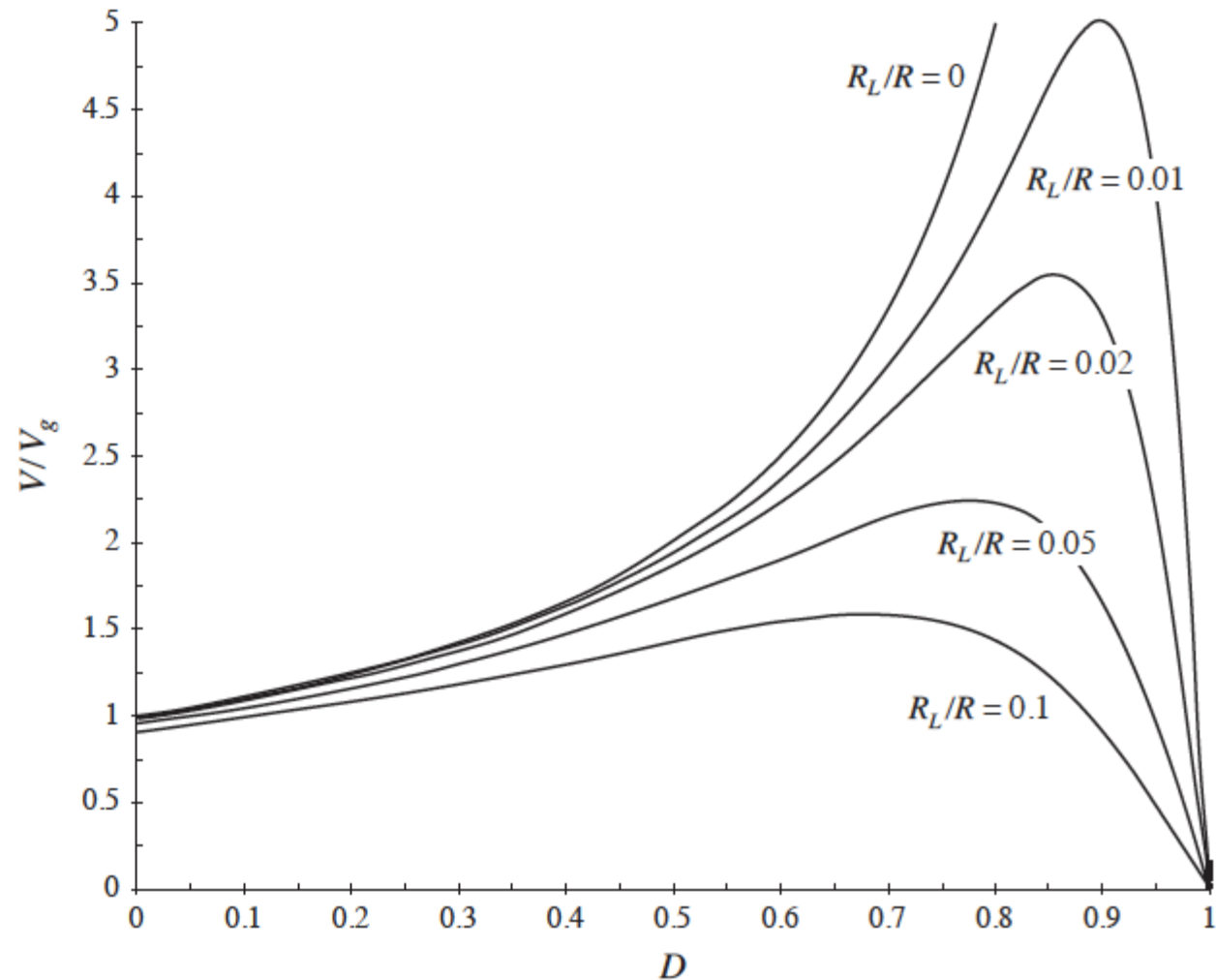
$$\frac{V}{V_g} = \frac{1}{D'} \frac{1}{(1 + R_L / D'^2 R)}$$




$$R_{ON,SP} = \frac{4BV^2}{\epsilon_S \mu_n E_C^3}$$

$R_{on,sp}$ is related to material properties

Baliga's figure of merit
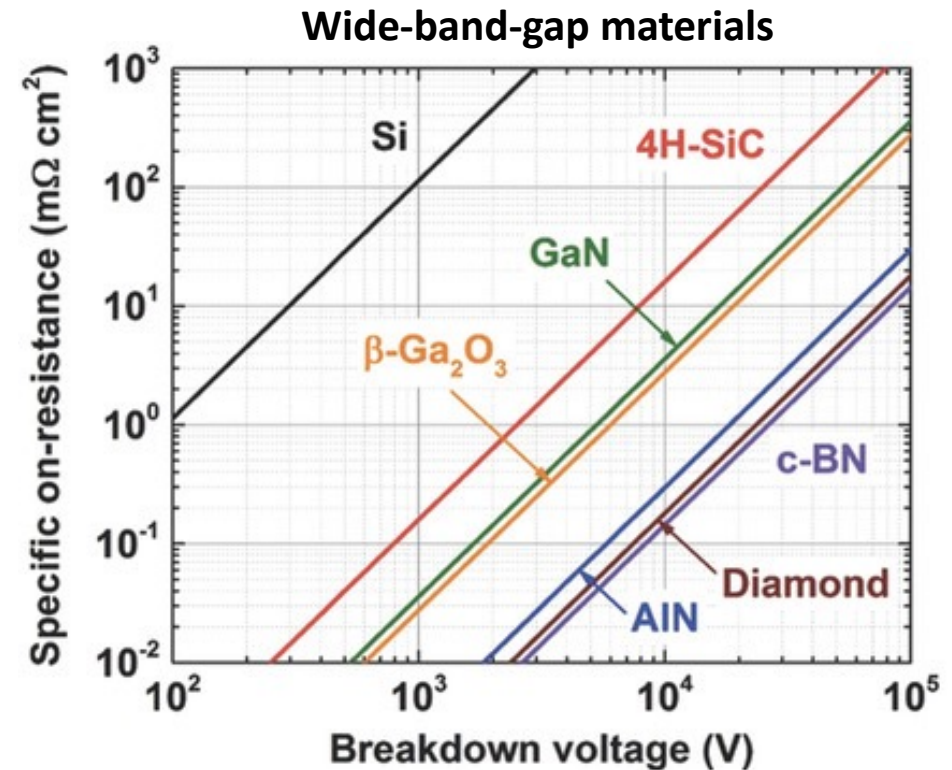
$$BFOM = \epsilon_S \mu_n E_C^3 = \frac{4BV^2}{R_{ON,SP}}$$



Parameter	Silicon	4H-SiC	GaN	Diamond
W_g , eV	1.12	3.26	3.39	5.47
E_{crit} , MV/cm	0.23	2.2	3.3	5.6
ϵ_r	11.8	9.7	9.0	5.7
μ_n , cm ² /V·s	1400	950	800/1700 ^b	1800
BFoM ^a relative to Si	1	500	1300/2700 ^b	9000
n_i , cm ⁻³	$1 \cdot 10^{10}$	$8 \cdot 10^{-9}$	$2 \cdot 10^{-10}$	$1 \cdot 10^{-20}$
λ , W/cm·K	1.5	3.8	1.3/3 ^c	20

Synthèse

