

Analyse de Fourier :

1

composante DC :

$$\langle v_s \rangle = \frac{1}{T_s} \cdot \int_0^{T_s} v_s(t) dt$$

$$= \frac{1}{T_s} \cdot D \cdot T_s \cdot V_g = D \cdot V_g$$

$$\therefore \langle v_s \rangle = \underbrace{D}_{[0,1]} \cdot V_g \Rightarrow \langle v_s \rangle \leq V_g \Rightarrow \boxed{\text{buck}}$$



$$f_s : 1\text{kHz} - 1\text{MHz}$$

$$T_s = \frac{1}{f_s}$$

D : rapport cyclique

2. filtre passe-bas : $Z = j\omega L$

2

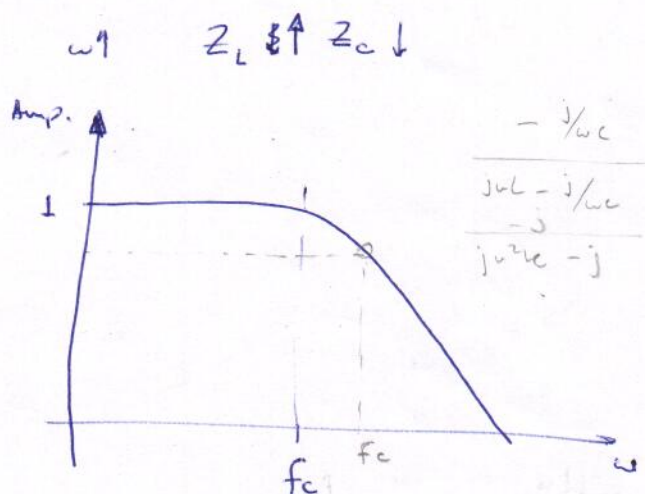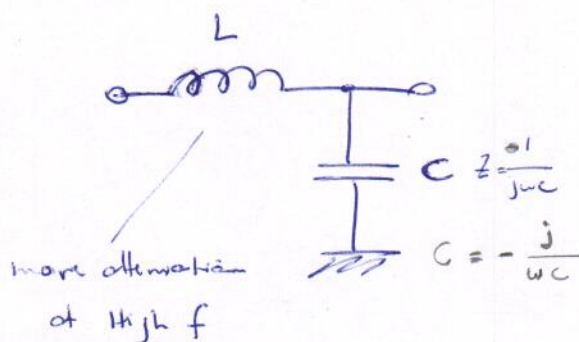

conversion ratio (facteur de conversion)

$$M(D) = V_{out}/V_{in}$$

$$M(D) = D : \text{buck}$$


$$M(D) = \frac{1}{1-D} : \text{boost}$$

$$\frac{V_{out}}{V_{in}} = \frac{\frac{1}{j\omega C}}{j\omega L + \frac{1}{j\omega C}} = \frac{1}{-\omega^2 LC + 1}$$


$$\frac{V_{out}}{V_{in}} = \frac{1}{1 - \omega^2 LC}$$



$$f_c = \frac{1}{2\pi\sqrt{LC}}$$

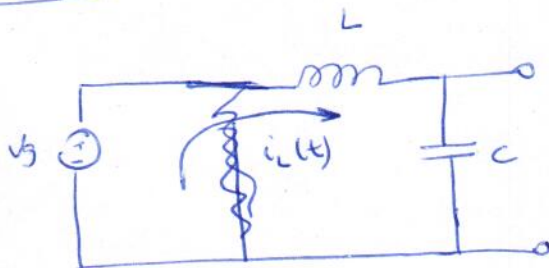
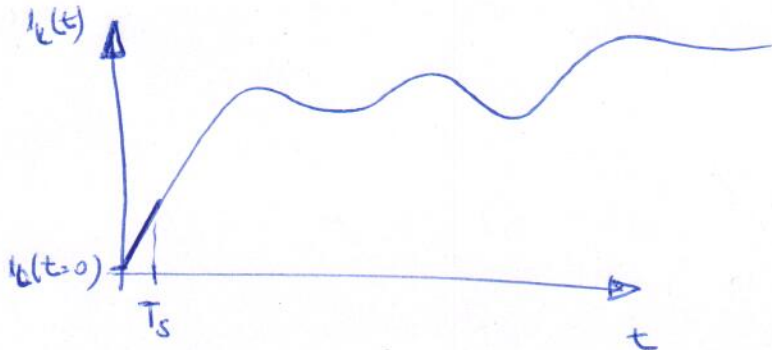
$$\begin{cases} v_L = L \frac{di}{dt} \\ i_C = C \frac{dv}{dt} \end{cases}$$



$$f_c = \frac{1}{2\pi\sqrt{LC}}$$

$$\begin{cases} f_c \ll f_s \\ T_c \gg T_s \end{cases}$$

⇒ approximation : ligne droite

small ripple = linear ripple

So

Variable ne peut pas être discontinue

on l'applique pour : $\begin{cases} i_L \\ v_C \end{cases} \Rightarrow$ peut approximer par une ~~courbe~~ ligne droite.


* Cela marche grâce à la commutation rapide

Slide 13 :

#4

periode 1: $\frac{V_g - V}{L} > 0$

periode 2: $-\frac{V}{L} < 0$

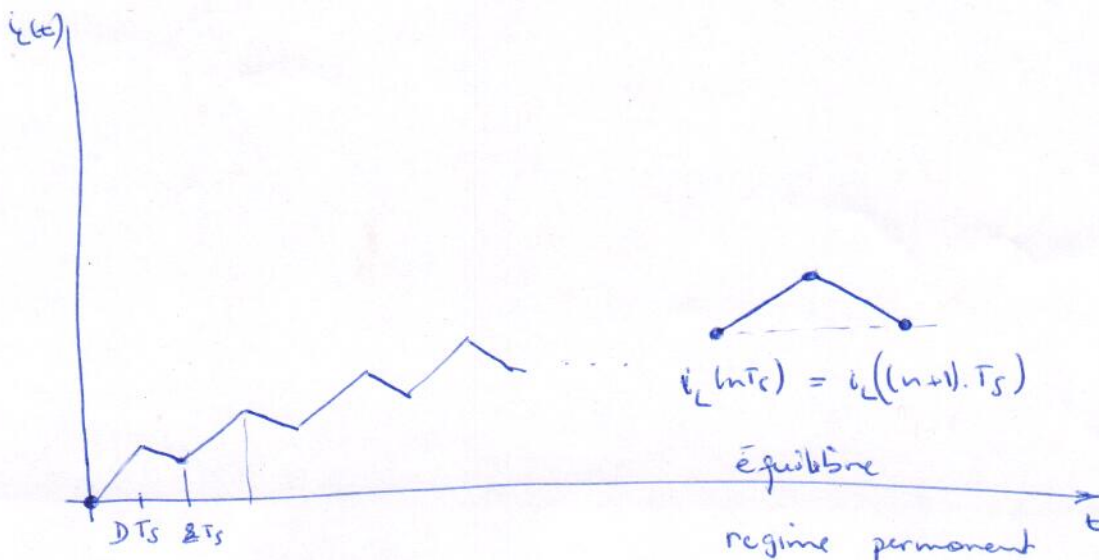

$$v_L(t) = L \frac{di_L(t)}{dt}$$

$$\int_0^{T_s} v_L(t) dt = \int_0^{T_s} L \frac{di_L(t)}{dt} dt =$$

$$\therefore i_L(T_s) - i_L(0) = \frac{1}{L} \int_0^{T_s} v_L(t) dt$$


$$\Rightarrow i_L(T_s) = i_L(0) \text{ in steady-state} \Rightarrow$$

$$0 = \int_0^{T_s} v_L(t) dt$$

thus

$$\frac{1}{T_s} \int_0^{T_s} v_L(t) dt = \langle v_L \rangle_{T_s} = 0$$
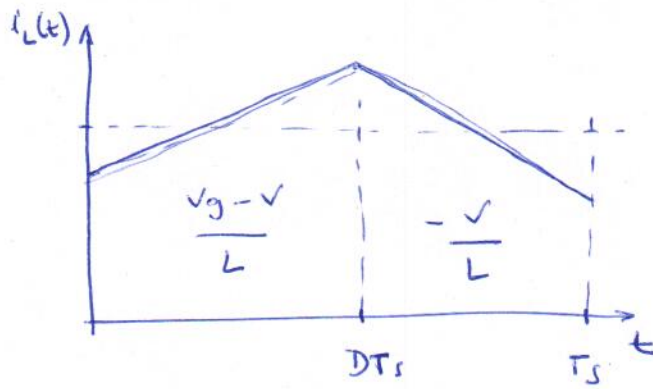
$$\therefore \boxed{\langle v_L \rangle_{\text{one periode}} = 0}$$



$$\Delta i_L^1 = \frac{V_g - V}{L} \times DT_s$$

$$\Delta i_L^2 = -\frac{V}{L} \times (1-D) \cdot T_s = -\frac{V + VD}{L} T_s$$

$$= -\frac{V/D + V}{L} \cdot DT_s$$

$$= -\frac{V_g + V}{L} \times DT_s$$

$$\uparrow$$

$$V_g = \frac{V}{D}$$


$$\therefore \Delta i_L^1 = -\Delta i_L^2 \Rightarrow \text{régime stationnaire}$$

why diode ?

$$V_L = L \frac{di}{dt}$$

on $\rightarrow$ off $\frac{di}{dt}$
 $\underbrace{\hspace{1cm}}_{-\infty}$


$$\therefore V_L \rightarrow -\infty$$

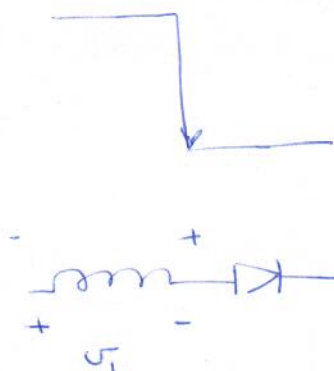


- diode conducts
- inductor current flows
- parfois $\Rightarrow$ roue libre

⊛ cellule de commutation n'a pas besoin de 2 composants actifs.

Slide 22

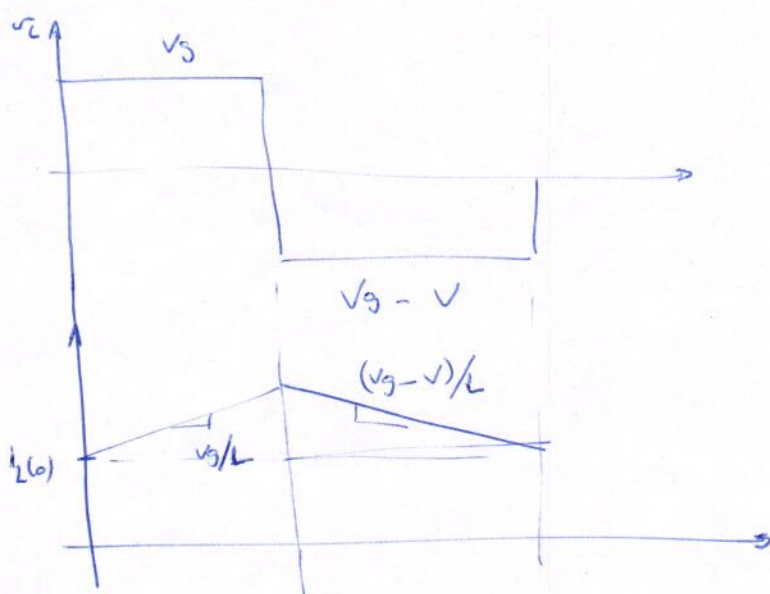

Slide 26

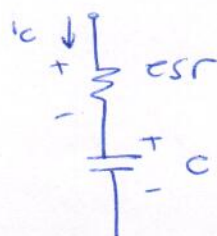

ripple:

$$\Delta i_c \times ESR + \Delta v_c$$

Boost:

(70) positive
volt-second

$$1) \quad v_L = V_g \quad i_c = -\frac{v}{R} = -\frac{V}{R}$$

$$v \approx V$$

volt-second balance

$$\frac{1}{T_s} \int_0^{T_s} v_L(t) dt = \langle v_L \rangle$$

$$2) \quad v_L = V_g - v \approx V_g - V \quad \left| \Rightarrow \text{must be negative!} \Rightarrow V > V_g \right.$$

$$i_c = i_L - \frac{v}{R} = i_L - \frac{V}{R} = I - \frac{V}{R}$$

Steady-state

$$\frac{1}{T_s} \int_0^{T_s} v_L(t) dt = \frac{V_g D T + (V_g - V) D' T}{T} = 0$$

$$V_g (D + D') = V D'$$

$$\boxed{\frac{V}{V_g} = \frac{1}{1-D}}$$

DC current: Capacitor charge balance principle

inductor current:

$$0 = \frac{1}{T_s} \int_0^{T_s} i_c(t) dt = \langle i_c \rangle = -\frac{V}{R} \frac{D T_s}{T_s} + \left(I - \frac{V}{R} \right) \frac{D' T_s}{T_s} = 0$$

$$-\frac{V}{R} (D + D') + I D' = 0$$

$$\therefore I = \frac{V}{D' R} = \frac{V_g}{D'^2 R}$$

Sketch inductor current:

$$1) \quad \frac{di_L(t)}{dt} = \frac{v_L(t)}{L} = \frac{V_g}{L} \quad \text{positive slope}$$


$$2) \quad \frac{di_L(t)}{dt} = \frac{V_g - V}{L}$$

$$\Delta i_L = \frac{V_g}{L} D \cdot T_s \Rightarrow \Delta i_L = \frac{V_g}{2L} \cdot D \cdot T_s$$

$$\frac{V_g}{D R} \cdot \frac{D T_s}{2L}$$

Wag

RLC filters

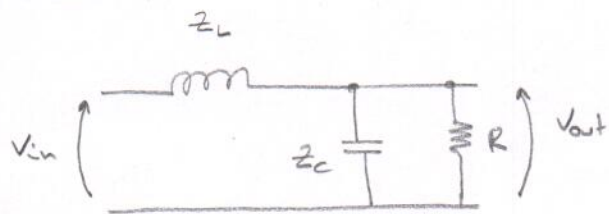

$$Z = Z_L + Z_C // R$$

$$1) Z_C // R = \frac{R/j\omega C}{R + \frac{1}{j\omega C}}$$

$$= \frac{R}{j\omega RC + 1}$$

$$\therefore V_{out} = \frac{V_{in} \cdot (Z_C // R)}{Z_L + Z_C // R}$$

$$2) Z_L + Z_C // R = j\omega L + \frac{R}{j\omega RC + 1}$$

$$= \frac{-\omega^2 RLC + j\omega L + R}{j\omega RC + 1}$$

$$\therefore \frac{V_{out}}{V_{in}} = \frac{\frac{R/j\omega RC + 1}{j\omega RC + 1}}{\frac{R - \omega^2 RLC + j\omega L}{j\omega RC + 1}}$$
$$= \frac{1}{1 - \omega^2 LC + j\omega L/R}$$

$$|Den| = \sqrt{(1 - \omega^2 LC)^2 + \frac{\omega^2 L^2}{R^2}}$$

$$1 - \omega^2 LC = \frac{\omega L}{R}$$

$$\omega^2 LC + \frac{L}{R} \omega - 1 = 0$$

$$\omega = \frac{-\frac{L}{R} \pm \sqrt{\frac{L^2}{R^2} + 4LC}}{2LC}$$

$$\omega = -\frac{1}{2RC} \pm \sqrt{\frac{1}{4C^2 R^2} + \frac{1}{LC}}$$