

Course Exercises

Power Systems Analysis


Fall 2024

2.1 Fundamental aspects for the study of AC circuits

Problem 2.1.1: Voltage and Current Phasors

If $v(t) = 141.4 \sin(\omega t + 30^\circ)$ V and $i(t) = 11.31 \cos(\omega t - 30^\circ)$ A, find for each:

- (a) the maximum value,
- (b) the RMS value, and
- (c) the phasor expression in polar and rectangular form if the voltage is the reference.
- (d) Is the circuit inductive or capacitive?

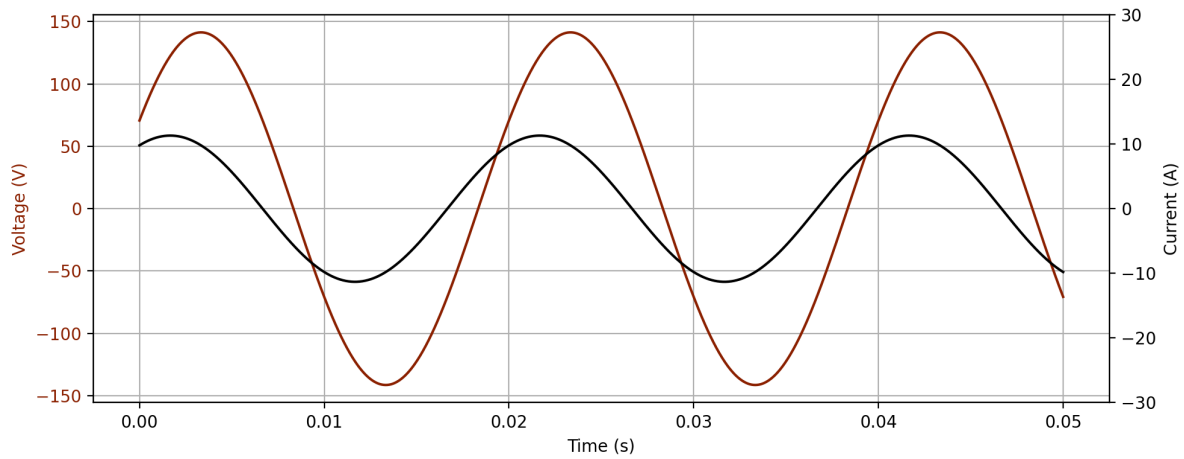

Problem 2.1.2: Impedance Calculation

If the circuit of Problem 2.1.1 consists of a purely resistive and a purely reactive element, find their parameters:

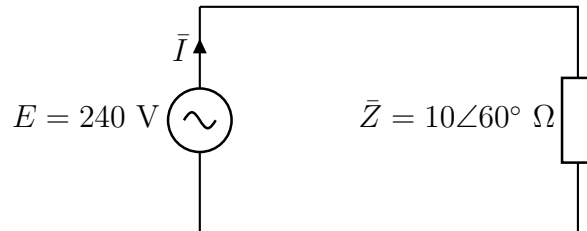
- (a) if the elements are in series, and
- (b) if the elements are in parallel.

Problem 2.1.3: Voltage Difference

In a single-phase circuit $\bar{E}_a = 120\angle 45^\circ$ (V) and $\bar{E}_b = 100\angle(-15^\circ)$ V with respect to a reference node O . Find $\bar{V}_{ba}$ in polar form.

Problem 2.1.4: AC Circuit Power Calculation

A single-phase AC voltage of 240 V is applied to a series circuit whose impedance is $10\angle 60^\circ$ (Ω). Find R , X , P , Q , and the power factor of the circuit.

**Problem 2.1.5: Effect of Parallel Capacitor**

If a capacitor is connected in parallel with the circuit of Problem 2.1.4, and if this capacitor supplies 1250 VAR, find the P and Q supplied by the 240-V source, and find the resultant power factor.

Problem 2.1.6: Power Factor Correction

A single-phase inductive load draws 10 MW at 0.6 power-factor lagging. Draw the power triangle and determine the reactive power of a capacitor to be connected in parallel with the load to raise the power factor to 0.85.

Problem 2.1.7: Three Phase Power

A balanced three-phase load is connected to a 415 V (line to line), 50 Hz, three-phase power supply. The load draws a line current of 20 A with a power factor of 0.8 lagging. Find the values of P and Q drawn by the load.

Solutions

Solution to Problem 2.1.1 (Voltage and Current Phasors):

(a) The maximum value of the voltage $v(t)$ is 141.4 V and the maximum value of the current $i(t)$ is 11.31 A.

(b) The RMS value of the voltage $v(t)$ is:

$$V_{\text{RMS}} = \frac{V_{\text{max}}}{\sqrt{2}} = \frac{141.4}{\sqrt{2}} = 100 \text{ V}$$

The RMS value of the current $i(t)$ is:

$$I_{\text{RMS}} = \frac{I_{\text{max}}}{\sqrt{2}} = \frac{11.31}{\sqrt{2}} = 8 \text{ A}$$


(c) Phasor expressions:

- Voltage phasor: $\bar{V} = 100\angle 0^\circ$ where the angle is 0° because it is taken as a reference. The Cartesian form is $\bar{V} = 100 + j0$ V.
- Current phasor: Convert cos to sin:


$$i(t) = 11.31 \cos(\omega t - 60^\circ) = 11.31 \sin(\omega t - 60^\circ + 90^\circ) = 11.31 \sin(\omega t + 30^\circ) \text{ A}$$

So, the current phasor is $\bar{I} = 8\angle 30^\circ$ A and, in its Cartesian form: $6.93 + j4$ A.

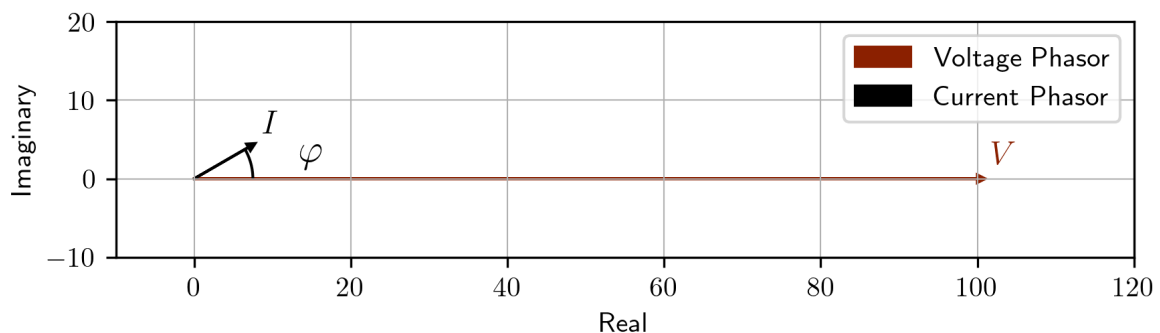
(d) The circuit is capacitive. The current is leading the voltage.



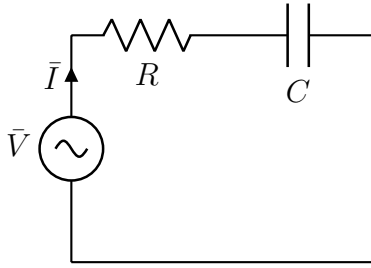Solution to Problem 2.1.2 (Impedance Calculation): Since the circuit is capacitive (2.1.1d), it consists of a resistive and capacitive element, R and C , respectively.



(a) Series RC Circuit

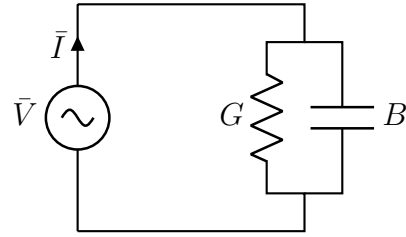

(b) Parallel RC Circuit

(a) **Series Connection:** The equivalent impedance can be expressed as:

$$\bar{Z} = R + jX$$

In the case of connection in series, the equivalent impedance is the sum of the impedances of both elements:

$$\bar{Z} = \bar{Z}_R + \bar{Z}_C$$

Therefore

$$\bar{Z} = R + \frac{1}{j\omega C} = R - j\frac{1}{\omega C}$$

The impedance can be calculated directly from the voltage and current phasors as:

$$\bar{Z} = \frac{\bar{V}}{\bar{I}} = \frac{V e^{j\theta_V}}{I e^{j\theta_I}} = \frac{V}{I} e^{j(\theta_V - \theta_I)} = Z e^{j\varphi}$$

- The magnitude of $\bar{Z}$ is:

$$|\bar{Z}| = \frac{V}{I} = \frac{100}{8} = 12.5 \Omega$$

- The phase angle φ of $\bar{Z}$ is:

$$\varphi = \theta_V - \theta_I = -30^\circ$$

- Solving for R and X :

$$R = |\bar{Z}| \cos(-30^\circ) = 12.5 \cdot \frac{\sqrt{3}}{2} = 10.83 \Omega$$

$$X = |\bar{Z}| \sin(-30^\circ) = 12.5 \cdot \left(-\frac{1}{2}\right) = -6.25 \Omega$$

Since in this case $X_C = \frac{1}{\omega C} = -X$, then

$$C = \frac{1}{\omega \cdot (-X)} = \frac{1}{2\pi \cdot 50 \cdot 6.25} = 509.3 \mu\text{F}.$$

(b) **Parallel Connection:** The equivalent admittance can be expressed as

$$\bar{Y} = G + jB$$

In the case of connection in parallel, the equivalent admittance is the sum of the admittances of both elements:

$$\bar{Y} = \bar{Y}_R + \bar{Y}_C$$

Therefore:

$$\bar{Y} = \frac{1}{R} + j\omega C$$

The equivalent admittance is:

$$\bar{Y} = \frac{1}{\bar{Z}} = \frac{1}{12.5e^{j(-30^\circ)}} = 0.0693 + j0.0400 \text{ S}$$

Therefore, $G = 0.0693 \text{ S}$ and $B = 0.04 \text{ S}$. In this case $R = \frac{1}{G} = 14.43 \text{ } \Omega$ and $X_C = \frac{1}{\omega C} = \frac{1}{B} = \frac{1}{0.04} = 25 \text{ } \Omega$. Therefore,

$$C = \frac{1}{\omega X_C} = \frac{1}{2 \cdot \pi \cdot 50 \cdot 25} = 127.3 \text{ } \mu\text{F}.$$

Solution to Problem 2.1.3 (Voltage Difference):

- Given $\bar{E}_a = 120\angle 45^\circ$ and $\bar{E}_b = 100\angle -15^\circ$, the voltage $\bar{V}_{ba}$ is found using:

$$\bar{V}_{ba} = \bar{E}_b - \bar{E}_a$$

- Converting to rectangular form:

$$\bar{E}_a = 120(\cos 45^\circ + j \sin 45^\circ) = 84.85 + j84.85, \text{ V}$$


$$\bar{E}_b = 100(\cos(-15^\circ) + j \sin(-15^\circ)) = 96.59 - j25.88 \text{ V}$$

- Subtracting:

$$\bar{V}_{ba} = (96.59 - j25.88) - (84.85 + j84.85) = 11.74 - j110.73 \text{ V}$$

- Converting back to polar form:
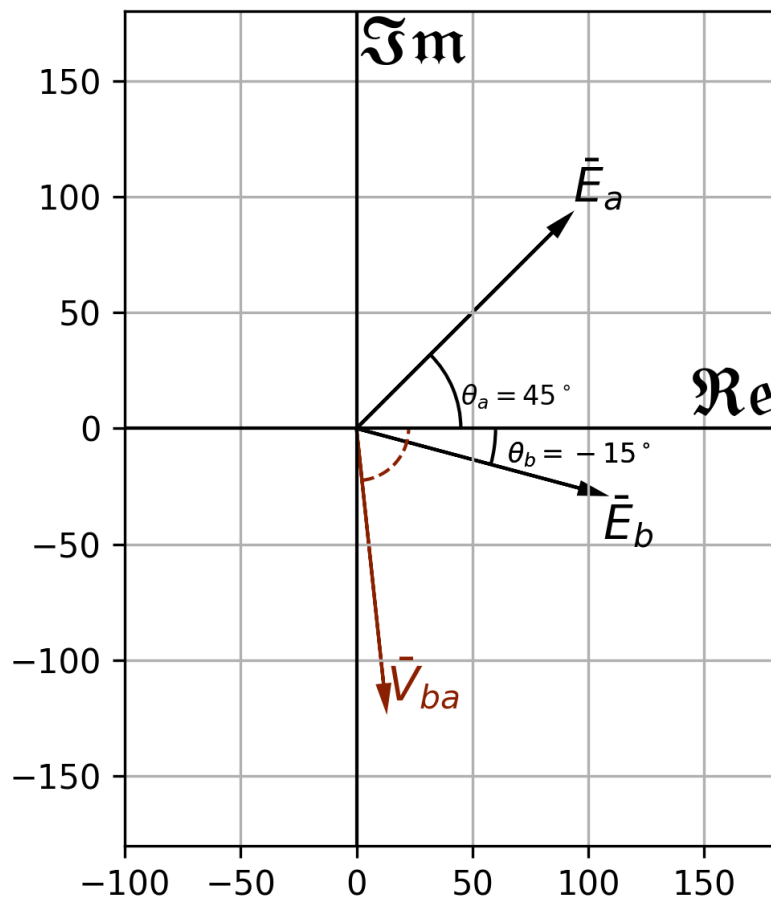
$$\bar{V}_{ba} = \sqrt{11.74^2 + (-110.73)^2} \angle \tan^{-1} \left(\frac{-110.73}{11.74} \right) = 111.35 \angle -84^\circ \text{ V}$$



Solution to Problem 2.1.4 (AC Circuit Power Calculation):

- Given impedance $\bar{Z} = 10\angle 60^\circ, \Omega$:

$$\bar{Z} = R + jX = 10(\cos 60^\circ + j \sin 60^\circ) = 5 + j8.66 \Omega$$

- The resistive component $R = 5 \Omega$, and the reactive component $X = 8.66 \Omega$.
- The current $\bar{I}$ is:

$$\bar{I} = \frac{\bar{V}}{\bar{Z}} = \frac{240}{10\angle 60^\circ} = 24\angle(-60^\circ) \text{ A}$$

- Real power P :


$$P = VI \cos \varphi = 240 \cdot 24 \cdot \cos 60^\circ = 2880 \text{ W}$$

- Reactive power Q :

$$Q = VI \sin \varphi = 240 \cdot 24 \cdot \sin 60^\circ = 4988 \text{ VAr}$$

- Power factor:
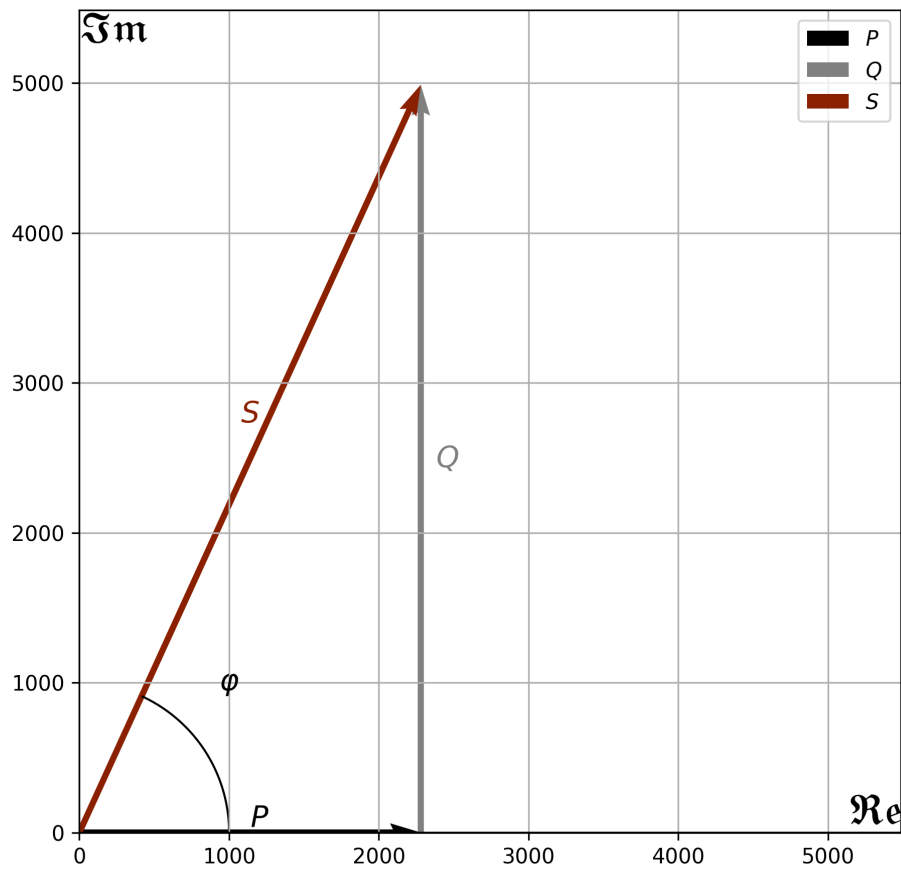
$$PF = \cos \varphi = \cos 60^\circ = 0.5$$



Solution to Problem 2.1.5 (Effect of Parallel Capacitor): Given that the capacitor supplies $Q_c = 1250\text{VAr}$.

- The total reactive power Q_t supplied by the source is:

$$Q_t = Q - Q_c = 4988 - 1250 = 3738 \text{ VAr}$$

- The apparent power S is:


$$S = \sqrt{P^2 + Q_t^2} = \sqrt{2880^2 + 3738^2} = 4718.8 \text{ VA}$$

- The resultant power factor is:

$$\text{Power Factor} = \frac{P}{S} = \frac{2880}{4718.8} = 0.61$$

or alternatively
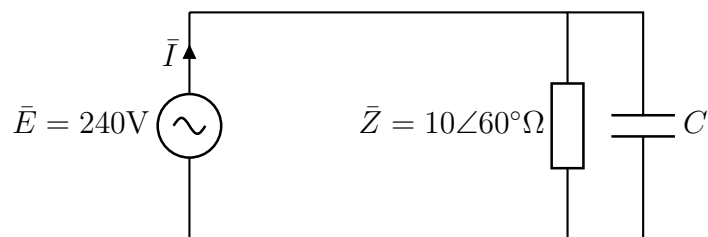
$$\text{Power Factor} = \cos \left(\tan^{-1} \left(\frac{3738}{2880} \right) \right) = 0.61$$



Solution to Problem 2.1.6 (Power Factor Correction):

- Real power $P = 10$ MW and initial power factor $PF_{\text{initial}} = 0.6$.
- Initial reactive power Q_{initial} :


$$Q_{\text{initial}} = P \tan \cos^{-1}(0.6) = 10 \times \tan \cos^{-1}(0.6) = 13.33 \text{ MVar}$$

- Final reactive power Q_{final} with power factor $PF_{\text{final}} = 0.85$:

$$Q_{\text{final}} = P \tan \cos^{-1}(0.85) = 10 \cdot \tan \cos^{-1}(0.85) = 6.20 \text{ MVar}$$

- Required capacitor reactive power Q_c :
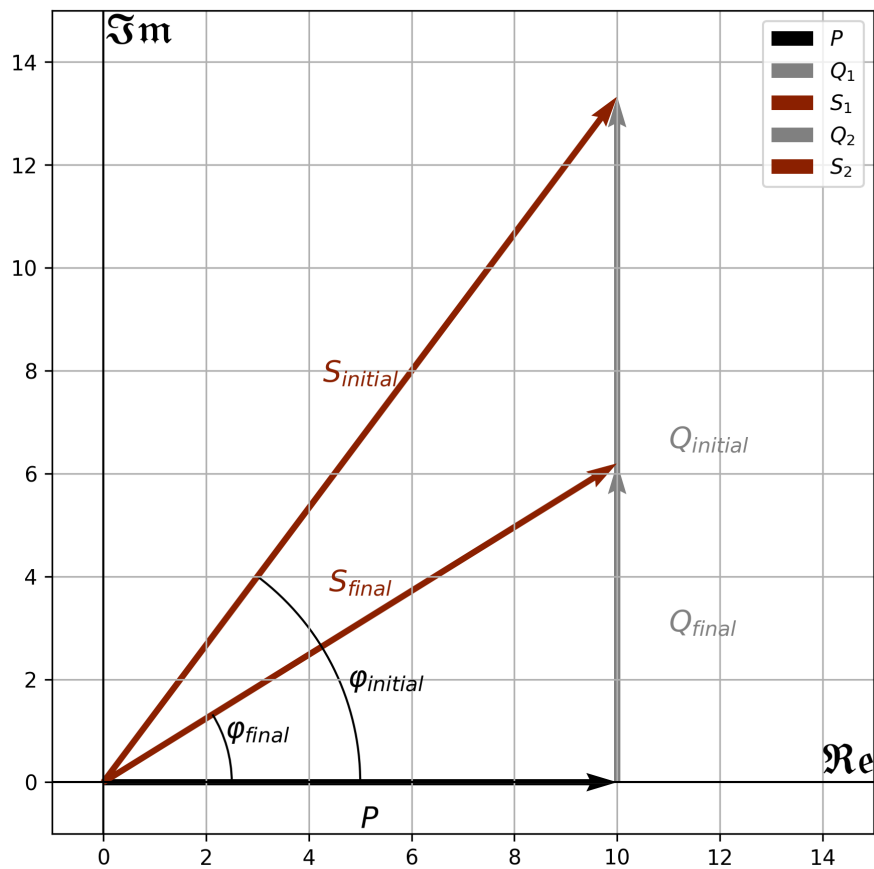
$$Q_c = Q_{\text{initial}} - Q_{\text{final}} = 13.33 - 6.20 = 7.13 \text{ MVar}$$



Solution to Problem 2.1.7 (Three Phase Power): The real power P drawn from the line can be calculated using:

$$P = \sqrt{3}VI \cos \varphi$$

Substituting the values:

$$P = \sqrt{3} \cdot 415 \cdot 20 \cdot 0.8 = 11.5 \text{ kW}$$

The reactive power Q can be calculated similarly by using:

$$Q = \sqrt{3}VI \sin(\cos^{-1}(\text{Power Factor}))$$

$$Q = \sqrt{3} \cdot 415 \cdot 20 \cdot 0.6 = 8.63 \text{ kVAr}$$

The power factor $\cos \varphi$ is also given by:

$$\cos \varphi = \cos \left(\tan^{-1} \left(\frac{Q}{P} \right) \right)$$

Substitute the values of P and Q calculated:

$$\varphi = \tan^{-1} \left(\frac{8.63}{11.5} \right) = \tan^{-1}(0.75) = 36.87^\circ$$

$$\cos \varphi = \cos(36.87^\circ) = 0.8$$

This confirms that the power factor is indeed 0.8.