

Course Exercises

Power Systems Analysis


Fall 2024

2.1 Fundamental aspects for the study of AC circuits

Problem 2.1.1: Voltage and Current Phasors

If $v(t) = 141.4 \sin(\omega t + 30^\circ)$ V and $i(t) = 11.31 \cos(\omega t - 30^\circ)$ A, find for each:

- (a) the maximum value,
- (b) the RMS value, and
- (c) the phasor expression in polar and rectangular form if the voltage is the reference.
- (d) Is the circuit inductive or capacitive?

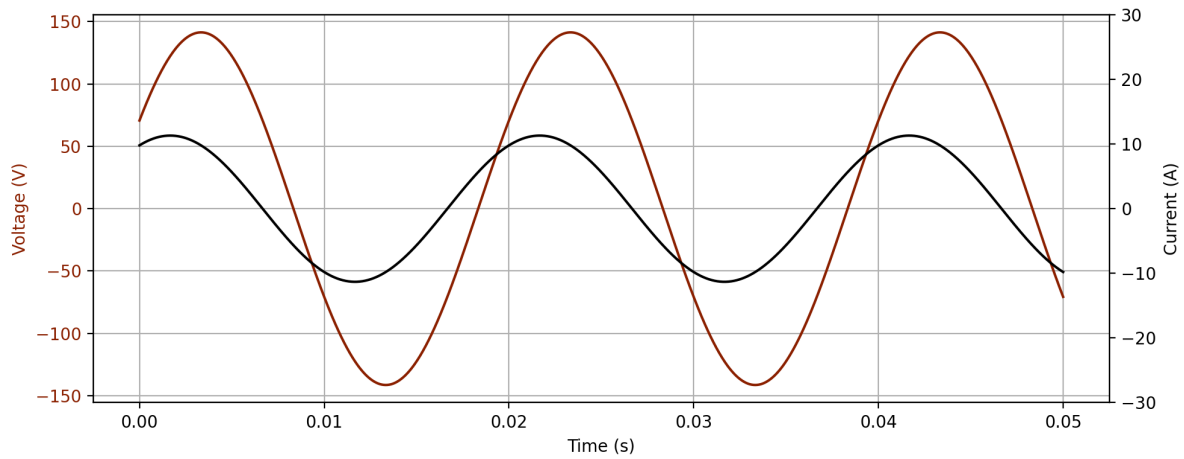

Problem 2.1.2: Impedance Calculation

If the circuit of Problem 2.1.1 consists of a purely resistive and a purely reactive element, find their parameters:

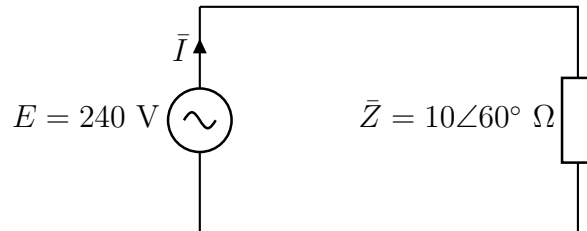
- (a) if the elements are in series, and
- (b) if the elements are in parallel.

Problem 2.1.3: Voltage Difference

In a single-phase circuit $\bar{E}_a = 120\angle 45^\circ$ (V) and $\bar{E}_b = 100\angle(-15^\circ)$ V with respect to a reference node O . Find $\bar{V}_{ba}$ in polar form.

Problem 2.1.4: AC Circuit Power Calculation

A single-phase AC voltage of 240 V is applied to a series circuit whose impedance is $10\angle 60^\circ$ (Ω). Find R , X , P , Q , and the power factor of the circuit.

**Problem 2.1.5: Effect of Parallel Capacitor**

If a capacitor is connected in parallel with the circuit of Problem 2.1.4, and if this capacitor supplies 1250 VAR, find the P and Q supplied by the 240-V source, and find the resultant power factor.

Problem 2.1.6: Power Factor Correction

A single-phase inductive load draws 10 MW at 0.6 power-factor lagging. Draw the power triangle and determine the reactive power of a capacitor to be connected in parallel with the load to raise the power factor to 0.85.

Problem 2.1.7: Three Phase Power

A balanced three-phase load is connected to a 415 V (line to line), 50 Hz, three-phase power supply. The load draws a line current of 20 A with a power factor of 0.8 lagging. Find the values of P and Q drawn by the load.