

Fundamentals of Electrical Circuits and Systems

Chapter 2: Fundamental Theorems of Linear Circuits

Farhad Rachidi

École Polytechnique Fédérale de Lausanne
Lausanne, Switzerland



Electrical Circuits: Fundamental Theorems

- Linear circuits
- Superposition theorem
- Source transformation
- Thévenin's theorem
- Norton's theorem
- Maximum power transfer theorem
- Tellegen's theorem

Linear circuits

- A linear circuit is one whose output is linearly connected to its input.
- A linear circuit has only linear elements, linear dependent and independent sources.

Question

- A resistor is a linear element

A. Yes

B. No

Question

- A capacitor is a linear element

A. Yes

B. No

Question

- An inductor is a linear element


A. Yes

B. No


Superposition theorem

- The current and voltages in any element of a linear circuit are given by the sum of the voltages and currents produced in that element by each source taken separately.
- Note: this theorem does not apply to power.

Superposition theorem: example

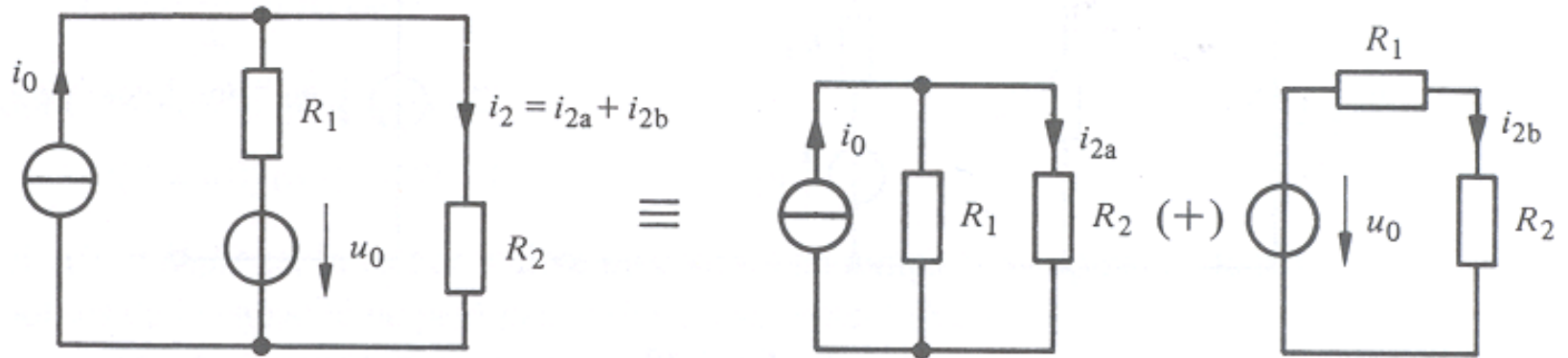

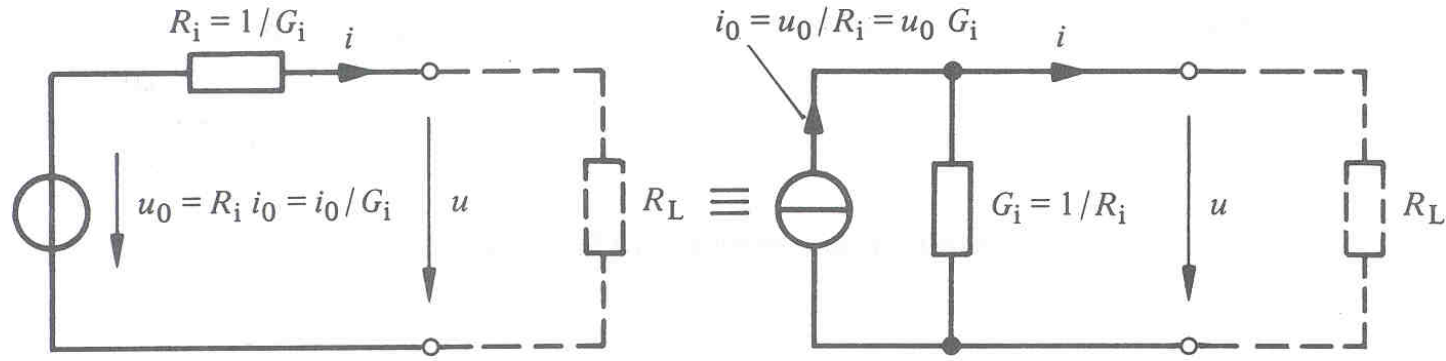Equivalence voltage source / current source



Question


- Which pair of circuits are equivalent circuits?

A. (a) and (b)


B. (b) and (d)

C. (a) and (c)


D. (c) and (d)

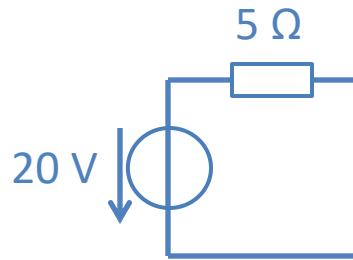


(a)

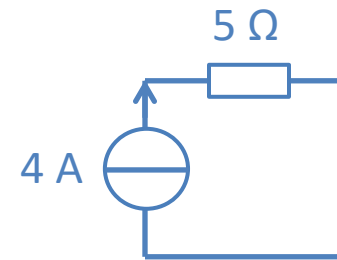

(b)

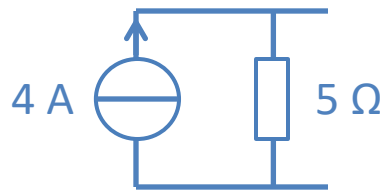


(c)

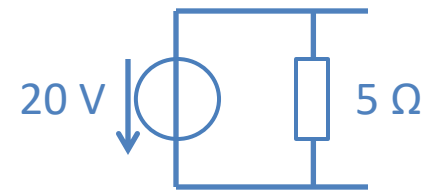

(d)


Equivalence voltage source / current source

Example:

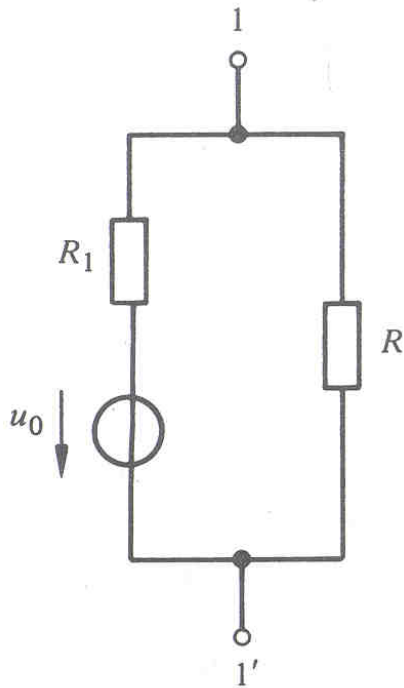


Equivalence voltage source / current source

Example:

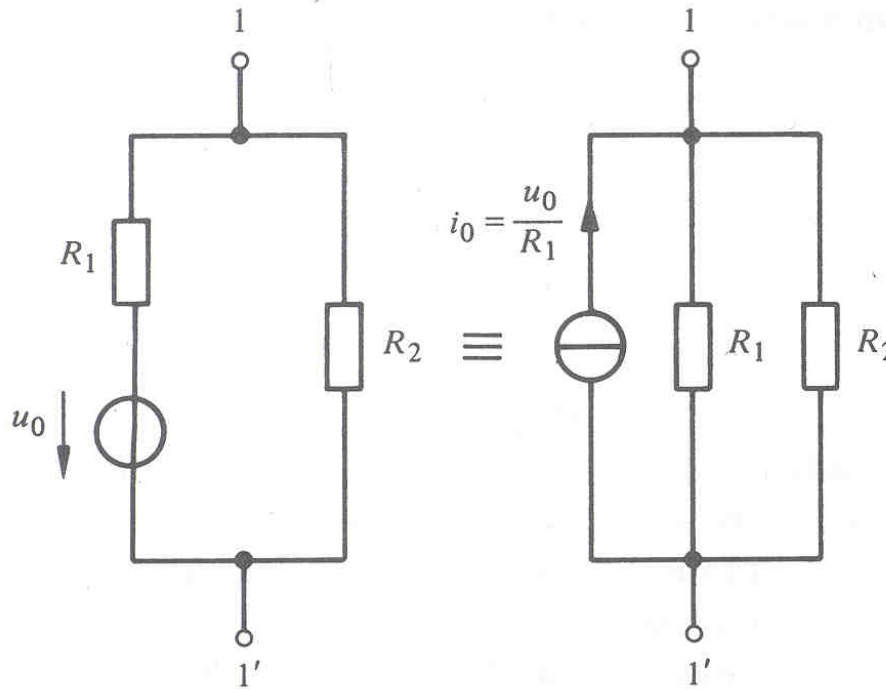


Equivalence voltage source / current source

Example:

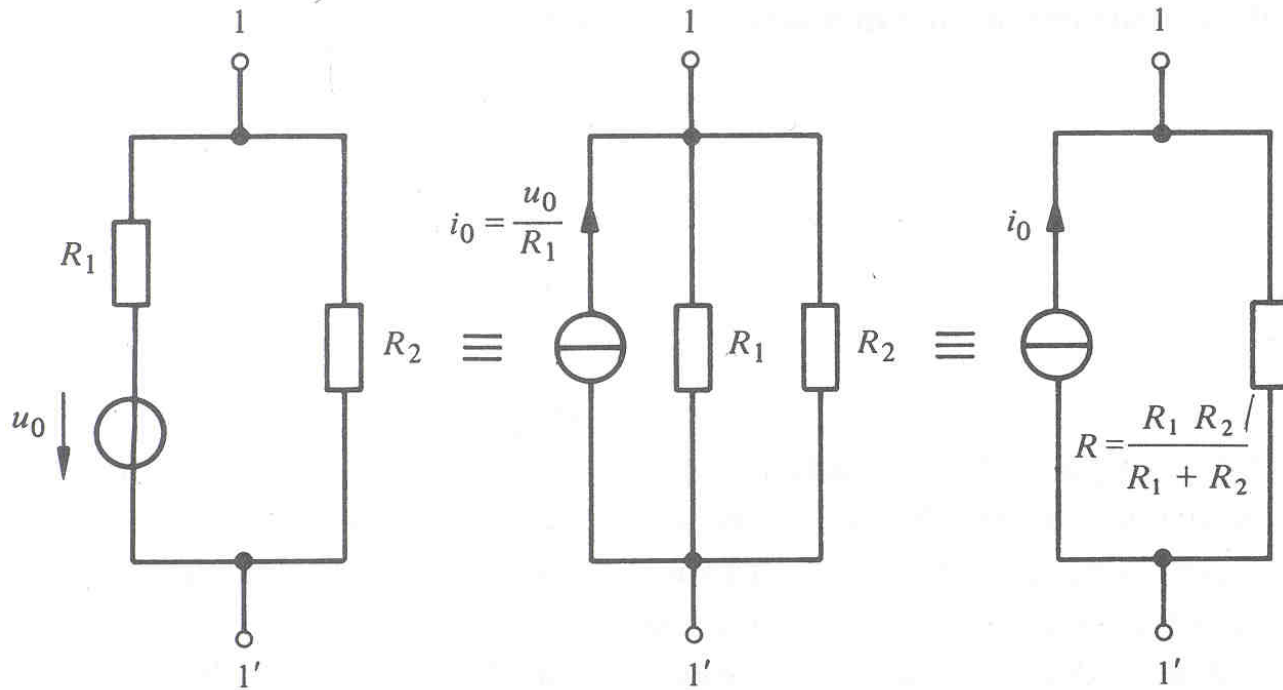


Equivalence voltage source / current source

Example:

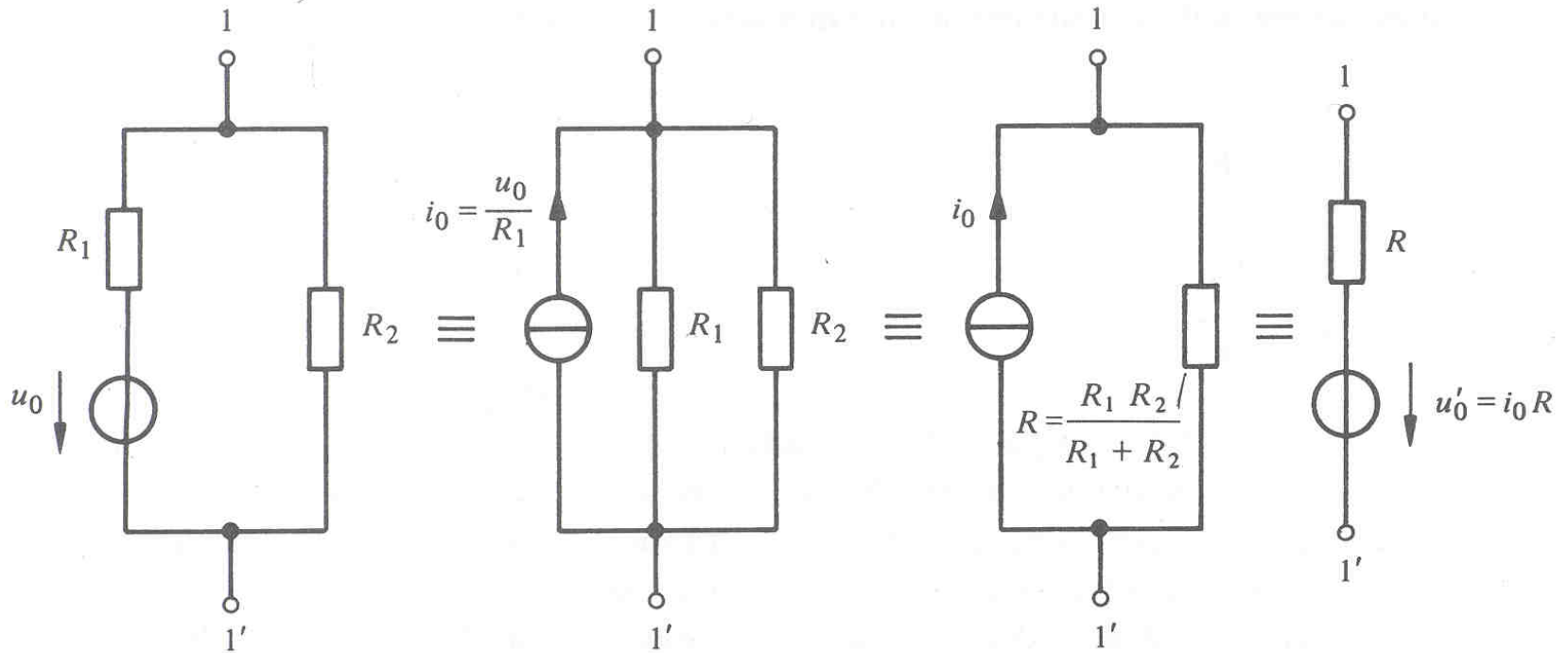


Equivalence voltage source / current source

Example:

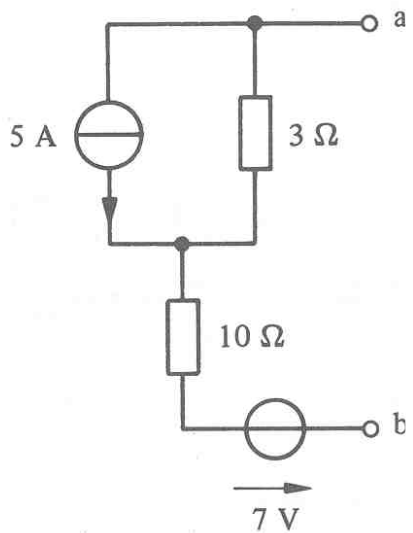


Equivalence voltage source / current source

Example:

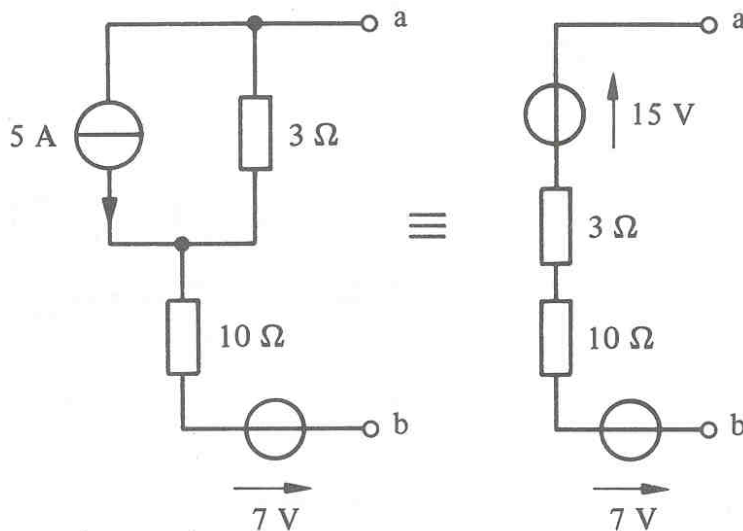


Equivalence voltage source / current source


Example:

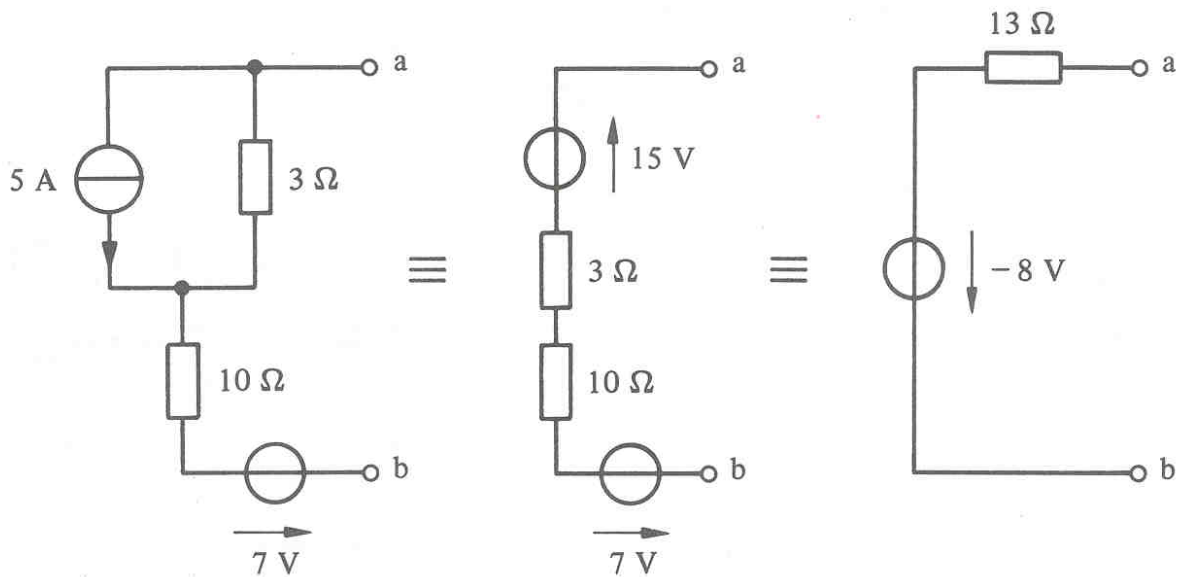


Substitution of sources

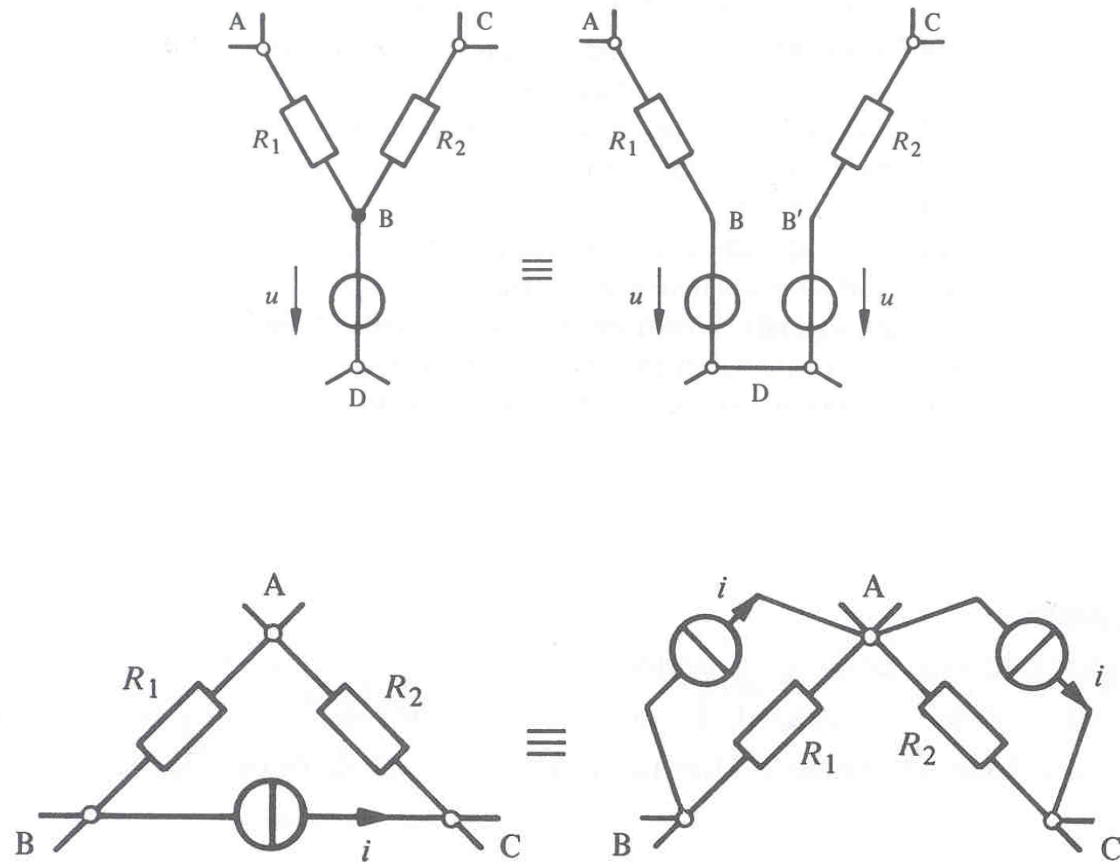


Example

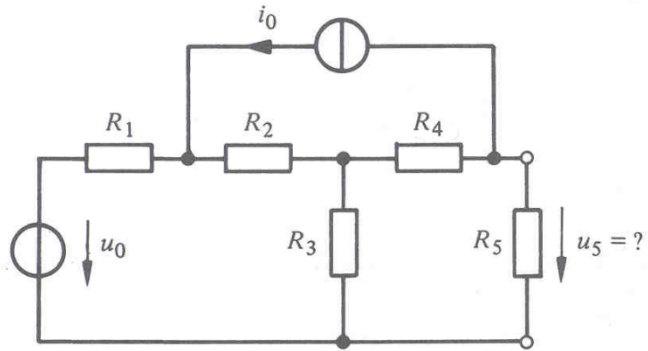


Example

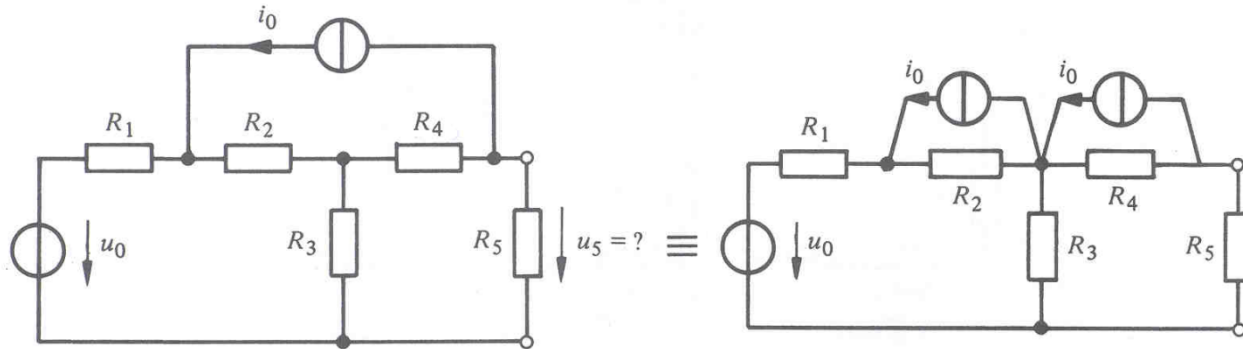


Example

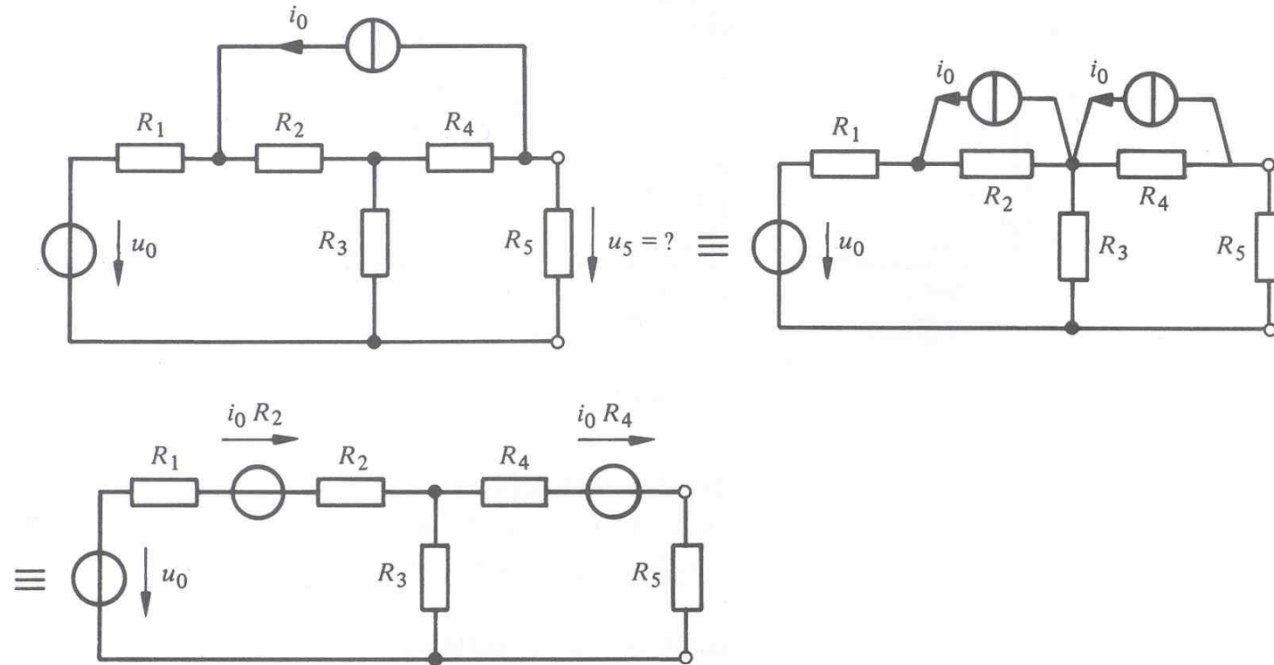


Example

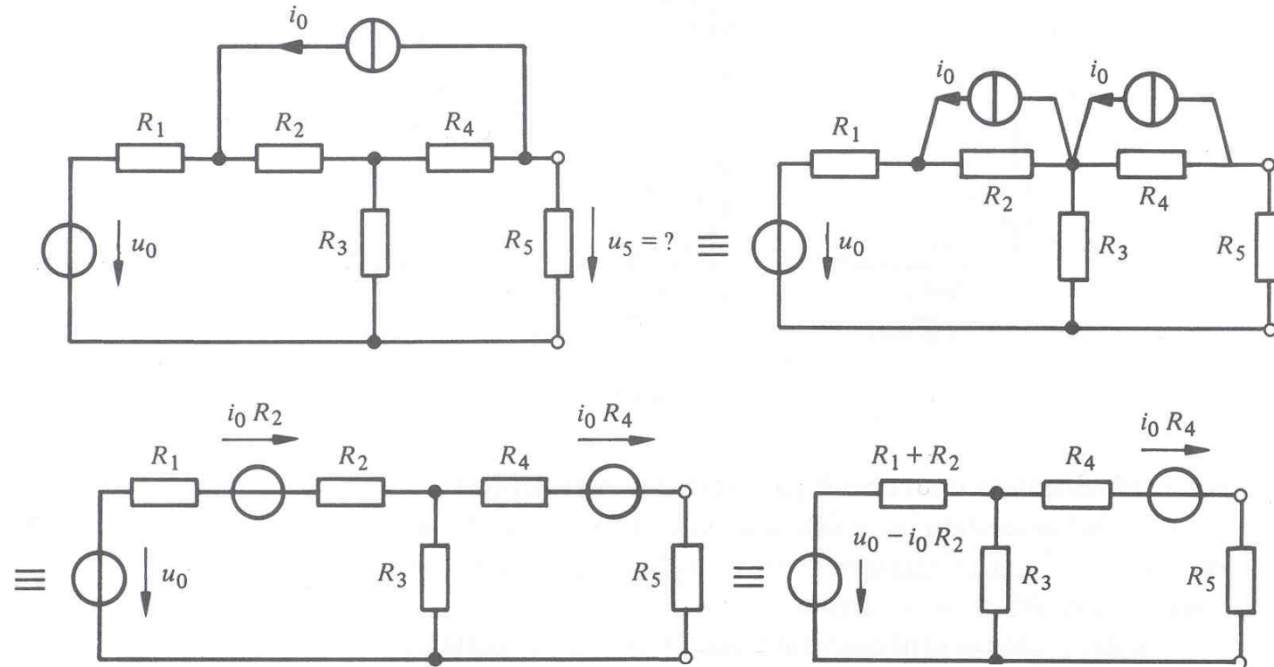

Example

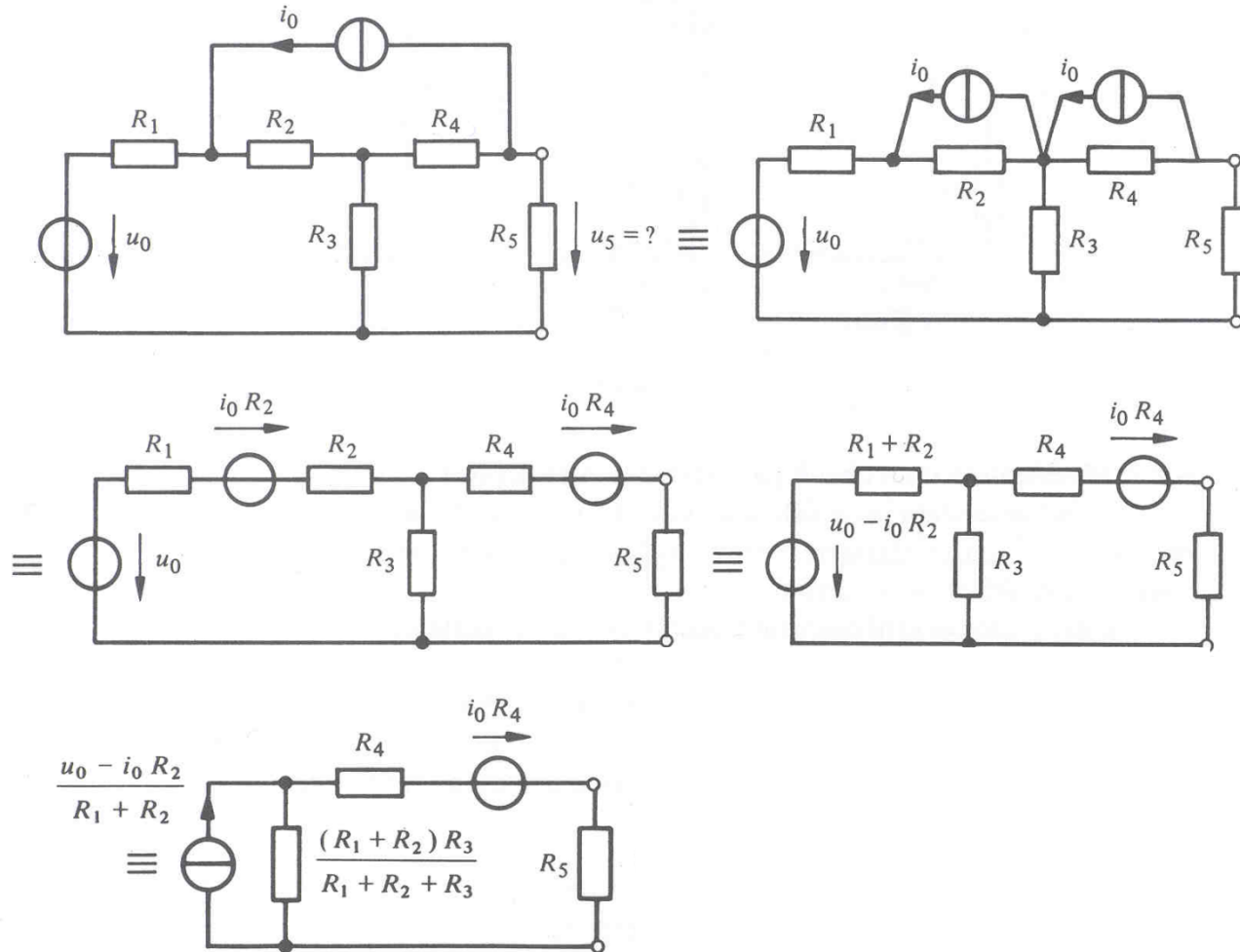

Example

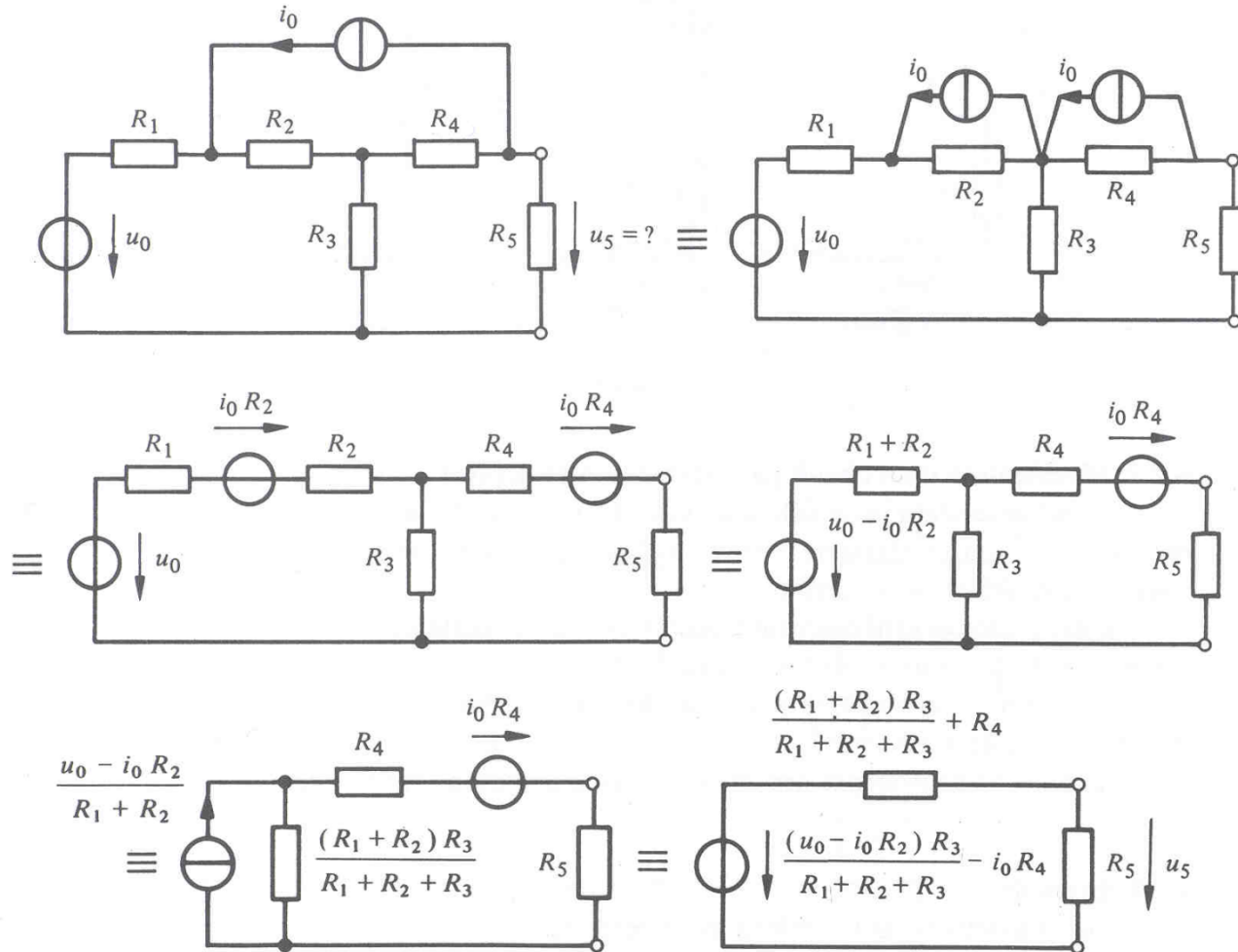

Thévenin's theorem


Léon **Thévenin** (1857-1926),
French physicist. He published
his 1883 theorem.



Hermann von **Helmoltz** (1821-1894),
German physicist and physiologist.
He published the theorem called
Thévenin in 1863.

Thévenin's equivalence

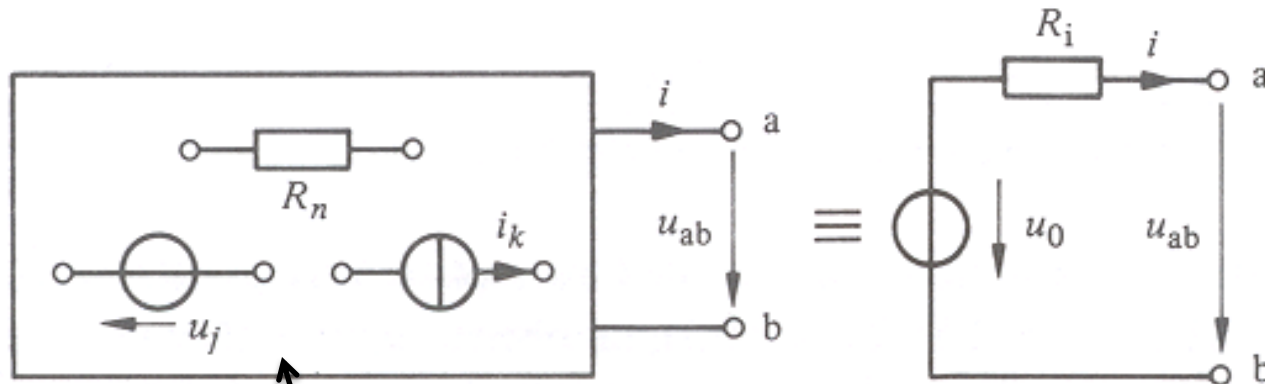
- Goal: replace a complex circuit with a circuit consisting of a voltage source and a resistor



Circuit composed of resistors, voltage sources (independent and controlled), current sources (independent and controlled)

Thévenin's equivalence

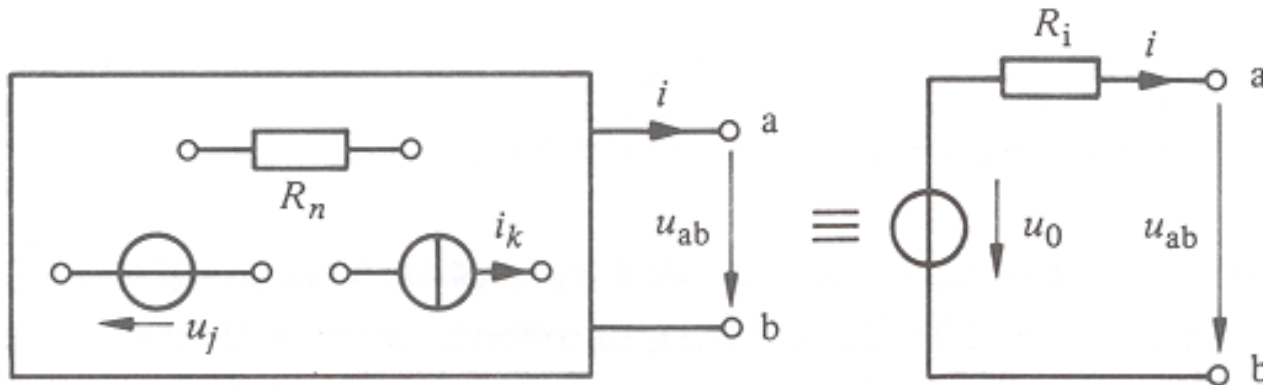- Goal: replace a complex circuit with a circuit consisting of a voltage source and a resistor



$$u_o = u_{ab} \Big|_{i=0}$$



$$R_i = R_{ab} \Big|_{u_j=0, i_k=0}$$

Thévenin's equivalence: Procedure

- Identify the terminals of the circuit and the external charge
- Measure or calculate the voltage across the circuit without external charge. This is Thévenin's voltage.
- Cancel the independent sources and determine the resistance seen from the terminals of the circuit. This is Thévenin's resistance.


Thévenin's theorem

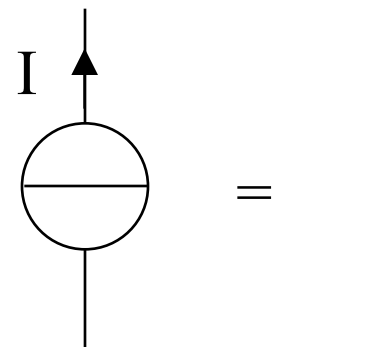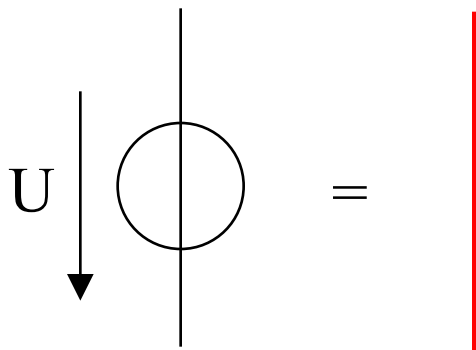- To cancel a voltage source is to replace it with a **short circuit**.
- To cancel a current source is to replace it with an **open circuit**.



Norton's equivalence

- Corollary of Thévenin's theorem

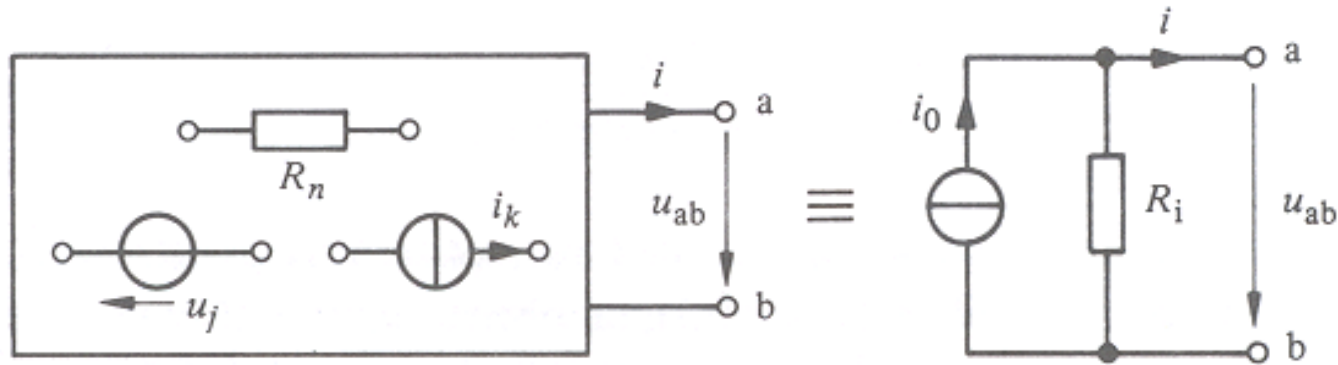

$$i_o = i \Big|_{u_{ab}=0}$$

$$R_i = R_{ab} \Big|_{u_j=0, i_k=0}$$

Norton

Edward Larry **Norton** (1898-?),
researcher at Bell Telephone Labs
(USA). The first mention of his
theorem dates from 1926.



Norton's equivalence: Procedure

- Identify the terminals of the circuit and the external charge
- Short-circuit the circuit terminals and theoretically or experimentally determine the intensity of the short-circuit current. This is Norton's power source.
- Cancel the independent sources and determine the resistance seen from the terminals of the circuit. This is the resistance of Norton (and Thévenin).

Question


- To establish the equivalent Thévenin and Norton diagrams of a circuit, it is necessary to measure:
 - A. No-load voltage and short-circuit current
 - B. No-load voltage, short-circuit current and circuit resistance (with sources canceled)

Resistance of Thévenin / Norton in case of dependent sources

- If the circuit has dependent sources, the resistance of Thévenin can be determined by two methods



Resistance of Thévenin / Norton in case of dependent sources: 1st method

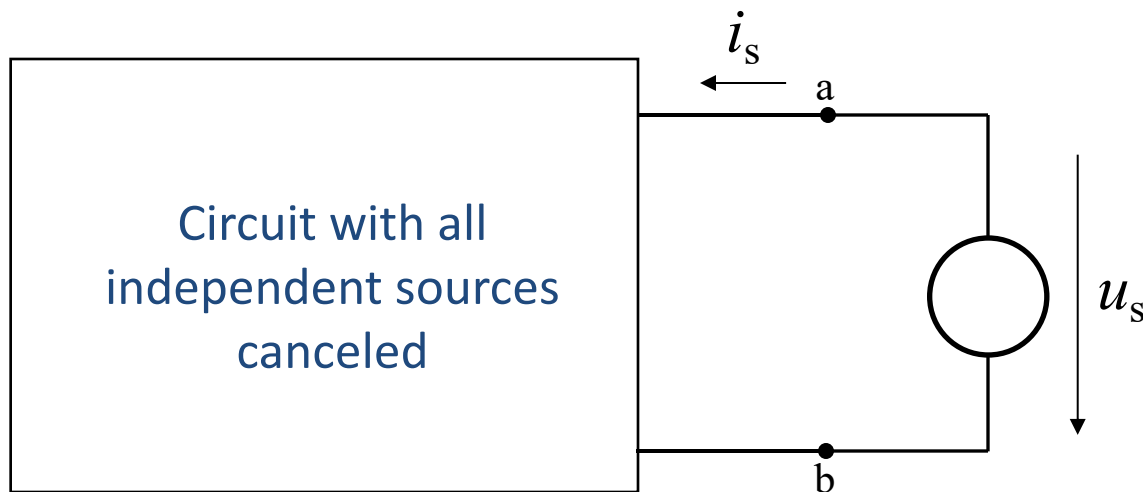- Cancel all independent sources and apply a voltage source u_s and determine the result current i_s . Thévenin's resistance is then $R_i = u_s / i_s$.




Resistance of Thévenin / Norton in case of dependent sources: 2nd method

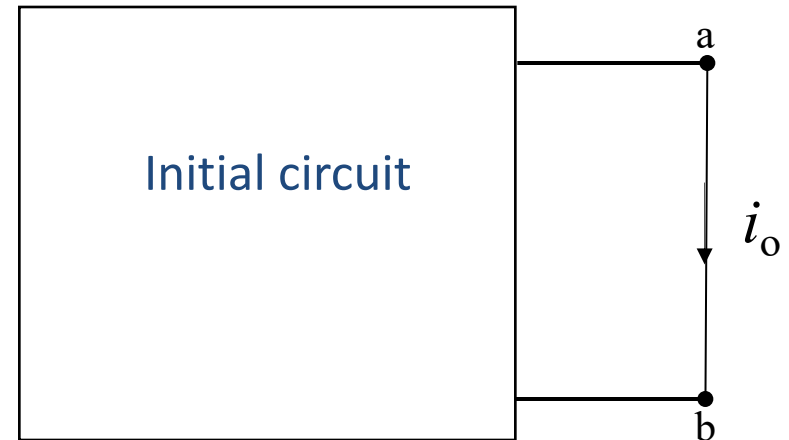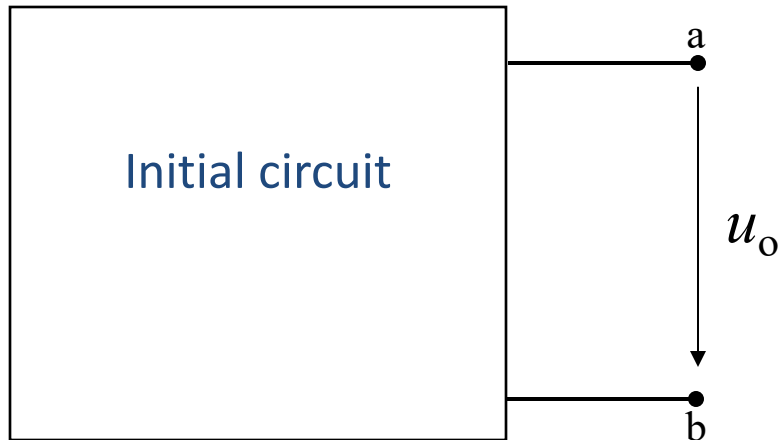- Determine the no-load voltage u_o and the short-circuit current i_o . The resistance of Thévenin is then $R_i = u_o / i_o$.




Maximum power transfer theorem

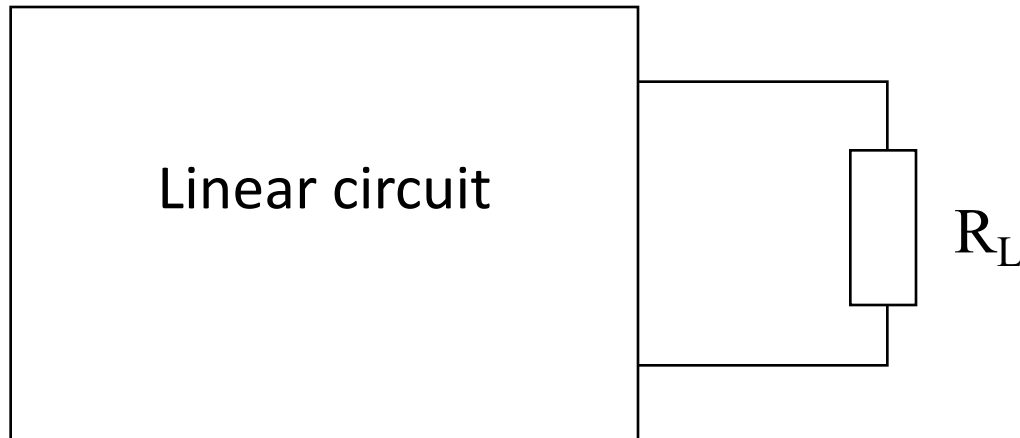- What is the value of the load resistor R_L for which the latter will dissipate a maximum of power ?



Maximal power transfer theorem

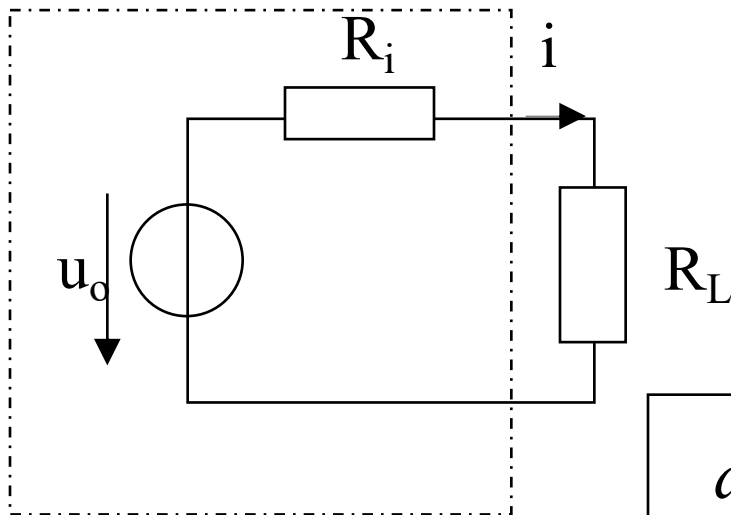- Answer: we replace the complex circuit with its Thévenin's equivalence :





$$i = \frac{u_o}{R_i + R_L}$$


$$P = R_L i^2$$

$$\frac{dP}{dR_L} = 0 \Rightarrow R_L = R_i, \quad P_{\max} = \frac{u_o^2}{4R_i}$$


Maximal power transfer theorem

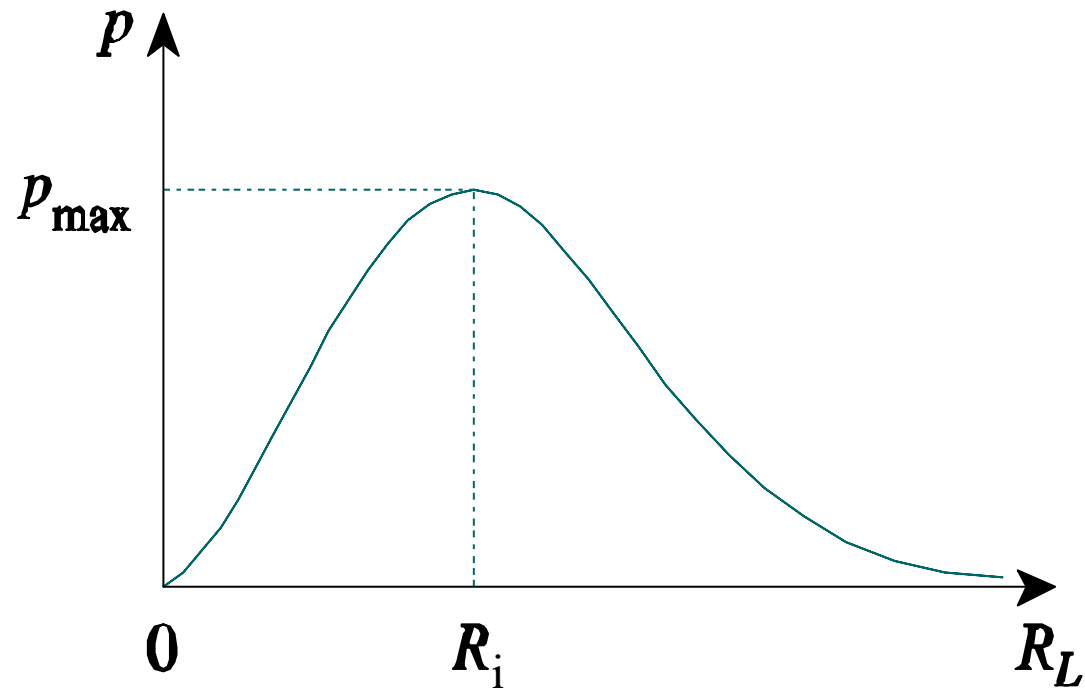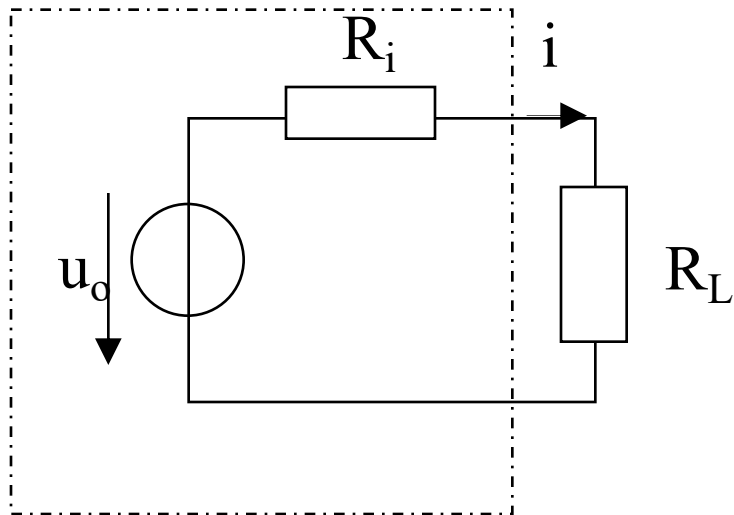

Reciprocity Theorem : 1st case

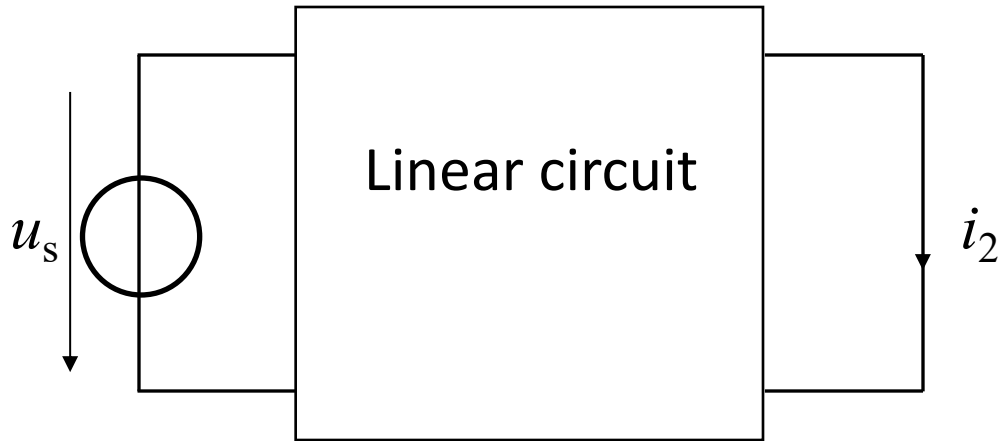


if $u_s = u'_s$ then $i'_1 = i_2$

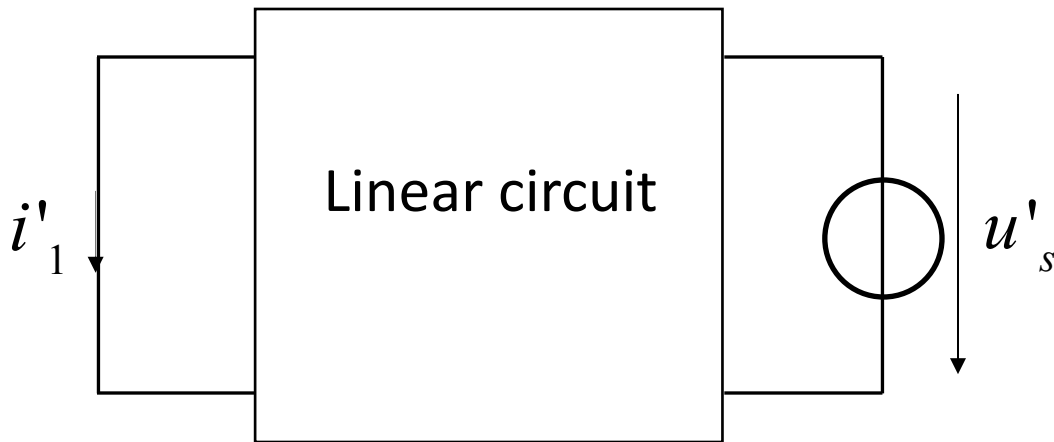


$$\frac{i'_1}{u'_s} = \frac{i_2}{u_s}$$

Reciprocity Theorem : 2nd case

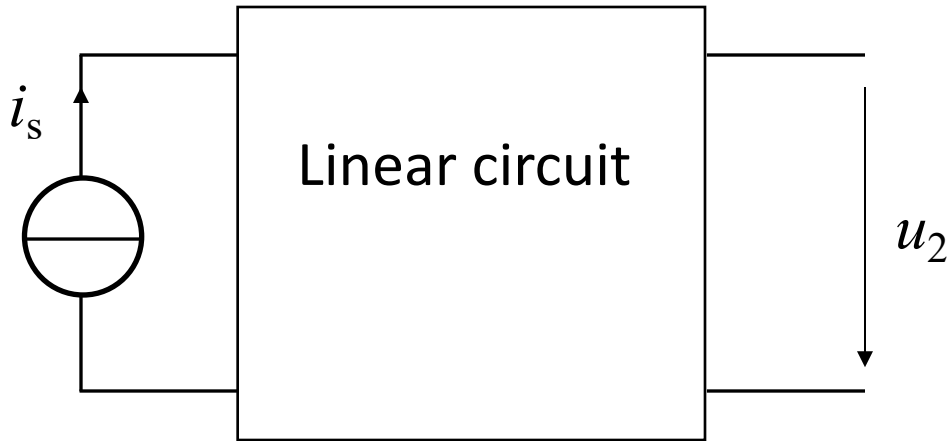

if $i_s = i'_s$ then $u'_1 = u_2$

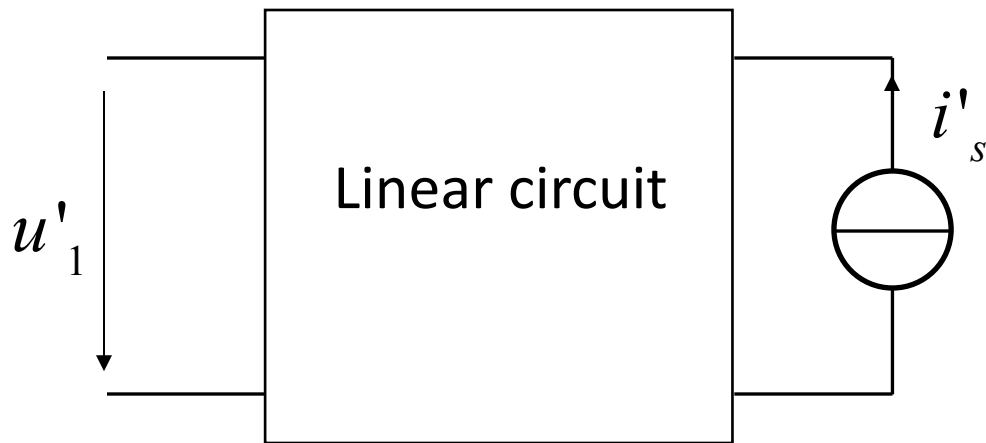

$$\frac{u'_1}{i'_s} = \frac{u_2}{i_s}$$


Tellegen's theorem

- If any electrical circuit has N branches, with voltages u_k and currents i_k at each branch k , then

$$\sum_{k=1}^N u_k i_k = 0$$

- This theorem is a consequence of Kirchhoff's laws and translates the conservation of energy in an electric circuit

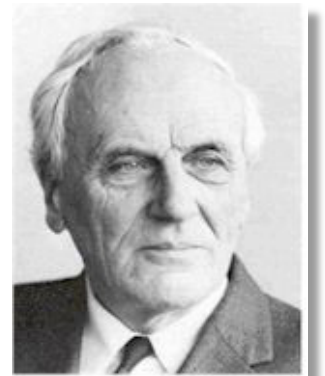Bernard D.H. Tellegen (1900-1990), Dutch electrical engineer. He formulated the so-called Tellegen theorem in 1953.



Tellegen's theorem: corollary

- If two circuits have the same topology, then

$$\sum_{k=1}^N u_k i_k = 0 \qquad \sum_{k=1}^N u'_k i'_k = 0$$

- But also

$$\sum_{k=1}^N u_k i'_k = 0 \qquad \text{and} \qquad \sum_{k=1}^N u'_k i_k = 0$$

Tellegen's theorem: example

On the board!