

SOLUTION SET I

EXERCISE I.1 : KIRCHHOFF'S LAW (1)

By applying Kirchhoff's law for voltages, we obtain :

$$-12 + 4I + 2U_0 - 4 + 6I = 0 \quad (1)$$

Ohm's law applied to the resistance of $6\ \Omega$ gives :

$$U_0 = -6I \quad (2)$$

Substituting in (1) :

$$-16 + 10I - 12I = 0 \quad \Rightarrow \quad \boxed{I = -8\text{ A}} \quad \Rightarrow \quad \boxed{U_0 = 48\text{ V}}$$

EXERCISE I.2 : EQUIVALENT RESISTANCE

The two resistors of $3\ \Omega$ and $6\ \Omega$ are in parallel because they are both connected between the points 2 and 3. Their equivalent resistance is therefore :

$$3\ \Omega \parallel 6\ \Omega = \frac{3 \times 6}{3 + 6} = 2\ \Omega \quad (1)$$


Similarly for the resistors of $12\ \Omega$ and $4\ \Omega$ which are both connected between the points 2 and 4. Their equivalent resistance is :

$$12\ \Omega \parallel 4\ \Omega = \frac{12 \times 4}{12 + 4} = 3\ \Omega \quad (2)$$


The resistor of $5\ \Omega$ is in series with a resistor of $1\ \Omega$, between points 2 and 4, which gives an equivalent resistance of :

$$1\ \Omega + 5\ \Omega = 6\ \Omega \quad (3)$$

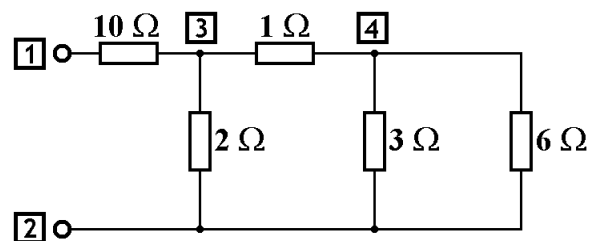We can redraw the initial diagram by means of these three partial equivalent resistances, which gives the simplified diagram opposite.



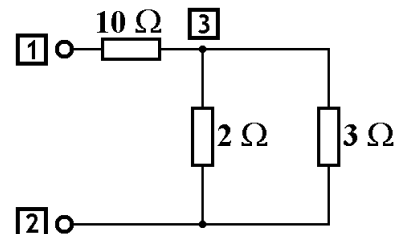In this simplified diagram, the resistors of $3\ \Omega$ and $6\ \Omega$ are in parallel between the points 2 and 4. Their equivalent resistance is therefore $2\ \Omega$ [as equation (1)]. The latter is in series with the resistor of $1\ \Omega$, which gives $3\ \Omega$ in total and makes it possible to further simplify the diagram as opposite.





We have only two resistors in parallel of $2\ \Omega$ and $3\ \Omega$, in series with $10\ \Omega$, which finally gives :


$$\boxed{R_{1-2} = 11,2\ \Omega}$$

EXERCISE I.3 : SOURCE TRANSFORMATION

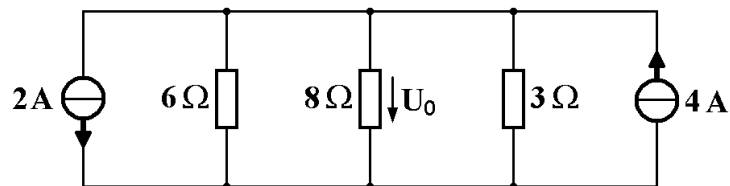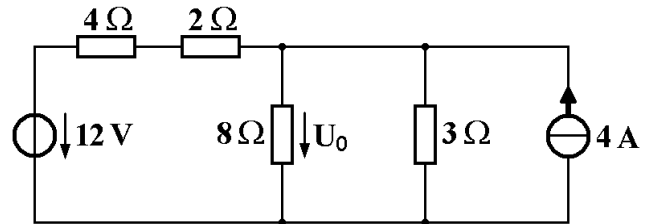- A. Transform the current and voltage sources, so as to obtain the diagram of the figure opposite.
- B. Group the resistors in series of $4\ \Omega$ and $2\ \Omega$, and transform the source of $12\ \text{V}$, to obtain the diagram of the figure below.



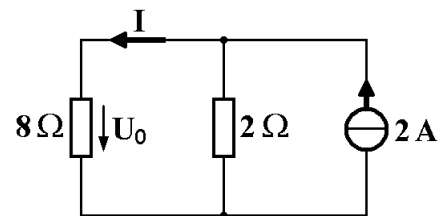- C. Group the resistors in parallel of $3\ \Omega$ and $6\ \Omega$, as well as the two sources of current also in parallel, which gives the diagram of the figure opposite.
- D. The current I is calculated by the relation of the current divider :



$$I = \frac{2}{2+8} \cdot 2\ \text{A} = 0,4\ \text{A}$$

By Ohm's law : $U_0 = 8\ \Omega \cdot 0,4\ \text{A} = 3,2\ \text{V}$