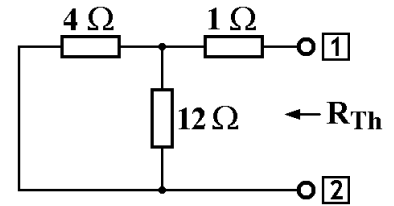


SOLUTION SET II

EXERCISE II.1 : THÉVENIN'S EQUIVALENT CIRCUIT


- A. We find the resistance of Thévenin R_{Th} by replacing the voltage source with a short circuit and the current source with an open circuit, as shown in the figure on the right.



Thévenin's resistance is obtained by grouping the resistors of $4\ \Omega$ and $12\ \Omega$ which are in parallel, then in series with the one of $1\ \Omega$:

$$R_{Th} = \frac{4 \times 12}{4 + 12} + 1 = 4\ \Omega$$

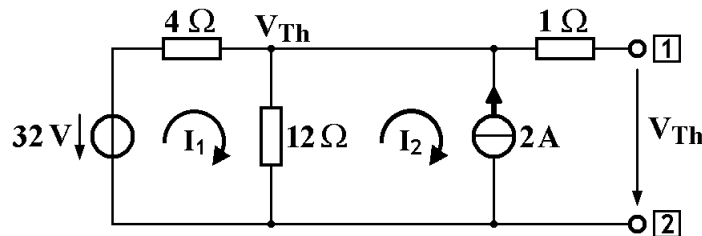- B. Determination of the voltage of Thévenin V_{Th} as shown in the figure below.



In the current mesh I_1 , the voltage equation is expressed as :


$$-32 + 4I_1 + 12(I_1 - I_2) = 0$$

As $I_2 = -2\text{ A} \Rightarrow I_1 = 0,5\text{ A}$

Thévenin's voltage can be calculated across the resistor of $12\ \Omega$:

$$V_{Th} = 12 \cdot (I_1 - I_2) = 12 \cdot (0,5 + 2) = 30\text{ V}$$

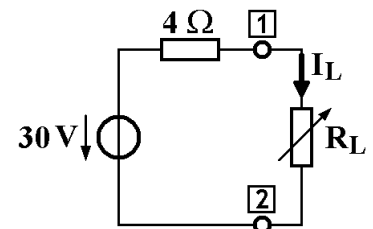
The figure opposite shows Thévenin's equivalent circuit, connected to the load resistors between the terminals $\boxed{1} - \boxed{2}$. Charge current I_L is given by :



$$I_L = \frac{V_{Th}}{R_{Th} + R_L} = \frac{30}{4 + R_L} \Rightarrow \begin{cases} R_L = 6\ \Omega & \Rightarrow I_L = 3\text{ A} \\ R_L = 16\ \Omega & \Rightarrow I_L = 1,5\text{ A} \\ R_L = 36\ \Omega & \Rightarrow I_L = 0,75\text{ A} \end{cases}$$

EXERCISE II.2 : NORTON'S THEOREM

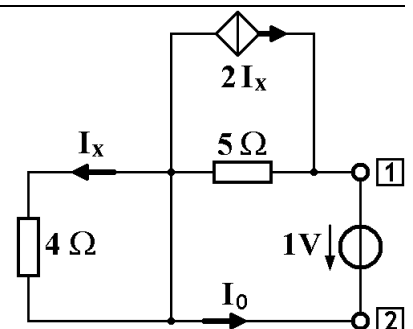- A. The Norton resistance is found by replacing the independent voltage source with a short circuit and connecting a 1 V voltage source between the terminals. $\boxed{1} - \boxed{2}$ of the circuit, which gives the diagram of the figure opposite.




In this diagram :

- The resistor of $4\ \Omega$ is short circuited ; we can ignore it and $I_x = 0$.
- The dependent current source, the voltage source and the resistor of $5\ \Omega$ are in parallel.

$$\Rightarrow I_0 = \frac{1\text{V}}{5\ \Omega} = 0,2\text{ A} \quad \Rightarrow \quad R_N = \frac{U_0}{I_0} \quad \Rightarrow \quad \boxed{R_N = 5\ \Omega}$$

B. Norton's current I_N is found by shorting the terminals **1** – **2** of the circuit, and calculating the current I_{sc} which is established in this short circuit.
In this diagram :

$$I_x = \frac{10\text{ V}}{4\ \Omega} = 2,5\text{ A} \quad \Rightarrow \quad I_{sc} = \frac{10\text{ V}}{5\ \Omega} + 2 \cdot I_x \quad \Rightarrow \quad \boxed{I_N = 7\text{ A}}$$

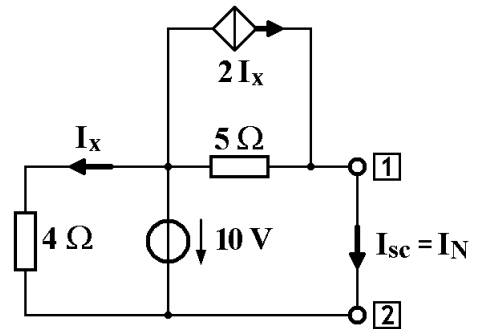


EXERCISE II.3 : POWER TRANSFER


We must find the resistance of Thévenin R_{Th} and the voltage of Thévenin V_{Th} .

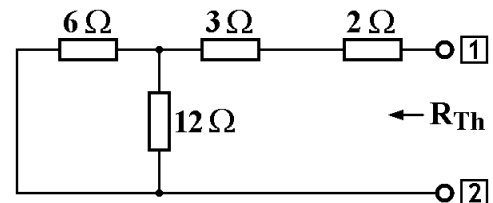A. We find the resistance of Thévenin R_{Th} by replacing the voltage source with a short circuit and the current source with an open circuit, as shown in the figure on the right. The resistors of $6\ \Omega$ and $12\ \Omega$ are in parallel with each other and in series with the resistors of $3\ \Omega$ and $2\ \Omega$:

$$R_{Th} = \frac{6 \times 12}{6 + 12} + 2 + 3 \quad \Rightarrow \quad \boxed{R_{Th} = 9\ \Omega}$$



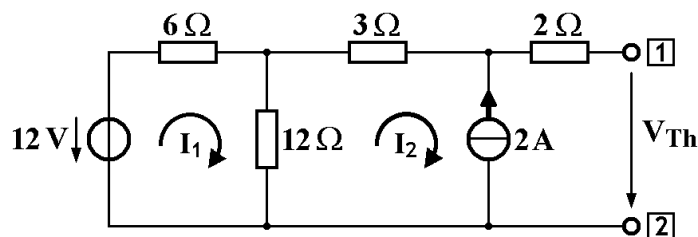We get the voltage of Thévenin V_{Th} by applying Kirchhoff's law of currents in the meshes of the figure below.



In the current mesh I_1 :

$$-12 + 18I_1 - 12I_2 = 0 \quad \text{avec} \quad I_2 = -2\text{ A} \quad \Rightarrow \quad I_1 = -2/3\text{ A}$$

In the large mesh formed by the whole circuit :

$$-12 + 6I_1 + 3I_2 + V_{Th} = 0 \quad \text{avec} \quad I_2 = -2\text{ A} \quad \Rightarrow \quad V_{Th} = 22\text{ V}$$

B. Maximum power transfer P_{max} is reached with $R_L = R_{Th}$ and the voltage V_{Th} between the terminals **1** and **2** :

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} \quad \Rightarrow \quad \boxed{P_{max} = 13,44\text{ W}}$$

EXERCISE II.4 : SUPERPOSITION THEOREM

We have three sources that each contribute to feed current I . Let's call :

- I_1 the component of the current due to the voltage source of 12 V
- I_2 the component of the current due to the voltage source of 24 V
- I_3 the component of the current due to the voltage source of 3 A.


1. Compute I_1 keeping only the 12 V source, as shown in the figure opposite.

In this diagram the resistor of $8\ \Omega$ is simply in series with the one of $4\ \Omega$ (to the right). These two resistors can therefore be replaced by a total resistance of $12\ \Omega$, which is then in parallel with the resistor of $4\ \Omega$ (to the left). The equivalent resistance is given by :

$$R_{\text{eq}} = \frac{12 \times 4}{12 + 4} = 3\ \Omega \quad (1)$$

The diagram above can be simplified as shown in the figure opposite.
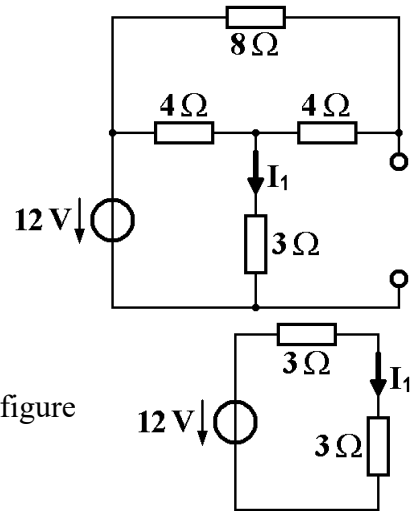
$$I_1 = \frac{12\ \text{V}}{6\ \Omega} = 2\ \text{A} \quad (2)$$



2. Compute I_2 retaining only the 24 V source, as shown in the figure. The analysis of the upper mesh gives :


$$16 I_a - 4 I_b + 24 = 0 \quad (3)$$

And in the mesh of the current I_b :

$$7 I_b - 4 I_a = 0 \quad (4)$$

By substituting (4) in (3) :

$$I_2 = I_b = -1 \quad (5)$$

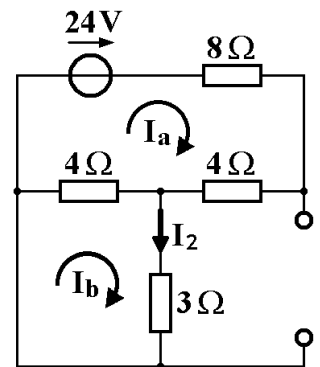

3. Compute keeping only the source of 3 A, as shown in the figure opposite. The sum of currents at the node V_2 gives :


$$3 = \frac{V_2}{8} + \frac{V_2 - V_1}{4} \Rightarrow 24 = 3 V_2 - 2 V_1 \quad (6)$$

And at node V_1 :

$$\frac{V_2 - V_1}{4} = \frac{V_1}{4} + \frac{V_1}{3} \Rightarrow V_2 = \frac{10}{3} V_1 \quad (7)$$

By substituting (7) in (6) we obtain $V_1 = 3\ \text{V}$:
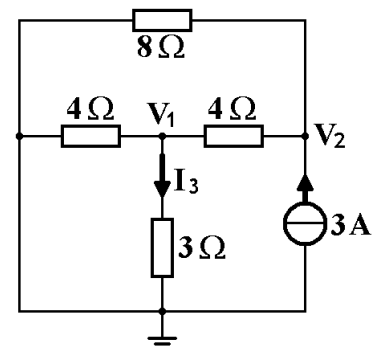
$$\Rightarrow I_3 = \frac{V_1}{3\ \Omega} = 1\ \text{A} \quad (8)$$



Finally, $I = I_1 + I_2 + I_3 \Rightarrow \boxed{I = 2\ \text{A}}$