

SOLUTION SET III

EXERCISE III.1 : NODES VOLTAGES


A. First method: superposition theorem.

a) **EFFECT OF THE 1ST SOURCE**

Voltage divider :

$$I_1 = \frac{2}{2+6+7} \cdot 1 \text{ A} = \frac{2}{15} \text{ A}$$
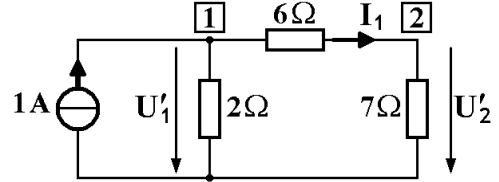
$$\Rightarrow U'_1 = (6+7) \cdot I_1 = \frac{26}{15} \text{ V} \quad \text{et} \quad U'_2 = 7 \cdot I_1 = \frac{14}{15} \text{ V}$$




b) **EFFECT OF THE 2ND SOURCE**

Voltage divider :

$$I_2 = \frac{7}{15} \cdot (-4 \text{ A}) = -\frac{28}{15} \text{ A}$$
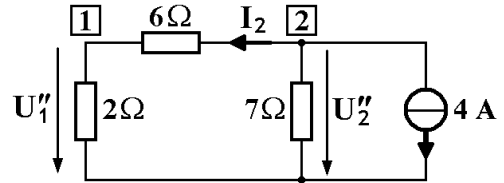
$$\Rightarrow U''_1 = 2 \cdot I_2 = -\frac{56}{15} \text{ V} \quad \text{et} \quad U''_2 = (6+2) \cdot I_2 = -\frac{224}{15} \text{ V}$$



c) **TOTAL VOLTAGES**

$$U_1 = U'_1 + U''_1 = \frac{26}{15} - \frac{56}{15} = -2 \text{ V} \quad \text{et} \quad U_2 = U'_2 + U''_2 = \frac{14}{15} - \frac{224}{15} = -14 \text{ V}$$

B. Second method: nodal analysis.

$$\begin{bmatrix} \frac{1}{2} + \frac{1}{6} & -\frac{1}{6} \\ -\frac{1}{6} & \frac{1}{6} + \frac{1}{7} \end{bmatrix} \cdot \begin{bmatrix} U_1 \\ U_2 \end{bmatrix} = \begin{bmatrix} 1 \\ -4 \end{bmatrix} \Leftrightarrow \begin{bmatrix} \frac{2}{3} & -\frac{1}{6} \\ -\frac{1}{6} & \frac{13}{42} \end{bmatrix} \cdot \begin{bmatrix} U_1 \\ U_2 \end{bmatrix} = \begin{bmatrix} 1 \\ -4 \end{bmatrix} \Leftrightarrow \begin{bmatrix} 28 & -7 \\ -7 & 13 \end{bmatrix} \cdot \begin{bmatrix} U_1 \\ U_2 \end{bmatrix} = \begin{bmatrix} 42 \\ -168 \end{bmatrix}$$

Cramer's method : $\Delta = 315$

$$U_1 = \frac{\begin{vmatrix} 42 & -7 \\ -168 & 13 \end{vmatrix}}{\Delta} = -2 \text{ V} \quad U_2 = \frac{\begin{vmatrix} 28 & 42 \\ -7 & -168 \end{vmatrix}}{\Delta} = -14 \text{ V}$$

EXERCISE III.2 : NODES VOLTAGES

At node **1** : $10 = I_1 + I_2 = \frac{U_1 - U_2}{3} + \frac{U_1 - U_3}{2}$

$$\Leftrightarrow 60 = 2 \cdot (U_1 - U_2) + 3 \cdot (U_1 - U_3)$$

$$\Leftrightarrow \boxed{5 U_1 - 2 U_2 - 3 U_3 = 60} \quad (1)$$

At node **2** : $I_1 = -3 I_x$

$$\Leftrightarrow \frac{U_1 - U_2}{3} = -3 \cdot \frac{U_2}{4}$$

$$\Leftrightarrow 4 U_1 - 4 U_2 = -9 U_2$$


$$\Leftrightarrow \boxed{4 U_1 + 5 U_2 = 0} \quad (2)$$

At node **3** : $I_2 = 4 I_x + I_3$

$$\Leftrightarrow \frac{U_1 - U_3}{2} = 4 \cdot \frac{U_2}{4} + \frac{U_3}{6}$$

$$\Leftrightarrow 3 U_1 - 3 U_3 = 6 U_2 + U_3$$
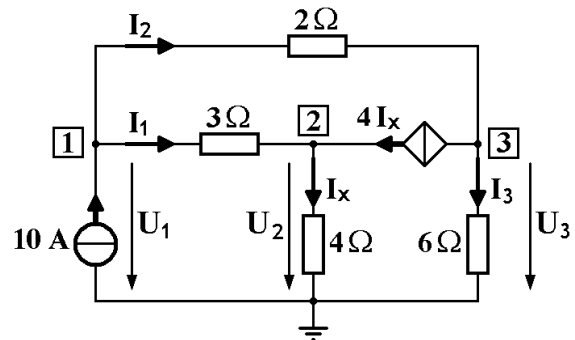
$$\Leftrightarrow \boxed{3 U_1 - 6 U_2 - 4 U_3 = 0} \quad (3)$$



Solving the system of equations (1), (2) et (3), we find :

$$\boxed{U_1 = 80 \text{ V}}$$

$$\boxed{U_2 = -64 \text{ V}}$$

$$\boxed{U_3 = 156 \text{ V}}$$

EXERCISE III.3 : MESH CURRENTS

$$\begin{bmatrix} 2+12+4 & -12 \\ -12 & 9+3+12 \end{bmatrix} \cdot \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ -V_2 \end{bmatrix} \Leftrightarrow \begin{bmatrix} 18 & -12 \\ -12 & 24 \end{bmatrix} \cdot \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 12 \\ -8 \end{bmatrix}$$

$$\Delta = 288$$

$$I_1 = \frac{\begin{vmatrix} 12 & -12 \\ -8 & 24 \end{vmatrix}}{\Delta} = 0,67 \text{ A} \quad I_2 = \frac{\begin{vmatrix} 18 & 12 \\ -12 & 8 \end{vmatrix}}{\Delta} = 0 \text{ A}$$

EXERCISE III.4 : NODES VOLTAGESAt node **1**:

$$3 = I_1 + I_x \Rightarrow 3 = \frac{U_1 - U_3}{4} + \frac{U_1 - U_2}{2}$$

$$\Rightarrow 3U_1 - 2U_2 - U_3 = 12 \quad (1)$$

At node **2**:


$$I_x = I_2 + I_3 \Rightarrow \frac{U_1 - U_2}{2} = \frac{U_2 - U_3}{8} + \frac{U_2}{4}$$

$$\Rightarrow -4U_1 + 7U_2 - U_3 = 0 \quad (2)$$

At node **3**:

$$I_1 + I_2 = 2I_x \Rightarrow \frac{U_1 - U_3}{4} + \frac{U_2 - U_3}{8} = \frac{2(U_1 - U_2)}{2}$$
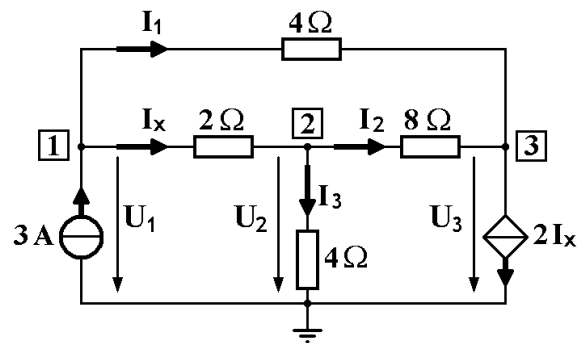
$$\Rightarrow 2U_1 - 3U_2 + U_3 = 0 \quad (3)$$



The system of equations (1), (2) and (3) can be solved by two methods.

A. Algebraic method.

$$\begin{cases} 3U_1 - 2U_2 - U_3 = 12 \\ -4U_1 + 7U_2 - U_3 = 0 \\ 2U_1 - 3U_2 + U_3 = 0 \end{cases} \Rightarrow \boxed{U_1 = 4,8 \text{ V}} \quad \boxed{U_2 = 2,4 \text{ V}} \quad \boxed{U_3 = -2,4 \text{ V}}$$

B. Cramer's method.

$$\begin{bmatrix} 3 & -2 & -1 \\ -4 & 7 & -1 \\ 2 & -3 & 1 \end{bmatrix} \cdot \begin{bmatrix} U_1 \\ U_2 \\ U_3 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \\ 0 \end{bmatrix} \quad U_1 = \frac{\Delta_1}{\Delta} \quad U_2 = \frac{\Delta_2}{\Delta} \quad U_3 = \frac{\Delta_3}{\Delta}$$

$$\Delta = \begin{vmatrix} 3 & -2 & -1 \\ -4 & 7 & -1 \\ 2 & -3 & 1 \end{vmatrix} = 10$$

$$\Delta_1 = \begin{vmatrix} 12 & -2 & -1 \\ 0 & 7 & -1 \\ 0 & -3 & 1 \end{vmatrix} = 48 \quad \Delta_2 = \begin{vmatrix} 3 & 12 & -1 \\ -4 & 0 & -1 \\ 2 & 0 & 1 \end{vmatrix} = 24 \quad \Delta_3 = \begin{vmatrix} 3 & -2 & 12 \\ -4 & 7 & 0 \\ 2 & -3 & 0 \end{vmatrix} = -24$$

$$\Rightarrow \boxed{U_1 = 4,8 \text{ V}} \quad \boxed{U_2 = 2,4 \text{ V}} \quad \boxed{U_3 = -2,4 \text{ V}}$$

EXERCISE III.5 : MESH ANALYSIS

Kirchhoff's law is applied to each mesh for the voltages.

In mesh I_1 :

$$-24 + 10(I_1 - I_2) + 12(I_1 - I_3) = 0 \quad \Rightarrow \quad 11 I_1 - 5 I_2 - 6 I_3 = 12 \quad (1)$$

In mesh I_2 :

$$-24 I_2 + 4(I_2 - I_3) + 10(I_2 - I_1) = 0 \quad \Rightarrow \quad -5 I_1 + 19 I_2 - 2 I_3 = 0 \quad (2)$$

In mesh I_3 :

$$4 I_0 + 12(I_3 - I_1) + 4(I_3 - I_2) = 0$$

But at node **A**, we have :

$$I_0 = I_1 - I_2$$

$$\Rightarrow 4(I_1 - I_2) + 12(I_3 - I_1) + 4(I_3 - I_2) = 0 \quad \Rightarrow \quad -I_1 - I_2 + 2 I_3 = 0 \quad (3)$$

The system of equations (1), (2) and (3) is written :

$$\begin{bmatrix} 11 & -5 & -6 \\ -5 & 19 & -2 \\ -1 & -1 & 2 \end{bmatrix} \cdot \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \\ 0 \end{bmatrix} \quad I_1 = \frac{\Delta_1}{\Delta} \quad I_2 = \frac{\Delta_2}{\Delta} \quad I_3 = \frac{\Delta_3}{\Delta}$$

$$\Delta = \begin{vmatrix} 11 & -5 & -6 \\ -5 & 19 & -2 \\ -1 & -1 & 2 \end{vmatrix} = 192$$

$$\Delta_1 = \begin{vmatrix} 12 & -5 & -6 \\ 0 & 19 & -2 \\ 0 & -1 & 2 \end{vmatrix} = 432 \quad \Delta_2 = \begin{vmatrix} 11 & 12 & -6 \\ -5 & 0 & -2 \\ -1 & 0 & 2 \end{vmatrix} = 144 \quad \Delta_3 = \begin{vmatrix} 11 & -5 & 12 \\ -5 & 19 & 0 \\ -1 & -1 & 0 \end{vmatrix} = 288$$

$$\Rightarrow I_1 = 2,25 \text{ A} \quad I_2 = 0,75 \text{ A} \quad I_3 = 1,5 \text{ A} \quad \Rightarrow \quad \boxed{I_0 = 1,5 \text{ A}}$$