

SOLUTION SET VI

EXERCISE VI.1 : IMPEDANCES LOCUS

A.

First circuit We start from the admittance of the circuit portion having elements in parallel. In the expression of the admittance, only the imaginary part is a function of the frequency, hence simple to represent :

$$\underline{Y}_2 = \frac{1}{R_2} + j\omega C = \frac{1}{33} + j \cdot 12 \cdot 10^{-6} \cdot \omega$$
$$\underline{Z}_2 = \frac{R_2 \cdot \frac{1}{j\omega C}}{R_2 + \frac{1}{j\omega C}} = \frac{R_2}{1 + (\omega R_2 C)^2} - j \cdot \frac{\omega C \cdot R_2^2}{1 + (\omega R_2 C)^2}$$

The impedance $\underline{Z}_2 = \frac{1}{\underline{Y}_2}$ is determined by inversion (the inverse of a line is a circle). The semicircle representing the locus of $\underline{Z}_2$ for $\omega = 0 \div \infty$ is defined by its two ends ($\omega = 0 \Rightarrow \underline{Z}_2 = R_2 = 33 \Omega$; $\omega = \infty \Rightarrow \underline{Z}_2 = 0 \Omega$) and its radius $\frac{R_2}{2} = 16,5 \Omega$.

The impedance of the rest of the circuit is : $\underline{Z}_1 = R_1 + j\omega L = 10 + j \cdot 6,5 \cdot 10^{-3} \cdot \omega$

The impedance of the whole circuit is the sum : $\underline{Z} = \underline{Z}_1 + \underline{Z}_2$:

$$\underline{Z} = R_1 + \frac{R_2}{1 + (\omega R_2 C)^2} + j\omega \left(L - \frac{C \cdot R_2^2}{1 + (\omega R_2 C)^2} \right)$$

The function $\underline{Z}$ crosses the real axis in 2 points (when $\text{Im}\{\underline{Z}\} = 0$) :

a. $\omega = 0$: $\underline{Z}_{(\omega=0)} = R_1 + R_2 = 10 + 33 = 43 \Omega$

b. $L - \frac{C \cdot R_2^2}{1 + (\omega R_2 C)^2} = 0 \Rightarrow \omega = \sqrt{\frac{C \cdot R_2^2 - L}{L \cdot (C \cdot R_2)^2}} = \sqrt{\frac{12 \cdot 10^{-6} \cdot 33^2 - 6,5 \cdot 10^{-3}}{6,5 \cdot 10^{-3} \cdot (12 \cdot 10^{-6} \cdot 33)^2}} = 2,53 \cdot 10^3$

$$\underline{Z}_{(\omega=2,53 \cdot 10^3)} = R_1 + \frac{R_2}{1 + (\omega R_2 C)^2} = 10 + \frac{33}{1 + (2,53 \cdot 10^3 \cdot 12 \cdot 10^{-6} \cdot 33)^2} = 26,5 \Omega$$

$$\omega = 2\pi f = 2,53 \cdot 10^3 \Rightarrow f = \frac{2,53 \cdot 10^3}{2\pi} = 400 \text{ Hz}$$


Second circuit Proceeding in the same way as for the first circuit, we find :

$$\underline{Y}_2 = \frac{1}{R_2} + \frac{1}{j\omega L} = \frac{1}{33} - j \cdot \frac{1}{6,5 \cdot 10^{-3} \omega}$$


$$\underline{Z}_2 = \frac{1}{\underline{Y}_2} = \frac{R_2 \cdot (\omega L)^2}{R_2 + (\omega L)^2} + j \frac{R_2^2 \cdot \omega L}{R_2 + (\omega L)^2} = \begin{cases} 0 & \omega = 0 \\ R_2 = 33 \Omega & \omega = \infty \end{cases}$$

$$\underline{Z}_1 = R_1 - j \frac{1}{\omega C} = \begin{cases} \infty & \omega = 0 \\ R_1 = 10 \Omega & \omega = \infty \end{cases}$$
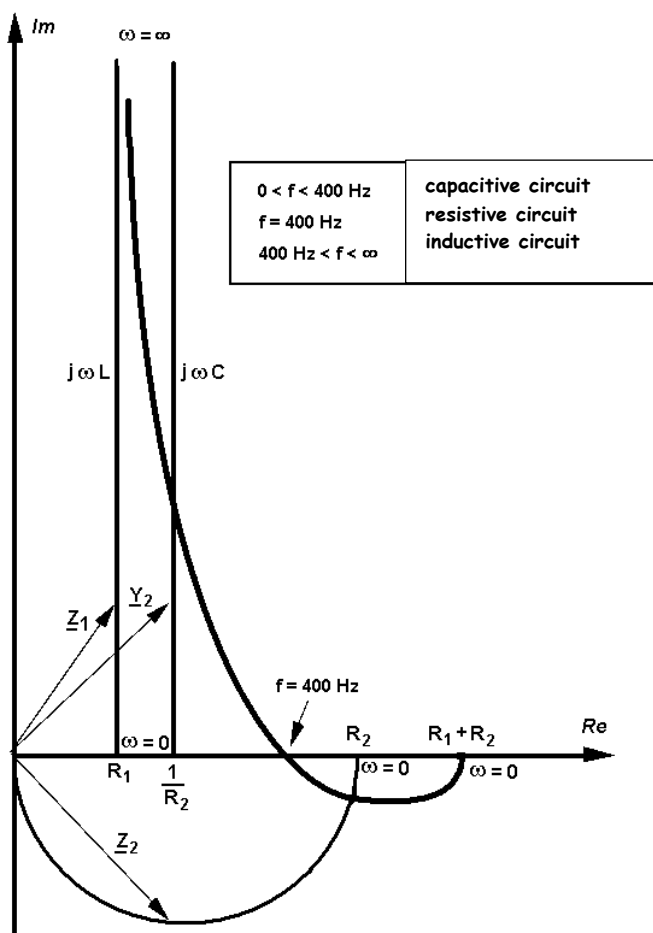
$$\underline{Z} = \underline{Z}_1 + \underline{Z}_2 = R_1 + \frac{R_2 \cdot (\omega L)^2}{R_2 + (\omega L)^2} - j \left(\frac{1}{\omega C} - \frac{R_2^2 \cdot \omega L}{R_2 + (\omega L)^2} \right) = \begin{cases} \infty & \omega = 0 \\ R_1 + R_2 = 43 \Omega & \omega = \infty \end{cases}$$



First circuit

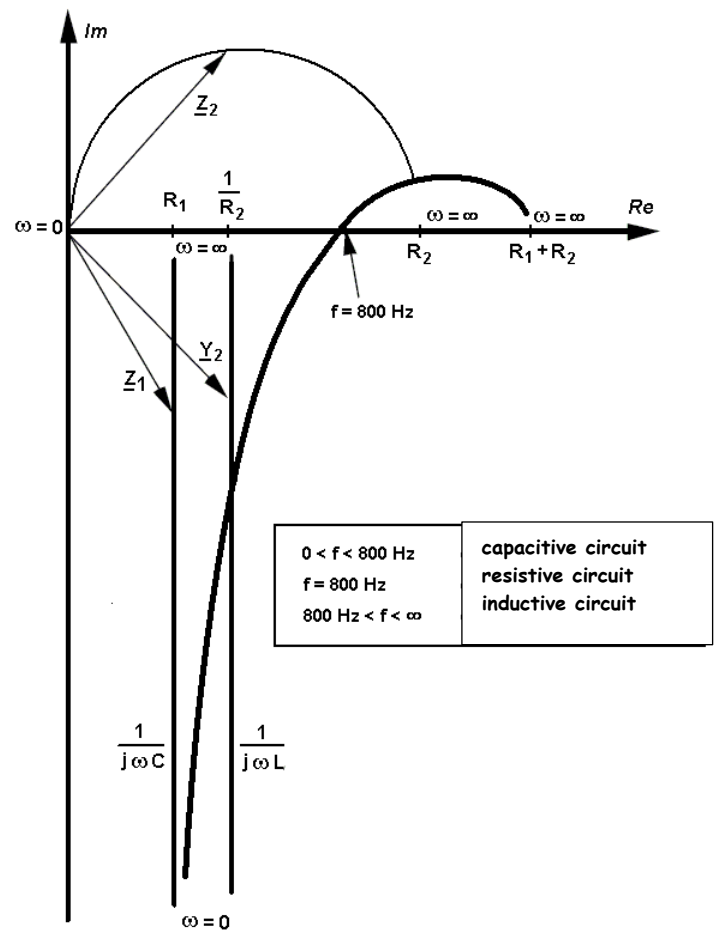

Second circuit

For $\omega \rightarrow 0$, the curve of $\underline{Z}(\omega)$ tends asymptotically to the right $\text{Re}\{\underline{Z}_1\} = R_1$.

B. See boxes in the graphs above.

EXERCISE VI.2 : POWER CALCULATION

A. $\underline{Z} = R + j\omega L = R + j(2\pi f)L = R + jX_L$

B. $R = \frac{U_R}{I} = \frac{60 \text{ V}}{2 \text{ A}} = \underline{30 \Omega}$

$$X_L = \frac{U_L}{I} = \frac{80 \text{ V}}{2 \text{ A}} = \underline{40 \Omega}$$

$$\underline{Z} = R + jX_L = 30 + j \cdot 40 = 50 \cdot e^{j53^\circ} \Omega$$

C. $L = \frac{X_L}{2\pi f} = \frac{40}{100\pi} = \underline{127,3 \text{ mH}}$


D. Rms value : $U = Z \cdot I = 50 \cdot 2 = \underline{100 \text{ V}}$

or : $U = \sqrt{U_R^2 + U_L^2} = \sqrt{60^2 + 80^2} = \underline{100 \text{ V}}$

In complex : $\underline{U} = \underline{Z} \cdot \underline{I} = 50 \cdot e^{j53^\circ} \cdot 2 \cdot e^{j0^\circ} = \underline{100 \cdot e^{j53^\circ} \text{ V}} = (60 + j80) \text{ V}$

or : $\underline{U} = U_R + jU_L = (60 + j80) \text{ V} = \underline{100 \cdot e^{j53^\circ} \text{ V}}$

E. Diagram of current and voltages

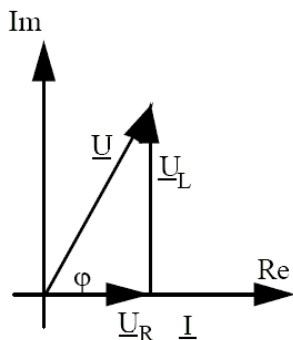

With $\underline{I}$ referred to 0°

Argument of $\underline{U}$: $\alpha = 53^\circ$

Argument of $\underline{U}_R$: $\beta = 0^\circ$

Phase difference of $\underline{I}$ and $\underline{U}$: $\varphi = \alpha - \beta = 53^\circ$

F. Active power

$$P = R \cdot I^2 = 30 \cdot 2^2 = \underline{120 \text{ W}}$$

or : $P = \frac{U_R^2}{R} = \frac{60^2}{30} = \underline{120 \text{ W}}$

or : $P = U_R \cdot I = 60 \cdot 2 = \underline{120 \text{ W}}$

or : $P = U \cdot I \cdot \cos \varphi = 100 \cdot 2 \cdot 0,6 = \underline{120 \text{ W}}$

Reactive power

$$Q = X_L \cdot I^2 = 40 \cdot 2^2 = \underline{160 \text{ VAr}}$$

or : $Q = \frac{U_L^2}{X_L} = \frac{80^2}{40} = \underline{160 \text{ VAr}}$

or : $Q = U_L \cdot I = 80 \cdot 2 = \underline{160 \text{ VAr}}$

or : $Q = U \cdot I \cdot \sin \varphi = 100 \cdot 2 \cdot 0,8 = \underline{160 \text{ VAr}}$

G. The compensation of the reactive powers is expressed by:

$$X_L I^2 = \frac{U^2}{X_C} = \omega C \cdot U^2 \Rightarrow C = \frac{X_L I^2}{\omega U^2} = \frac{160}{100\pi \cdot 100^2} = \underline{50,9 \mu\text{F}}$$