

SOLUTION SET VII

EXERCISE VII.1 : INCREASE OF $\cos\phi$ OF A RL LOAD

$$\text{A. } P = U \cdot I \cdot \cos\phi \quad \Rightarrow \quad I = \frac{P}{U \cdot \cos\phi} = \frac{45,5 \cdot 10^3}{380 \cdot 0,6} = \underline{199,56 \text{ A}}$$

$$\phi = \arccos(0,6) = 53,13^\circ$$

$$\underline{I} = \underline{199,56 \cdot e^{-j53,13^\circ} \text{ A}}$$

$$\underline{Z} = Z \cdot \cos\phi + j Z \cdot \sin\phi = R + j\omega L \quad \Rightarrow \quad R = Z \cdot \cos\phi \quad ; \quad \omega L = Z \cdot \sin\phi$$

$$Z = \frac{U}{I} = \frac{380}{199,56} = 1,9 \Omega$$

$$R = 1,9 \cdot 0,6 = \underline{1,14 \Omega} \quad \text{and} \quad L = \frac{1,9 \cdot 0,8}{100 \cdot \pi} = \underline{4,84 \text{ mH}}$$

$$\text{B. } \underline{Z}_M = R + j\omega L \quad \Rightarrow \quad \underline{Y}_M = \frac{1}{R + j\omega L} = \frac{R - j\omega L}{R^2 + (\omega L)^2} \quad \text{and} \quad \underline{Y}_C = j\omega C$$

$$\underline{Y} = \underline{Y}_M + \underline{Y}_C = \frac{R - j\omega L}{R^2 + (\omega L)^2} + j\omega C = \frac{R}{R^2 + (\omega L)^2} - j\omega \left(\frac{L}{R^2 + (\omega L)^2} - C \right)$$

$$\phi' = \arccos(0,95) = \pm 18,19^\circ \quad (2 \text{ possible solutions})$$

$$\phi' = \arg(\underline{Z}) = -\arg(\underline{Y})$$

$$\tan \phi' = \frac{\frac{\omega L}{R^2 + (\omega L)^2} - \omega C}{\frac{R}{R^2 + (\omega L)^2}} = \frac{\omega L - \omega C [R^2 + (\omega L)^2]}{R}$$

$$C = \frac{\omega L - R \tan \phi'}{\omega [R^2 + (\omega L)^2]} = \begin{cases} \underline{1008 \mu\text{F}} & (\text{pour } \phi' = +18,19^\circ) \\ \underline{1667 \mu\text{F}} & (\text{pour } \phi' = -18,19^\circ) \end{cases}$$

$$\text{C. } \underline{Y} = (0,316 - j \cdot 0,104) \text{ S} = \underline{0,3327 \cdot e^{-j18,19^\circ} \text{ S}}$$

$$\underline{I}' = \underline{Y} \cdot \underline{U} = \underline{126,4 \cdot e^{-j18,19^\circ} \text{ A}}$$

$$\text{D. } P_{\text{pertes}} = R_L \cdot I^2 = \underline{1,99 \text{ kW}}$$

$$P'_{\text{pertes}} = R_L \cdot I'^2 = \underline{0,79 \text{ kW}}$$

E. Decrease of losses in lines

EXERCISE VII.2 : POWER IN ALTERNATIVE REGIME**If $\underline{Z}_1$ is capacitive :**

$$\underline{Z}_1 = R_1 - j \frac{1}{\omega C_1} \quad \text{where } C_1 \text{ is a capacitor supposed to be in series with } R_1$$

$$\Rightarrow R_1 = \frac{U}{I_1} \cos \phi = \underline{8 \, \Omega} \quad \text{and : } X_1 = \frac{U}{I_1} \sin \phi = \frac{1}{C_1 \omega} \Rightarrow C_1 = \frac{I_1}{U} \cdot \frac{1}{\omega \sin \phi} = \underline{530,5 \, \mu\text{F}}$$

When adding a capacitor C in series with $\underline{Z}_1$, C_1 is replaced by $C'_1 = \left(\frac{1}{C} + \frac{1}{C_1} \right)^{-1}$, X_1 becomes

X'_1 , ϕ becomes ϕ' and I_1 becomes I_2 :

$$R_1 = \frac{U}{I_2} \cos \phi' = 8 \, \Omega \quad \text{and : } X'_1 = \frac{U}{I_2} \sin \phi' = \frac{1}{C'_1 \omega}$$

$$\Rightarrow I_2 = \frac{U \cos \phi'}{R_1} = \underline{7,5 \, \text{A}} \quad \text{and : } R_1 \tan \phi' = \frac{1}{\omega} \cdot \left(\frac{1}{C} + \frac{1}{C_1} \right) \Rightarrow C = \frac{1}{\omega R_1 \tan \phi' - 1/C_1} = \underline{682,1 \, \mu\text{F}}$$

If $\underline{Z}_1$ is inductive :

$$\underline{Z}_1 = R_1 + j \omega L_1 \quad \text{where } L_1 \text{ is an inductor supposed to be in series with } R_1$$

$$\Rightarrow R_1 = \frac{U}{I} \cos \phi = \underline{8 \, \Omega} \quad \text{and : } X_1 = \frac{U}{I} \sin \phi = L_1 \omega \Rightarrow L_1 = \frac{U}{I} \cdot \frac{\sin \phi}{\omega} = \underline{19,1 \, \text{mH}}$$

When adding a capacitor, the impedance becomes $\underline{Z}_2$:

$$\underline{Z}_2 = R_1 + j \left(L_1 \omega - \frac{1}{\omega C} \right)$$

$$\Rightarrow R_1 = \frac{U}{I_2} \cos \phi' = 8 \, \Omega \quad \text{and : } X'_1 = \frac{U}{I_2} \sin \phi' = L_1 \omega - \frac{1}{C \omega}$$

$$\Rightarrow I_2 = \frac{U \cos \phi'}{R_1} = \underline{7,5 \, \text{A}} \quad \text{and : } R_1 \tan \phi' = L_1 \omega - \frac{1}{C \omega}$$

Note that if we add a small capacitance, the phase shift decreases, so $\cos \phi$ increases, which does not correspond to the problem given. To obtain a reduction of $\cos \phi$, it is necessary to add a capacitor large enough so that the total impedance becomes capacitive. In these conditions, ϕ' is negative :

$$\tan \phi' = - \tan[\arccos(\cos \phi')]$$

$$\Rightarrow -R_1 \tan(\arccos(\cos \phi')) = L_1 \omega - \frac{1}{C \omega} \Rightarrow C = \frac{1}{\omega \cdot [L_1 \omega + R_1 \tan(\arccos(\cos \phi'))]} = \underline{191 \, \mu\text{F}}$$

EXERCISE VII.3 : ACTIVE AND REACTIVE POWER

A. The phase shift $\varphi = -\frac{\pi}{3} - \left(-\frac{\pi}{18}\right) = -\frac{5\pi}{18} = -50^\circ < 0$: current ahead of the voltage

$\Rightarrow$ the load is capacitive.

B. We have rms values: $U = \hat{U}/\sqrt{2}$; $I = \hat{I}/\sqrt{2}$.

Apparent power : $S = U \cdot I = \frac{1}{2} \hat{U} \cdot \hat{I} = \underline{120 \text{ VA}}$

Active power : $P = U \cdot I \cos \varphi = \underline{77,1 \text{ W}}$

Reactive power : $Q = U \cdot I \sin \varphi = \underline{91,9 \text{ var}}$

C. The resistance $R = \frac{P}{I^2} = \frac{2P}{\hat{I}^2} = \underline{1,1 \Omega}$ and the reactance $X = \frac{Q}{I^2} = \frac{2Q}{\hat{I}^2} = \underline{-1,28 \Omega}$