

LNA design summary

15.11.23

ZIN & V gain calculation

Under input match condition:

Setting the voltage gain to e.g. -9 (19dB)


Imposes $g_{m2} \cdot R_S = 0.1 \rightarrow g_{m2} = 1/500\Omega = 2\text{mS}$

IB current could be sized vs IC

$I_B = 50\mu\text{A}$ in WI ($g_{m2} = I_B / U_T$)

$A_V = -g_{m1} \cdot R_L = -9$

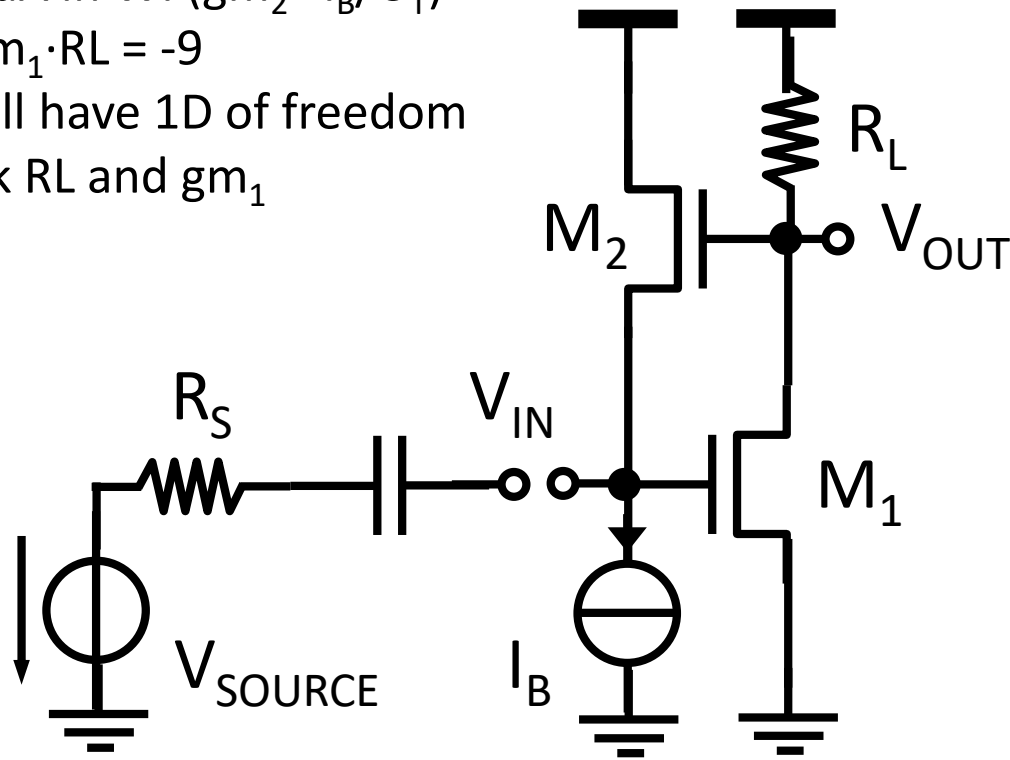We still have 1D of freedom to pick R_L and g_{m1}



KIRCHHOFF equations

$$\begin{pmatrix} I_{IN} \\ 0 \end{pmatrix} = \begin{pmatrix} g_{ms2} & -g_{m2} \\ g_{m1} & 1/R_L \end{pmatrix} \cdot \begin{pmatrix} V_{IN} \\ V_{OUT} \end{pmatrix}$$

$$A_V = \frac{V_{OUT}}{V_{IN}} = -g_{m1} \cdot R_L$$

$$Z_{IN} = \frac{V_{IN}}{I_{IN}} = \frac{1}{g_{ms2} + g_{m2} \cdot g_{m1} \cdot R_L}$$

If $g_{ms2} = g_{m2}$

$$\frac{1}{g_{m2} \cdot (1 + g_{m1} \cdot R_L)} = R_S$$

Rewriting the input match condition

$$\frac{1}{(1 + g_{m1} \cdot R_L)} = g_{m2} \cdot R_S < 1$$

$$\frac{1}{(1 - A_V)} = g_{m2} \cdot R_S$$

If $A_V = -9$
 $g_{m2} \cdot R_S = 0.1$

$$\frac{V_{OUT}}{V_{SOURCE}} = \frac{V_{OUT}}{V_{IN}} \cdot \frac{V_{SOURCE} \cdot Z_{IN}}{2 \cdot R_S} = \frac{V_{OUT}}{V_{IN}} \cdot \frac{V_{SOURCE}}{2 \cdot R_S} = \frac{-g_{m1} \cdot R_L \cdot R_S}{2 \cdot R_S} = \frac{-g_{m1} \cdot R_L}{2} = \frac{A_V}{2}$$

Zout calculation with and without Rs

Without RS (conceptual, not real case) we get:
The injected output current is split between $1/R_L$ and g_{m1} via the voltage follower formed by M2

$$\begin{pmatrix} 0 \\ I_{OUT} \end{pmatrix} = \begin{pmatrix} g_{ms2} & -g_{m2} \\ g_{m1} & 1/R_L \end{pmatrix} \cdot \begin{pmatrix} V_{IN} \\ V_{OUT} \end{pmatrix} \quad Z_O = \frac{V_{OUT}}{I_{OUT}} = \frac{1}{g_{m1} + 1/R_L}$$

If $g_{ms2}=g_{m2}$


With R_S , the reverse voltage gain is

$$\frac{V_{IN}}{V_{OUT}} = \frac{g_{m2}}{1/R_S + g_{ms2}} = \frac{g_{m2} \cdot R_S}{1 + g_{m2} \cdot R_S}$$

If $g_{ms2}=g_{m2}$

$$= \frac{\frac{1}{(1 - A_V)}}{1 + \frac{1}{(1 - A_V)}} = \frac{1}{2 - A_V}$$

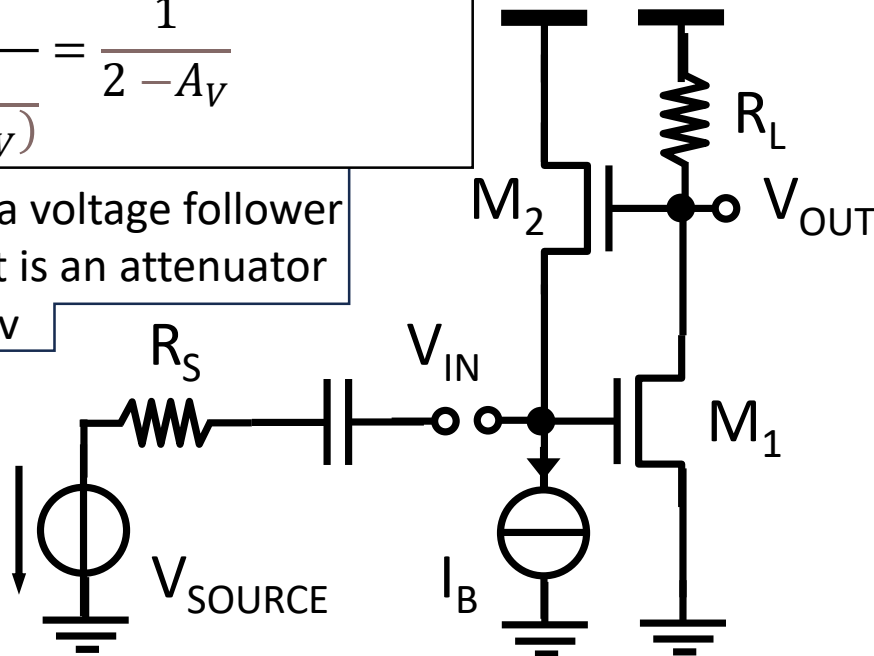If $R_S \gg$, M2 is a voltage follower
With $R_S=50\Omega$ it is an attenuator
by a factor $2-A_V$



With R_S

$$\begin{pmatrix} 0 \\ I_{OUT} \end{pmatrix} = \begin{pmatrix} 1/R_S + g_{ms2} & -g_{m2} \\ g_{m1} & 1/R_L \end{pmatrix} \cdot \begin{pmatrix} V_{IN} \\ V_{OUT} \end{pmatrix}$$

$$Y_{OUT} = \frac{I_{OUT}}{V_{OUT}} = g_{m1} \cdot \frac{g_{m2}}{1/R_S + g_{ms2}} + 1/R_L$$

If $g_{ms2}=g_{m2}$

$$Z_{OUT} = \frac{1}{\frac{R_S \cdot g_{m2} \cdot g_{m1}}{1 + R_S \cdot g_{m2}} + 1/R_L}$$


Now using $Z_{in}=R_S$, we may remove g_{m1} or g_{m2}

$$g_{m1} = \frac{1}{R_S \cdot R_L} \cdot \frac{1}{g_{m2}} - 1/R_L \quad \frac{1}{R_S \cdot (1 + g_{m1} \cdot R_L)} = g_{m2}$$

If $A_V=-9$, $g_{m2} \cdot R_S = 0.1$, $Z_O \sim R_L/2$ $(2-A_V)/(1-A_V)=11/10=1.1$

$$Z_{OUT} = \frac{R_L \cdot (1 + R_S \cdot g_{m2})}{2} \quad Z_{OUT} = \frac{R_L}{2} \cdot \frac{2 + g_{m1} \cdot R_L}{1 + g_{m1} \cdot R_L}$$

Equivalent noise calculation

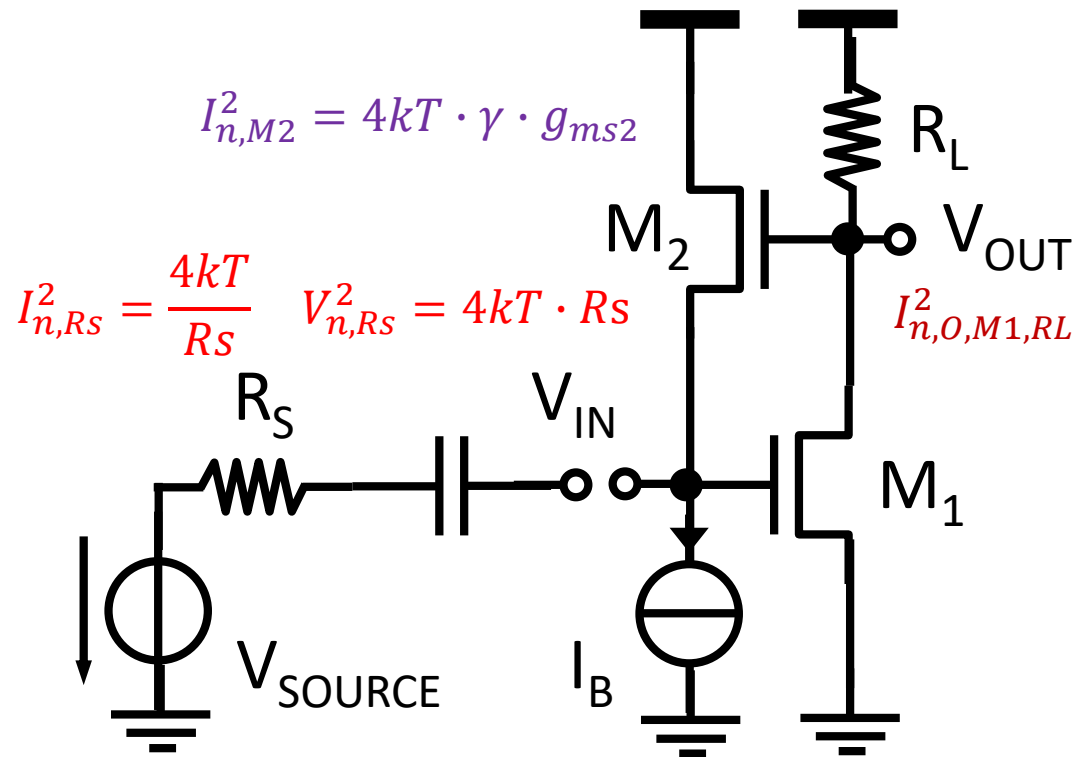

We neglect $1/f$ noise from MOS, superposition applies
 Use $V_n^2 = Z^2 \cdot I_n^2$ with Z_{OUT} and $Z_{IN}/2$ computed previously
 Noise from IB current source to be added to that of M2!

$$V_{n,O,M1,RL}^2 = kT \cdot \left(\frac{1}{R_L} + \gamma \cdot g_{ms1} \right) \cdot \underbrace{R_L^2 \cdot (1 + R_S \cdot g_{m2})^2}_{/4 = Z_{OUT}^2}$$

$$V_n^2 = Z_{OUT}^2 \cdot I_n^2$$

$$V_{n,in,M2}^2 = kT \cdot \gamma \cdot g_{ms2} \cdot R_S^2 \quad \underbrace{\quad}_{A_V^2}$$

$$V_{n,O,M2}^2 = kT \cdot \gamma \cdot g_{ms2} \cdot R_S^2 \cdot \underbrace{g_{m1}^2 \cdot R_L^2}_{A_V^2}$$

$$V_n^2 = 1/4 \cdot Z_{IN}^2 \cdot I_n^2 \quad V_{n,O}^2 = V_{n,IN}^2 \cdot A_V^2$$

Indeed we see R_S and Z_{IN} in parallel hence $R_S/2$

Multiply then by A_V^2 to get output noise @ V_{OUT}

Equivalent noise calculation

$$F = \frac{V_{n,O,RS}^2 + V_{n,O,M2}^2 + V_{n,O,M1,RL}^2}{V_{n,O,RS}^2}$$
$$= 1 + \frac{kT \cdot \gamma \cdot g_{ms2} \cdot R_S^2 \cdot g_{m1}^2 \cdot R_L^2 + kT \cdot \left(\frac{1}{R_L} + \gamma \cdot g_{ms1} \right) \cdot R_L^2 \cdot (1 + R_S \cdot g_{m2})^2}{kT \cdot R_S \cdot g_{m1}^2 \cdot R_L^2}$$

$$F = 1 + \gamma \cdot g_{ms2} \cdot R_S + \left(\frac{1}{R_L} + \gamma \cdot g_{ms1} \right) \cdot \frac{(1 + R_S \cdot g_{m2})^2}{R_S \cdot g_{m1}^2}$$

$$A_V = -g_{m1} \cdot R_L = 1 - \frac{1}{g_{m2} \cdot R_S} < 0$$

Final form after simplifications $\frac{1}{(1 - A_V)} = g_{m2} \cdot R_S$

$$\frac{P_{OUT}}{P_{SOURCE}} = \frac{V_{OUT}^2}{2 \cdot Z_{OUT}} \cdot \underbrace{\frac{2 \cdot R_S}{V_{SOURCE}^2}}_{4 \cdot V_{IN}^2} = \frac{A_V^2 \cdot R_S}{4} \cdot \frac{2}{R_L} \cdot \frac{1 - A_V}{2 - A_V} \approx \frac{g_{m2}^2 \cdot R_L \cdot R_S}{2}$$

$$F = 1 + \gamma \cdot g_{ms2} \cdot R_S + (1 + \gamma \cdot g_{ms1} \cdot R_L) \cdot \frac{(1 + R_S \cdot g_{m2})^2}{R_L \cdot R_S \cdot g_{m1}^2}$$

M2 contrib

RL and M1 contrib

$$F = 1 + \gamma \cdot \underbrace{\frac{1}{(1 - A_V)}}_{\gg 1} + \underbrace{(1 - \gamma \cdot A_V)}_{\gg 1} \cdot \frac{R_L}{R_S} \cdot \frac{1}{A_V^2} \cdot \underbrace{\left(\frac{2 - A_V}{1 - A_V}\right)^2}_{\approx 1} \approx 1 - \frac{\gamma}{A_V} \cdot \left(1 + \frac{R_L}{R_S}\right)$$

$$Z_O = \frac{R_L \cdot (1 + R_S \cdot g_{m2})}{2} = \frac{R_L}{2} \cdot \frac{(2 - A_V)}{(1 - A_V)}$$

Design summary

- Setting the voltage gain, $g_{m1} \cdot R_L$ imposes g_{m2}
- Choosing g_{m1} and R_L impacts consumption and NF
- Compute power gain and NF for various values of R_L , different gain to see impact.
- The gain will be limited by the CL at the output and the voltage drop across R_L , going to stronger inversion increases $R_L \cdot I_{D1}$ by $1/g(I_C)$
- Find the best trade-off!
- E.g. $R_L=100\Omega$, in WI: $I_{D1}=3\text{mA}$, $I_{D2}=70\mu\text{A}$, $P_G=13\text{dB}$, $F=1.2$