
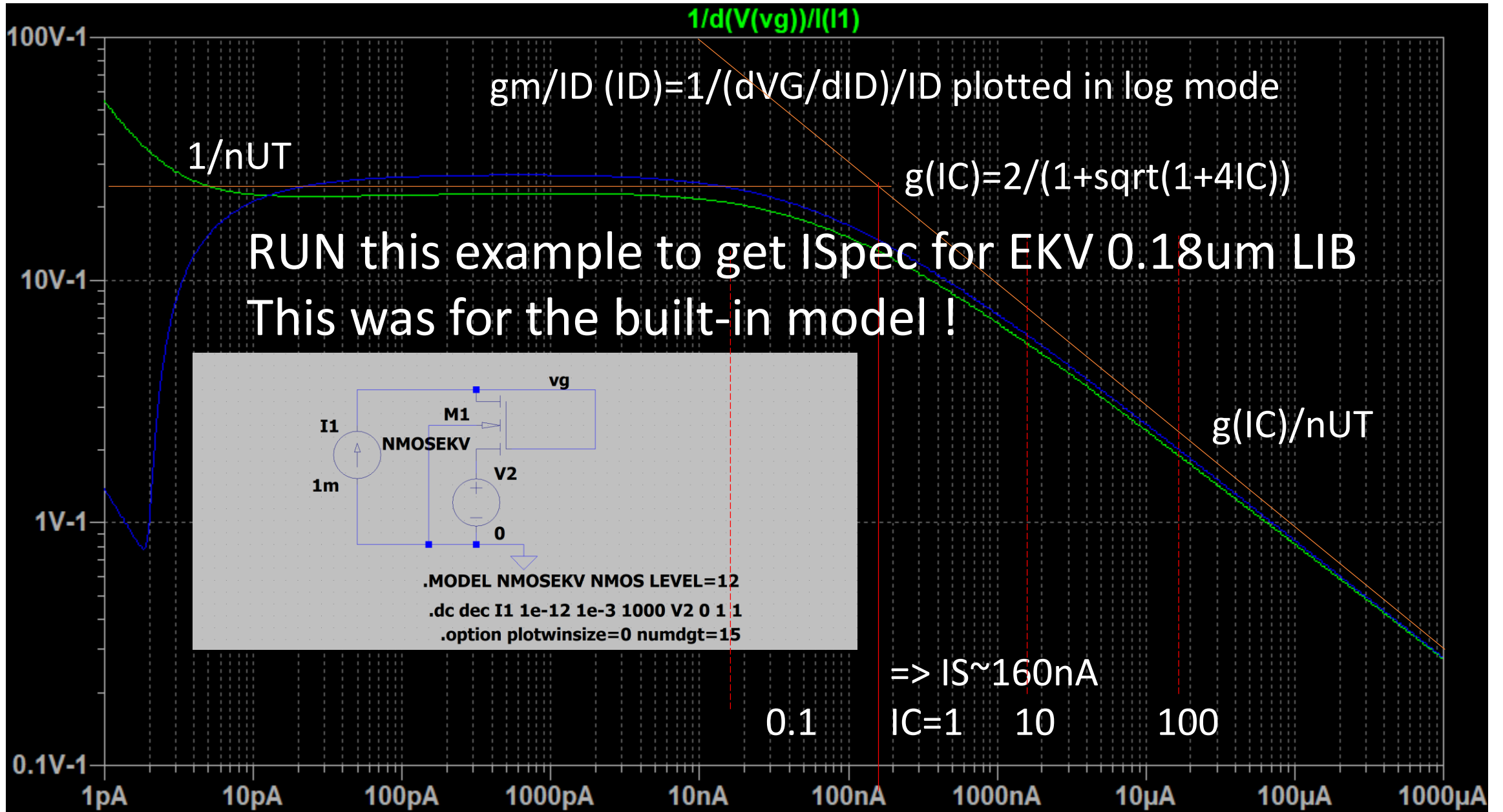


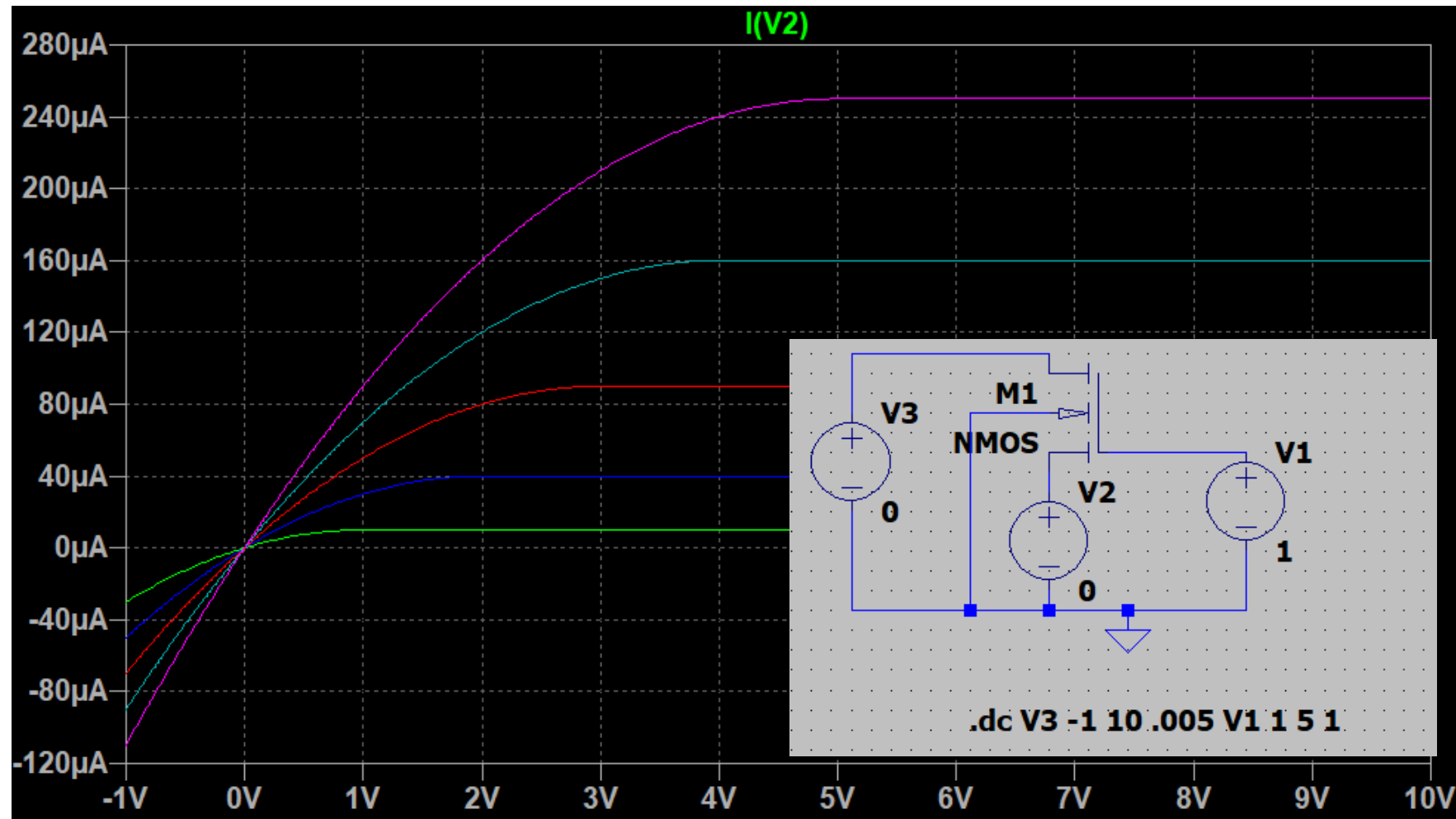


Determine V_{DSAT} (normally $(V_G - V_T)/n$)


Redo this with EKV 0.18um model $V_{DD}=1.8V$


- Sweep $-1V < V_D < 10V$, 1st sweep is X-axis
- $V_S=0$, $I(V_S) > 0$ (plt)
- $V_G=1, 2, \dots, 5V$
- $V_T=0$, $n=1 \Rightarrow$
 - $V_{DSAT}=V_G$
 - $V_{DG} \geq 0$!
- Mirror ok !




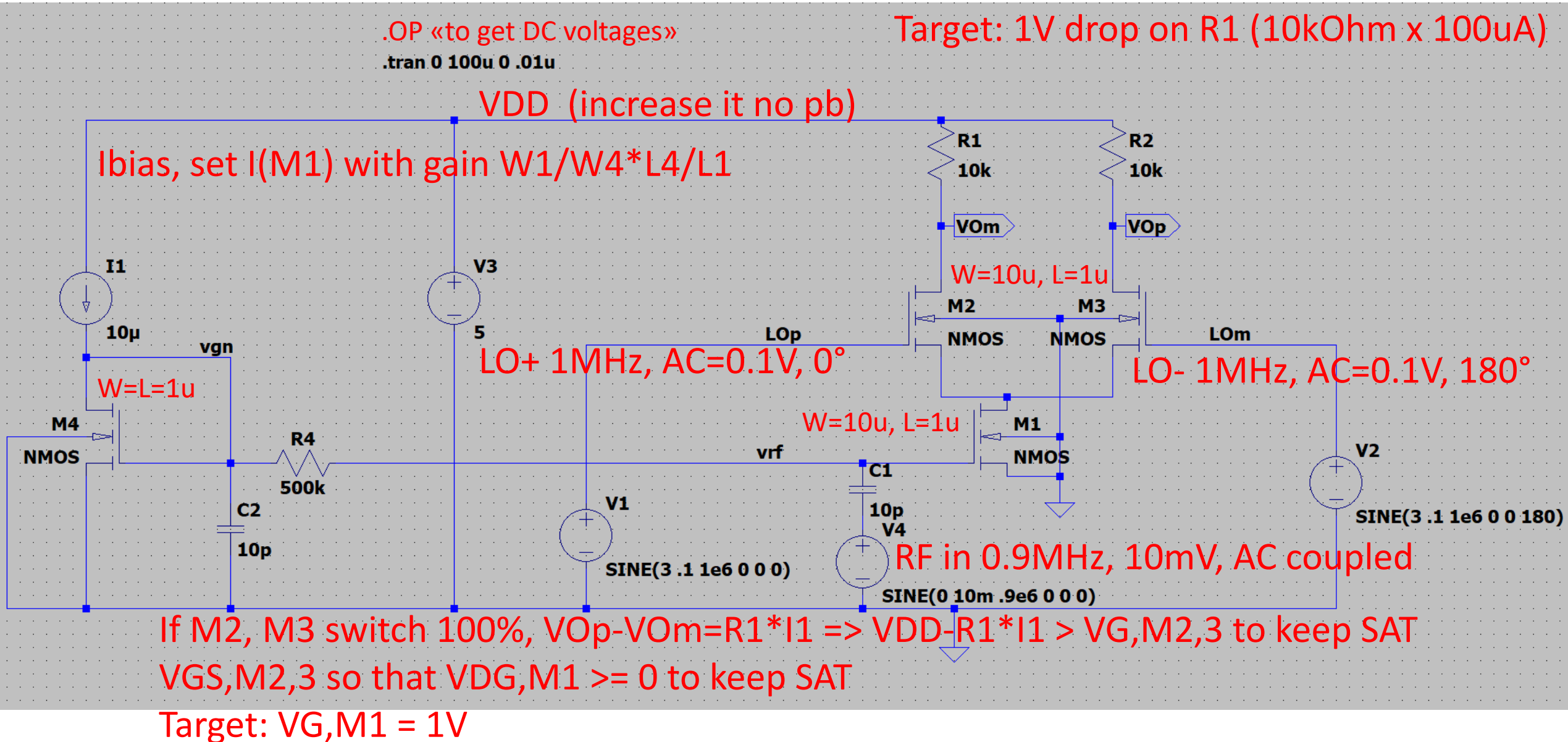Mixer schematic (use EKV L=0.18um LIB, VDD=1.8V)




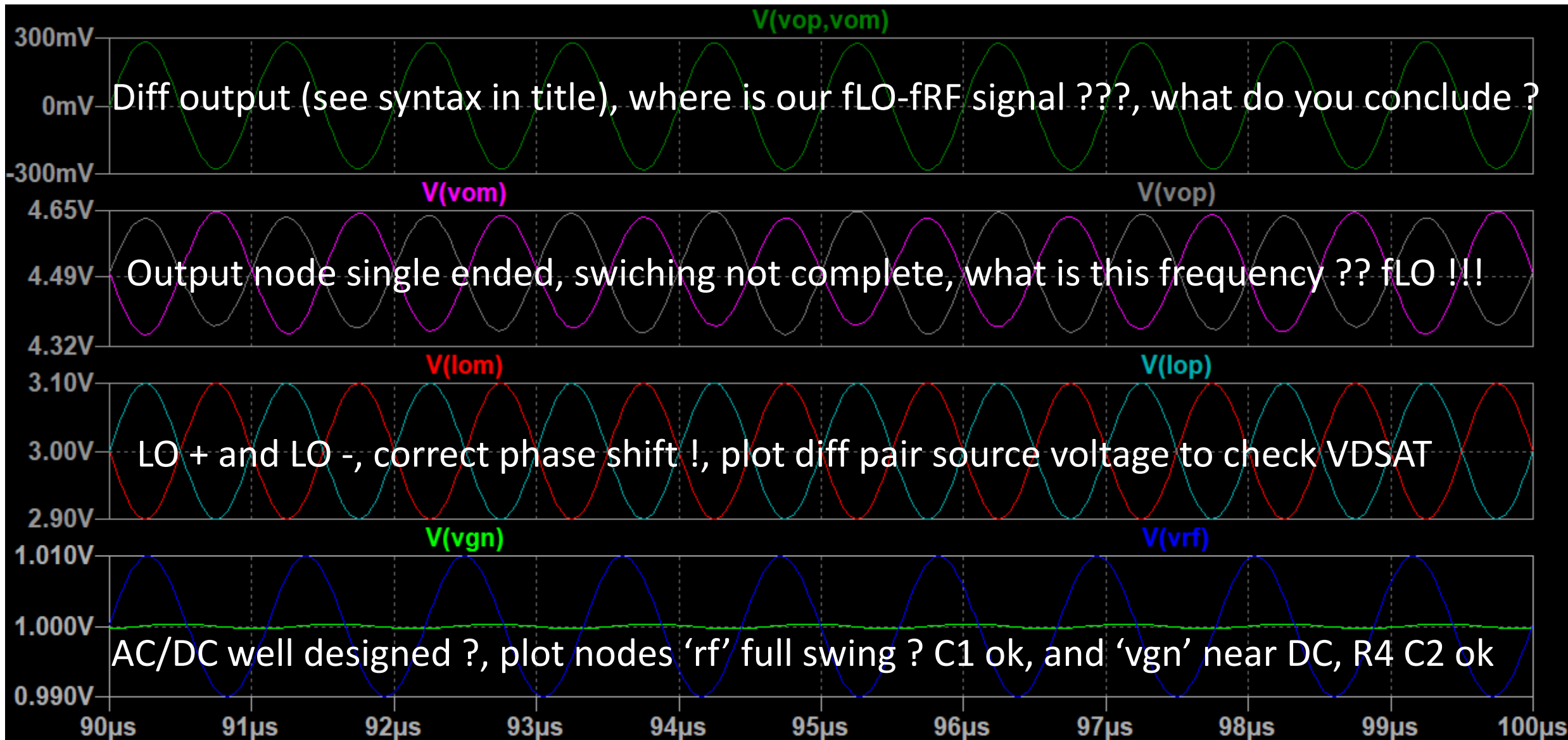

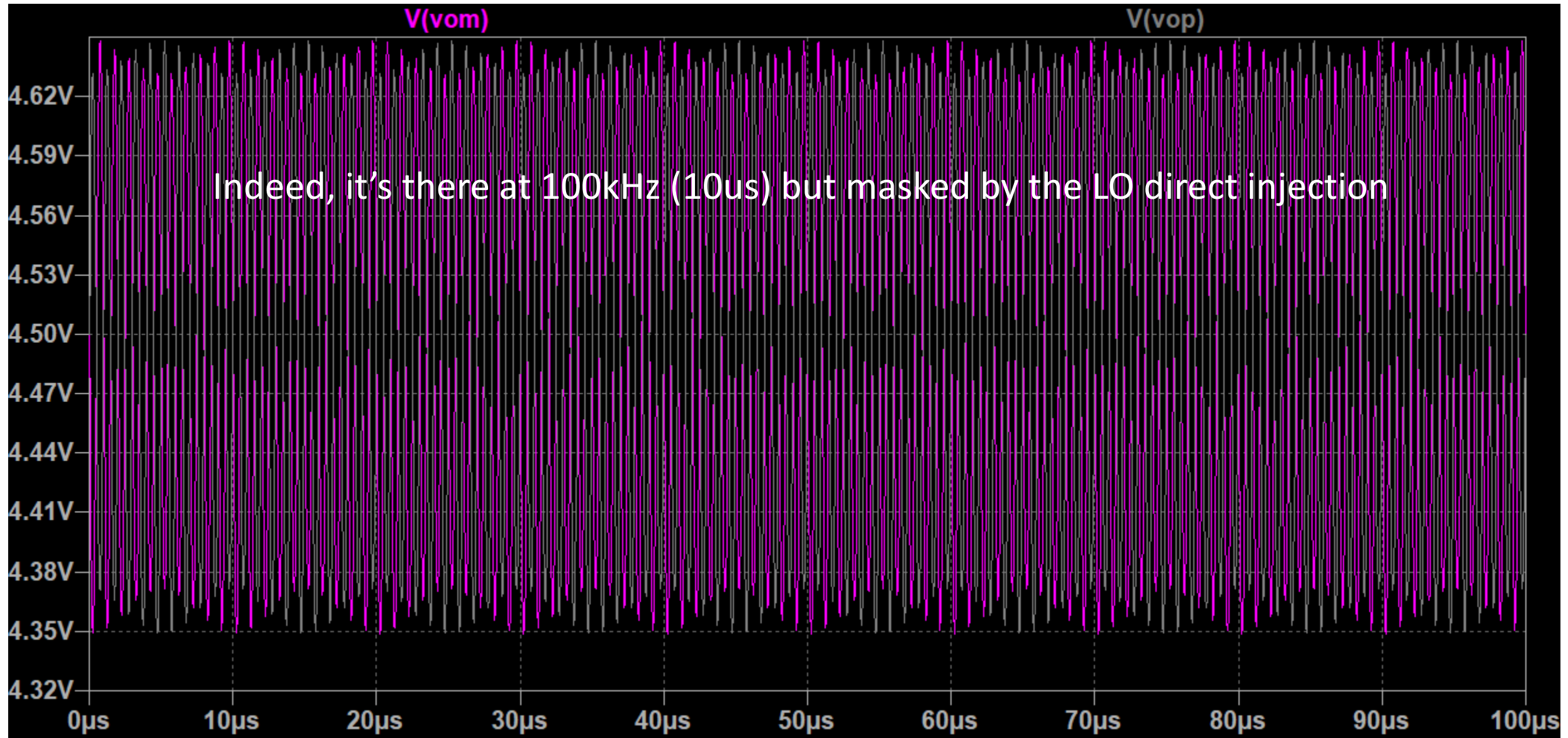


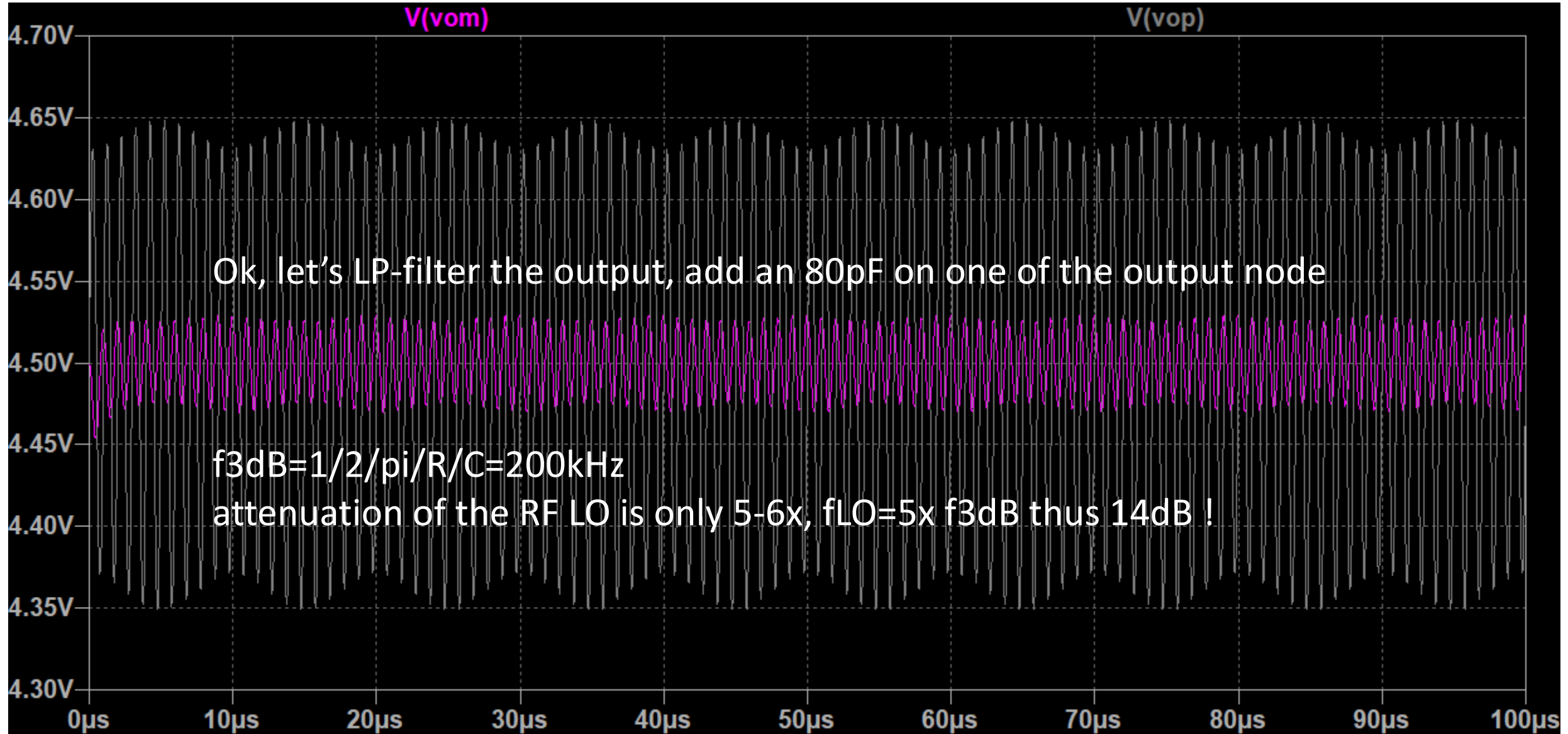

Lowering f_{IF}/f_{LO} ratio

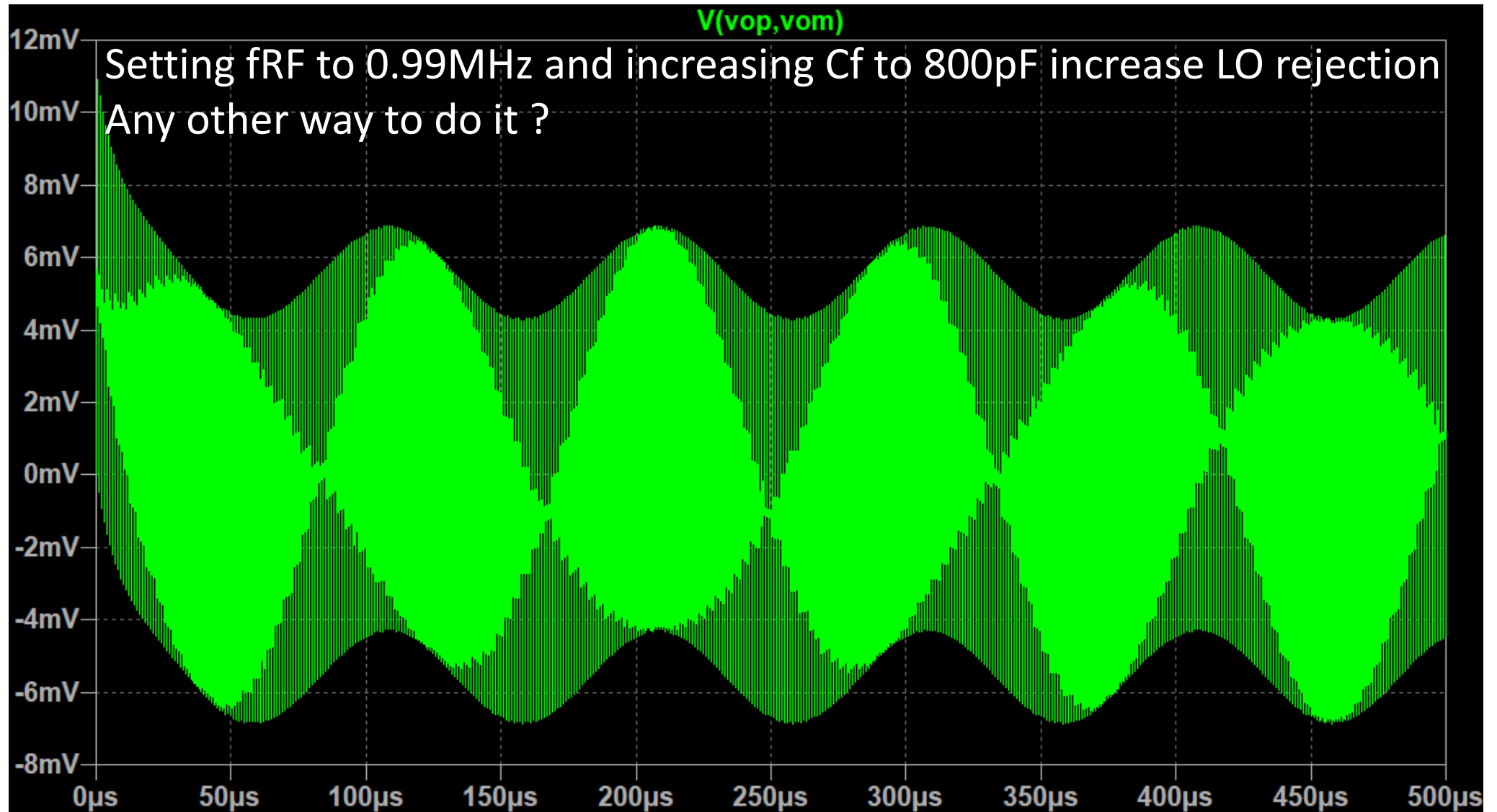

Yes ! Double-balanced mixers !

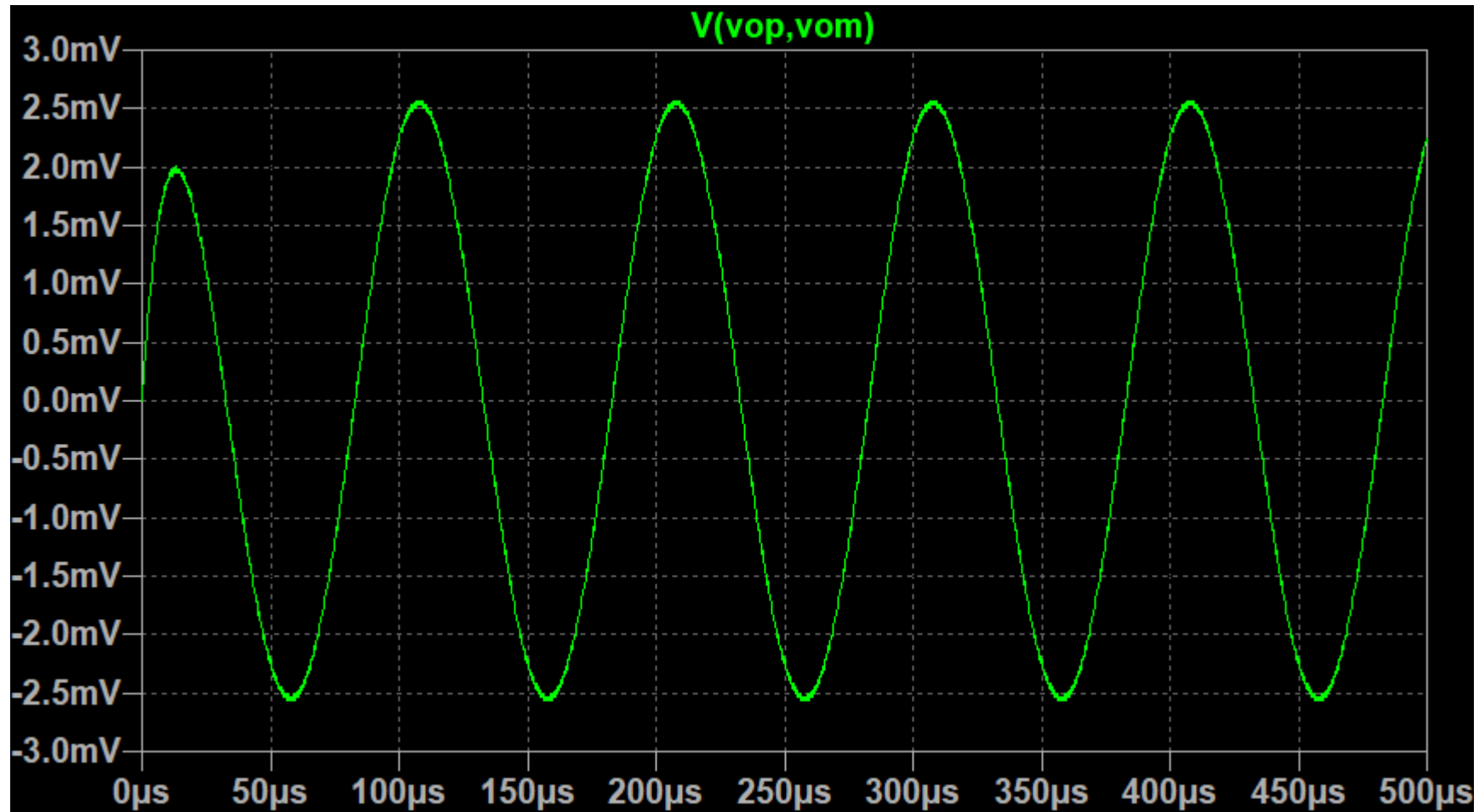


Differential RF input and duplicated diff pair !

Issue is DC current from RF input MOS M1 which is steered by M2,3 and $\gg$ IRF

Solution: inject that same DC current on opposite node and AC with -1 gain (hence 180° RF)


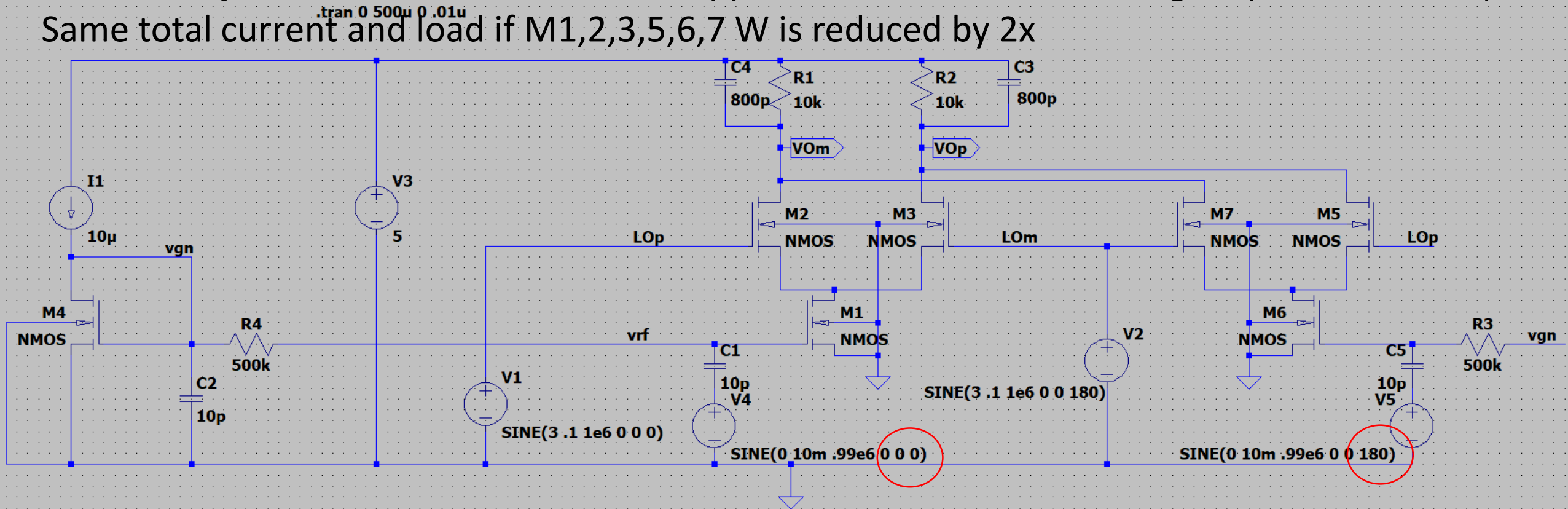
Same total current and load if M1,2,3,5,6,7 W is reduced by 2x



Replicate that structure and vary RF, LO swings to extract gain, compression (☺?)

- Check the .measure help in LTSpice or use below syntax directives
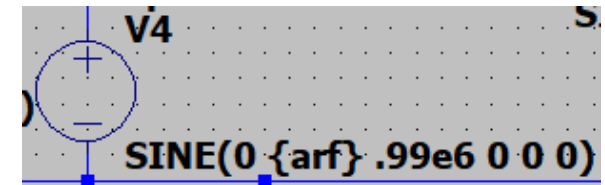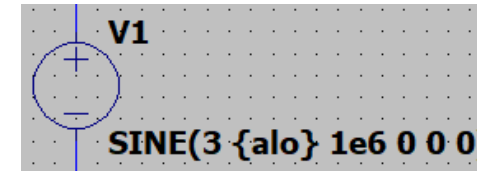
```
.PARAM arf=10m alo=100m  
.step param arf list 1m 2m 4m 8m 16m 32m 64m 128m 256m 512m  
.step param alo list 100m 200m 400m 800m 1.6  
.meas TRAN if_amp MAX V(VOp,VOm)
```



- Select View -> Spice Error Log
- Right click inside window
- Select Plot stepped meas data


SPICE Error Log: C:\Users\dru\OneDrive - CSEM S.A\Documents\LTspiceXVII\mixer.log

```
.step arf=0.256 alo=1.6  
.step arf=0.512 alo=1.6
```


Measurement: if_amp

step	MAX (v (vop, vom))	FROM	TO
1	0.000257492	0	0.0005
2	0.000514984	0	0.0005
3	0.00102901	0	0.0005
4	0.00205851	0	0.0005
5	0.00411749	0	0.0005
-	- - - - -	-	- - - -


Gain as a function of LO swing

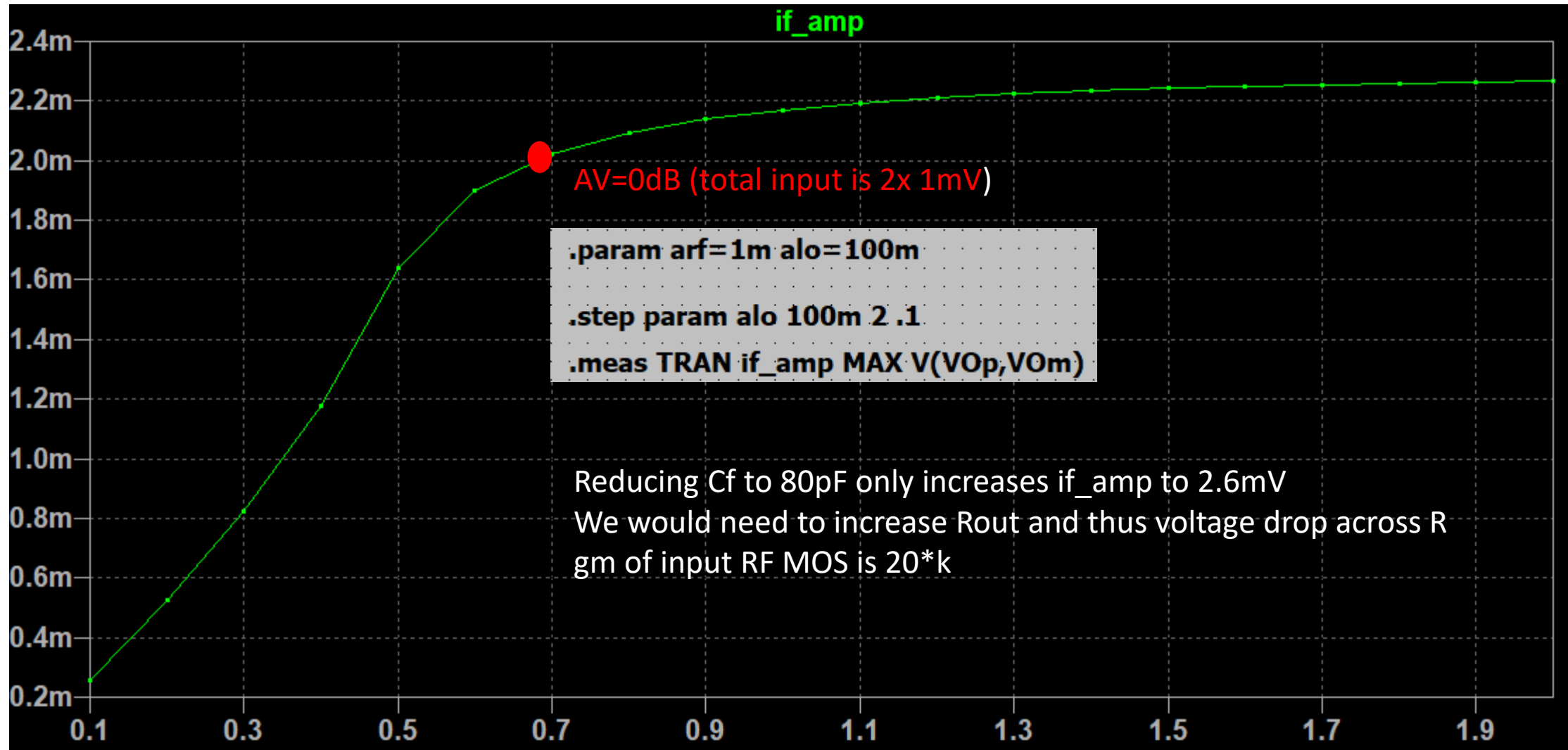


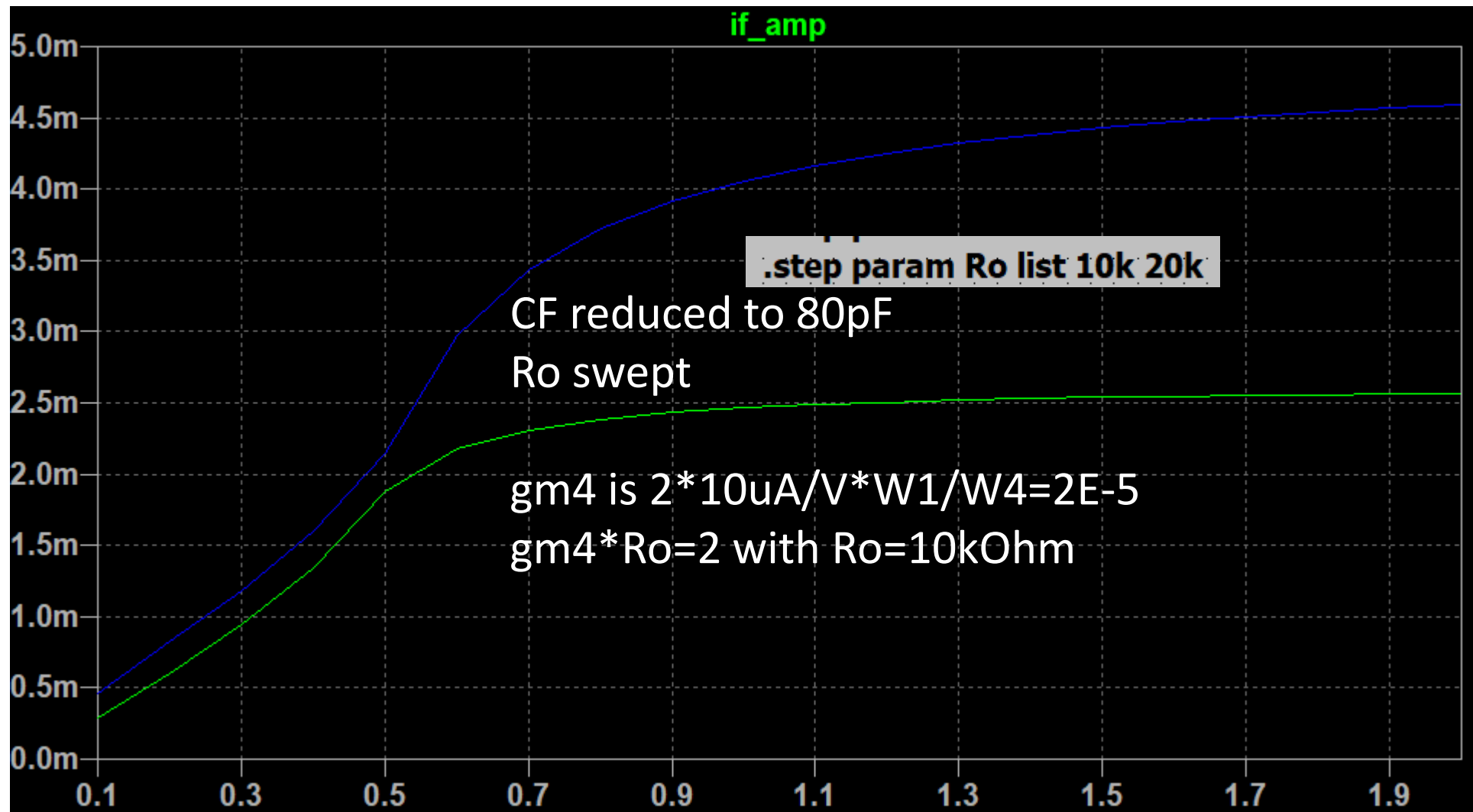Doubling R_o indeed does increase our gain !



Changing gm/ID (to be updated with EKV!)

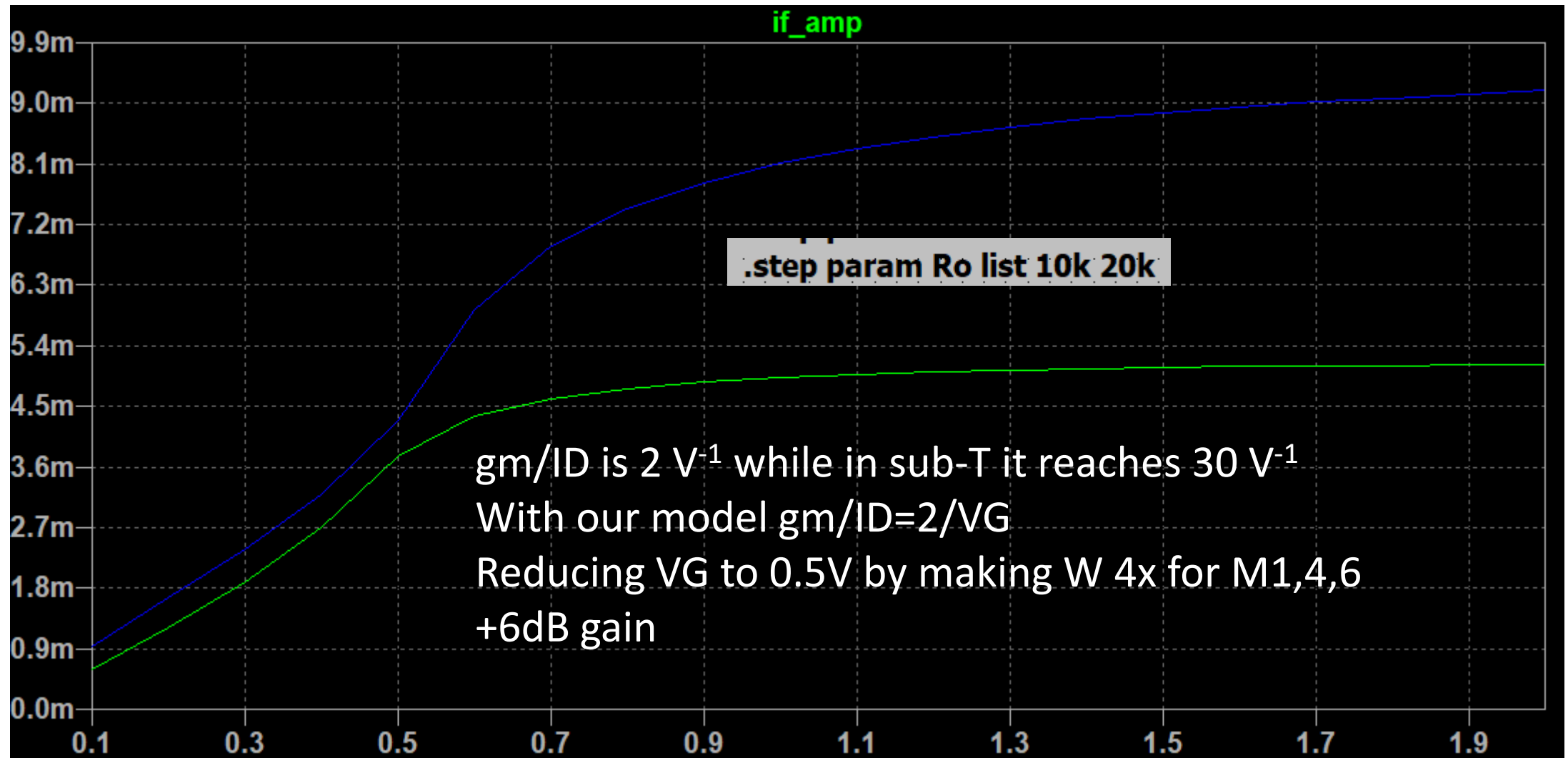

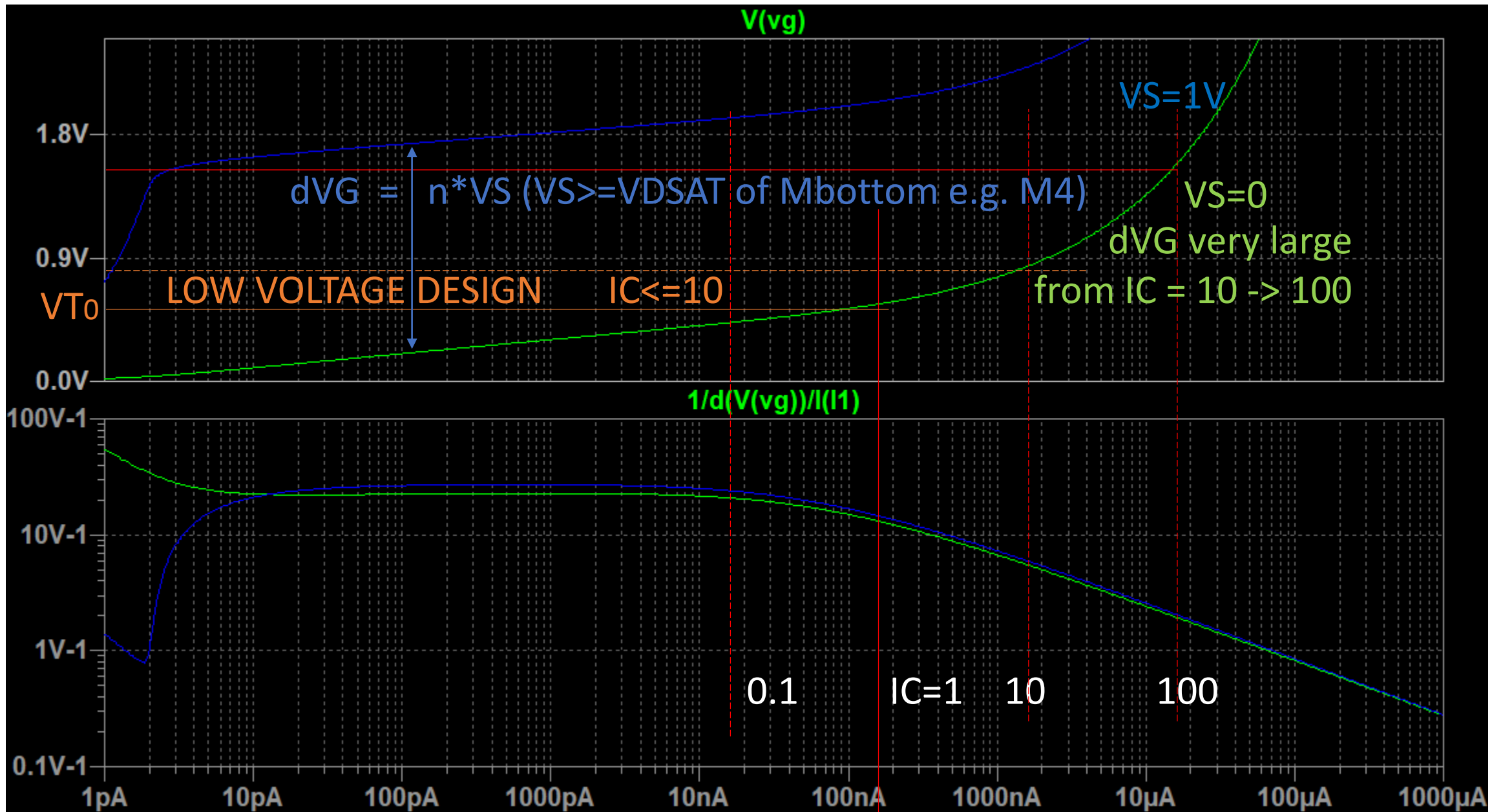

Exercises

- Try to vary the W & L of MOS to vary I_C
 - $AD(S)$ is drain, source area, $PD(S)$ perimeter
 - $AD(S)=W*1\mu=1p$ for $W=1\mu$; $PD(S)=2W+2*1\mu$
 - You could go with $L=.1\mu$ to limit cap, likely no effect modelled
 - Try to verify cst W/L curves to check this, plot I_D , g_m/I_D , ...
- Study compression of gain especially as you get closer to sub-T
- Try to modulate RF in amplitude or in frequency ($f_{RF}=f_{LO}\pm 10kHz$)
 - You may use switches with two voltage sources
 - And look at transient waveforms
- What do you conclude ?