

# Low phase noise and low jitter 0.1-10GHz VCO

David Ruffieux, senior expert & head of system-on-chip research

Swiss Center for Electronics and Microtechnology, CSEM

[david.ruffieux@csem.ch](mailto:david.ruffieux@csem.ch)

Lausanne, 28.06.2018

# Outline

---

- Introduction & Motivations
- Q-factor definition and calculation
- Review of classical VCO topologies
- Discussion on phase noise and LC tank design
  - Choice of  $L$  and  $C_v$  to optimize phase noise power performances
- Presentation of low voltage VCO structure suitable for high swings
- 2.4GHz 65nm CMOS BLE VCO measurement results
- Alternative synthesizer architecture based on FBAR
  - Performance comparison with LC/XO PLL

# PLL performance is limited by XTAL and VCO phase noise

## Close-in noise limited by:


- XO phase noise
- Increased by  $20 \log(N)$

## Far-from-carrier noise by:

- VCO phase noise
 
## PLL Loop BW


- Chosen when those noise sources are equal


 
## Simple VCO structure


- Cross-coupled pair provides negative conductance
  - $-g_m/2$  with  $g_m = I_B / (2 \cdot n \cdot U_T)$  in sub-T
- Should balance tank loss ( $g_p = 1/R_p$ )
  - Calc  $R_p$  with series/parallel transformation
- Large swing feasible ( $\sim 2 \cdot V_{CC}$ )
- Barkhausen criterion

$$\omega_o = \sqrt{\frac{1}{L \cdot C}} \quad g_m \cdot R_p = -1$$



 
## Another simple VCO structure

- Current can be fed on both drains if only a 2 terminals single coil is available
  - Drain junction cap loading tank
  - Limited swing  $(V_{CC} - V_{DSAT})/2$
- Feed inductor midpoint instead
  - Same  $V_{OSC}(I_B)$  as calculated for XO
  - Large swing feasible
- What happens if constant  $V_{CC}$  bias?
  - Current keeps increasing until  $M_{1,2}$  leave saturation
  - Strong non-linearity reduces gain
  - Leads to increased phase noise


 
## Complementary VCO structure (most popular)

- Equivalent to two cross-coupled inverters
- Could potentially halve bias current
  - $g_m$  of PMOS usually lower as same W/L
- Ampl. control with one biasing current source
  - Without  $I_B$ , desaturation and PN degradation
- Poor PSRR: LDO can be used to provide clean  $V_{CC}$
- Sensitive to PVT variations, limited  $V_{OSC}$  at low  $V_{CC}$
- Watch-out for proper start-up in SS,  $V_{MIN}$ ,  $T_{LOW}$
- Operation in sub/near threshold permit higher swings owing to a reduced  $V_{DSAT}$



- With  $V_{G,P}$  the peak gate voltage  $V_{DSAT} = \max \left( 5 \cdot U_T, \frac{V_{G,P} - V_T}{n} \right)$

# How to optimize the phase noise power product of a VCO

- Noise


$$\phi_n = \frac{(1+\gamma) \cdot kT}{Q} \cdot \sqrt{\frac{L}{C}} \cdot \left( \frac{\omega_o}{\Delta\omega} \right)^2 \cdot \frac{1}{V_{OSC}^2}$$

- Power

$$I_{OSC} \cdot V_{DD} \rightarrow \frac{V_{OSC} \cdot V_{DD}}{\sqrt{\frac{L}{C}} \cdot Q} \Big|_{V_{OSC} \gg 0}$$

- Noise x Power
 
$$\phi_n \cdot P_{OSC} \propto \frac{(1+\gamma)}{Q^2} \cdot \frac{V_{DD}}{V_{OSC}}$$



**To get lower PN**

1. Max Q
2. Max  $V_{OSC}$
3. Min  $\gamma$
4. Increase C

$$\omega_o = \sqrt{\frac{1}{L \cdot C}}$$

$$g_m \cdot R_P = -1$$

# How to design the VCO tank? (obviously an iterative process!)


- Selection of coil type
  - External coil Q up to 100, up to 2-3GHz, reproducibility of PCB
  - Bondwire Very good Q but reproducibility issues (L=1nH/mm)
  - PCB trace, microstrip line Suitable for SHF, IO modelling + ESD issues
  - Integrated Attractive above 1GHz, Q~10-20@ 2.4GHz
- Determine the fixed VCO load ( $C_F$ ) mixers & PA, buffers, PLL dividers, VCO, routing
- Varactor  $C_V$  need to cover desired BW & all manufacturing tolerances
- Using  $k = \frac{C_F + C_{V,MAX}}{C_F + C_{V,MIN}}$  and  $k' = \frac{C_{V,MAX}}{C_{V,MIN}}$   $\frac{\Delta f}{f} = \frac{1}{2} \cdot \left( \frac{\Delta C}{C} + \frac{\Delta L}{L} + BW \right)$
- The tuning range and the min varactor size can be expressed as
 
$$TR = \pm \frac{f_{MAX} - f_{MIN}}{f_{MAX} + f_{MIN}} = \pm \frac{\sqrt{k} - 1}{\sqrt{k} + 1} \quad C_{V,MIN} = \left( \frac{k - 1}{k' - k} \right) \cdot C_F$$
- The max possible inductor value can be determined, phase noise perfs estimated

# Coil Q-factor limitation due to skin depth effect

- Skin depth simplified calculation



$$\delta = \sqrt{\frac{2\rho}{(2\pi f)(\mu_0\mu_r)}} \approx 503 \sqrt{\frac{\rho}{\mu_r f}}$$

 - For copper,  $\mu_r = 1$ ,  $\rho = 1.68\text{E-}8 \text{ }\Omega\cdot\text{m}$
  - $\delta = 1.33 \text{ }\mu\text{m}$  @ 2.4 GHz
  - $\delta = 0.27 \text{ }\mu\text{m}$  @ 60 GHz
- It can't be neglected
    - Use EM solver to study impact more carefully (e.g. Momentum)



  
## Equivalent model for discrete coils

- $R_2$  is DC resistance
- $R_{VAR}$  accounts for skin effect
 
$$R_{VAR} = k \cdot \sqrt{f} \quad k \text{ in } [\Omega \cdot s^{0.5}]$$
- $C_1$  defines Self Resonance Frequency
- $R_1$  &  $R_{VAR}$  define Q @ SRF
- Model PCB, bondwire, bumps, PADS, routing wires properly ( $L=1\text{nH/mm}$ )
- Use S/P transformations to get  $Q_L$



| Part number | R1<br>( $\Omega$ ) | R2<br>( $\Omega$ ) | C(pF) | L(nH) | k        | Upper<br>limit<br>(MHz) |
|-------------|--------------------|--------------------|-------|-------|----------|-------------------------|
| 0402HP-1N0  | 6                  | 0.038              | 0.030 | 1.00  | 2.70E-06 | 20000                   |
| 0402HP-2N0  | 5                  | 0.038              | 0.050 | 2.00  | 5.22E-06 | 20000                   |
| 0402HP-2N2  | 4                  | 0.038              | 0.040 | 2.20  | 5.70E-06 | 20000                   |
| 0402HP-2N4  | 13                 | 0.042              | 0.044 | 2.40  | 6.20E-06 | 20000                   |
| 0402HP-2N7  | 11                 | 0.056              | 0.044 | 2.70  | 6.46E-06 | 20000                   |
| 0402HP-3N3  | 15                 | 0.045              | 0.032 | 3.30  | 7.80E-06 | 20000                   |
| 0402HP-3N6  | 10                 | 0.045              | 0.022 | 3.60  | 8.10E-06 | 20000                   |
| 0402HP-3N9  | 12                 | 0.045              | 0.042 | 3.90  | 9.70E-06 | 14000                   |
| 0402HP-4N3  | 10                 | 0.040              | 0.048 | 4.30  | 1.12E-05 | 12000                   |
| 0402HP-4N7  | 13                 | 0.060              | 0.052 | 4.70  | 1.29E-05 | 12000                   |
 
## Typical discrete 402 coil Q-factor and Self Resonance Frequency



| Inductance <sup>2</sup><br>(nH) | Percent<br>tol <sup>3</sup> | 900 MHz |                    | 1.7 GHz |                    | SRF typ <sup>4</sup><br>(GHz) |
|---------------------------------|-----------------------------|---------|--------------------|---------|--------------------|-------------------------------|
|                                 |                             | L typ   | Q typ <sup>4</sup> | L typ   | Q typ <sup>4</sup> |                               |
| 1.0                             | 5                           | 0.97    | 46                 | 0.99    | 72                 | 16.0                          |
| 2.0                             | 5                           | 1.96    | 58                 | 1.98    | 85                 | 15.2                          |
| 2.2                             | 5                           | 2.17    | 60                 | 2.17    | 86                 | 15.1                          |
| 2.4                             | 5,3,2                       | 2.37    | 60                 | 2.38    | 83                 | 14.0                          |
| 2.7                             | 5,3,2                       | 2.66    | 62                 | 2.68    | 85                 | 13.0                          |
| 3.3                             | 5,3,2                       | 3.26    | 66                 | 3.28    | 95                 | 12.8                          |
| 3.6                             | 5,3,2                       | 3.56    | 65                 | 3.58    | 94                 | 11.7                          |
| 3.9                             | 5,3,2                       | 3.87    | 64                 | 3.91    | 98                 | 9.50                          |
| 4.3                             | 5,3,2                       | 4.26    | 63                 | 4.33    | 90                 | 7.15                          |
| 4.7                             | 5,3,2                       | 4.67    | 58                 | 4.74    | 83                 | 6.85                          |
| 5.1                             | 5,3,2                       | 5.07    | 54                 | 5.16    | 76                 | 6.80                          |

## Integrated coils

- Use Al RDL (aluminum redistribution layer) + ultra-thick metal process option
- Use RF-PDK coil generator to get expected performances
  - Usually limited to single layer coil
- Designing your own coil is feasible but requires expertise and is time-consuming
  - Use EM-solver such as e.g. Momentum
  - Difficult to guarantee error free design (LVS is tricky)
  - Multi-layer coils and transformers can be engineered
- Typical performance of a compact integrated coil at 2.4GHz
  - $L=7.9\text{nH}$ ,  $R=8\Omega$ ,  $Q=13$ ,  $\text{SRF}=7.5\text{GHz}$ ,  $C_{\text{SRF}}=65\text{fF}$ ,  $C_{\text{TOT}}=637\text{fF}$
- A wider area could lead to better performances



# Varactor design

---


- There are different types of analog varactors
  - Junction diodes, Inversion & accumulation MOS capacitance
- Digitally-controlled varactors can be made with
  - MOM cap and switches
  - Inversion capacitance
- Combined analog and digitally controlled varactor for fine and coarse tuning
- DCO using 2<sup>nd</sup> order  $\Delta\Sigma$  modulator on 3-unit caps for fine frequency interpolation
- Varactor tuning ratio and Q-factor is a compromise
  
# Analog varactor using MOS capacitor (I)

- NMOS C(V) curve (neglecting overlap capacitance)



 
- Inversion or depletion capacitance has very abrupt C(V) change leading to high gain
- Place substrate tap regularly to provide maj carriers as well to prevent Q degradation




- Q scales as  $1/L^2$ , watch out for  $R_G$  (W)
- Overlap capacitance limit  $CM/C_m$
- Alternate + & - fingers (virtual gnd)
- No contact required in active zone
 
## Analog varactor using MOS capacitor (II)

- Accumulation varactor has lower and more linear  $dC/dV$  curve than inversion
- $dC/dV$  curve is max near 0V bias provided G and S/D doping is reverted




 
$C_{V_M} / C_{V_m} = 2.6$  ( $l = 0.46 \mu\text{m}$  in  $0.18 \mu\text{m}$  CMOS)



- Equivalent to NMOS in NW or PMOS in PW using triple well
  - Inverse doping shifts curve by  $V_{BG}$
- Q scales as  $1/L^2$ , watch out for  $R_G$  (W)
- Overlap capacitance limit  $CM/C_m$
- Alternate + & - fingers (virtual gnd)
- No contact required in active zone
  
## Digitally controlled varactor


- Finger type fringe MOM capacitor with MOS switch (no  $V_{CC}, V_{CM}$  dependency on C)
  - Size switch properly to get desired Q ( $1/R_{on} = \beta \cdot (V_{CC} - V_T)$ )
  - Parasitic cap (MOS + fringe cap) determines on/off ratio
- Accumulation (switch shorted SDB terminals) or inversion (switch SD) MOSCAP
  - Beware of the common mode potential to operate in low gain zone
- Frequency interpolation can be obtained with  $\Delta\Sigma$  modulator for fine tuning


 
# How to get large swings: VCO core structure using cap attenuation


Use capacitive attenuation,  $k$ , to

- Linearize MOS and control its biasing
  - Negative  $g_m$ ,  $V_{OSC}$  are scaled by  $1/k$
  - Permit WI operation
- Decouple drain and gate voltages at DC
  - High  $V_{OSC} / V_{CC}$  ratio
    - $V_{OSC,MAX} = V_{CC} - V_{DSAT}$
  - No PVT influence on  $V_{OSC}$
- Suitable for very low  $V_{CC}$  operation
  - 0.5V VCO with 0.7V diff 0-to-peak feasible


 
# Biasing of the VCO core structure using cap attenuation (I)


- Gate biasing with diode-connected MOS
- $I_{VCO}$  set by mirror ratio (use a fraction for  $M_{3,4}$ )
- $g_m$  loss scaled by square of attenuation factor
- Resistors can be used to make diode connection
  - Cap at the drain nodes is at CM voltage


 
## Biasing of the VCO core structure using cap attenuation (II)

- Gate biasing with diode-connected MOS
- $I_{VCO}$  set by mirror ratio (use a fraction for  $M_{3,4}$ )
- $g_m$  loss scaled by square of attenuation factor
- Resistors can be used to make diode connection
  - Cap at the drain nodes is at CM voltage
- Add  $M_{6,7,8}$  mirrors to control via  $I_B$
- Similar  $I(V_{OSC})$  behaviour as that derived for XO

$$I_{D1\omega}(A) \frac{I_{B0} \left( \frac{A}{n \cdot U_T} \right)}{2 \cdot I_{B1} \left( \frac{A}{n \cdot U_T} \right)} = \bar{I}_D(A)$$




# Complete VCO structure including AGC loop

Amplitude regulation formed by


- R1,R2,C5 (BW)
- M5,R3 (PTAT  $I_{REF}$ )

Benefits

 - constant amplitude
  - insensitive to dQ, dC
- Suppression of amplitude noise
  - Min AM to PM conversion
  - 1/f noise of  $M_{1,2}$
- Min power consumption
- Great design freedom



 
## $V_{OSC}$ vs $I$ for VCO & REG and different $k$ values



 
## Details of the varactors implementation

- AC-coupled accumulation varactors can be used ( $dC/dV$  max near 0V!)
  - Yields differential tuning (good at low  $V_{CC}$ )
  - Much better PSRR
- Size properly the resistors (Q-degradation)
- Study common-mode behaviour to add missing elements & watch-out for added pole!
- Coarse tuning obtained with SC- $C_{MOM}$ 
  - Ensure sufficient overlap with  $C_{V,ANA}$
  - Obviously more than 2 bits feasible



 
# Complementary AC-coupled VCO topology

- Relaxed phase noise or  $V_{\text{OSC}}$  requirements ?
  - Complementary structure may halve  $P_{\text{DISS}}$
  - $V_{\text{OSC}}$  up to  $(V_{\text{CC}} - V_{\text{DSAT}})/2$
- Implement biasing, AGC and CM ctrl loops
- Truly low voltage structure
  - $V_{\text{CC}} = 1\text{V}$  over PVT in production



 
## Layout view and things to care about (65nm CMOS)

- Calculate loaded-Q and equivalent series resistor
  - Size routing lines adequately (R vs C trade-off)
- Perform layout extract (RC)
- Investigate where the energy flows
  - Make good virtual ground
  - Optimize Q of each branch
- Evaluate biasing resistors cut-off
  - DC noise up-converted but  $R_{RF} \ll R_{DC}$  !
- Connect both gate ends of MOS
  - Calculate  $R_{GATE}$  to find max  $W_G$
- Watch-out for vias, evaluate their resistance



VCO is ~50% of PLL area  
~0.2x0.3mm<sup>2</sup>
 
# Measurements of the VCO gain across its sub-bands



- **Wide frequency range** with 16 sub-bands ( $\pm 9\%$ )
- Very good overlap
- Almost constant KVCO over 2.4-2.48GHz


## 2.4GHz PLL phase noise with 48MHz XO and consumption

### VCO noise

- 1/f noise corner as high as 1MHz
- PN of -110dBc/Hz @  $\Delta f = 1\text{MHz}$
 
### Current consumption

- VCO 850 $\mu\text{A}$
- XO w/ buffer 100  $\mu\text{A}$
- Total PLL 1.5mA




# Quadrature generation

- 2 cross-coupled VCOs
- LO @ carrier frequency & phase shifter + limiter (RC-CR)
- LO @  $2 \cdot f_c$  &  $\div 2$  in quadrature
- Phase shifter in RX path
- Doubles the power & area, L matching
- Power dissipation, Q degradation
- Avoids LO pulling, usually better Q, higher power since load is not absorbed by tank
- Linearity, noise figure, LO pulling
 
## Avoiding quadrature generation

- Since quadrature is not required in TX, use RC-CR phase shifter in signal path
- High LNA gain to mitigate 3dB RC-CR loss and NF of passive mixers
  - Compromise on linearity



# Quadrature LO generation with source coupled logic divider

## Small signal Kirchhoff equations

$$\begin{bmatrix} 1/R_{1,2} - gm_{1,2} + s \cdot Cp_{1,2} & gm_{7,8} \\ -gm_{3,4} & 1/R_{3,4} - gm_{5,6} + s \cdot Cp_{3,4} \end{bmatrix} \cdot \begin{bmatrix} V_{1,2} \\ V_{3,4} \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

## Barkhausen criterion


$$(1/R_{1,2} - gm_{1,2}) \cdot (1/R_{3,4} - gm_{5,6}) = 0$$

$$s^2 \cdot Cp_{1,2} \cdot Cp_{3,4} - (j)^2 \cdot gm_{3,4} \cdot gm_{7,8} = 0$$
 
## Large signal equations

$$\hat{V} = 2 \cdot \frac{I_{M1}}{gm_{1,crit}} = 2 \cdot R \cdot I_{M1}$$

$$\omega_o = \frac{gm_3}{C} \cdot \frac{I_{M1,crit}}{I_{M1}} \rightarrow \frac{2 \cdot I_{M3}}{C \cdot \hat{V}}$$



if  $\omega_o$  close to  $\omega_{LO}/2$ , injection locking