

EE-429

Fundamentals of VLSI Design

Alternative Logic Styles


Andreas Burg

Different Logic Styles

- **Static CMOS is the most popular logic style due to its**
 - Robustness against noise (good noise margins)
 - Robust against variations in transistor parameters (un-ratioed logic)
 - Almost-zero static power consumption
 - Ability to easily cascade multiple logic stages of any type of gates
 - Ease of use and very good suitability for abstracting delay models (good for EDA)
- **Other styles have been proposed to improve some short-comings of CMOS**
 - Limited fanin (number of inputs to a single-stage gate)
 - Inability to describe certain Boolean functions in a single logic stage
 - Notable area overhead due to the need for complementary PMOS and NMOS
 - Imbalance between PMOS and NMOS stage (differences in mobility)

Pass-Transistor Logic (PTL)

 - **CMOS always drives gate-output from the rails**
 - Good for output noise margins
 - Less obvious when outputs are trivial functions of the inputs (e.g., MUX) or for some basic non-unate gates such as XORs
- **Solution: drive output from one of the inputs** using switches made from **NMOS** or **PMOS** transistors
- **Systematic construction** from Boolean equations using **Shannon expansion**



PTL: Construction (N-MOS)

- **Based on the Shannon Expansion of a Boolean equation**

- Start from a Boolean equation of the form:

$$Z = f(x_1, x_2, \dots, x_n)$$

- Co-factor expansion: decompose into two equations, one conditioned (AND) on x_1 and one on $\bar{x}_1$


$$f(x_1, x_2, \dots, x_n) = x_1 \cdot f(1, x_2, \dots, x_n) + \bar{x}_1 \cdot f(0, x_2, \dots, x_n)$$

- Continue as above, now expanding $f(1/0, x_2, x_3, \dots, x_n)$ and so forth ...

- Translate into N-MOS based logic:

- Interpret the **product ($\cdot$)** as a **pass-transistor N-MOS** that passes the logic value of the RHS term based on x_i or $\bar{x}_i$ (term is passed if x_i or $\bar{x}_i$ are 1, otherwise not)

 - Interpret a **sum ($+$)** as “**connecting**” **two product-term results** from x_i and $\bar{x}_i$




PTL: Construction (N-MOS) Example

- EXAMPLE: NAND-2 gate


$$\begin{aligned} f(x, y) &= \bar{x} + x \cdot y = \\ \bar{x} \cdot (1 + 0 \cdot y) + x \cdot (0 + 1 \cdot y) &= \\ \bar{x} \cdot (1) + x \cdot (y) \end{aligned}$$

x	y	f
0	0	1
0	1	1
1	0	0
1	1	1

 


Pass-Transistor Logic

 - **Problem:** VT drop as NMOS and PMOS lack the ability to drive a strong '1' and a strong '0' respectively




 - **Solution:** drive output from one of the inputs using switches made from Transmission gates instead of **NMOS or PMOS transistors**



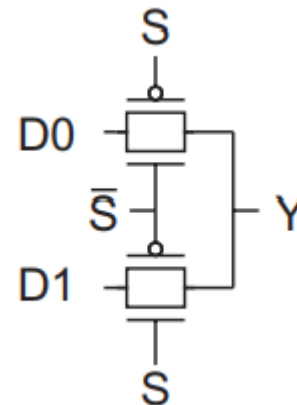- **Example 2-input MUX**

- Doubles the number of transistors
- Adds PMOS to an otherwise NMOS-only circuit
- Need for inverted inputs



Pass-Transistor Logic

- **Systematic construction** from Boolean equations using **Shannon expansion**

- **Many disadvantages:** with various solutions

- Logic output can depend directly on the input: **signal level degrades** gradually across multiple logic stage


Solution **CMOSTG**: regularly buffer outputs with CMOS inverters

- Typically **requires** inputs and **also inverted inputs**

Solution (DPL): generate both outputs and inverted outputs


- Large **overhead from transmission gates**

 Solution (CPL): accept a VT drop in one branch of the differential (complementary) output







Ratioed Logic Gates

- **CMOS gates “waste” 50% of the transistors** to cut one of the supplies when the other supply rail is connected to the output
- **Solution: replace pull-up or pull-down switch** with constant “resistance” that is
 - Sufficiently strong to **pull** the output **when it is not pulled actively to the other side**
 - Sufficiently weak to **marginally impact** the output **when it is actively pulled to the other side**
- **Especially attractive to remove the larger PMOS**

 




Pseudo NMOS Logic

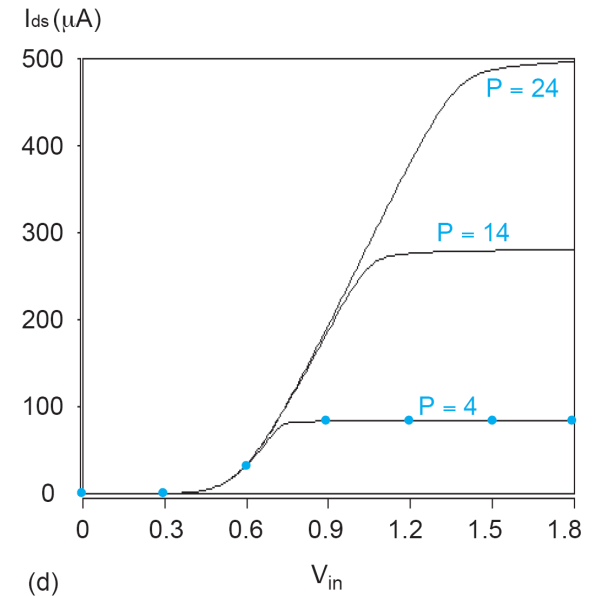   - **Replaces PMOS network with an always weakly-on biased PMOS**
 - Constant power consumption due to short-circuit when output is low
 - Fall time determined by sizing of the NMOS network
 - Rise time determined by sizing of the always-on PMOS
 - Determines static power consumption
 - Strong PMOS (short rise time) degrades output low-level noise margin
- **Example: inverter**



Dynamic Logic


- **Drawback of Ratioed Logic: short-circuit current** (for one of the outputs)
 - **Limits the drive strength** of the always-on (pull-up or pull-down) device
- **Solution: operation in two phases separates pull-up from pull-down**
 - **Phase 1** pre-charge (pre-discharge): always pull-up (pull-down) (optional footer prevents short-circuit during precharge)
 - **Phase 2** evaluate output: conditionally pull-down (pull-up) depending on inputs

 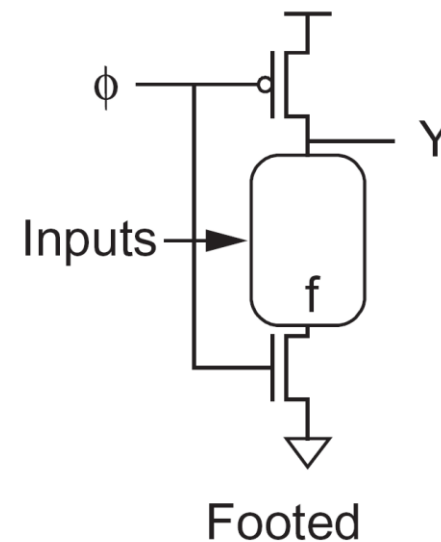 


Dynamic Logic Examples

Unfooted


Inverter

 

NAND2

 

NOR2

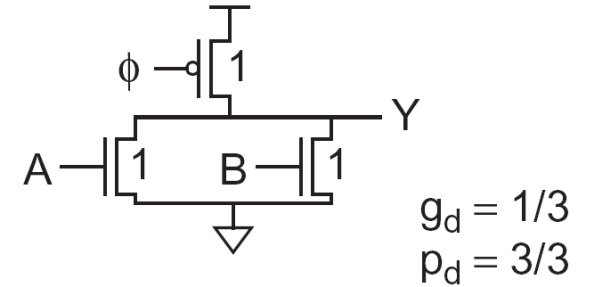

Footed

