

EE-429

Fundamentals of VLSI Design



Quick Review of the MOS Transistor for Digital Designers

Andreas Burg, Alexandre Levisse


Acknowledgement: Prof. Adam Teman (BIU)

Fundamental Element: nMOS & pMOS Transistors

 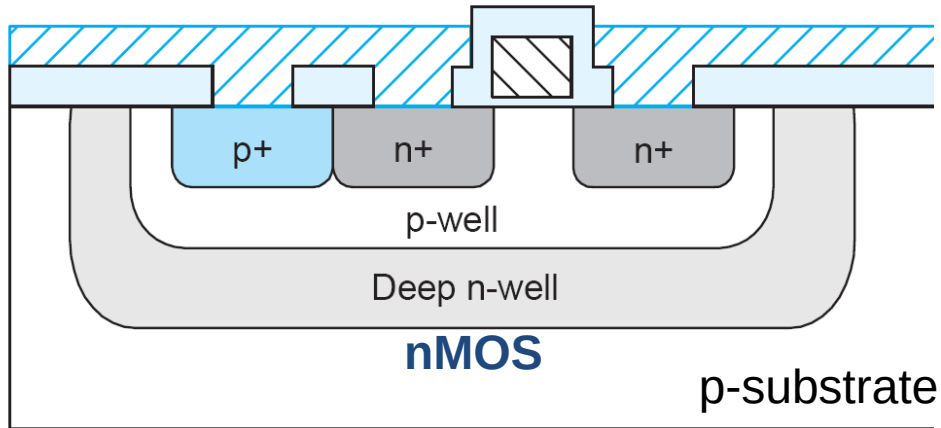- Complementary Metal Oxide Semiconductor (**CMOS**) circuits are build from complementary transistors: **nMOS** and **pMOS** transistors



 - CMOS transistors have 4-terminals:** source (S), Drain (D), Gate (G), Bulk (B)
 - We will often connect Bulk (B) to Source (S) and omit the Bulk (B) terminal




The Switch Model


- **Boolean** electric **model** for **functional considerations**
 - Logic '0' = GND Logic '1' = VDD
 - Boolean terminals $S \rightarrow s$, $D \rightarrow d$, $G \rightarrow g$
- **Gate** terminal (g) **controls current flow** between source (s) and drain (d)

pMOS and nMOS
complementary


nMOS

 



pMOS

 

$g = 0$

 

$g = 1$

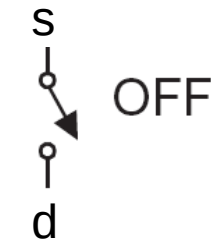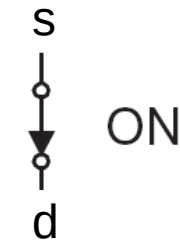


Basic CMOS logic Principal

- With the switch model, we can construct the basic CMOS gates

- **Basic idea:**

- Start from the truth table (input/output relationship)
 - **Pull-Up network (PUN):**
Connect OUT to VDD for input combinations that lead to a '1'
 - **Pull-Down network (PDN):**
Connect OUT to GND for input combinations that lead to a '0'

A/B/C	000	001	010	011	100	101	110	111
Y	0/1	0/1	0/1	0/1	0/1	0/1	0/1	0/1

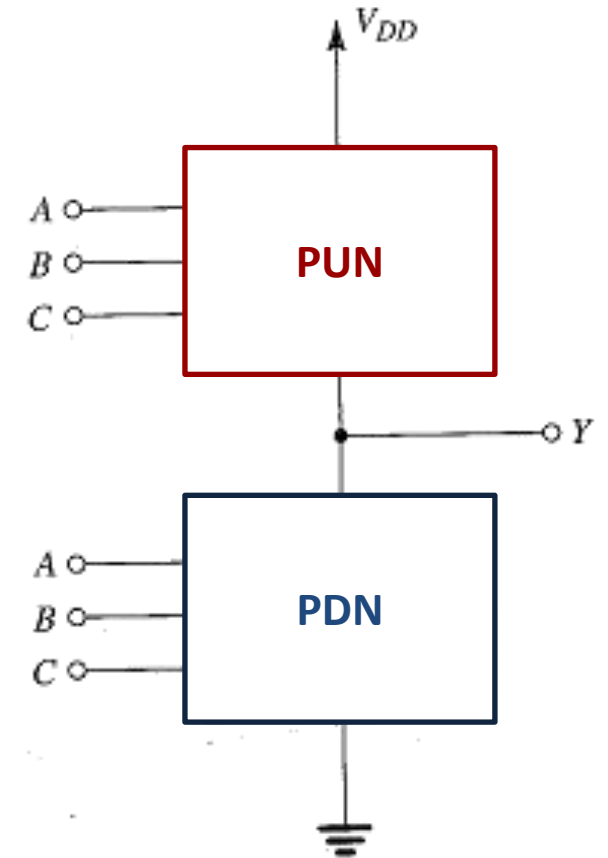



A Simple Inverter

- The most simple combinational CMOS logic gate is the INVERTER (INV)

A	Y
0	1
1	0



INV truth table

- PUN: pMOS
- PDN: nMOS

 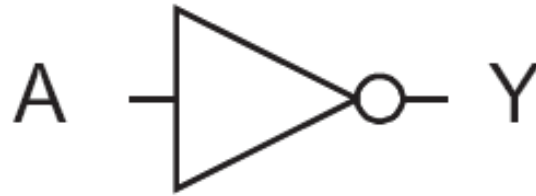

A Simple Linear Model

  - **Controlled switch** with an **internal resistance** between source and drain
- Characterized by two transfer functions
 - I_{DS} vs V_{GS} characteristics
 - I_{DS} vs V_{DS} characteristics
- **Small signal model**: only accurate over a small V_{DS} range
 -
- Still **often used** even for a large swing of V_{DS} **with a properly fitted R_{on}**





So why not this one?

- Can we also build a BUFFER (BUF) in a similar way?

A	Z
0	0
1	1


INV truth table

  

- PUN: nMOS
- PDN: pMOS

nMOS Operation

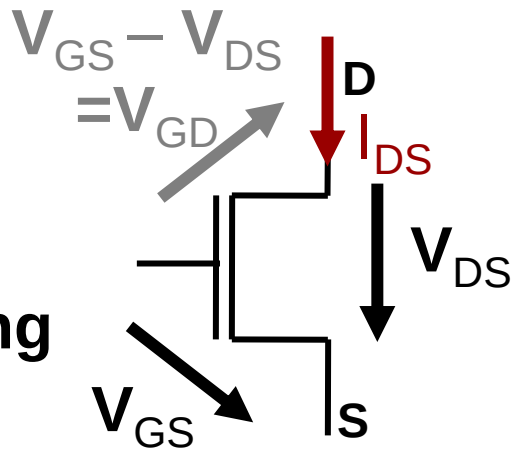- MOS transistor has three operating regions depending on V_{GS} and V_{DS}




$V_{Tn} > 0$: Threshold voltage of the nMOS transistor

SOURCE: most negative terminal

Cutoff:

$$V_{GS} < V_{Tn}$$

$$I_{DS} = 0$$

 

Linear:


(Resistor)

$$V_{GS} > V_{Tn}$$

$$V_{DS} < V_{GS} - V_{Tn}$$

$$V_{GD} > V_{Tn}$$

$$I_{DS} = \text{linear in } V_{DS}$$

 

Saturation:


(Current source)

$$V_{GS} > V_{Tn}$$

$$V_{DS} > V_{GS} - V_{Tn}$$

$$V_{GD} < V_{Tn}$$


 
$$I_{DS} = \sim \text{independent of } V_{DS}$$



pMOS vs. nMOS Operation

- **pMOS and nMOS operation are symmetric**

  - Source and drain swapped (nMOS: most negative terminal $\leftrightarrow$ pMOS: most positive terminal)
- All inequality conditions swapped




$V_{GS} < V_{Tn}$	Cutoff	$V_{GS} > V_{Tp}$
$V_{GS} > V_{Tn}$ $V_{DS} < V_{GS} - V_{Tn}$ $V_{GD} > V_{Tn}$	Linear	$V_{GS} < V_{Tp}$ $V_{DS} > V_{GS} - V_{Tp}$ $V_{GD} < V_{Tp}$
$V_{GS} > V_{Tn}$ $V_{DS} > V_{GS} - V_{Tn}$ $V_{GD} < V_{Tn}$	Saturation	$V_{GS} < V_{Tp}$ $V_{DS} < V_{GS} - V_{Tp}$ $V_{GD} > V_{Tp}$

Transistor Parameter

Design parameters

L : channel length

W : channel width

 


Technology parameters

V_T : Threshold voltage

C_{ox} : Oxide capacitance

μ_n, μ_p : Carrier mobility

 $k'_{n/p} = \mu_{n/p} * C_{ox}$: **Transconductance**




$\beta_{n/p} = k'_{n/p} \frac{W}{L}$: **Drive strength**

Shockley 1st Order nMOS and pMOS Models

- nMOS model:**

 
$$I_{DSn} = \begin{cases} 0 & V_{GS} < V_{Tn} & \text{cutoff} \\ \beta_n \left(V_{GS} - V_{Tn} - \frac{V_{DS}}{2} \right) V_{DS} & V_{GS} > V_{Tn} \quad V_{DS} < V_{GS} - V_{Tn} \quad V_{GD} > V_{Tn} & \text{linear} \\ \frac{\beta_n}{2} (V_{GS} - V_{Tn})^2 & V_{GS} > V_{Tn} \quad V_{DS} > V_{GS} - V_{Tn} \quad V_{GD} < V_{Tn} & \text{saturation} \end{cases}$$




- pMOS model:**

- Currents are reversed (since source and drain are swapped), $I_{DSp} < 0$
- Relation operators for operating region are swapped

 
$$I_{DSp} = \begin{cases} 0 & V_{GS} > V_{Tp} & \text{cutoff} \\ -\beta_p \left(V_{GS} - V_{Tp} - \frac{V_{DS}}{2} \right) V_{DS} & V_{GS} < V_{Tp} \quad V_{DS} > V_{GS} - V_{Tp} \quad V_{GD} < V_{Tp} & \text{linear} \\ -\frac{\beta_p}{2} (V_{GS} - V_{Tp})^2 & V_{GS} < V_{Tp} \quad V_{DS} < V_{GS} - V_{Tp} \quad V_{GD} > V_{Tp} & \text{saturation} \end{cases}$$



nMOS and pMOS I-V Characteristics

 

(a)

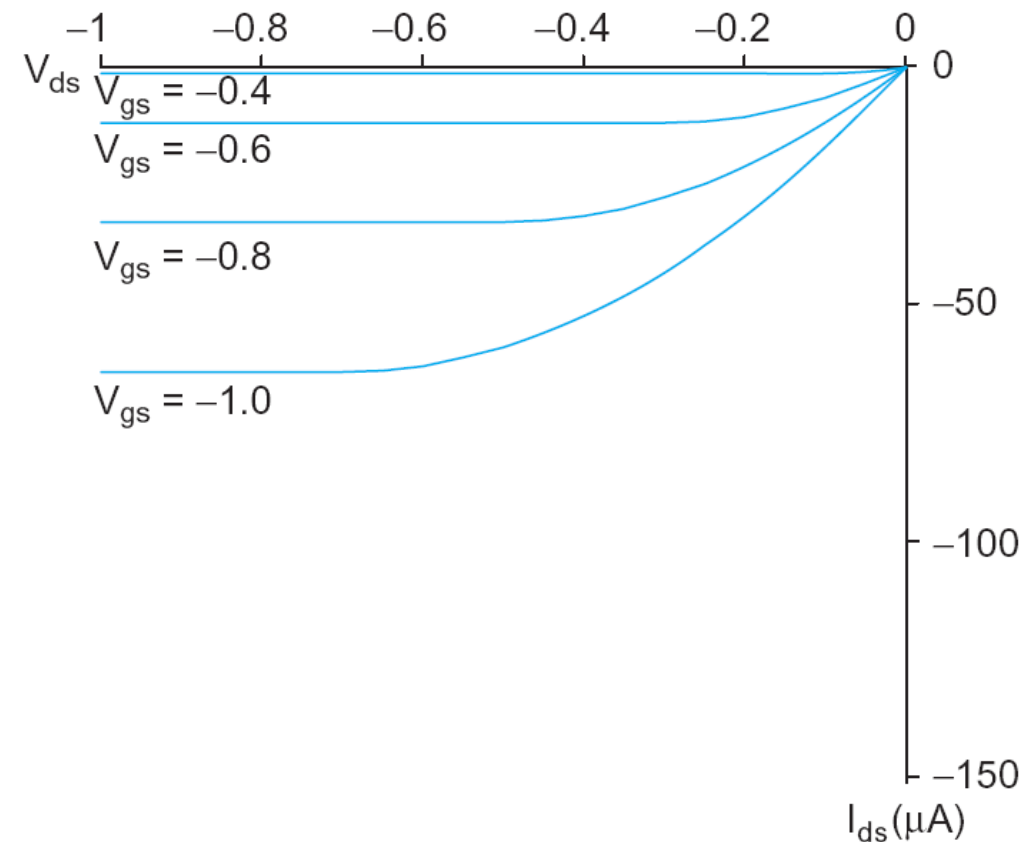


(b)


Implications of the MOS Transistor on CMOS Logic

- Realization of **PUN** and **PDN** from **nMOS** and **pMOS** determines if a function is
 - **Positive unate**: rising input causes rising output
 - **Negative unate**: rising input causes falling output
 - **Non unate**: rising input can cause both falling or rising output

negative unate


 


positive unate

 

  Problem of Positive Unate Functions in CMOS


- **Positive unate** (or non unate) functions **would imply** driving the output
 - to '0' with an pMOS or
 - to '1' with an nMOS
- **Unfortunately, for a pMOS**
 - A Gate-Source voltage $< V_t$ is needed to turn on the PDN and pull output low (non-inverting)
 - PDN network turns off before output reaches GND level



- The nMOS shows the opposite behavior

CMOS is Limited to Negative Unate Functions

 - **Driving a '0' with a pMOS or a '1' with an nMOS prevents rail-to-rail outputs**
 - pMOS is a good driver for a '1'
 - nMOS is a good driver for a '0'



EE-429

Fundamentals of VLSI Design

Inverter Voltage Transfer and DC Characteristic

Andreas Burg


CMOS Inverter VTC

- **Voltage Transfer Characteristic**


- Input-output relationship of a component (e.g., digital gate)
- DC characteristic (i.e., not immediately useful for dynamic considerations – no time aspect)

- **The VTC provides important information on**

 - Useful input range and achievable output range
- Voltage gain and sensitivity
- Voltage margins



$$V_{out} = f(V_{in})$$

 

CMOS Inverter VTC

- To construct the VTC of the CMOS inverter, we need to graphically superimpose the I-V curves of the nMOS and pMOS onto a common coordinate set.
- **Basic idea:** equal pMOS and nMOS current


$$I_{DSp} = -I_{DSn}$$

$$V_{GSn} = V_{in}$$

$$V_{GSp} = V_{in} - V_{DD}$$


$$V_{DSn} = V_{out}$$

$$V_{DSp} = V_{out} - V_{DD}$$

 

CMOS Inverter VTC

 - **Graphical approach:** transfer I-V curves of nMOS and pMOS into the same coordinate system
 - Start with the I-V characteristics of the nMOS transistor, parameterized on V_{in}




CMOS Inverter VTC

- **Graphical approach:** transfer I-V curves of nMOS and pMOS into the same coordinate system
 - More complex for pMOS since V_{in} , V_{out} , and I_{DSn} are only indirectly related to the pMOS I-V

$$I_{DSn} = -I_{DSp}$$


$$V_{out} = V_{DD} + V_{SDp}$$

$$V_{in} = V_{DD} + V_{GSp}$$

 



CMOS Inverter VTC

 - The **intersection of corresponding load lines**, where the currents of the nMOS and pMOS are equal, **shows the DC operating points**.
 - Putting all the intersection points on a graph with the corresponding output voltage will give us the CMOS inverter's VTC




CMOS Inverter VTC

  - The **intersection of corresponding load lines**, where the currents of the nMOS and pMOS are equal, **shows the DC operating points**.
 - Putting all the intersection points on a graph with the corresponding output voltage will give us the CMOS inverter's VTC
- **Different points on the VTC fall into different n/pMOS operating regions**



CMOS Inverter VTC: Operating Regions

 
- Analytical analysis requires **different equations for each operating region** due to the non-linear model



$$V_{in} < V_{Tn}$$

$$\left. \begin{aligned} V_{GS p} &= V_{in} - V_{DD} < V_{Tp} \\ V_{GD p} &= V_{in} - V_{out} < V_{Tp} \end{aligned} \right\} \rightarrow \text{Linear}$$

 
$$V_{GS n} = V_{in} < V_T \rightarrow \text{Cutoff}$$



Considering Long Channel Transistors with $V_T < V_{DD}/2$

CMOS Inverter VTC: Operating Regions

 
- Analytical analysis requires **different equations for each operating region** due to the non-linear model



$$V_{in} > V_{Tn}$$

$$\left. \begin{array}{l} V_{GS p} = V_{in} - V_{DD} < V_{Tp} \\ V_{GD p} = V_{in} - V_{out} < V_{Tp} \end{array} \right\} \rightarrow \text{Linear}$$

 
$$\left. \begin{array}{l} V_{GS n} = V_{in} > V_{Tn} \\ V_{GD n} = V_{in} - V_{out} < V_{Tn} \end{array} \right\} \rightarrow \text{Sat}$$



Considering Long Channel Transistors with $V_T < V_{DD}/2$

CMOS Inverter VTC: Operating Regions

 
- Analytical analysis requires **different equations for each operating region** due to the non-linear model



$$V_{in} > V_{DD}/2$$

$$\left. \begin{array}{l} V_{GS p} = V_{in} - V_{DD} < V_{Tp} \\ V_{GD p} = V_{in} - V_{out} > V_{Tp} \end{array} \right\} \rightarrow Sat$$

 
$$\left. \begin{array}{l} V_{GS n} = V_{in} > V_{Tn} \\ V_{GD n} = V_{in} - V_{out} < V_{Tn} \end{array} \right\} \rightarrow Sat$$



Considering Long Channel Transistors with $V_T < V_{DD}/2$

CMOS Inverter VTC: Operating Regions

 
- Analytical analysis requires **different equations for each operating region** due to the non-linear model



$$V_{in} < V_{DD} - V_{Tp}$$

$$\left. \begin{array}{l} V_{GS p} = V_{in} - V_{DD} < V_{Tp} \\ V_{GD p} = V_{in} - V_{out} > V_{Tp} \end{array} \right\} \rightarrow Sat$$

 
$$\left. \begin{array}{l} V_{GS n} = V_{in} > V_{Tn} \\ V_{GD n} = V_{in} - V_{out} > V_{Tn} \end{array} \right\} \rightarrow Linear$$



Considering Long Channel Transistors with $V_T < V_{DD}/2$

CMOS Inverter VTC: Operating Regions

 
- Analytical analysis requires **different equations for each operating region** due to the non-linear model



$$V_{in} > V_{DD} - V_{Tp}$$

$$V_{GSp} = V_{in} - V_{DD} > V_{Tp} \rightarrow \text{Cutoff}$$

 
$$\left. \begin{array}{l} V_{GSn} = V_{in} > V_{Tn} \\ V_{GDn} = V_{in} - V_{out} > V_{Tn} \end{array} \right\} \rightarrow \text{Linear}$$




Considering Long Channel Transistors with $V_T < V_{DD}/2$

CMOS Inverter VTC: Operating Regions

 - Analytical analysis requires **different equations for each operating region** due to the non-linear model



 - Towards the rails, one of the transistors is cut off, and the other is resistive.
- Once the cut off transistor starts conducting, it immediately is saturated.
- As we approach the middle input voltages, both transistors are saturated.
- The VTC slope is known as the Gain of the gate.



Considering Long Channel Transistors with $V_T < V_{DD}/2$

EE-429


Fundamentals of VLSI Design

Inverter DC Characteristic

Andreas Burg


Switching Threshold

- The **Switching Threshold, V_M** , is the point where $V_{in}=V_{out}$
 - Inverter has the largest gain at this point
 - Knowing V_M is desired to define threshold for delay measurements
 - Skewing V_M skews the delay for rising or falling
 - Placing V_M at $V_{DD}/2$ maximized noise margins
- **Graphical calculation:**
intersection of the VTC with $V_{in}=V_{out}$
- To understand the impact of design parameters on V_M we are interested in an analytical solution

 

Switching Threshold

 - **Analytical computation of V_M** : equating the currents through pMOS and nMOS
 - Switching threshold V_M lies around the point of **largest gain** (center of the VTC)



Switching Threshold

- **Analytical computation of V_M** : equating the currents through pMOS and nMOS
 - Switching threshold V_M lies around the point of **largest gain** (center of the VTC)
 - Both **pMOS** and **nMOS** in saturation


$$I_{DSn} = \frac{\beta_n}{2} (V_{in} - V_{Tn})^2$$

$$I_{DSp} = -\frac{\beta_p}{2} (V_{in} - V_{DD} - V_{Tp})^2$$

$$I_{DSn} = -I_{DSp}$$

- Threshold defined as $V_{in} = V_M$
 
$$\frac{\beta_n}{2} (V_M - V_{Tn})^2 = \frac{\beta_p}{2} (V_M - V_{DD} - V_{Tp})^2$$



Switching Threshold

- **Analytical computation of V_M**
 - Switching threshold lies around the point of largest gain (center of the VTC)
 - Both **pMOS** and **nMOS** in saturation

$$I_{DSn} = \frac{\beta_n}{2} (V_{in} - V_{Tn})^2$$

$$I_{DSp} = -\frac{\beta_p}{2} (V_{in} - V_{DD} - V_{Tp})^2$$

$$I_{DSn} = -I_{DSp}$$

- Threshold defined as $V_{in}=V_M$

$$\frac{\beta_n}{2} (V_M - V_{Tn})^2 = \frac{\beta_p}{2} (V_M - V_{DD} - V_{Tp})^2$$

Solving for V_M

$$V_M = \frac{V_{Tn} + r(V_{DD} + V_{Tp})}{1 + r}$$


$$r = \sqrt{\frac{\beta_p}{\beta_n}}$$

Switching Threshold

- **r is an important factor** in setting the switching threshold
- **r is set by the drive strength ratio** of nMOS and pMOS

$$r = \sqrt{\frac{\beta_p}{\beta_n}} \quad \beta_{n/p} = \mu_{n/p} C_{ox} \frac{W_{n/p}}{L_{n/p}}$$

 - **Using the current equations again, we can find the drive strength ratio for a desired V_M :**
 - $\mu_{n/p}$ are technology parameters
 - $W_{n/p}$ and $L_{n/p}$ are controlled by the designer



$$\frac{\beta_p}{\beta_n} = \left(\frac{V_M - V_{Tn}}{V_{DD} - V_M + V_{Tp}} \right)^2$$

Switching Threshold Optimization


- A **symmetric VTC** ($V_M = V_{DD}/2$) is often desired.
 - In practice, **we often find** that $\mu_n > \mu_p$ and hence
- **Adjust the switching threshold** with **W** and **L** of nMOS and pMOS
 - Consider $V_{Tn} = -V_{Tp} = V_T$

$$\frac{\beta_p}{\beta_n} = \left(\frac{\frac{V_{DD}}{2} - V_T}{V_{DD} - \frac{V_{DD}}{2} - V_T} \right)^2 = 1 \quad \longrightarrow \quad \frac{W_p}{L_p} = \frac{\mu_n}{\mu_p} \left(\frac{W_n}{L_n} \right)$$

- For **digital circuits**, we often use **minimum length** (L_{min}) to maximize drive
 - **Adjust** only the **width of the weaker pMOS** to compensate the drive mismatch $\frac{W_p}{W_n} = \frac{\mu_n}{\mu_p} \approx 2 \dots 4 \quad W_p = W_n \frac{\mu_n}{\mu_p}$

Impact of Noise on Synchronous Digital Circuits

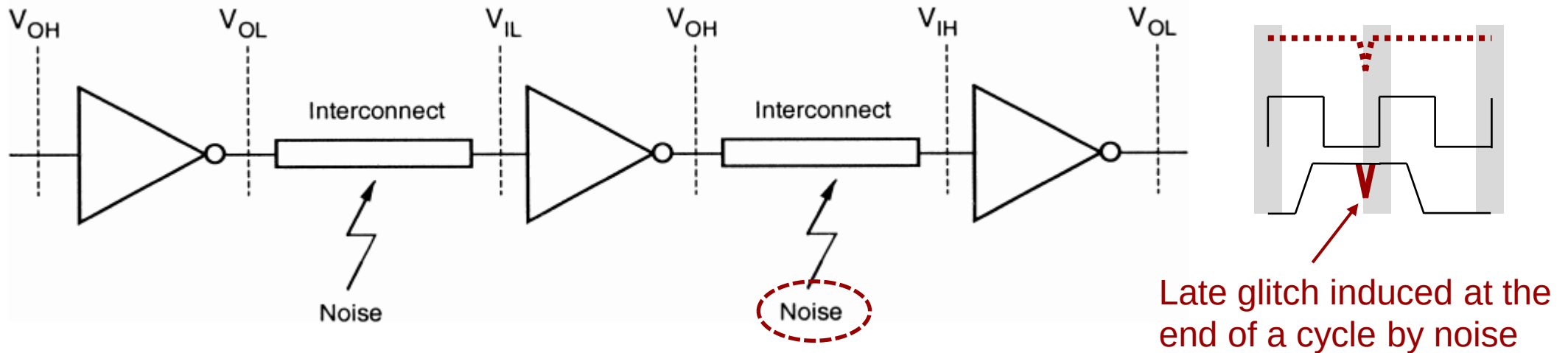
- In practice, **digital circuits are affected by noise** (e.g., coupling or supply noise)
 - Other non-idealities affecting the output levels of a gate may also be understood as noise



- **Noise may increase the delay OR may cause failures in synchronous systems** due to transitions from noise late in the clock cycle
- **Reducing** the impact and **propagation of noise** improves stability

Propagation of Noise

 - Inject noise at the input of a gate.
- **How does** this **noise propagate** to the output of the gate?




- Large gain in the **transition region** amplifies the noise

$$\left. \frac{\partial V_{out}}{\partial V_{in}} \right|_{V_{in}=V_{DD}/2} \gg 1$$



- Saturation to the rails limits gain and attenuates the noise

$$\left. \frac{\partial V_{out}}{\partial V_{in}} \right|_{V_{in}=0, V_{DD}} \ll 1$$

 

Noise Margins

 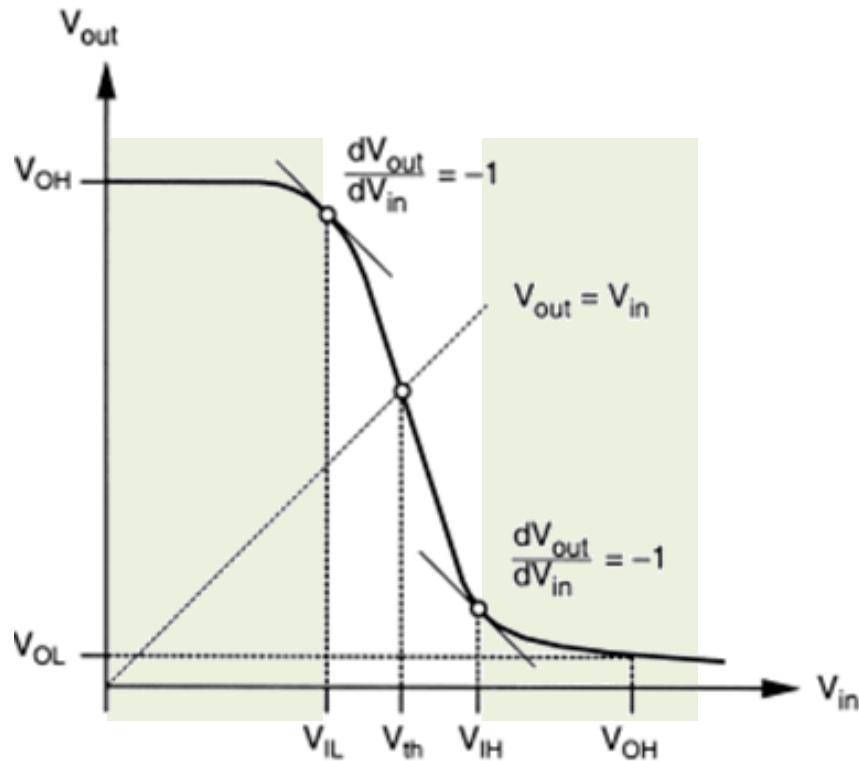- **Noise insensitive region** of a gate: $\frac{\partial V_{out}}{\partial V_{in}} \ll 1$
- **Noise margin**: margin between the min/max high/low output of one gate and the noise insensitive region of the next gate



$$NM_H = V_{OH\ min} - V_{IH}$$

$$NM_L = V_{IL} - V_{OL\ max}$$

Analytical Derivation of Noise Margins

- Assume **balanced inverter**: $\beta_n = \beta_p = \beta$ and $V_{Tn} = -V_{Tp} = V_T$
- Find the **unit-gain points** of the VTC
 - Consider only V_{IH}
 - nMOS linear, pMOS saturation


$$I_{DSn}(res) = \cancel{\beta} \left[(V_{in} - V_T)V_{out} - \frac{V_{out}^2}{2} \right] = -I_{DSp}(sat) = \cancel{\beta} \frac{(V_{in} - V_{DD} + V_T)^2}{2}$$

- Note that **β does not impact the NM** if the inverter is **balanced**
- Obtain $\frac{\partial V_{out}}{\partial V_{in}}$ through **implicit derivation** (without the need to first solve for $V_{out} = \dots$).
- Set $\frac{\partial V_{out}}{\partial V_{in}} = -1$ and solve for V_{in}

$$\rightarrow V_{IH} = \frac{1}{8}(5V_{DD} - 2V_T)$$

$$\rightarrow V_{IL} = \frac{1}{8}(3V_{DD} + 2V_T)$$
 
$$NM_H = NM_L \approx V_{DD} - V_{IH} = V_{IL} - 0 = \frac{1}{8}(3V_{DD} + 2V_T)$$



EE-429



Fundamentals of VLSI Design

Inverter Dynamic Characteristics

Andreas Burg


Origin of Delay in Digital Circuits

 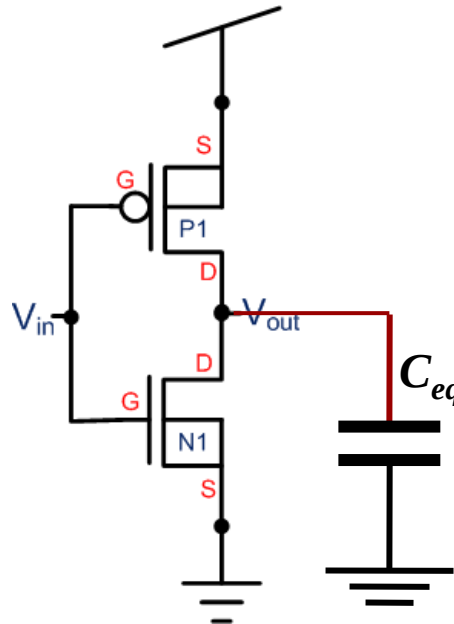- DC characteristic only indicates the steady-state behaviour
 - Capacitances are removed (replaced by an open circuit)
- **For the dynamic behaviour** (speed) of a circuit, **capacitances play a major role**
 - **Time to charge/discharge the load** (output capacitance) of a circuit **determines the speed**



Delay Parameters



- **Delays impact the speed of a digital circuit**
- **Propagation Delay:**
 - **Measures the delay from** 50% transition point at the **input** to the 50% transition point at the **output**
 - Often different for rise-rise, rise-fall, fall-rise, fall-fall
 - Measured between 2 signals
- **Rise/Fall Time:**
 - **Time for a transition from** 10%-to-90% or 90%-to-10% of the full swing
 - Measured on one signal only

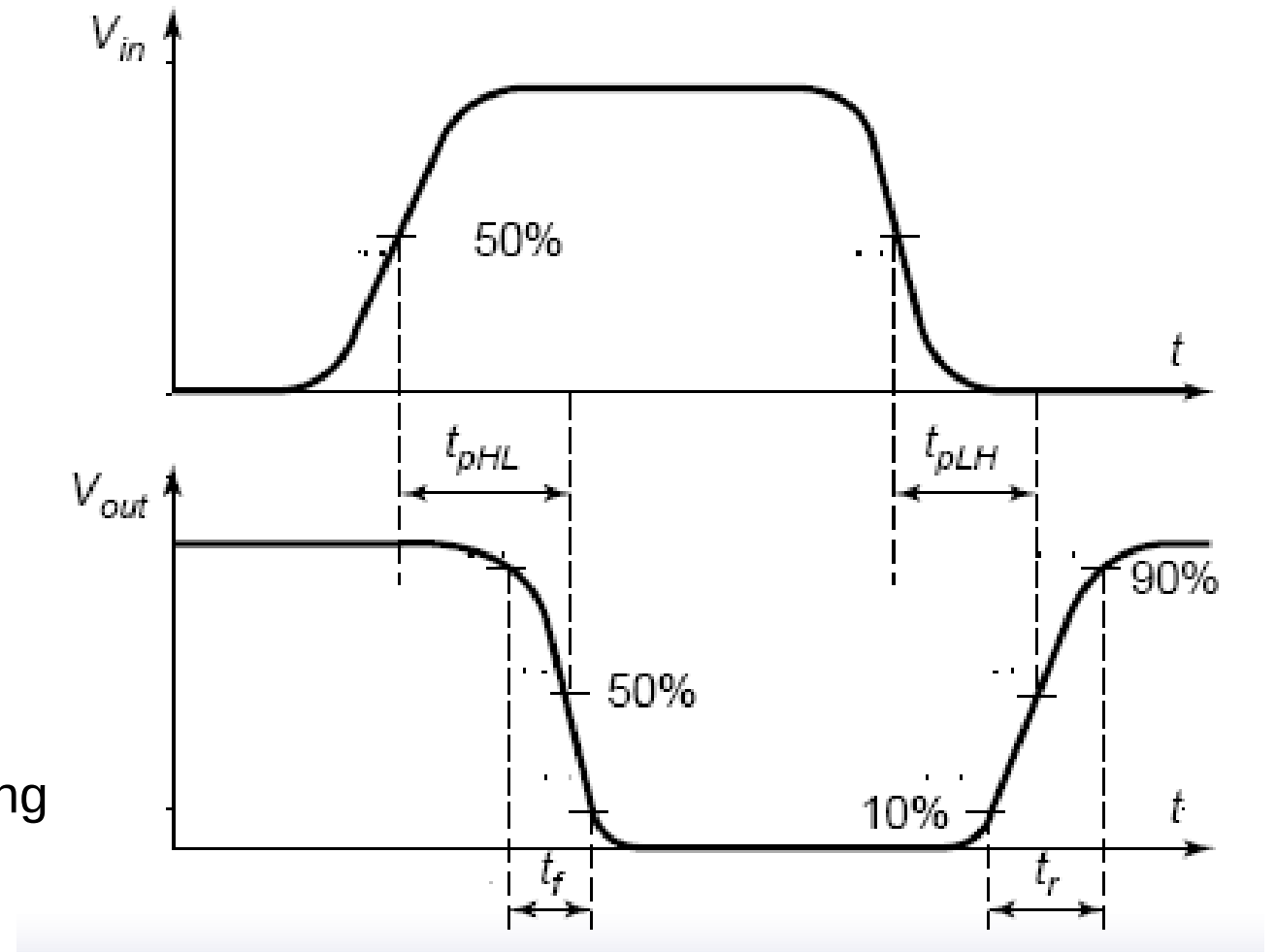

Parasitic Capacitances

- The **capacitive load** C_{load} on a gate results **from three main origins**
 - Intrinsic capacitance** C_{INT} from the **transistors of the driving gate**
 - Wire capacitance** from the **connected routing wires**
 - Input load** of the connected (driven) **gate(s)**

Extrinsic: C_{EXT}

  

$$C_{load} = C_{out} + C_{wire} + N \cdot C_{in}$$

Parasitic Capacitance of Transistors



- **Intrinsic capacitance** and **input load** are caused by MOS transistors and **depend on transistor parameters**

- Unfortunately, MOS capacitors are highly non-linear and depend on terminal voltages (non-constant)
- For better intuition, we use **a simple constant capacitance model that only scales with transistor geometries**

- Dominant capacitances:



- **Gate/Channel Capacitance:** capacitance caused by the insulating oxide layer under the gate $\sim \underline{W} \cdot \underline{L}$
- **Junction Capacitance:** pn-Junction capacitance between the diffusions and the substrate $\sim \underline{W} \cdot D_{drain}$

  - **Larger transistors also bring larger load**





Gate and Diffusion Capacitances

  - Affects delay of previous gate
- Approximate channel as connected to source
- $C_{gs} = \epsilon_{ox} WL / t_{ox} = C_{ox} WL \sim W \cdot L$
- Affects delay of same gate
- Depends on area $\sim W \cdot D_{drain}$ & perimeter
 - Use small diffusion nodes
 - Comparable to C_g for contacted diff
 - $\frac{1}{2} C_g$ for uncontacted



A Simple Delay Model: Current Source Model

  - **Simplest delay model** considers **transistor as a current source** assuming it operates in saturation during the entire transition
 - Transition measured from V_{DD} to $V_{DD}/2$




$$t_{HL} = \frac{C_L \cdot \frac{V_{DD}}{2}}{I_{DS}} = \frac{C_L \cdot V_{DD}}{\beta (V_{DD} - V_{Tn})^2}$$



The RC Delay Model

- Unfortunately, the **current source model**

 - Produces a rather inaccurate waveform
- Becomes inaccurate with more sophisticated transistor models (e.g., long channel models)




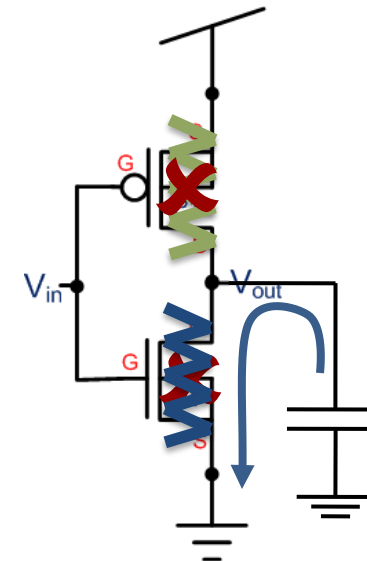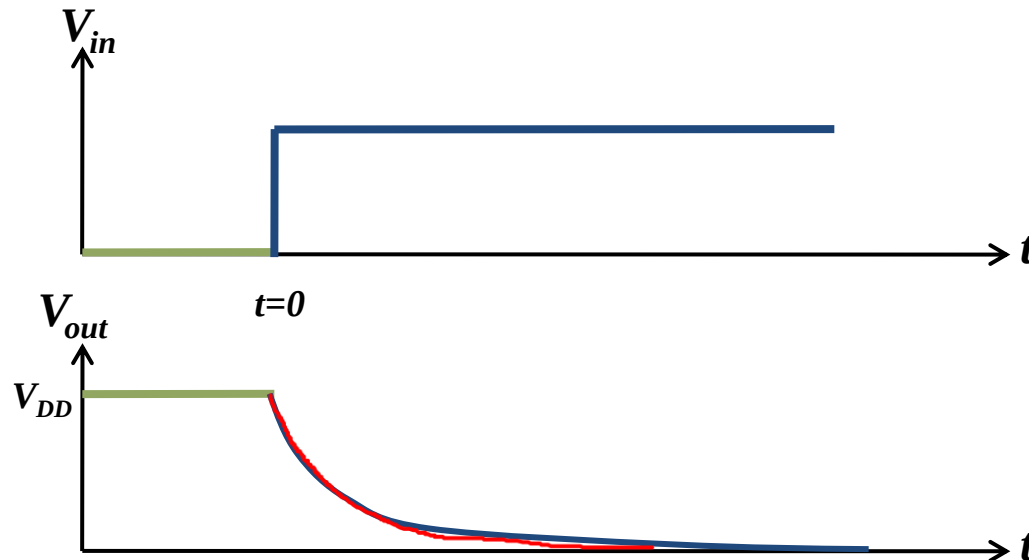- Better model: replace driving transistor with an equivalent resistor**



Delay of an RC Network

 - Delay can be derived from well-known equations from RC networks



$$V_{out}(\uparrow) = V_{DD} \left(1 - e^{-\frac{t}{RC}}\right)$$

$$V_{out}(\downarrow) = V_{DD} e^{-\frac{t}{RC}}$$

Time required to reach x%:

$$x = e^{-\frac{t}{RC}} \rightarrow t = -R \cdot C \cdot \ln x$$


50% rise/fall delay:

$$t_{50\%} = R \cdot C \cdot 0.69$$

Computing an Equivalent Resistance

- **On-resistance** of the MOSFETS **changes** during transition
- **Use** an **equivalent resistance** reflecting a good average of the transition region
 - Start from onset of the transition: $V_{out} = V_{DD}$
 - Up to the midpoint: $V_M \approx V_{DD}/2$
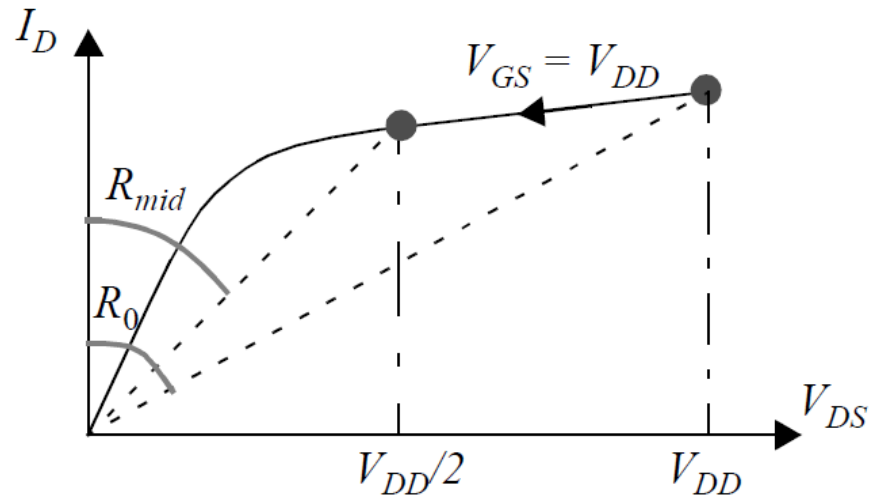
$$R_{eq} = \text{average}_{t=t_1 \dots t_2} (R_{on}(t)) = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} R_{on}(t) dt = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} \frac{V_{DS}(t)}{I_{DS}(t)} dt$$



$$\approx \frac{1}{2} [R_{on}(t_1) + R_{on}(t_2)]$$


$$R_{eqn} = \frac{1}{V_{DD}/2} \int_{V_{DD}/2}^{V_{DD}} \frac{2V_{DS}}{\beta_n (V_{DD} - V_T)^2} dV_{DS} \approx \frac{3}{2} \frac{V_{DD}}{\beta_n (V_{DD} - V_T)^2}$$

Propagation Delay with Equivalent Resistance

- Analyze the parameters that affect the propagation delay:

$$t_{pHL} = 0.69 \cdot \frac{3}{2} \frac{V_{DD}}{\beta_n (V_{DD} - V_T)^2} C_{load} = 1.035 \frac{L}{W} \frac{1}{k_n} \frac{V_{DD}}{(V_{DD} - V_T)^2} C_{load}$$

 - Accordingly, we can minimize the delay in the following ways:
 - Minimize C_{load}
 - Increase W/L typically by making W wider
 - Increase V_{DD}




Effect of Device Sizing

- To reduce propagation delay, it is tempting to increase the device width **W**
- **At the same time we usually need $\beta_p > \beta_n$ to compensate for the mobility ratio of holes and electrons for a balanced inverter**
 - This generally equates the propagation delay of High-to-Low and Low-to-High transitions.
 - However, this does not imply that this ratio yields the minimum overall propagation delay.
- **For this, we will discuss **two** sizing parameters:**
 - **Beta Ratio ($\beta = \beta_p / \beta_n$):** ratio between pMOS and nMOS drive strength
 - **Upsizing Factor (**S**):** ratio of the nMOS to a minimum-size nMOS

pMOS/nMOS Ratio

- Consider the **average propagation delay** for rise and fall
 
$$t_{pd} = \frac{t_{pLH} + t_{pHL}}{2} = \frac{0.69C_{load}(R_{eqp} + R_{eqn})}{2}$$



- With $W_p = W_n$, we get an **unbalanced inverter** since $\mu_p < \mu_n$ which leads to
 - $V_M < V_{DD}/2$
 - $R_{eqp} > R_{eqn}$ and therefore $t_{pdr} > t_{pdf}$
- We usually **enlarge** the pMOS to get a **“balanced” inverter** setting $W_p = W_n\gamma$ with $\gamma \approx 2 \dots 4$ for $V_M = V_{DD}/2$
- It is worth asking: **is the balanced inverter also the fastest?**


Optimizing pMOS/nMOS Ratio for Minimum Delay

- Consider **two identical cascaded CMOS inverters**:

- The load capacitance on the driving gate is:

$$C_{load} = C_{out1} + C_{in2} + C_{wire}$$

 - The **input capacitance of the 2nd gate C_{in2}** and the **output capacitance of the driving gate C_{out1}** **contain both pMOS and nMOS parasitics**



$$C_{load} = (C_{dp1} + C_{dn1}) + (C_{gp2} + C_{gn2}) + C_{wire}$$

- Gate and drain **capacitances scale linear in the width** of the transistors

$$C_{dn1} \sim W_n \quad C_{dp1} \sim W_p = \gamma W_n$$

$$C_{gn1} \sim W_n \quad C_{gp1} \sim W_p = \gamma W_n$$

$$C_{load} = (1 + \gamma)(C_{dn1} + C_{gn2}) + C_{wire}$$

Optimizing pMOS/nMOS Ratio for Minimum Delay

- Formulate the **propagation delay**, including the **impact of γ on the parasitics and on the pMOS** $R_{eqp}(W_n\gamma) = R_{eqp}(W_n)/\gamma$

$$t_{pd} = \frac{0.69C_{load}}{2} (R_{eqn} + R_{eqp}) = \frac{0.69}{2} [(1 + \gamma)(C_{dn1} + C_{gn2}) + C_{wire}] \left(R_{eqn} + \frac{R_{eqp}(W_n)}{\gamma} \right)$$

- Find γ to minimize the delay: $\frac{\partial t_{pd}}{\partial \gamma} = 0$


$$\gamma_{opt} = \sqrt{\frac{R_{eqp}(W_n)}{R_{eqn}} \left(1 + \frac{C_{wire}}{C_{dn1} + C_{gn2}} \right)} \Bigg|_{(C_{dn1} + C_{gn2} \gg C_{wire})} \rightarrow \sqrt{\frac{R_{eqp}}{R_{eqn}}}$$

- A **typical optimum** γ_{opt} is usually **around 2**

Optimizing pMOS/nMOS Ratio for Minimum Delay

- **Balanced inverter** usually does **not** provide **the shortest delay**

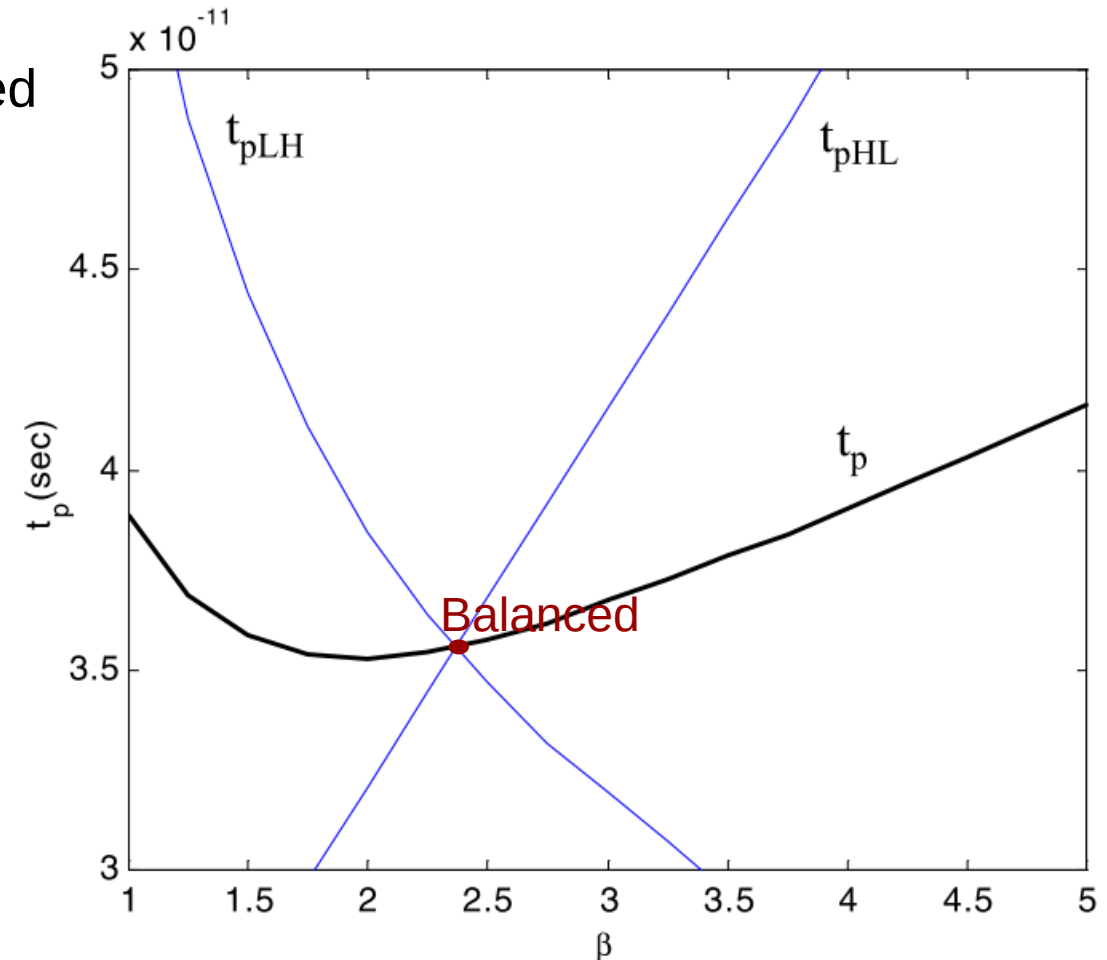- Delay penalty compared to a delay-optimized inverter is often small.



Impact of Device Sizing on Delay

- **Recap:** pMOS/nMOS ratio can be optimized to minimize delay
 - The balanced inverter is not always optimal, but often close
- See how **upsizing both pMOS and nMOS** affects the delay?
- Consider a **minimum size balanced** (γ_0 for $V_M = V_{DD}/2$) **inverter as reference**
 - $W_n^0 = W_{min}$, $W_p^0 = \gamma_0 W_{min}$, $L_{n/p}^0 = L_{min}$

Common upsizing factor S

$$W_p = S W_p^0 \quad W_n = S W_n^0$$

$$C_{int}(S) = S \cdot C_{int}^0$$

$$R_{eq}(S) = R_{eq}^0 / S$$

Impact of Device Sizing on Delay

- Start by writing the delay as a function of the **intrinsic capacitance** and the **external capacitances** (fanout and wiring)
 - **Intrinsic capacitance**: scales with S compared to that of a minimum size inverter
 - **External capacitance**: constant

$$C_{load} = C_{int}(S) + C_{ext}$$


$$t_{pd} = 0.69 \cdot R_{eq}(S) \cdot C_{load} = 0.69 \cdot R_{eq}(S) \cdot [C_{int}(S) + C_{ext}]$$

$$= 0.69 \cdot \frac{R_{eq}^0}{S} [S \cdot C_{int}^0 + C_{ext}]$$

$$= \underbrace{0.69 \cdot R_{eq}^0 \cdot C_{int}^0}_{t_{p0}} \cdot \left(1 + \frac{C_{ext}}{S \cdot C_{int}^0}\right) = t_{p0} \left(1 + \frac{C_{ext}}{S C_{ref}}\right)$$

Impact of Device Sizing on Delay

 - The intrinsic delay of an inverter (t_{p0}) is independent of the sizing of the gate and is purely determined by technology.
- When no load is present, an increase in the drive of the gate is totally offset by the increased capacitance.
- **Upsizing becomes relevant once the external capacitance starts to dominate**



EE-429

Fundamentals of VLSI Design

CMOS Power Consumption

Andreas Burg, Alexandre Levisse

CMOS: Two Types of Power Consumption


- **CMOS circuit power/energy consumption comes in two forms:**
 - **Dynamic energy/power consumption:** depends on activity
 - Charging and discharging of capacitors
 - Cross (short-circuit) currents while pMOS and nMOS are on during switching
 - **Static power consumption:** independent from activity
 - Constant biasing currents (intentional)
 - Various types of leakage currents (parasitic)
 - Contention currents when driving opposite directions (mostly accidents)

Basic Inverter (Unloaded)

- PMOS performs pull-up to V_{DD} , NMOS performs pull-down to GND

- Complementary gate


 
- Static (steady state): **output connected to either V_{DD} or GND**



- Ideally, no current path from V_{DD} to GND : ideally, no static power consumption

CMOS Gates With Capacitive Load

 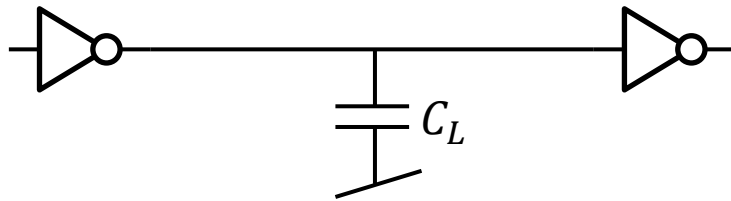- **Every CMOS gate sees a capacitive load from various sources**
 - **Intrinsic** MOS transistor capacitors (driver)
 - **Extrinsic** (fanout) MOS transistor capacitances
 - **Interconnect** capacitance
- **Various load capacitances are merged into a single load capacitor C_L**



- Wider transistors increase the gain factor (drive) but also increase the load (capacitance)

Energy of an Inverter with Capacitive Load

- **Switching** the **output from 0 to 1** charges the capacitor

- Energy delivered by the power supply

$$E_{VDD} = \int_0^\infty I(t)V_{DD}dt = \int_0^\infty C \frac{dV}{dt} V_{DD}dt = CV_{DD} \int_0^{V_{DD}} dV = CV_{DD}^2$$

- Once the output transition is complete, the energy stored on the capacitor is given by


$$E_C = \frac{1}{2} CV_{DD}^2$$

- Energy difference is dissipated to heat in pMOS


- **Switching** the **output from 1 to 0** discharges the capacitor

- Energy on capacitor is dissipated to heat in nMOS

 - **NOTE: energy consumption is independent of the waveform**



Active Energy Consumption Waveforms

 

Active Power/Energy Consumption

- Energy consumed during one pair of transitions $E_{\downarrow\uparrow}$:

$$E_{\downarrow\uparrow} = (CV_{dd})V_{dd} = CV_{dd}^2$$

- Energy/transition

$$E_t = CV_{dd}^2/2$$

- **Average power consumption:** energy per time T

- Depends on the switching frequency f_{sw} of the output $P_{sw} = \frac{E_t}{T} = \frac{2f_{sw}TCV_{dd}^2/2}{T} = f_{sw}CV_{dd}^2$
- **Activity factor α :** average number of transitions per cycle
 - Relates activity of a node to the clock frequency f_{clk}
 - Energy/transition * average-transition/cycle (α) * clock frequency (f_{clk})


$$P = \frac{\alpha}{2} CV_{dd}^2 f_{clk}$$

Short Circuit Currents

- CMOS gates have a large, but **finite gain** in the transition region
 - Cross-over currents lead to power consumption** during transients

PROBLEMATIC


range	applies when	n-channel ▼	p-channel ▲
A	$0 \leq U_{inp} \leq U_{th\,n}$	subthreshold	linear
B	$U_{th\,n} < U_{inp} < U_{inv}$	saturation	linear
C	$U_{inp} \approx U_{inv}$	saturation	saturation
D	$U_{inv} < U_{inp} < U_{dd} + U_{th\,p}$	linear	saturation
E	$U_{dd} + U_{th\,p} \leq U_{inp} \leq U_{dd}$	linear	subthreshold

 


Dominant during transition region:
rapid opening of the driver for the new level

- Note:** short-circuit power is irrelevant if


$$V_T < \frac{V_{DD}}{2}$$

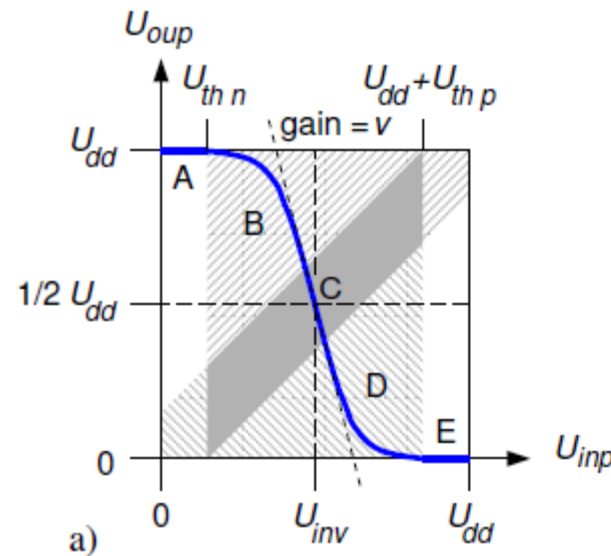

a)

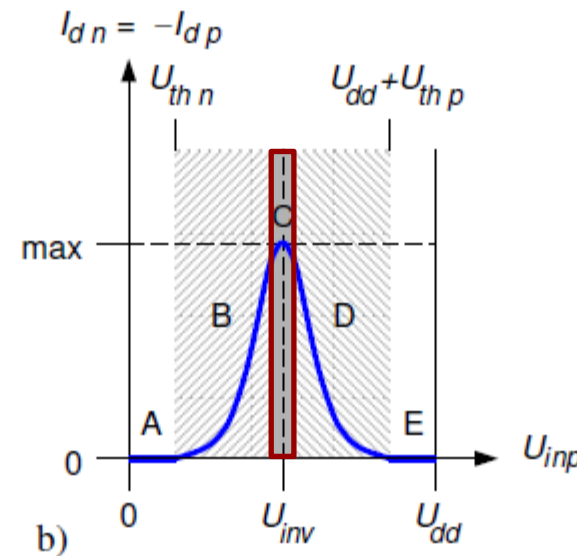

b)



 


c)

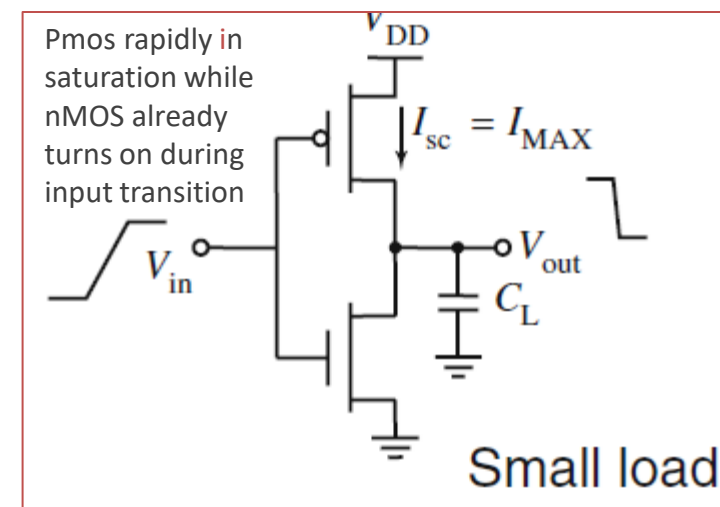  (a) Transfer characteristic (b) Crossover current (c) Logic states

Minimizing Short-Circuit Currents





- **Obvious approach:** reduce input transition time
 - However, short input transitions require stronger driver => increase transition time (and load) on the driver of the driver
- **Control short circuit current by controlling the output slope:**
 - Fast input slow output: driving device mostly in linear regime => good for low power
 - Slow input fast output: driving device remains long in saturation => bad for low power



- **Best compromise: balance input slope and output slope**

Leakage Power

    - Transistors leak currents even when in off-state
- Sources for leakage
 - Sub-threshold leakage
 - Dominant component in most circuits
 - Gate tunneling
 - Generally low, even in modern technologies due to high-k gate dielectrics
 - Decreases very rapidly with decreasing V_{dd}
 - Junction current
 - Generally low
 - Decreases very rapidly with decreasing V_{dd}




Leakage Power

- Long channel deices (>130nm)

$$I_{DS} = I_0 e^{\frac{V_{GS} - V_T}{v_t n}}$$

v_t : thermal voltage
 n : constant

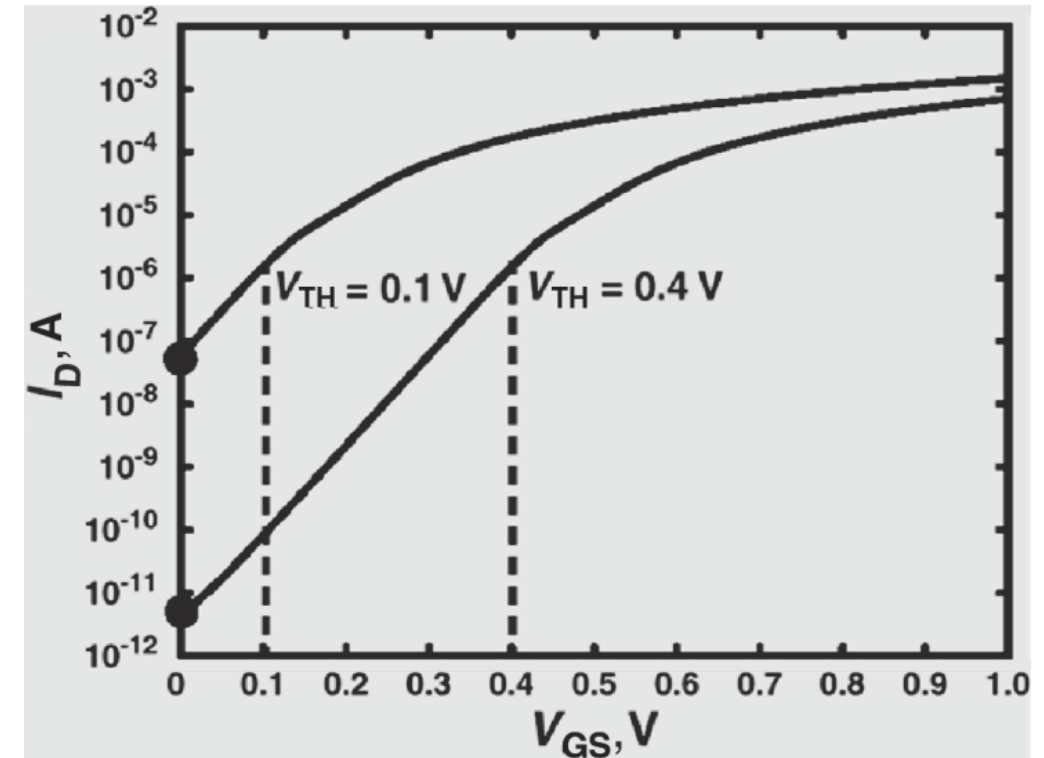- I_{DS} mostly independent from Drain-Source voltage
- Leakage current depends strongly on $V_{GS} - V_T$
 - Lower threshold voltage increases leakage
 - Higher threshold voltage decreases leakage
- **Subthreshold slope**: slope of the logarithmic leakage current for $V_{GS} - V_T < 0$





Leakage Power over Temperature

- Sub-threshold current depends exponentially on **thermal voltage** $v_t = kT/q$

$$I_{DS} = I_0 e^{\frac{V_{GS} - V_{th}}{kTn/q}}$$

  
- Exponential sub-threshold leakage (I_{DS}) increase with temperature**



 Example: 0.7V, 100nm
process, 15mm² die

Leakage Power (DIBL)


- **Impact of technology scaling on sub-threshold leakage (<130nm)**
 - Drain-Induced Barrier Lowering (DIBL): V_{DS} modulates threshold voltage
 - I_{DS} becomes a function of V_{DS}



$$I_{DS} = I_0 e^{\frac{V_{GS} - V_{th} + \lambda_{DS} V_{DS}}{v_t n}}$$

λ_{DS} : DIBL coefficient
 v_t : thermal voltage
 n : constant

 - **Impact on inverter leakage:** no longer supply independent



$$I_{leak} = I_0 e^{\frac{-V_{th} + \lambda_{DS} V_{DD}}{v_t n}}$$

Reducing voltage
reduces leakage

Leakage in Transistor Stacks (Short Channel)


- **Stacking occurs**

- In many logic gates (> 1 input)
- When introduced intentionally for leakage reduction

$$I_{leak,M1} = I_0 e^{\frac{-V_M - V_{th} + \lambda_{DS}(V_{dd} - V_M)}{v_{tn}}}$$

$$I_{leak,M2} = I_0 e^{\frac{-V_{th} + \lambda_{DS}V_M}{v_{tn}}}$$

Small speed
penalty: ~25%

 

Leakage Reduction	
2 NMOS	9
3 NMOS	17
4 NMOS	24
2 PMOS	8
3 PMOS	12
4 PMOS	16

