

EE-429

Fundamentals of VLSI Design

Complex Logic Gates

Andreas Burg, Alexandre Levisse

CMOS Has Many Advantages

- Full rail-to-rail swing: **high noise margins**
- Logic levels not dependent upon the relative device sizes: **ratioless**
- Always a path to Vdd or Gnd in steady state: **low output impedance**
- Extremely high input resistance: **nearly zero** steady-state **input current**
- No direct path steady state between power and ground: **no static power** dissipation
- Propagation **delay is function of** load **capacitance and resistance** of transistors

Basic CMOS Logic Principal

- With the switch model, we can construct the basic CMOS gates


- **Basic idea:**

- Start from the truth table (input/output relationship)
 - **Pull-Up network (PUN):**
Connect OUT to VDD for input combinations that lead to a '1'
 - **Pull-Down network (PDN):**
Connect OUT to GND for input combinations that lead to a '0'

A/B/C	000	001	010	011	100	101	110	111
Y	0/1	0/1	0/1	0/1	0/1	0/1	0/1	0/1







- **PUN and PDN are dual logic networks**

 - In steady state, only either VDD OR GND are connected to the output → no short circuit current



Impact of Limiting to Negative Unate Gates

  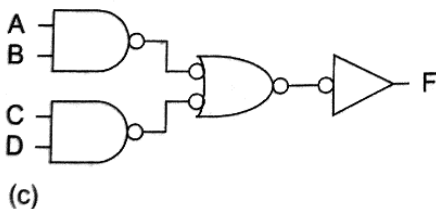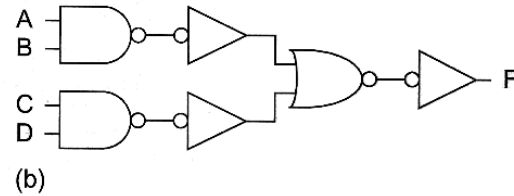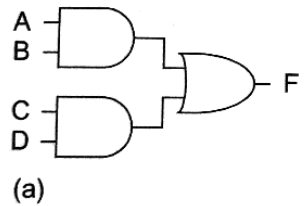 - All logic stages must be inherently inverting
- Two options/tools to achieve this:
 - Using inverted input signals
 - Bubble pushing
 - Start by replacing all AND / OR gates with NAND / NOR followed by an inverter
 - Propagate inversions through the netlist and substitute gates based on DeMorgan's Laws




$$\overline{A \cdot B} = \bar{A} + \bar{B}$$

$$\overline{A + B} = \bar{A} \cdot \bar{B}$$

Example: NAND Gate

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

Truth Table of a 2 input NAND gate

 


PDN: $G = A B \Rightarrow$ Conduction to GND

PUN: $F = \overline{A} + \overline{B} = \overline{AB} \Rightarrow$ Conduction to V_{DD}

$$\overline{G(In_1, In_2, In_3, \dots)} \equiv F(\overline{In_1}, \overline{In_2}, \overline{In_3}, \dots)$$


General CMOS Gate Design

 1. Get into inverted form.
2. Design SERIES/PARALLEL $\Leftrightarrow$ AND/OR circuit for NMOS pull-down
3. Design the Dual circuit for the PMOS pull-up




P-channel side: AND $\Rightarrow$ Parallel
OR $\Rightarrow$ Series

 
N-channel side: AND $\Rightarrow$ Series
OR $\Rightarrow$ Parallel




$Y = X$ if A and B

 

$Y = X$ if A OR B

 

 $Y = X$ if $\bar{A}$ AND $\bar{B} = \overline{A + B}$



$Y = X$ if $\bar{A}$ OR $\bar{B} = \overline{AB}$

General CMOS Gate Design


Example: $f = \overline{a \cdot b + c}$

N-channel (pull-down)

Format: $\overline{(\text{Ands}, \text{Ors})}$

$$f = \overline{a \cdot b + c}$$

 (a AND b) OR c
↓ ↓
(a SERIES b) PARALLEL c




PDN is **inverting** function with
uncomplemented inputs

P-channel (pull-up)

Format: DUAL((a AND b) OR c)

(a PARALLEL b) SERIES c

 


PUN is **non-inverting** function
with **complemented inputs**

Example Synthesis of a Complex Gate

- Consider the following Boolean function

$$F = \overline{D + A \cdot (B + C)}$$

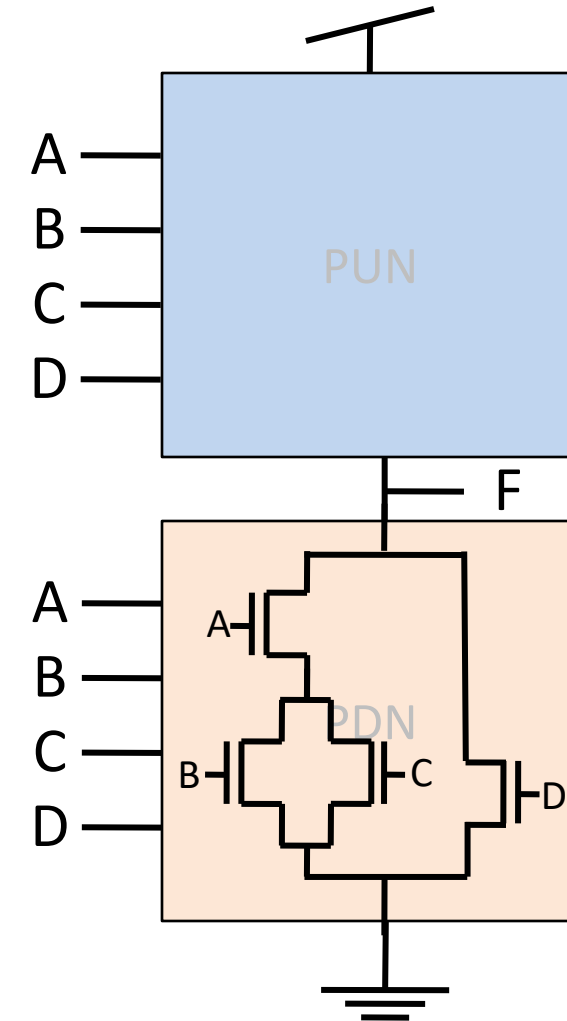- Function is *inverting* with *uncomplemented inputs*, so we can immediately derive the **PDN** from the given function.
- B** and **C** are *parallel*
- A** is in *series* with the **B+C** network
- D** is *parallel* to the **A(B+C)** network.




Synthesis of a complex gate

- Next: use *DeMorgan* to derive the *PUN*:



$$\begin{aligned} F &= \overline{D + A \cdot (B + C)} = \overline{D} \cdot \overline{A \cdot (B + C)} = \\ &= \overline{D} \cdot (\overline{A} + \overline{B + C}) = \overline{D} \cdot (\overline{A} + \overline{B} \cdot \overline{C}) \end{aligned}$$

 - Our *PUN* function is *non-inverting* with *complemented* inputs.
 - B* and *C* are in *series*
 - A* is *parallel* with the *BC* network
 - D* is in *serial* with the *A+(BC)* network.
- The PUN can also be derived from the PDN




Transistor Sizing for Complex Gates (Static)

- Similar to the inverter, we **first aim for a balanced gate**
 - **Upsizing** comes as a second step: **increase of all transistor sizes by a common factor S**
- Unfortunately, even the **VTC** of a complex gate **depends on all inputs**
- **Example VTC: 2-input NAND** (with compensated μ_p/μ_n)
 - VTC (**transition of a single input**) **depends on state of other inputs**
 - However, **differences are small**
 - **Concurrent input changes have the strongest impact**

  


Transistor Sizing for Complex Gates (Dynamic)

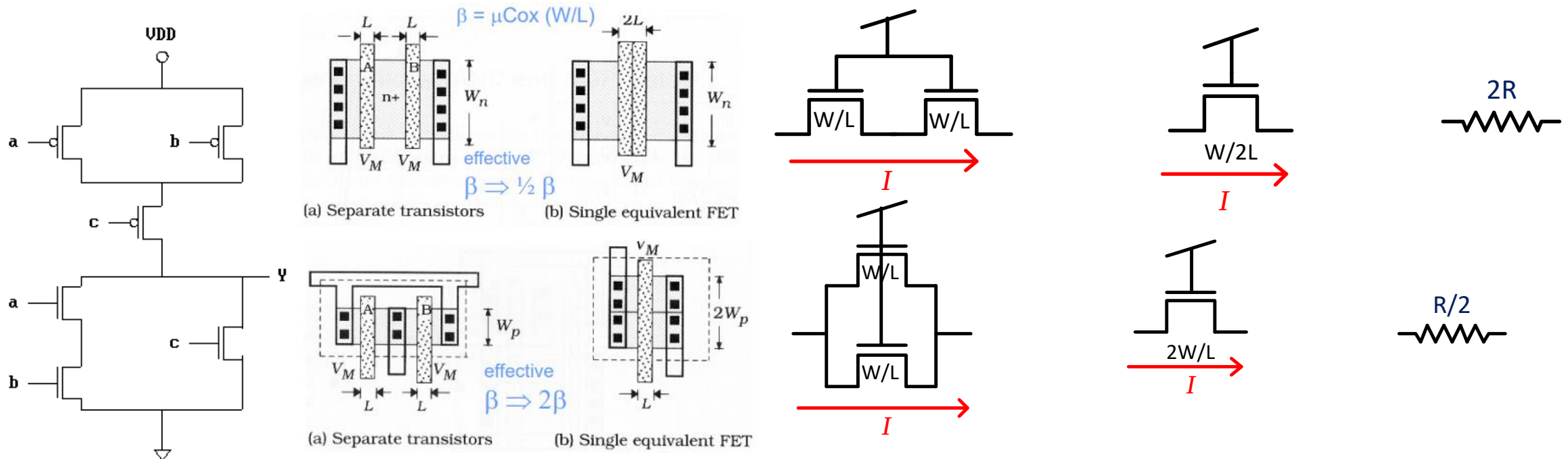- In the dynamic case, the **delay depends on the on-resistance** of the path **that charges or discharges the output**
- In complex gates, **different paths may contain different number of transistors**
 - Transistors in series, have a higher on-resistance
 - Transistors in parallel have a lower on-resistance (depending on the input)




Transistor Sizing for Complex Gates

- **How to balance a complex gate** with multiple different VTCs AND different paths that determine the on-resistance (i.e., speed)?
- **Consider the following:**
 - Multiple inputs are unlikely to change exactly at the same time:
Consider only single-input transitions
 - VTC state dependency with a single input change is small:
Ignore (steady-) state dependency for the optimization
 - **Optimize speed for the worst-case:**
Upsize slow paths to match the fast (single transition) paths
 - Target same drive strength for all “minimum size” gates without the need to artificially slow down the fastest minimum size gate (=INVERTER)
- **Size transistors of a minimum-size complex gate to match the minimum drive strength to that of a minimum size inverter**

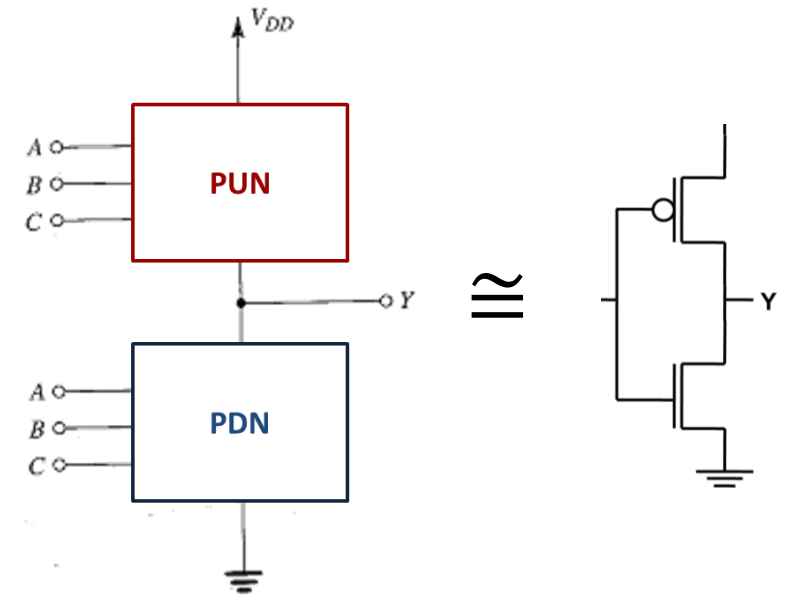


Transistor Sizing for Complex Gates (Example)

 - **Compensate for higher resistance in series connected transistors** by upsizing
 - Assume: series resistance is linear in the number of transistors
- **For parallel paths, assume worst case (only one turned on)**
- **Example: NAND-2**







Transistor Sizing for Complex Gates (Example)

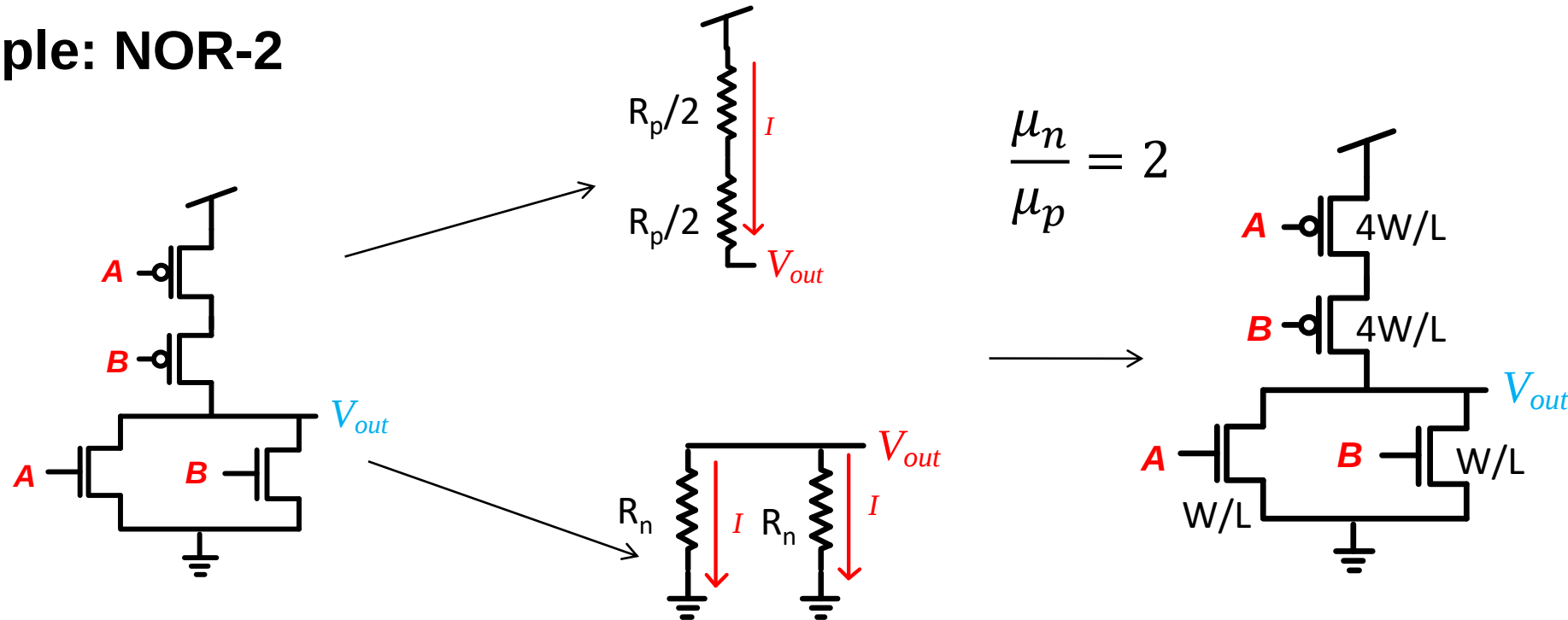- **Compensate for higher resistance in series connected transistors** by upsizing
 - Assume: series resistance is linear in the number of transistors
- **For parallel paths, assume worst case (only one turned on)**
- **Example: NOR-2**





Strategy for Transistor Sizing for Complex Gates

- The algorithm below applies to both nMOS and pMOS transistors
 1. Start from all minimum size transistors (pMOS start from the mobility ratio μ_n/μ_p)
 2. The first **target drive strength is 1** and the **first group includes all devices**
 3. Identify the **largest stack** of devices **N** in the group
 4. Scale the width of devices to match the **target drive strength**
 5. Identify those devices that are in parallel to the resized stack or any part thereof **as new group**
 6. The **new target drive strength is set to match it to the strongest parallel group**

    

Residual Input Pattern Effects

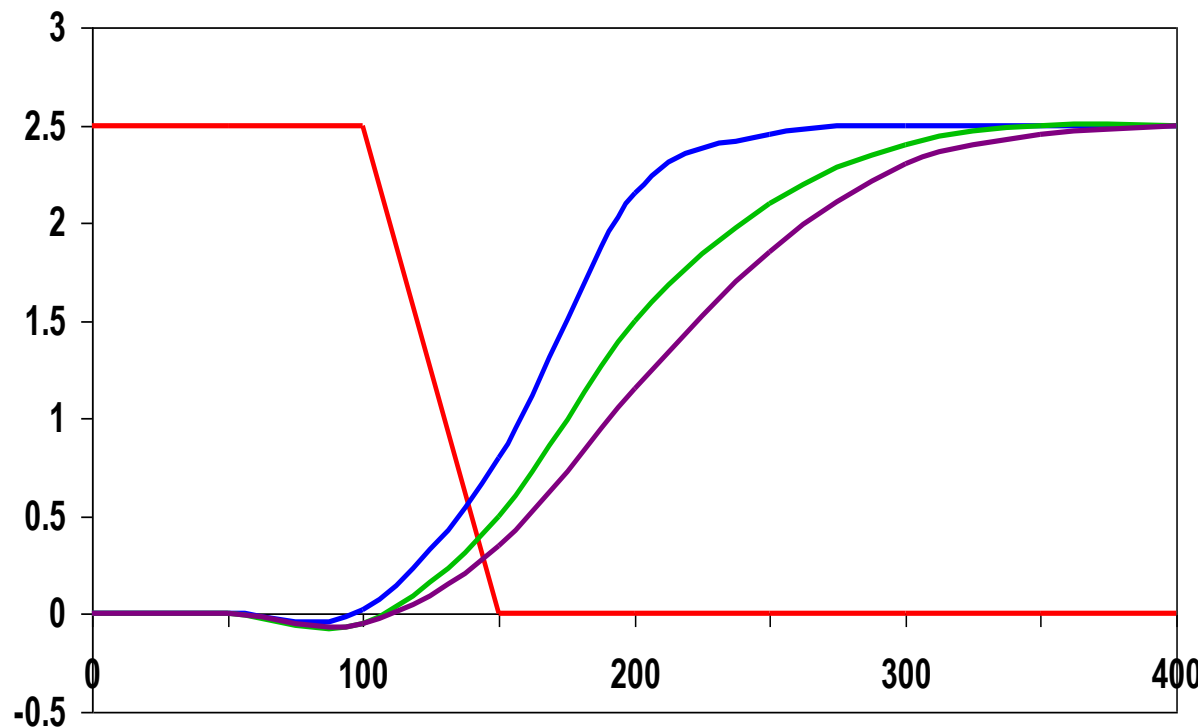 - Equalizing on-resistance should equalize the delays
- However, we still observe differences in delays, even through the same path




Input Data Pattern	Delay (psec)
A=B=0→1	69
A=1, B=0→1	62
A= 0→1, B=1	50
A=B=1→0	35
A=1, B=1→0	76
A= 1→0, B=1	70

NMOS = $0.5\mu\text{m}/0.25\mu\text{m}$
 PMOS = $0.75\mu\text{m}/0.25\mu\text{m}$
 $C_L = 100\text{ fF}$

- Reason: distributed intrinsic capacitance

Delay Estimation using the Elmore Delay Model

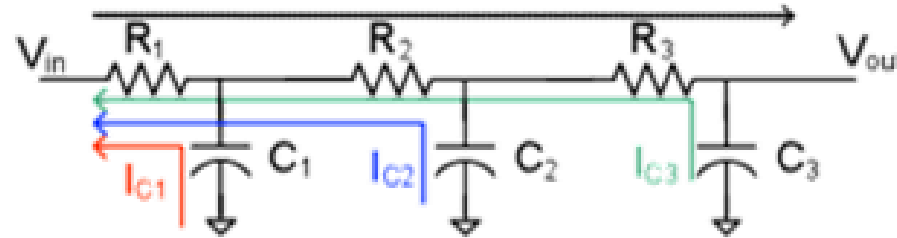- Charging and discharging of the internal (distributed) capacitances can be computed with a special case of the **Elmore Delay Model**



$$\tau_{elmore} = R_1 C_1 + (R_1 + R_2) C_2 + (R_1 + R_2 + R_3) C_3$$

- Upsizing** to keep a constant delay (for the compact model) **yields**

- Assume: N series transistors


$$R_n = R_{eq} / N$$

$$C_n = C_{eq} \cdot N$$

$$\begin{aligned} \tau_{elmore} &= \frac{R_{eq}}{N} \cdot N \cdot C_{eq} \cdot (1 + 2 + \dots + N) \\ &= R_{eq} \cdot C_{eq} \cdot \frac{N(N+1)}{2} \sim N^2 \end{aligned}$$

- Delay scales quadratically with number of inputs even after sizing**

Delay Scaling with Number of Inputs

 


- **Avoid gates with more than four (4) inputs**


Optimizations: Stack Re-Ordering

- **When stacking** heterogeneous groups of transistors, **different orders provide**
 - the same functionality
 - In our simple model, order has no impact on series resistance
- **Stack-order of transistors (or groups of transistors) can be optimized**
- **Objective: minimize capacitance that is far from the rails**

 - Example:
 - Layout may play a role as well





vs.

 

Optimizations: Progressive Sizing


- **Progressive sizing**

  - Note that M1 is on the path of all Capacitors, while MN is only on the path of CL.
- M1 is more critical than MN and should be wider
 - $M1 > M2 > M3 > \dots > MN$
 - the FET closest to the output is the smallest
- Delay reduction by more than 20% possible
- However, often **large area overhead in layout...**




Optimizations: Input Reordering

 - **Transistor ordering** based on arrival times of the inputs
- Place **latest arriving signal** (critical path) **closest to the output**, to minimize the capacitance that needs to be discharged when the signal arrives




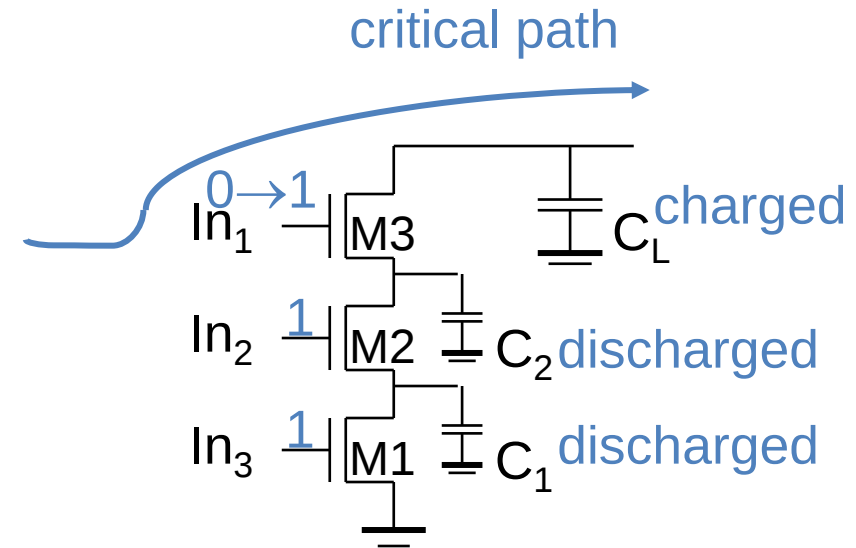
delay determined by time to discharge C_L , C_1 and C_2



delay determined by time to discharge C_L

Optimizations: Logic Restructuring

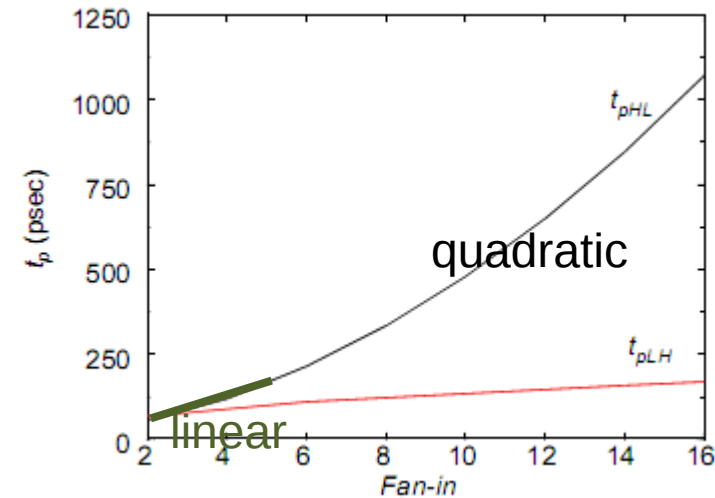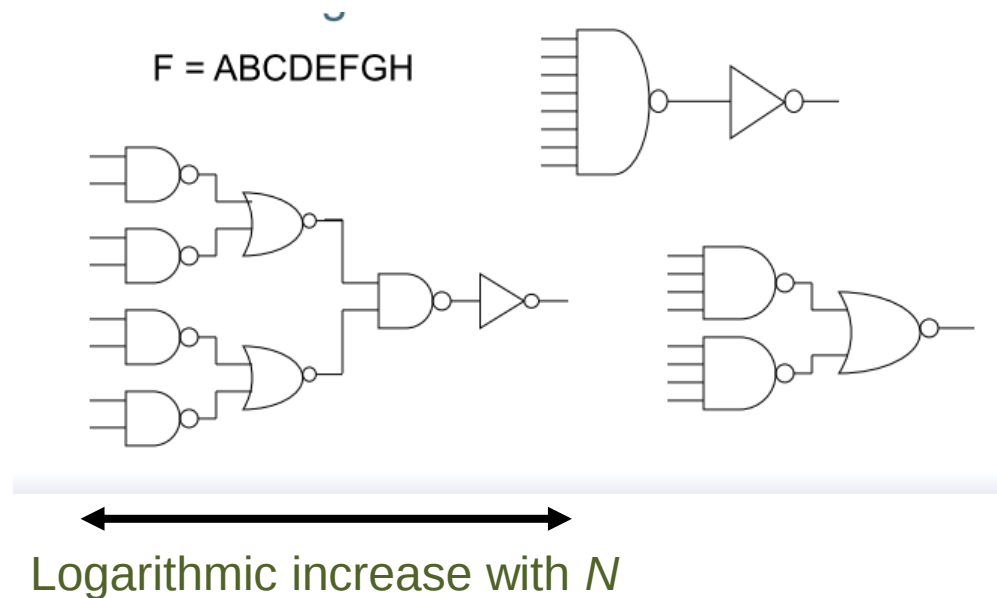- Logic can be **re-written in multiple stages**
 - Large fan in gates (with quadratic dependence) **reduce to** low fan in gates (linear dependence)
 - Number of stages grows only logarithmically with overall Fan-In cone



Optimizations: Buffer Insertion

- **A complex gate is a “weak driving gate”**
- **Upsizing the entire gate is costly in terms of area and internal capacitance (intrinsic delay)**
- **Better solution:** minimum size complex high fan-in gate followed by a strong driver (buffer or inverter)
 - Isolates fan-in from fan-out
 - Avoids increasing the load on the previous stage
 - Complex gate only worries about its intrinsic delay

