

EE-429

Fundamentals of VLSI Design

CMOS Power Consumption

Andreas Burg, Alexandre Levisse

CMOS: Two Types of Power Consumption


- **CMOS circuit power/energy consumption comes in two forms:**
 - **Dynamic energy/power consumption:** depends on activity
 - Charging and discharging of capacitors
 - Cross (short-circuit) currents while pMOS and nMOS are on during switching
 - **Static power consumption:** independent from activity
 - Constant biasing currents (intentional)
 - Various types of leakage currents (parasitic)
 - Contention currents when driving opposite directions (mostly accidents)

Basic Inverter (Unloaded)

- PMOS performs pull-up to V_{DD} , NMOS performs pull-down to GND

- Complementary gate


 
- Static (steady state): **output connected to either V_{DD} or GND**



- Ideally, no current path from V_{DD} to GND : ideally, no static power consumption

CMOS Gates With Capacitive Load

  - **Every CMOS gate sees a capacitive load from various sources**
 - **Intrinsic** MOS transistor capacitors (driver)
 - **Extrinsic** (fanout) MOS transistor capacitances
 - **Interconnect** capacitance
- **Various load capacitances are merged into a single load capacitor C_L**



- Wider transistors increase the gain factor (drive) but also increase the load (capacitance)

Energy of an Inverter with Capacitive Load

- **Switching** the **output from 0 to 1** charges the capacitor

- Energy delivered by the power supply

$$E_{VDD} = \int_0^\infty I(t)V_{DD}dt = \int_0^\infty C \frac{dV}{dt} V_{DD}dt = CV_{DD} \int_0^{V_{DD}} dV = CV_{DD}^2$$

- Once the output transition is complete, the energy stored on the capacitor is given by


$$E_C = \frac{1}{2} CV_{DD}^2$$

- Energy difference is dissipated to heat in pMOS


- **Switching** the **output from 1 to 0** discharges the capacitor

- Energy on capacitor is dissipated to heat in nMOS

 - **NOTE: energy consumption is independent of the waveform**



Active Energy Consumption Waveforms

 

Active Power/Energy Consumption

- Energy consumed during one pair of transitions $E_{\downarrow\uparrow}$:

$$E_{\downarrow\uparrow} = (CV_{dd})V_{dd} = CV_{dd}^2$$

- Energy/transition

$$E_t = CV_{dd}^2/2$$

- **Average power consumption:** energy per time T

- Depends on the **switching frequency** f_{sw} of the output $P_{sw} = \frac{E_t}{T} = \frac{2f_{sw}TCV_{dd}^2/2}{T} = f_{sw}CV_{dd}^2$
- **Activity factor α** : average number of transitions per cycle
 - Relates activity of a node to the clock frequency f_{clk}
 - Energy/transition * average-transition/cycle (α) * clock frequency (f_{clk})


$$P = \frac{\alpha}{2} CV_{dd}^2 f_{clk}$$

Short Circuit Currents

- CMOS gates have a large, but **finite gain** in the transition region
 - Cross-over currents lead to power consumption** during transients

PROBLEMATIC


range	applies when	n-channel ▼	p-channel ▲
A	$0 \leq U_{inp} \leq U_{th\,n}$	subthreshold	linear
B	$U_{th\,n} < U_{inp} < U_{inv}$	saturation	linear
C	$U_{inp} \approx U_{inv}$	saturation	saturation
D	$U_{inv} < U_{inp} < U_{dd} + U_{th\,p}$	linear	saturation
E	$U_{dd} + U_{th\,p} \leq U_{inp} \leq U_{dd}$	linear	subthreshold

 


Dominant during transition region:
rapid opening of the driver for the new level

- Note:** short-circuit power is irrelevant if


$$V_T < \frac{V_{DD}}{2}$$

 

a)

 

b)



 


c)

   (a) Transfer characteristic (b) Crossover current (c) Logic states

Minimizing Short-Circuit Currents





- **Obvious approach:** reduce input transition time
 - However, short input transitions require stronger driver => increase transition time (and load) on the driver of the driver
- **Control short circuit current by controlling the output slope:**
 - Fast input slow output: driving device mostly in linear regime => good for low power
 - Slow input fast output: driving device remains long in saturation => bad for low power



- **Best compromise: balance input slope and output slope**

Leakage Power

    - Transistors leak currents even when in off-state
- Sources for leakage
 - Sub-threshold leakage
 - Dominant component in most circuits
 - Gate tunneling
 - Generally low, even in modern technologies due to high-k gate dielectrics
 - Decreases very rapidly with decreasing V_{dd}
 - Junction current
 - Generally low
 - Decreases very rapidly with decreasing V_{dd}




Leakage Power

- Long channel deices (>130nm)

$$I_{DS} = I_0 e^{\frac{V_{GS}-V_T}{v_t n}}$$

v_t : thermal voltage
 n : constant

 - I_{DS} mostly independent from Drain-Source voltage
- Leakage current depends strongly on $V_{GS} - V_T$
 - Lower threshold voltage increases leakage
 - Higher threshold voltage decreases leakage
- **Subthreshold slope**: slope of the logarithmic leakage current for $V_{GS} - V_T < 0$





Leakage Power over Temperature

- Sub-threshold current depends exponentially on **thermal voltage** $v_t = kT/q$

$$I_{DS} = I_0 e^{\frac{V_{GS} - V_{th}}{kTn/q}}$$

  
- Exponential sub-threshold leakage (I_{DS}) increase with temperature**



 Example: 0.7V, 100nm
process, 15mm² die

Leakage Power (DIBL)


- **Impact of technology scaling on sub-threshold leakage (<130nm)**
 - Drain-Induced Barrier Lowering (DIBL): V_{DS} modulates threshold voltage
 - I_{DS} becomes a function of V_{DS}



$$I_{DS} = I_0 e^{\frac{V_{GS} - V_{th} + \lambda_{DS} V_{DS}}{v_t n}}$$

λ_{DS} : DIBL coefficient
 v_t : thermal voltage
 n : constant

 - **Impact on inverter leakage:** no longer supply independent



$$I_{leak} = I_0 e^{\frac{-V_{th} + \lambda_{DS} V_{DD}}{v_t n}}$$

Reducing voltage
reduces leakage

Leakage in Transistor Stacks (Short Channel)


- **Stacking occurs**

- In many logic gates (> 1 input)
- When introduced intentionally for leakage reduction

$$I_{leak,M1} = I_0 e^{\frac{-V_M - V_{th} + \lambda_{DS}(V_{dd} - V_M)}{v_{tn}}}$$

$$I_{leak,M2} = I_0 e^{\frac{-V_{th} + \lambda_{DS}V_M}{v_{tn}}}$$

Small speed
penalty: ~25%

 

Leakage Reduction	
2 NMOS	9
3 NMOS	17
4 NMOS	24
2 PMOS	8
3 PMOS	12
4 PMOS	16

