

EE-429


Fundamentals of VLSI Design

Logical Effort – Modelling and Analysis

Andreas Burg

Modelling Delay and Sizing Gates

- **CMOS logic designers often face the problem of**
 - Sizing gates in multiple stages of logic to minimize delay
 - Determining the optimum number of logic stages (especially for driving large loads)
 - Rapidly comparing circuit alternatives with optimal sizing
- **Difficulty lies in the impact of sizing one gate to reduce delay on the delay of the preceding gate**
 - Up-sizing one gate to reduce delay increases load (delay) on previous gate
 - Down-sizing one gate increase its delay, but also decreases the load (delay) of the previous gate
- **Example:** driving a large load starting from a small inverter

 

The Logical Effort model

- **Logical effort is a method to quickly analyze and optimize logic delay**
 - Uses a simple **linear delay model that includes**
 - the **impact of load on delay**
 - the **impact of sizing on the load/delay** of the previous gate
 - Allows back-of-the-envelope calculations
 - Helps make rapid comparisons between alternatives
- **The method is useful for**
 - **Digital circuit designers** trying to optimize their (high-speed) designs by hand
 - **CAD tool developers** to incorporate the key ideas into their tools for design automation
- **Developed in 1999 by Sutherland and Sproull:**

I. Sutherland, B. Sproull, and D. Harris, Logical Effort: Designing Fast CMOS Circuits, San Francisco, CA: Morgan Kaufmann, 1999.
- See: <http://bibl.ica.jku.at/dc/build/html/logicaleffort/logicaleffort.html>

Technology Independent Delay Model

- **Basic idea: decomposition of the delay**
 - **Decompose the normalized delay** of a gate **into** two components
 - A constant **intrinsic delay (stage effort)** term p that depends only on the gate itself
 - A load-dependent **effort delay** $f(\text{type}, \text{load}, \text{size})$
$$d = p(\text{type}) + f(\text{type}, \text{load}, \text{size})$$
 - **Decompose the load dependent delay** term $f(\text{load})$ **into a product of two components**
 - The **logical effort** g which covers the complexity of the gate (effort to drive a load: increases with the complexity of the gate)
 - The **electrical effort** h which describes the load and the sizing of the gate
$$f(\text{type}, \text{load}, \text{size}) = g(\text{type}) * h(\text{load}, \text{size})$$
 - p and f **express the two delays** $\tau_{p,f}(\text{gate})$ of a gate **relative to the delay of a minimum size, balanced inverter** $\tau_{p,f}(\text{inv})$ (**reference inverter**)

$$\text{Normalized delays: } p = \frac{\tau_p(\text{gate})}{\tau_p(\text{inv})} \text{ and } f = \frac{\tau_f(\text{gate})}{\tau_f(\text{inv})}$$

Derivation of the Relative Intrinsic Delay

- **Reminder:** Intrinsic delay of a gate depends on on-resistance and the **intrinsic load capacitance** C_{int}^{gate}

$$\tau_p(\text{gate}) = 0.69 \cdot R_{eq}^{gate} C_{int}^{gate}$$

- Normalizing with the delay of the reference inverter

$$p = \frac{R_{eq}^{gate} C_{int}^{gate}}{R_{eq}^{inv} C_{int}^{inv}}$$

- For a **balanced gate that is matched to a reference inverter with the same current drive capability** ($R_{eq}^{gate} = R_{eq}^{inv}$)

$$p = \frac{C_{int}^{gate}}{C_{int}^{inv}}$$

Balanced (reference) inverter (same driving strength as considered gate)

Unloaded: $\tau_p(\text{inv}) = 0.69 \cdot R_{eq}^{inv} C_{int}^{inv}$

C_{int}^{inv} : inverter intrinsic load

Driving itself: $\tau_f(\text{inv}) = 0.69 \cdot R_{eq}^{inv} C_{IN}^{inv}$




C_{IN}^{inv} : inverter input load

Model for the Internal Load $C_{int}^{??}$ for Intrinsic Delay

- Internal load is difficult to define precisely, especially since it also depends significantly on the layout. Nevertheless, we need a basic model.

- Intrinsic load:** dominated by the diffusion capacitance

 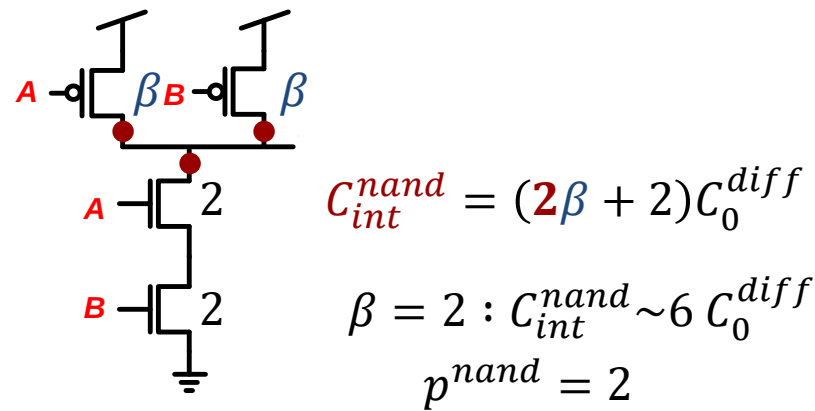 - **Relative to the diffusion capacitance of a minimum size nMOS** C_0^{diff}
- **Depends linearly on the width** of the transistors that contribute to it
- **Consider only the load that is attached directly to the output node of the gate**



Split Effort Delay into Logical- and Electrical-Effort

- Start from the **effort delay** of a gate

$$\tau_f(\text{gate}) = 0.69 \cdot R_{eq}^{gate} \cdot C_L$$

- Normalizing with the effort delay of a reference inverter with same current drive capability ($R_{eq}^{gate} = R_{eq}^{inv}$)

Balanced (reference) inverter (same driving strength as considered gate)

Unloaded: $\tau_p(\text{inv}) = 0.69 \cdot R_{eq}^{inv} C_{int}^{inv}$

C_{int}^{inv} : inverter intrinsic load

Driving itself: $\tau_f(\text{inv}) = 0.69 \cdot R_{eq}^{inv} C_{IN}^{inv}$

C_{IN}^{inv} : inverter input load

$$f(C_L) = \frac{R_{eq}^{gate} \cdot C_L}{R_{eq}^{inv} \cdot C_{IN}^{inv}} * \underbrace{\frac{C_{IN}^{gate}}{C_{IN}^{gate}}}_1 = \frac{C_L}{C_{IN}^{inv}} * \underbrace{\frac{C_{IN}^{gate}}{C_{IN}^{gate}}}_1 = \underbrace{\frac{C_{IN}^{gate}}{C_{IN}^{inv}}}_g * \underbrace{\frac{C_L}{C_{IN}^{gate}}}_h$$


- Logical effort**: complexity of the gate represented by the additional input load compared to an equally strong inverter
- Electrical effort**: difficulty to drive the output relative to the difficulty of the previous gate to drive the input

Logical effort

Electrical effort

Deriving the Input Capacitance/Load


- **Input capacitance:** load that the input of a gate presents to the preceding gate
 - **Relative to gate capacitance of a minimum size nMOS** C_0
 - **Depends linearly on the width** of the transistors that contribute to it
 - Value of C_0 is irrelevant when
 - used to calculate $g = C_{IN}^{gate} / C_{IN}^{inv}$ (ratio of gate capacitances)
 - when the C_L is only the input of other gates since then $C_L \sim C_0$ and $h = C_L / C_{IN}^{inv}$ independent of C_0

 

$$C_{IN}^{inv} = (\beta + 1)C_0$$

$$\beta = 2 : C_{IN}^{inv} \sim 3C_0$$

$$g = 1$$

 


$$C_{IN}^{nand}(A) = (\beta + 2)C_0$$

$$\beta = 2 : C_{IN}^{nand}(A) \sim 4C_0$$

$$C_{IN}^{nand}(B) = (\beta + 2)C_0$$

$$\beta = 2 : C_{IN}^{nand}(B) \sim 4C_0$$

$$g = 4/3$$

 

$$C_{IN}^{nor}(A) = (2\beta + 1)C_0$$

$$\beta = 2 : C_{IN}^{nor}(A) \sim 5C_0$$

$$C_{IN}^{nor}(B) = (2\beta + 1)C_0$$

$$\beta = 2 : C_{IN}^{nor}(B) \sim 5C_0$$

$$g = 5/3$$

Logical Effort Gate Delay Summary

- Gate delay is modelled as

$$d = p + g * h$$

- **Intrinsic delay p :** load independent delay

- Depends only on the gate
- Approximated by the number of unit diffusion capacitances (C_0^{diff}) connected to the output of the gate, relative to an equivalent inverter

$$p = \frac{C_{int}^{gate}}{C_{int}^{inv}}$$

- **Logical effort g :** cost for driving an output load (due to the complexity of the gate)

- Depends only on the gate (not on the load), but can be different for different inputs of the gate
- Given by the ratio of capacitances at the input of a gate compared to the capacitances of an equivalent inverter

$$g = \frac{C_{IN}^{gate}}{C_{IN}^{inv}}$$


- **Electrical effort h :** size of the load relative to the load the gate to a previous gate

- Depends on the gate and the load
- Given by the ratio of the load to the input capacitance of the gate

$$h = \frac{C_L}{C_{IN}^{gate}}$$

Logical Effort Gate Delay Examples

- **Consider two examples: INV & NAND**
 - NAND has a larger intrinsic delay
 - Drive capability of NAND is the same as for the inverter, hence, **delay increase with higher absolute load should be the same**
 - “Normalized delay” reflects how well the gate with the same input capacitance as an inverter can drive a load
 - However, we consider the load relative to the input capacitance of the gate (**FANOUT**):
 - This reflects the impact of facilitating drive through up-sizing on the previous gate
 - Driving a larger relative load, is more “difficult” and leads to larger delay
 - **Delay increase with higher relative (to the input) load is more**

 

Logical Effort for Popular Gates

- **Intrinsic delay** and **logical effort** for frequently used gates with $\beta = 2$:
 - **Note that** Intrinsic delay and logical effort are independent of the gate sizing, but they depend on the PMOS/NMOS ratio (β)

intrinsic delay

Gate Type	Number of Inputs				
	1	2	3	4	n
inverter	1				
NAND		2	3	4	n
NOR		2	3	4	n
tristate, multiplexer	2	4	6	8	$2n$

logical effort

Gate Type	Number of Inputs				
	1	2	3	4	n
inverter	1				
NAND		4/3	5/3	6/3	$(n+2)/3$
NOR		5/3	7/3	9/3	$(2n+1)/3$
tristate, multiplexer	2	2	2	2	2
XOR, XNOR		4, 4	6, 12, 6	8, 16, 16, 8	

Difference between NAND and NOR becomes apparent in logical effort

Extracting Delay Constant from Ring Oscillator

- Relating the logical effort “relative” delay to an absolute delay requires **two delay constants**: $\tau_p(inv)$ and $\tau_f(inv)$
- Delay constants are related by their unit loads (diffusion load vs. gate load)
$$\tau_p(inv)/\tau_f(inv) = C_0^{diff}/C_0$$
 - For many modern processes, we find that $C_0^{diff} \approx C_0 \rightarrow \tau_p(inv) = \tau_f(inv) = \tau(inv)$
- Experimental setup to extract $\tau(inv)$: **N-stage ring oscillator**


Logical effort delay

$$p_{inv} = 1$$

$$g_{inv} = 1$$

$$h = 1$$
 
$$d_{osc} = N \cdot p_{inv} + N \cdot g_{inv} \cdot h = 2N$$




$$\text{Measured oscillator frequency } f_{osc} = \frac{1}{2 \cdot 2N \cdot \tau(inv)} \rightarrow \tau(inv) = 4Nf_{osc}$$

Path Delay Calculation with Logical Effort

- **Logical effort** model allows to easily **calculate path delays**
 - Normalized **path delay obtained by summing** of normalized **gate delays**
- **Procedure for path delay calculation**
 1. For each gate i **calculate input capacitance C_{IN}^i** and **output load C_L^i** relative to min. inverter
 - Without branching (drives only one next gate... see later): $C_L^i = C_{IN}^{i+1}$
 - Consider that **C_{IN}^i scales with size γ** compared to the minimum size gate
 2. **Evaluate intrinsic delay p , logical effort g , and electrical effort h for each gate** in the path
 3. **Compute gate delays and sum up to obtain the path delay**


Path Delay Calculation Examples

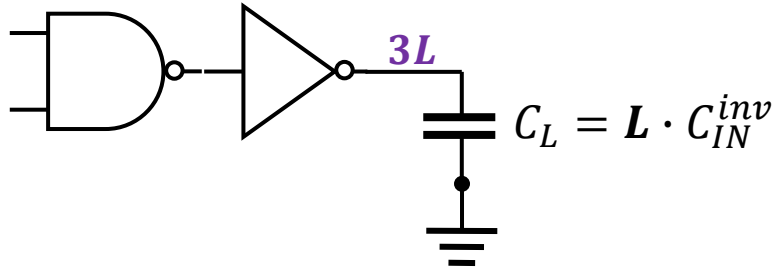- **Example 1:** compare two AND gate implementations (min. size, $\beta = 2$)



	i = 1	i = 2
p		
g		
h		


DELAY:

 

	i = 1	i = 2
p		
g		
h		

Path Delay Calculation Examples

 
- Example 1:** compare two AND gate implementations (min. size, $\beta = 2$)



	i = 1	i = 2
p	2	1
g	$4/3$	1
h	$3/4$	$3L/3$

DELAY:

$$4 + L$$

 


	i = 1	i = 2
p	1	2
g	1	$5/3$
h	$5/3$	$3L/5$

$$\frac{14}{3} + L$$


Gate Sizing

- How to adjust the size of gates in a path to minimize delay?
 - **Up-Sizing factors γ_i** : specifies size of gate i relative to the corresponding minimum size gate
 - Assume that the **size of the first gate** in a chain is **given** (e.g., $\gamma_1 \equiv 1$) and **can not be altered**

 - Implications of up-sizing a gate on a path



 
- Delay (electrical effort h) of the up-sized gate reduces
- Delay (electrical effort h) of the previous gate increases



- **Local optimization is not sufficient:** need to capture impact of sizing on full path


Impact of Gate Sizing Example

 - **Two inverters driving a load of $C_L = 4 \cdot C_{IN}^{inv}$ ($\beta = 2$)**
 - Consider three configurations




	i = 1	i = 2
p		
g		
h		

DELAY:

 


	i = 1	i = 2
p		
g		
h		

 

	i = 1	i = 2
p		
g		
h		


Impact of Gate Sizing Example

 - **Two inverters driving a load of $C_L = 4 \cdot C_{IN}^{inv}$ ($\beta = 2$)**
 - Consider three configurations




	i = 1	i = 2
p	1	1
g	1	1
h	3/3	12/3

DELAY: 7

 

	i = 1	i = 2
p	1	1
g	1	1
h	6/3	12/6

6

 


	i = 1	i = 2
p	1	1
g	1	1
h	9/3	12/9

 
6.33

Topology Analysis

- Consider the following **two options to implement the same logic function**: $Z = \overline{\overline{A} \cdot B}$ that drives a large load ($L \times \text{INV}$)
 - Which option is better (potentially as a function of L)?



	i = 1	i = 2
p		
g		
h		

 


	i = 1	i = 2
p		
g		
h		

DELAY:

Topology Analysis

 
- Consider the following **two options to implement the same logic function**: $Z = \overline{\overline{A} \cdot \overline{B}}$ that drives a large load ($L \times \text{INV}$)
 - Which option is better (potentially as a function of L)?



	$i = 1$	$i = 2$
p	2	1
g	$4/3$	1
h	$3/4$	$3L/3$

DELAY: $4 + L$

Always better

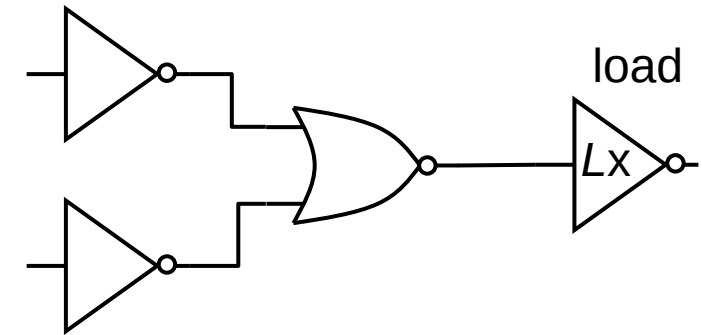

	$i = 1$	$i = 2$
p	1	2
g	1	$5/3$
h	$5/3$	$3L/5$

$4.66 + L$

EE-429


Fundamentals of VLSI Design

Logical Effort – Optimization

Andreas Burg

Optimum Sizing with Logical Effort (Derivation)

 - Consider the schematic and the delay of a generic path



	$i = 1$	$i = 2$	$i = 3$	$i = N$	
Fixed: given by circuit topology	$\mathbf{p}$	$\mathbf{p}_1$	$\mathbf{p}_2$	$\mathbf{p}_3$	$\mathbf{p}_N$
	$\mathbf{g}$	$\mathbf{g}_1$	$\mathbf{g}_2$	$\mathbf{g}_3$	$\mathbf{g}_N$
unknown $\mathbf{h}$	$\mathbf{h}_1$	$\mathbf{h}_2$	$\mathbf{h}_3$	$\mathbf{h}_N$	$\mathbf{h}_i \sim \frac{\gamma_{i+1}}{\gamma_i} \longrightarrow \text{unknown}$

$$D = \mathbf{p}_1 + \underbrace{g_1 h_1}_{f_1} + \mathbf{p}_2 + \underbrace{g_2 h_2}_{f_2} + \mathbf{p}_3 + \underbrace{g_3 h_3}_{f_3} + \dots + \mathbf{p}_N + \underbrace{g_N h_N}_{f_N}$$

- Minimize delay $\Rightarrow$ **minimize $f_1 + f_2 + \dots + f_N = \sum_{i=1}^N f_i$ (path effort delay) $\longrightarrow$ DIFFICULT!**

Optimum Sizing with Logical Effort (Derivation)

- How to **minimize** the path effort **delay** $\sum_{i=1}^N f_i$

- Trick:** consider the **path effort**

$$F = f_1 \cdot f_2 \cdot \dots \cdot f_N = \prod_{i=1}^N f_i = \underbrace{\prod_{i=1}^N g_i}_G \cdot \underbrace{\prod_{i=1}^N h_i}_H = G \cdot H$$

G is known from the topology

▪ Computing $H = \frac{\gamma_2 C_0^2}{\underbrace{\gamma_1 C_0^1}_{h_1}} \cdot \frac{\gamma_3 C_0^3}{\underbrace{\gamma_2 C_0^2}_{h_2}} \cdot \frac{\gamma_4 C_0^4}{\underbrace{\gamma_3 C_0^3}_{h_3}} \cdot \dots \cdot \frac{C_L}{\underbrace{\gamma_N C_0^N}_{h_N}} = \frac{C_L}{\gamma_1 C_0^1}$

→ Independent of internal sizes

C_0^i : input capacitance of gate i with minimum size

as **geometric mean** is possible without knowledge of $\gamma_2 \dots \gamma_N$!

- H depends only on the first gate and the last load of the path
- Exploit ability to compute H with **theorem of arithmetic mean & geometric mean**

$$\frac{1}{N} \sum_{i=1}^N f_i \geq \sqrt[N]{F}$$

Equality if $f_1 = f_2 = \dots = f_N$

Equality minimizes $f_1 + f_2 + \dots + f_N$

Delay with Optimum Sizing with Logical Effort

- **Effort delay is minimized if**

$$\hat{f} = f_1 = f_2 = \cdots f_N = \sqrt[N]{F} = \sqrt[N]{G \cdot H}$$

$$G = \prod_{i=1}^N g_i \quad H = \prod_{i=1}^N h_i = \frac{C_L}{C_0^1 \gamma_1}$$


- G : from gate types given by the path topology
 - C_L : load given by the problem statement (in same unit as C_0^1)
 - C_0^1 : minimum size input capacitance of first gate type (in same unit as C_L)
 - γ_1 : given relative sizing of the first gate
- **Minimum achievable path delay**
 - Can be derived without knowledge of the corresponding gate sizes!

$$p_i: \text{ given, } \quad g_i \cdot h_i = \sqrt[N]{\frac{C_L}{C_0^1 \gamma_1} \cdot \prod_{i=1}^N g_i} = \hat{f}$$

$$\text{Total path delay with optimum sizing} = \sum_{i=1}^N p_i + N \cdot \sqrt[N]{\frac{C_L}{C_0^1 \gamma_1} \cdot \prod_{i=1}^N g_i}$$

Calculating Delay with Optimum Sizing (Example)

 - Consider the following path ($\beta = 2$) :



$N =$

$H =$


$G =$

$\hat{f} =$

$D_{min} =$

Calculating Delay with Optimum Sizing (Example)

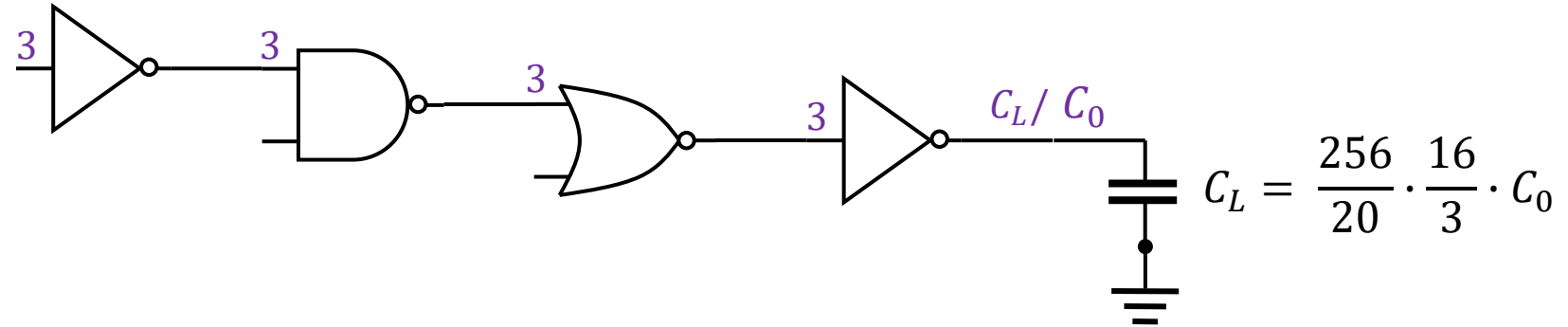- Consider the following path ($\beta = 2$) :



	i = 1	i = 2	i = 3	i = 4
p	1	2	2	1
g	1	4/3	5/3	1

$$N = 4 \quad H = \frac{256}{20} \cdot \frac{16}{3}$$

$$G = 1 \cdot \frac{4}{3} \cdot \frac{5}{3} \cdot 1 = \frac{20}{9}$$

$$\hat{f} = \sqrt[4]{HG} = \frac{8}{3}$$

$$D_{min} = \sum p_i + N \cdot \hat{f} = 6 + \frac{32}{3} \approx 16.66$$

Deriving Optimum Gate Sizes with Logical Effort

- **Optimum gate sizes γ_i can be derived from knowledge of $\hat{f} = g_i \cdot h_i$**

- h_i depends only on γ_i and γ_{i+1} OR on γ_i and C_L
- γ_1 and C_L are known

$$\hat{f} = \sqrt[N]{\frac{C_L}{C_0^1 \gamma_1} \cdot \prod_{i=1}^N g_i}$$

$$\gamma_1 = 1$$

- **Two strategies:**

- Input → Output (left to right)

$$f_1 = \hat{f} = g_1 \cdot \frac{\gamma_2}{\gamma_1} \cdot \frac{C_0^2}{C_0^1} = \frac{\gamma_2}{\gamma_1} \cdot g_2 \quad \mapsto \quad \frac{C_0^i}{C_0^j} = \frac{g_i}{g_j}$$

$$f_2 = \hat{f} = g_2 \cdot \frac{\gamma_3}{\gamma_2} \cdot \frac{C_0^3}{C_0^2} = \frac{\gamma_3}{\gamma_2} \cdot g_3 \quad \mapsto$$

$$f_3 = \hat{f} = g_3 \cdot \frac{\gamma_4}{\gamma_3} \cdot \frac{C_0^4}{C_0^3} = \frac{\gamma_4}{\gamma_3} \cdot g_4 \quad \mapsto$$

$$\gamma_2 = \hat{f} \cdot \frac{\gamma_1}{g_2}$$

$$\gamma_3 = \hat{f} \cdot \frac{\gamma_2}{g_3} = \hat{f}^2 \cdot \frac{\gamma_1}{g_2 g_3}$$

$$\gamma_4 = \hat{f} \cdot \frac{\gamma_3}{g_4} = \hat{f}^3 \cdot \frac{\gamma_1}{g_2 g_3 g_4}$$

$$f_n = \dots$$

$$\mapsto \gamma_n = \hat{f}^{n-1} \cdot \gamma_1 \cdot \prod_{i=2}^n g_i^{-1}$$

Deriving Optimum Gate Sizes with Logical Effort

- Output → Input (right to left)

$$\begin{aligned}
 f_N = \hat{f} &= g_N \cdot \frac{1}{\gamma_N} \cdot \frac{C_L}{C_0^N} & \mapsto & \gamma_N = \frac{1}{\hat{f}} \frac{C_L}{C_0^N} \cdot g_N \\
 f_{N-1} = \hat{f} &= g_{N-1} \cdot \frac{\gamma_N}{\gamma_{N-1}} \cdot \frac{C_0^N}{C_0^{N-1}} & \mapsto & \gamma_{N-1} = \frac{1}{\hat{f}} \cdot g_{N-1} \cdot \gamma_N \cdot \frac{C_0^N}{C_0^{N-1}} = \frac{1}{\hat{f}^2} \cdot \frac{C_L}{C_0^{N-1}} \cdot g_{N-1} \cdot g_N \\
 f_{N-2} = \hat{f} &= g_{N-2} \cdot \frac{\gamma_{N-1}}{\gamma_{N-2}} \cdot \frac{C_0^{N-1}}{C_0^{N-2}} & \mapsto & \gamma_{N-2} = \frac{1}{\hat{f}} \cdot g_{N-2} \cdot \gamma_{N-1} \cdot \frac{C_0^{N-1}}{C_0^{N-2}} = \frac{1}{\hat{f}^3} \cdot \frac{C_L}{C_0^{N-2}} \cdot g_{N-2} \cdot g_{N-1} \cdot g_N \\
 f_n = \dots & & \mapsto & \gamma_n = \frac{1}{\hat{f}^{N-n+1}} \cdot \frac{C_L}{C_0^n} \cdot \prod_{i=n}^N g_i
 \end{aligned}$$


- Drive strength scales exponentially with every stage by a factor of $\hat{f}$, corrected by the logical effort of the stage

$$\frac{\gamma_n}{\gamma_{n-1}} = \hat{f} / g_n$$

Calculating Delay with Optimum Sizing (Example)

- Consider the following path ($\beta = 2$) :
 
$$D_{min} = \sum p_i + N \cdot \hat{f} = 6 + \frac{32}{3} \approx 16$$



$$C_L = \frac{256}{20} \cdot \frac{16}{3} \cdot C_0$$

$$\gamma_2 = \hat{f} \frac{\gamma_1}{g_2} = 2 \quad \gamma_3 = \hat{f} \frac{\gamma_2}{g_3} = \frac{16}{5} \quad \gamma_4 = \hat{f} \frac{\gamma_3}{g_4} = \frac{384}{45}$$

	i = 1	i = 2	i = 3	i = 4
p	1	2	2	1
g	1	4/3	5/3	1
h	8/3	16/8	24/15	8/3


$$\hat{f} = \sqrt[4]{HG} = \frac{8}{3}$$

$$D = \sum p_i + \sum g_i h = 6 + \frac{8}{3} + \frac{4}{3} \frac{16}{8} + \frac{5}{3} \frac{24}{45} + \frac{8}{3} \approx 16.66 = D_{min}$$

Driving Large Loads

- We often face the **challenge to drive a large load** starting **from a small gate**
 - Single large buffer is not efficient as it puts too much load on the small initial gate

 - Solution:** chain of multiple buffers with increasing size
 - More buffers, more intrinsic delay, but less effort delay...



- How to size those inverters? $\gamma_n = \hat{f}^{n-1} = \left(\frac{C_L}{C_{INV}} \right)^{\frac{n-1}{N}} \longrightarrow$ **geometric sizing**

$$D_{min}(N) = N + N \sqrt[N]{C_L / C_{INV}^{inv}}$$

Driving Large Loads

- **How many buffers/inverter stages should we use for min. delay?**

- Find the minimum of $D_{min}(N)$ with respect to N

$$\frac{\partial D_{min}(N)}{\partial N} = -H^{\frac{1}{N}} \ln H^{\frac{1}{N}} + H^{\frac{1}{N}} + 1 = 0$$

$$D_{min}(N) = N + N^N \sqrt[N]{H}$$
$$H^{\frac{1}{N}} = \hat{f}$$

- Difficult to solve for N !

- Rewrite to **find stage effort** $\rho = H^{\frac{1}{N}}$ that minimizes $D_{min}(N)$

$$-\rho \ln \rho + \rho + 1 = \rho(1 - \ln \rho) = 1$$

- Numerical evaluation leads to $\rho_{opt} \approx 3.69$ (optimum stage effort) $\longrightarrow$ **We often use FO4 as a reference since is close to the optimum stage effort**

- Reconstruct the **optimum number of stages** from ρ_{opt} and H

$$\hat{N} = 1 / \log_H(\rho_{opt})$$

Driving Large Loads


- **Engineering solution: smart trial and error**

- Useful when for example $p > 1$
- Use that **only integer choices** are allowed for N
- For inverters, may even restrict N to be even

- A simple procedure **with binary search**

 
1. Start with $N = 1$
2. Compute $D_{min}(N)$ and $\partial D_{min}(N)/\partial N$
3. As long as $\frac{\partial D_{min}(N)}{\partial N} < 0$ double N and proceed with 2.

Once $\frac{\partial D_{min}(N)}{\partial N} > 0$, proceed with a binary search targeting $\frac{\partial D_{min}(N)}{\partial N} = 0$




Driving Large Loads

 - **Finding the exact optimal solution for the best number of stages is tricky** and has many approximations
- **How sensitive is the delay to small errors in the solution?**
- Consider the delay as a function of the deviation from the optimal number of stages:
 - **Sensitivity of the delay to variations in the number of stages is low**



Dealing with Branches

 - **Digital Circuits** are rarely linear, but **typically branch out** (tree-like, with $FO > 1$)



- **Path logical effort:** $G = g_1 \cdot g_2 \cdot \dots \cdot g_N$ **not affected**

- **Path electrical effort:** $H = h_1 \cdot \dots \cdot h_{i-1} \cdot \underbrace{\frac{\gamma_{i+1}C_0^{i+1} + C_{off}^{i+1}}{\gamma_i C_0^i}}_{\neq h_{i+1} = \frac{\gamma_{i+1}C_0^{i+1}}{\gamma_i C_0^i}} \cdot h_{i+1} \dots \cdot h_N \neq \frac{C_L}{C_0^1}$ **is affected**

Dealing with Branches using Branch Efforts

- **Basic idea:** for consistency, move branching overhead into separate factor

- Keep same definition of $H = \frac{C_L}{C_0^1}$ also with branches
- Define a per-stage **branch effort** c so that $b_i \cdot \underbrace{\frac{\gamma_{i+1}C_0^{i+1}}{\gamma_i C_0^i}}_{h_i} = \frac{\gamma_{i+1}C_0^{i+1} + c_{off}^{i+1}}{\gamma_i C_0^i}$

- **Path logical effort** with branches:


$$G = \prod_{i=1}^N g_i \quad H = \prod_{i=1}^N h_i = \frac{C_L}{C_0^1 \gamma_1} \quad B = \prod_{i=1}^N b_i$$

$$\text{Path effort: } F = GBH \quad \text{Stage effort: } \hat{f} = \sqrt[N]{GBH}$$

Sizing with Branches

- The **path branch effort** B depends on the sizing γ_i at the branches
 - Calculation of $\hat{f} = \sqrt[N]{GB(\gamma)H}$ prior to sizing is no longer possible**
- Trick** to re-enable sizing: **perform same sizing on all paths on branch**
 - Branch effort becomes again independent of γ_{i+1}
 
$$b_i = \frac{\gamma_{i+1} C_0^{i+1} + \gamma_{i+1} C_{off}^{i+1}}{\gamma_{i+1} C_0^{i+1}} = \frac{C_0^{i+1} + C_{off}^{i+1}}{C_0^{i+1}}$$



- Updated sizing rules include b_i** similar to g_i


– Left-to-right: $\gamma_n = \hat{f}^{n-1} \cdot \gamma_1 \cdot \prod_{i=2}^n b_{i-1}^{-1} g_i^{-1} = \hat{f} \cdot \frac{\gamma_{n-1}}{b_{n-1} g_n}$

– Right-to-left: $\gamma_n = \frac{1}{\hat{f}^{N-n+1}} \cdot \frac{C_L}{C_0^n} \cdot \prod_{i=n}^N b_i g_i = \frac{b_n g_{n+1}}{\hat{f}} \cdot \gamma_{n+1} \quad \gamma_N = \frac{1}{\hat{f}} \cdot \frac{C_L}{C_0^N} \cdot b_N g_N$
 usually 1 unless C_L is per branch

- Not always realistic, but **many important circuits** are structured and **continue similarly after a branch**
- Useful also as a starting point, even when branches are finally not scaled as assumed (overdesign)

Sizing with Branches (Example)

- Consider the following circuit:

 

	i = 1	i = 2	i = 3
p			
g			
b			

$H =$

$G =$

$B =$

$\hat{f} =$

$=$

$D_{min} =$

$=$

$\gamma_1 = 1$

$\gamma_2 =$


$=$

$\gamma_3 =$

$=$

Sizing with Branches (Example)

- Consider the following circuit:

 

	$i = 1$	$i = 2$	$i = 3$	
$N = 3$	$p = 2$	$p = 2$	$p = 2$	$H = 18/4$
	$g = 4/3$	$g = 4/3$	$g = 4/3$	$G = (4/3)^3$
	$b = 2$	$b = 3$	$b = 1$	$B = 2 \cdot 3 \cdot 1$

$$\hat{f} = \sqrt[3]{GBH} = 4$$

$$D_{min} = 6 + N \cdot \hat{f} = 22$$

$$\gamma_1 = 1$$

$$\gamma_2 = \gamma_1 \frac{\hat{f}}{b_1 g_2} = \frac{3}{2}$$

$$\gamma_3 = \gamma_2 \frac{\hat{f}}{b_2 g_3} = \frac{3}{2}$$

EE-429


Fundamentals of VLSI Design

Logical Effort – Interconnect & Irregularities

Andreas Burg

Logical Effort with Routing Capacitance (1/2)

- The logical effort model can not account for routing resistance, but routing capacitance is anyway often more relevant
- **We often face the following scenario**
 - A **path** (to be optimized) with some random logic **contains a very long wire with a high capacitive load C_w**
 - Often, this occurs in the location of a branch with many nodes which add additional load
 - The path continues after the segment with the high load
 - The path ends with a defined load C_L (which may also be high)
- **We would like to optimize the entire path ...**

 

Logical Effort with Routing Capacitance (2/2)

- The **common optimization procedure is not applicable** since the wire load does not scale with the sizing γ .

- **Procedure:** multi-step iterative process

1. Ignore parasitics C_w and size all gates from **A** to **C**

- Identify the appropriate fanout load on node **B**
- Include any rounding-up on the drivers loading **B**

2. Optimize the partial path from **A** to **B** with the load defined by C_w and the fanout from the first optimization step.

