

EE-429


Fundamentals of VLSI Design

Basic Sequential Elements

Andreas Burg



Fundamental Components of Digital Circuits

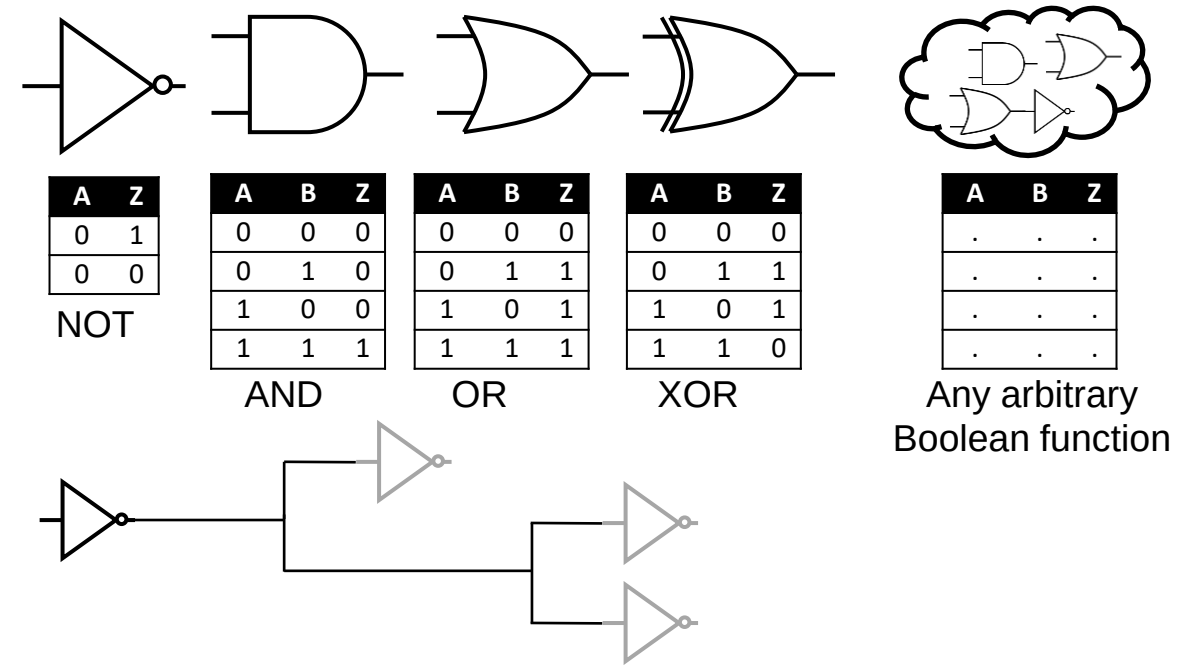- Combinatorial logic: memoryless
 - Built from basic Boolean logic gates
 - Output is only a function of the current input
 - Combinational logic has no state
- Nets (wires): memoryless
 - Connect components, carrying logic signals
 - One input (driver) and one or multiple outputs



Storage (sequential) elements: memory

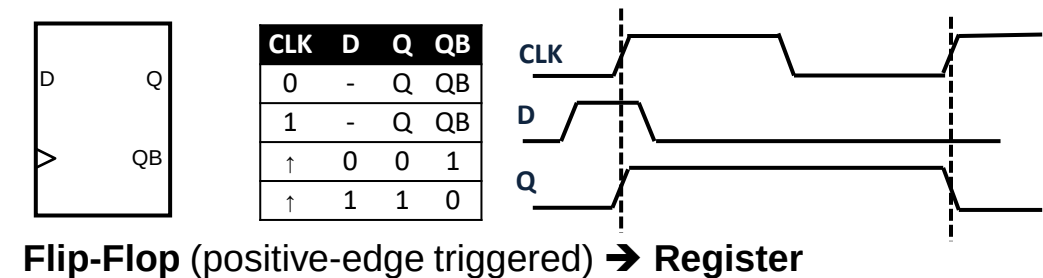 
- Output depends on current input *and* on an internal state, defined by previous inputs



Why do we need Sequential Elements



- **Functional storage:**

 - Collect data that arrives in sequence and is required as a whole



- **Non-functional storage**



 
 
- Re-use of logic for different data over time for resource sharing
- Isolation of parts of the logic to operate in parallel through pipelining



Naming Conventions

- Two types of sequential elements:

   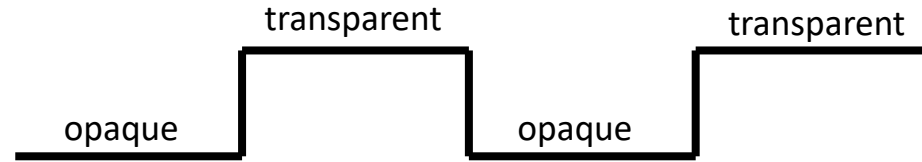- a **latch** is **level sensitive**
- a **register** or a **flip-flop** is **edge-triggered**




- There are many different naming conventions

- For instance, many books call any bi-stable element **flip-flops** (such as an SR Latch)
- However, this **leads to confusion**, so we will use the convention above (as used in industry).


Latch Vs. Register

- A **Latch** is **transparent** during one phase of the clock and **keeps its output** (irrespective of the input) **during the other clock phase**.
- However, a **Flip Flop** only **samples the input on the edge**.

 


Static Vs. Dynamic Latch

 - **Dynamic storage elements store data** (the state) **as charge** on a capacitance
 - No active element involved in keeping the state
 - Since charge leaks away, the stored data degrades over time
- **Static storage elements include a feedback** to constantly restore the state
 - **Active feedback** involved in keeping the state: **KEEPER**




Dynamic Latch

 


Static Latch

Ratioed vs. Non-Ratioed Latch

 - **Writing** to the latch involves **overriding its internal state**
 - **Driver must prevail** over the internal keeper
- **Ratioed latch: strong driver overrides a weak keeper**
 - Sensitive to drive strength of the components
- **Non-ratioed logic: deactivate keeper while writing**





Static
Ratioed
Latch

 


Static
Non-ratioed
Latch

Disconnecting the Feedback Driver

  
- Using a series transistor as a switch
- Which polarity to use: nMOS or pMOS → **both not very well suited...**
 - nMOS can only pass a strong zero
 - pMOS can only pass a strong one



 Vgs drops below Vth:
transistor turns off before
output reaches VDD



 
Vsg drops below Vth:
transistor turns off before
output reaches GND



Combine nMOS
and pMOS
to achieve full
swing output

Transmission (T) Gates and Tristate-Inverter



 
- Driving both strong '0' and '1' requires a “hybrid” nMOS/pMOS switch
- Two almost identical options:



- Each part of the switch still used where it is most effective (almost no impact on on-resistance)
- Reduced output load

Robust Latches



- As **basic building blocks**, latches **need to be robust** and work in all conditions
- Ensuring a **clean input interface** (capacitive load)
 - Add extra input inverter to T-gate OR
 - Use a tristate input inverter
- **Protecting the storage node (SN)**
 - Any spikes (e.g., from coupling or kickback) on the output (from external circuits) can alter the state
 - Shield output from the storage node with an inverter

   



Latch Polarities

- Latches can be built with **different polarities**

Low-Transparent

  


High-Transparent

  

Master-Slave Register (Flip Flop)

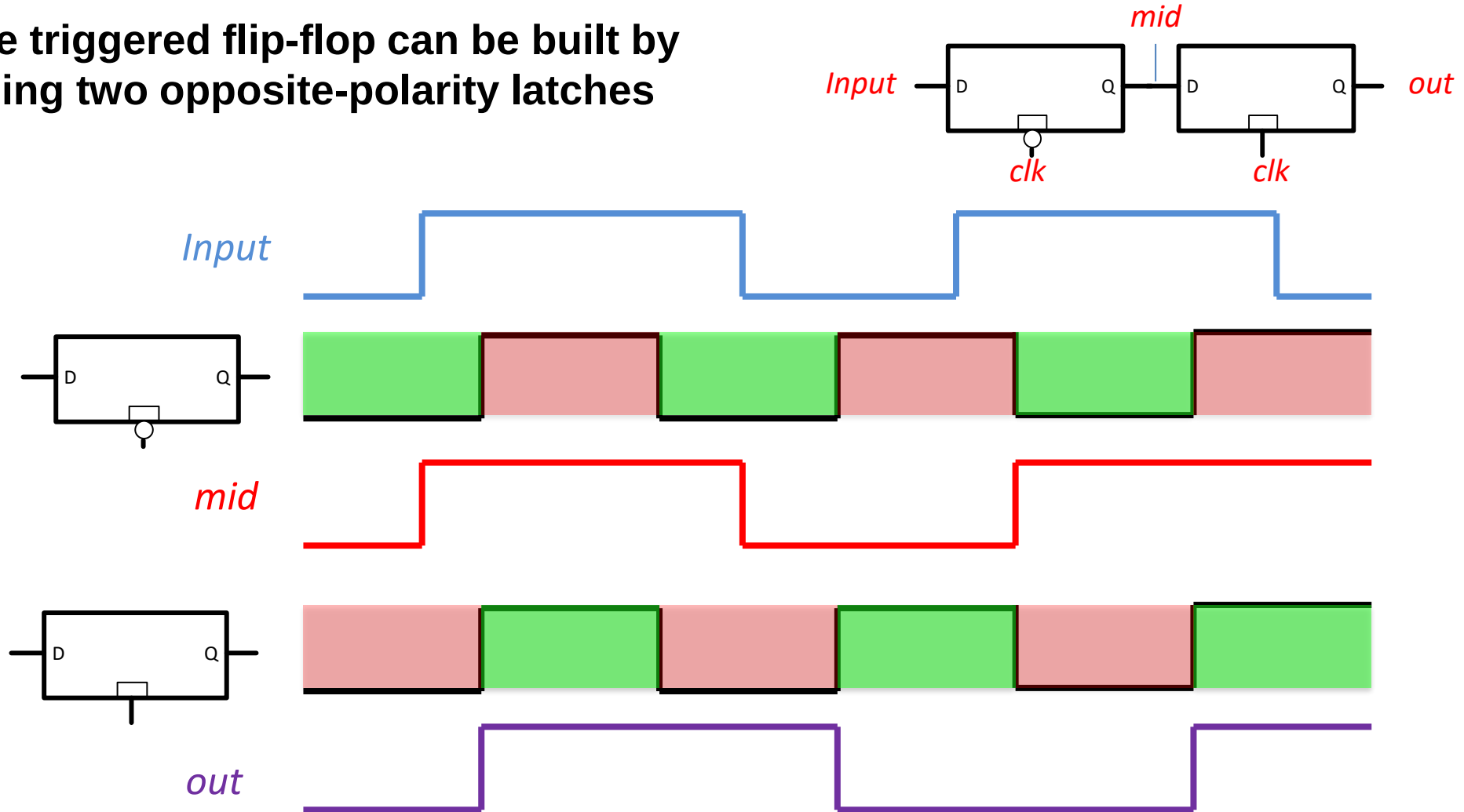
- An edge triggered flip-flop can be built by combining two opposite-polarity latches



Master-Slave Register


- **Basic ingredients**

 - Two tristate-based pair of latches
- Output buffers to shield the SN
- Input buffer to present a capacitive load
- Output inverters to isolate the storage node




Set / Reset

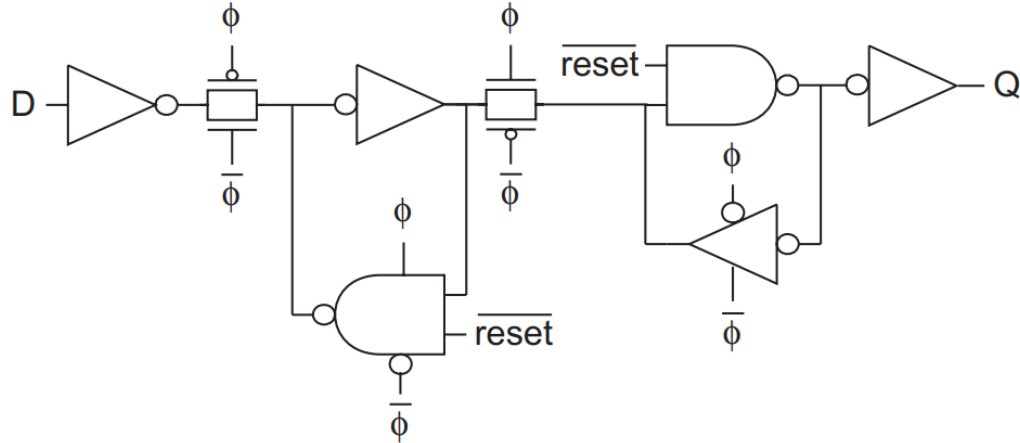- To reach a known initial state, **most FFs need to be set and/or reset**
 - Set/Reset refer to **ASYNCHRONOUS set/reset** (state change independent of clock)
 - Typically either set or reset (both is rare)
- Circuit design examples:
 - **Set/reset** required **on BOTH** master and slave **latches**





RESET
(low active)

 

SET and RESET (low active)

Flip-Flop Delay and Timing Requirements

  - As opposed to logic, **Flip-Flops have a delay and timing requirements**
 - Propagation delay t_{cq} : defined from CLK-input to Q-output
 - Setup time t_{su} : defined from D-input to CLK-input
 - Hold time t_{hold} : defined from CLK-input to D-input



Impact of Timing Requirements

- **Timing requirements for all register-to-register paths**

- Path starts from the clock pin of a register and ends on the data pin of a register


- **Setup condition:** latest arrival

$$\underbrace{t_{pd}^{FF} + t_{pd}^{logic}}_{t_{ss}^{max}} < t_{clk} - t_{setup}^{FF}$$

**Determines
maximum
frequency**


- Hold condition: earliest arrival
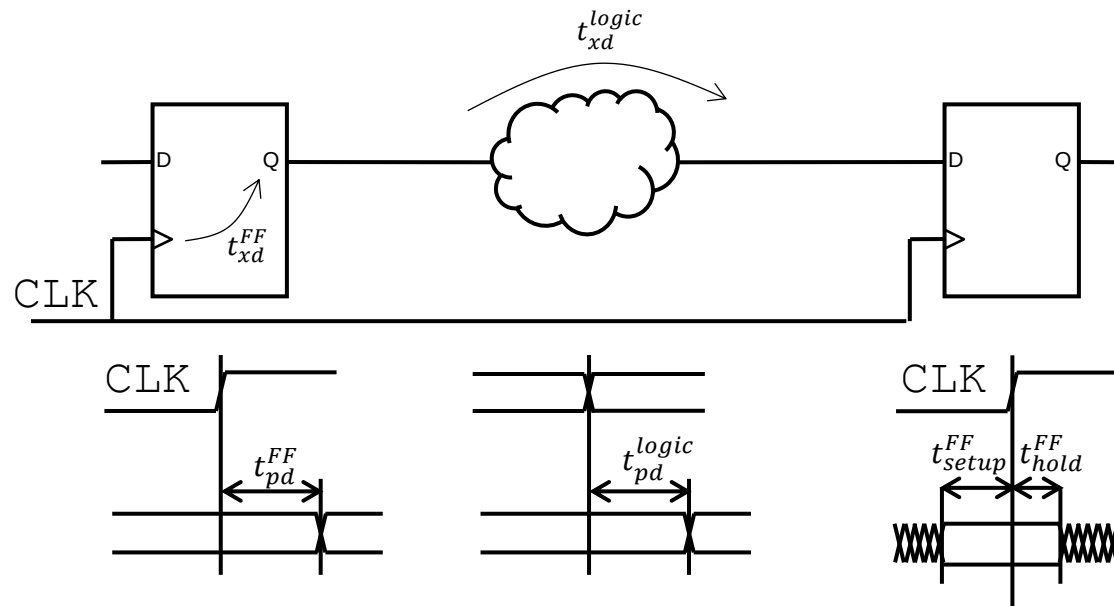
$$\underbrace{t_{cd}^{FF} + t_{cd}^{logic}}_{t_{ss}^{min}} > t_{hold}^{FF}$$




Propagation Delay Calculation

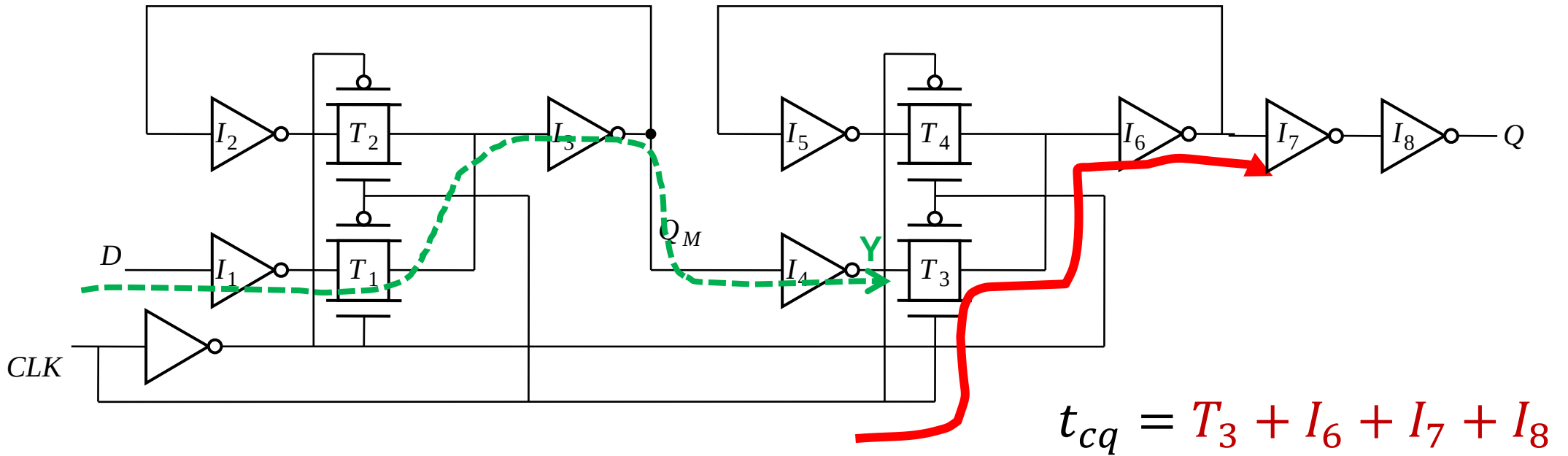- **Output changes when slave latch turns transparent** after positive clock edge
 - New output already stable at node **Y (slave latch T-gate input)**
- **When clock rises, data still has to propagate through pass gate and inverter**




Setup Time Definition

 - **Setup time is the time the data has to arrive *before* the clock to ensure correct sampling**



Setup Time Calculation

 
- **Master latch closes on positive clock edge**
 - Feedback loop of the **latch SN** must be stable at the new value before opening
- **Before the clock edge, data should have propagated to SN to avoid restoration of the previous state**



$$t_{su} = I_1 + T_1 + I_3 + I_2 = T + 3I$$

Hold Time Definition

 
- Hold time is the time the data has to be stable *after* the clock to ensure correct sampling.



- Often (optimally), Hold Time is *negative*!

Hold Time Calculation


 
- **Master latch closes on positive clock edge**
 - SN must be stable until driving T-gate closes
 - Additional delays in the data path help to keep SN even after the input changes
- **The hold time can be negative**




$$t_{hold} = -I_1$$

Impact of Setup Violations & Simulation

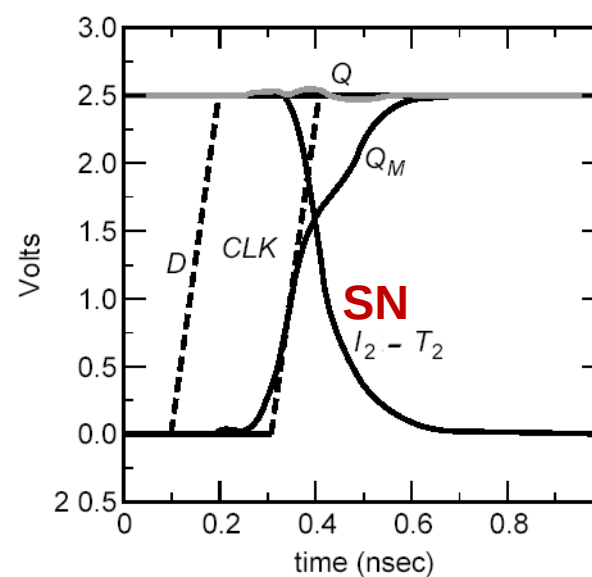 - **Example** for setup violation
 - SN: storage node (inverted)
 - QM: output of the master latch
- We obtain the **setup time** of the register using **SPICE simulations**, by progressively skewing the input with respect to the clock edge until the circuit fails



 (a) $T_{\text{setup}} = 0.21 \text{ nsec}$






(b) $T_{\text{setup}} = 0.20 \text{ nsec}$

Impact of Marginal Setup Condition

- **Setup violations do not always cause a complete failure (error)**

   
- Marginal triggering leads to increase in the propagation delay before failing
- Timing models do not represent this case properly
- Constraints are for accuracy to ensure timing analysis remains valid



Simulation Based Setup/Hold Characterization


- **Setup/hold can not be measured directly** (requirements rather than delays)
- **Two options to bound these requirements**

 1. Brute force simulations (trial and error) with pass fail constraint based on correct output or clk->Q delay constraint




 
2. Conservative constraint based on delays of data and clock to internal nodes to ensure sufficient margins for proper operation

- Setup: **A** must be stable (new value) before Tgate opens:
 $T_{su} = T(D \rightarrow A) - T(CLK \rightarrow T_2)$
- Hold: **B** must be stable (old value) until T-gate closes:
 $T_{ho} = T(CLK \rightarrow T_1) - T(D \rightarrow B)$




Metastability

  - **Metastability:** third, **instable state** in bi-stable circuits
- **Metastability can** happen when violating setup/hold times
 - **Metastability** is a temporary phenomenon and **resolves by itself after some time**
 - **Time to resolve** must be considered a **random** variable (uncertain)



Metastability Failure Mechanism

 - Time available to resolve a metastability depends on the available **margin S (slack)** **with no metastability** t_{slack}
- Any **metastability reduces** this **timing slack**
- If **no slack remains** (zero or negative slack), **timing errors occur in the next flip-flop**
 - Circuit no longer operates correctly (FAILURE)



Mean-Time-Between-Failure (MTBF)

- Since metastability duration varies, not every metastability leads to an error
- **Mean-Time-Between-Failures (MTBF)** provides an estimate of the reliability
- **The MTBF depends on**
 - Distribution of the metastability duration
 - The available timing slack t_{slack}
 - How often a potentially metastable data input signal toggles f_{DATA}
 - How often the data input signal is sampled (i.e., the sampling clock) f_{CLK}
 - Some empirically determined constants that depend on process, operating conditions, circuit, ... : T_0, τ_s

Failures per second



$$P_{failure} = T_0 \cdot f_{DATA} \cdot f_{CLK} \cdot e^{-t_{slack}/\tau_s}$$

$$MTBF = \frac{e^{t_{slack}/\tau_s}}{T_0 \cdot f_{DATA} \cdot f_{CLK}}$$


Reasons for Metastability Failures

- A well-built synchronous circuit with the right clock should never face metastability issues (ensured by static timing analysis)
- Unfortunately, still sometimes inputs are not synchronized to their clock
- Examples:

Example 1:
asynchronous primary inputs
(buttons or low-frequency inputs from other chips)

  

 
Example 2:
signals between asynchronous clock domains



Measures to Reduce Impact of Metastability


- If metastability can not be avoided we need to reduce its impact
- Three main principles to reduce impact of metastability (reduce risk of failure)

 Avoid any logic in potentially metastable signals



NO FANOUT: only impact one subsequent register

 MAXIMIZE time to resolve metastability before using the signal



EE-429


Fundamentals of VLSI Design

More Sequential Elements

Andreas Burg


The Clock Overlap Problem

 - Master/Slave FlipFlops use both CLK and $\overline{CLK}$, which is generate from CLK
 - Generating $\overline{CLK}$ from CLK usually involves a delay
 - Locally generating $\overline{CLK}$ may cause this delay when 2 inverters are used






The Clock Overlap Problem

- Delay of $\overline{CLK}$ leads to **clock overlap on both edges**
- During the overlaps both Master and Slave latches are briefly open
 - Signal can pass directly from input to output **causing a race-condition**

 


Solution 1: Clocked CMOS (C²MOS)

   - Master/Slave-FlipFlop from dynamic latches avoids sensitivity to clock overlap





Used a lot by IBM

 


Solution 2: True Single Phase Clock (TSPC) Latch

- **C²MOS still requires two clocks** a positive and an inverted one (overhead)
- **TSPC: different Master/Slave structures** for different phases with same clock
 - Two subsequent inverters that keep either a ZERO (high-transparent) or a ONE (low-transparent)
 - Input levels of '0' and '1' are kept on two different nodes

  


Solution 2: TSPC Latch with Integrated Logic

 - **TSPC latches allow to replace the initial inverter with any PMOS/NMOS network to realize an integrated logic function**




 
Arbitrary Logic in an TSPC Latch ('1' transparent)



 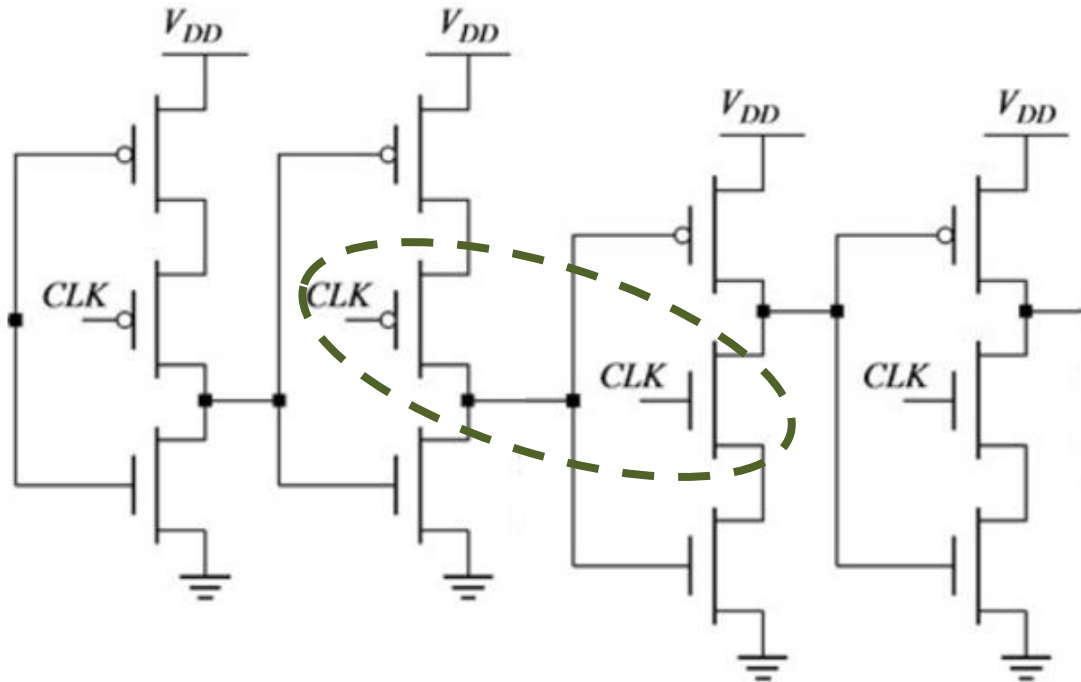Example: 2-input AND

Solution 2: TSPC FlipFlops



- TSPC FlipFlops are built by **two TSPC latches in Master/Slave configuration**
- **Two center-stages can be combined** to remove one stage
 - Results in an **inverted output**



Compact TSPC FF with
shielded output


Solution 3: Pulsed (dynamic) Latch as FlipFlop

  - **Build a FlipFlop from a latch that is triggered by a short pulse**
 - Pulse generator (dynamic EDGE detector) built from delay elements
- **Many different forms: static, dynamic, single and double-edge triggered**
- **Main issue: pulse duration is tradeoff between robustness and hold time**



Dual/Double Edge Triggered FlipFlops

 - In single-edge (positive or negative) edge-triggered logic, one (the inactive) transition of the clock signal has no functional role
 - Every “operation” cycle requires two clock transitions => inefficient in terms of power
- **Solution:** dual-edge triggered FlipFlops store data on both (positive and negative) clock edges



Dual/Double Edge Triggered FlipFlops (cont.)

- Different realizations of dual-edge triggered FlipFlops are possible
- Most straightforward and most practical **implementation is based on two latches and a MUX**
 - Setup and hold times defined by a latch
 - No clock-overlap problem
 - Clock load is higher than for a simple single-edge triggered FlipFlop (power!!)
 - Need to avoid sneak-paths through the MUX between latches during switching

