
Analog Integrated Circuits Design (2024-25)

- **MOST Operation, Modelling**
 - [13-17 Sep](#) MOSFETs: Operation and Modelling
 - [20-24 Sep](#) Noise1 : (in time and frequency domains)
 - [27 Sep-1 Oct](#) Noise-2 : (Analog circuits noise analysis)
- **Voltage references and regulators**
 - [04 Oct](#) Current Sources and Mirrors
 - [08 Oct](#) Voltage and Temperature independent References
 - [11 Oct](#) Exercises
- **OTA and Op-Amp Design**
 - [15 Oct](#) OTA Analysis and Design (DC, AC, Stability ...) (1)
 - [18-22-25 Oct](#) Vacation
 - [29 Oct](#) OTA Analysis and Design (DC, AC, Stability ...) (2)
 - [1 Nov](#) **Lab1-a: OTA Structural Design (g_m/I_D Methodology) theory**
 - [05 Nov](#) **Lab1-b: OTA Structural Design (g_m/I_D Methodology) Lab (CO5)**
 - [08 Nov](#): Multistage OTA (Stability and Frequency Compensation)
 - [12 Nov](#): Fully-Diff Amplifiers & CMFB
 - [15 Nov](#): Variability, offset and noise in OpAmp (1)
 - [19 Nov](#) **Lab2: Fully diff dolted cascode amplifier & its CMFB (CO5)**
 - [22 Nov](#): Variability, offset and noise in OpAmp (2)
 - [26 Nov](#): Rail to Rail input and output amplifiers
- **Mixed-signal design**
 - [29 Nov](#): Comparators
 - [03 Dec](#) **Lab3: Comparators (CO5)**
 - [06-10 Dec](#): AD and DA converters (introduction)
 - [13 Dec](#): Digital calibration of analog circuits
- [20 Dec](#) General revision (zoom)

Variability, offset and noise in OpAmp

A. KOUKAB


Swiss Federal Institute of Technology (EPFL)

Outline

- Variability and Mismatch in CMOS technology
 - Global vs Local Process variations
 - Statistical Analysis (Standard deviation)
 - Design techniques for better matching
 - Layout techniques for better matching
- DC-offset
 - Random offset
 - Systematic offset
 - Impacts on analog and mixed-signal design
- Noise
 - Background
 - Noise in OTA (simple and advanced topologies)
 - Basic methodology for low noise

Process Variation and Mismatch

 - Studies of amplifiers usually assume the circuits are perfectly symmetric
- In reality nominally-identical devices suffer from a finite mismatch




- Variation in process parameters
 - Oxide thickness
 - Doping Profile of the channel
 - Channel length/width
 - Silicon/oxide interface traps and charges
 - ...
 - Variation in electrical parameters
 - Threshold voltage mismatch ΔV_{th}
 - Current factor mismatch $\Delta \beta$
- Impact the performances


Global vs Local Process variations

- Two categories of process variations Global and Local:
- **Global Process variation or Corners:**
 - Represent the parameter variations from **wafer-to-wafer** and lot-to-lot.
 - Five corners: (TT/FF/SS/FS/SF): F, S, T means Fast, Slow, Typical
 - The first letter refers to nMOS, and the second to pMOS.
 - Independent on the design and layout.
 - More important in digital design
- **Local Process Variation or Mismatch**
 - Represent the parameter variations from **device to device** on the same circuit.
 - Dependent on the design and layout.
 - More important in analog design (diff pair, mirrors ...)
 - Characterized by a statistical model (standard deviation σ).

 Local Process Variation and Mismatch LPVM: Statistical Analysis (Standard deviation)



Measure Param. (ex V_{th})

 

- 99.73% of the devices have their $P \in [\bar{P} - 3\sigma, \bar{P} + 3\sigma]$
- Larger components exhibit smaller mismatches

$$\sigma = \frac{A}{\sqrt{WL}}$$

$$\frac{\sigma_\beta}{\beta} = \frac{\sigma_{kp}}{kp} = \frac{A_\beta}{\sqrt{WL}} \quad \text{and} \quad \sigma_{V_{T0}} = \frac{A_T}{\sqrt{WL}}$$

foundry

Characteristics of σ

$$\sigma_{F(X,Y)}^2 = \sigma_X^2 \left(\frac{\partial F}{\partial X} \right)^2 + \sigma_Y^2 \left(\frac{\partial F}{\partial Y} \right)^2; \quad \sigma_{G(X,Y)}^2 = \sigma_{F(X,Y)}^2 \left(\frac{dG}{dF} \right)^2$$

Mismatch calculation of I_D and V_G and their optimization by design

- A simple mismatch Model for I_D and V_G (in SI and Sat):
 - based on the assumption that V_T and β are independent

$$I_D = \frac{\beta}{2} (V_G - V_T)^2 ; \quad V_G = \sqrt{\frac{2I_D}{\beta}} + V_T \quad \text{and} \quad \frac{g_m}{I_D} = \frac{2}{V_G - V_T}$$

➤ $\frac{\sigma_{I_D}}{I_D} = ?$

$$\sigma_{I_D(\beta, V_{T0})}^2 = \sigma_{\beta}^2 \left(\frac{\partial I_D}{\partial \beta} \right)^2 + \sigma_{V_{T0}}^2 \left(\frac{\partial I_D}{\partial V_{T0}} \right)^2$$

$$\left(\frac{\sigma_{I_D}}{I_D} \right)^2 = \left(\frac{\sigma_{\beta}}{\beta} \right)^2 + \sigma_{V_{T0}}^2 \left[\frac{2}{V_G - V_{T0}} \right]^2 = \left(\frac{\sigma_{\beta}}{\beta} \right)^2 + \sigma_{V_{T0}}^2 \left[\frac{g_m}{I_D} \right]^2$$

To minimize $\Delta I_D \rightarrow$ we have to minimize $g_m / I_D \rightarrow$ Strong Inv.

➤ $\sigma_{V_G} = ?$

$$\sigma_{V_G(\beta, V_{T0})}^2 = (\sigma_{I_D})^2 \left(\frac{dV_G}{dI_D} \right)^2 = \left(\frac{\sigma_{I_D}}{g_m} \right)^2 = \left[\frac{I_D}{g_m} \right]^2 \left(\frac{\sigma_{\beta}}{\beta} \right)^2 + \sigma_{V_{T0}}^2 = \left[\frac{I_D}{g_m} \right]^2 \left(\frac{\sigma_{I_D}}{I_D} \right)^2$$


To minimize $\Delta V_G \rightarrow$ we have to maximize $g_m / I_D \rightarrow$ weak inv.

Outline


- Variability and Mismatch in CMOS technology
 - Global vs Local Process variations
 - Statistical Analysis (Standard deviation)
 - Design techniques for better matching
 - Layout techniques for better matching
- DC-offset
 - Random offset
 - Systematic offset
 - Impacts on analog and mixed-signal design
- Noise
 - Background
 - Noise in OTA (simple and advanced topologies)
 - Basic methodology for low noise

Layout technics for a better matching

 Interdigitated and Common centroid Layout



$G_{1,2}$ to D_1 contact

 


Objective:

On average, the two devices occupy the same location on the wafer


→ to distribute evenly the influences of process parameters or temperature gradients

 → to minimize electrical parameters mismatch e.g. V_T and β .




More sophisticated Layout

 Guard ring: a ring of contacts encircles the two transistors, providing a low and the same resistance of the body terminals to the ground or V_{DD} → To avoid problems such as latch-up and substrate coupling.



Dif. Pair

 


Dummy fingers at the borders → to keep the same environment for each transistor. Their gates are connected to ground (resp. to V_{dd}) to ensure they are always turned off

Min C_{GD} : Drain connections are routed in the side opposite the gate routing, to minimize parasitic gate-drain (Miller) capacitance.

Layout rules for better matching


- Combine single-sized units to draw transistors (same L same W)
- Keep the layout of the matched transistors as compact as possible
- Orient transistors in the same direction (keep current propagation symmetrical)
- Use interdigitated fingers and common-centroid layout
- Add dummy fingers (in the borders)
- Add a ring of contacts (guard ring) encircling the transistors.
- Use several contacts to connect two different layers in order to reduce interlayer resistance (via are quite resistive)
- Do not place contacts on top of active gate areas (Whenever possible, extend the poly beyond the diffusion and place the gate contacts over thick field oxide.
- Connect gate fingers using metal straps (avoid poly connections. Poly is a bad conductor).
- Do not route metal across the active gate area.

 


Outline

- Variability and Mismatch in CMOS technology
 - Global vs Local Process variations
 - Statistical Analysis (Standard deviation)
 - Design techniques for better matching
 - Layout techniques for better matching
- DC-offset
 - Random offset
 - Systematic offset
 - Impacts on analog and mixed-signal design
- Noise
 - Background
 - Noise in OTA (simple and advanced topologies)
 - Basic methodology for low noise

Random DC-offset: (diff. pair)

 


Ideal diff. pair

 

Real diff. pair
Random Mismatch effect

 $\sigma_{\text{cox}}, \sigma_{\mu}, \dots$




I_D Mismatch
to V_G mismatch
 $\rightarrow V_{\text{off}}$

$$\sigma_{V_{\text{off}}(\beta, V_{T0})}^2 = \left(\frac{1}{g_m} \right)^2 \sigma_{I_D}^2$$

OTA - Random Offset Voltage(V_{off})

with $\frac{\sigma_\beta}{\beta} = \frac{A_\beta}{\sqrt{WL}}, \sigma_{V_{T0}} = \frac{A_T}{\sqrt{WL}}, g_{m,diff} = g_{m1,2}, g_{m,mir} = g_{m3,4}$


$$\begin{aligned} \sigma_{V_{off}(\beta, V_T)}^2 &= \left(\frac{\sigma_{I_{D,dif}}}{g_{m,dif}} \right)^2 + \left(\frac{\sigma_{I_{D,mir}}}{g_{m,dif}} \right)^2 \\ &= \left[\frac{I_0}{2g_{m,dif}} \right]^2 \left(\frac{A_\beta^2}{W_{dif}L_{dif}} \right) + \frac{A_T^2}{W_{dif}L_{dif}} + \\ &\quad \left[\frac{I_0}{2g_{m,dif}} \right]^2 \left(\frac{A_\beta^2}{W_{mir}L_{mir}} + \frac{A_T^2}{W_{mir}L_{mir}} \left(\frac{2g_{m,mir}}{I_0} \right)^2 \right) \end{aligned}$$

 

min Offset $\rightarrow$ Maximize $g_{m,dif}/I_D$ and minimize $g_{m,mir}/I_D$
 $\rightarrow g_{m,dif} \gg g_{m,mir}$
 i.e. Diff pair in weak inversion and Active load in strong inversion


Systematic or Electrical DC-offset: (Ex. Miller Amp)

 - Offset due to asymmetries in the circuits.
- For instance, here, M3 is diode-connected but not M4.
- In addition V_{SD4} is set by M6 ($V_{SD4} = V_{GS6}$)



Systematic DC-offset: Design solution

 - M_4 , M_3 and M_6 are carefully matched



$$(W/L)_{M7} = K(W/L)_{M5}$$

- Condition for a low systematic offset :
- $I_{D3} \approx I_{D4} \approx I/2 \rightarrow V_{SD4} \approx V_{SD3} \approx V_{SG3}$

Since $V_{SD4} = V_{SG6}$
 $\rightarrow$ we should have $V_{SG6} \approx V_{SG3}$

$$(W/L)_{M6} = 2K(W/L)_{M4,3}$$

- Residual systematic offset at the input :



$$V_{os,sys} = (V_{D3} - V_{D4})/A_{v1}$$

$$\text{With } A_{v1} = g_{m1}/(g_{DS1} + g_{DS4})$$

Offset in Comparators

- Nominally-identical devices of OTA suffer from a finite mismatch
→ represented by an input-referred DC offset voltage

Model of real OTA

 
 


For comparators

$\pm 3\sigma(v_{io})$ = lower bound
on ΔV that can be
detected reliably


- Several Offset cancellation Technics exist:
- It is worth noting that these technics usually also reduce LF noise and drift

  Lack of accuracy in CMOS comparators: Consequences in ADC Performance



Theoretical Yield on monotonicity (i.e. The probability that the comparators switch in the correct order), here for a signal swing is 2 V

 Consequences on dynamic range of amplifiers




DC Offset (meanly V_{io1}) may experience so much gain that it drives the latter stages into nonlinear operation.

Outline

- Variability and Mismatch in CMOS technology
 - Global vs Local Process variations
 - Statistical Analysis (Standard deviation)
 - Design techniques for better matching
 - Layout techniques for better matching
- DC-offset
 - Random offset
 - Systematic offset
 - Impacts on analog and mixed-signal design
- Noise
 - Background
 - Noise in OTA (simple and advanced topologies)
 - Basic methodology for low noise

Background 1

MOSFET

 


$$\overline{i_n^2} = 4kT\gamma g_m$$

(Thermal noise)

$$\overline{v_n^2} = \frac{K}{C_{ox}LW} \cdot \frac{1}{f}$$


(Flicker noise)

 

$$\overline{v_n^2} = 4kT\gamma \frac{1}{g_m} + \frac{K}{C_{ox}LW} \cdot \frac{1}{f}$$

(Thermal noise + Flicker noise)

Common source Amp

 


$$\overline{v_{n,i}^2} = \frac{\overline{v_{n,o}^2}}{|A_v|^2} = 4kT\gamma \frac{1}{g_{m1}} \left(1 + \frac{g_{m2}}{g_{m1}} \right) + \frac{K}{C_{ox}(LW)_1} \cdot \frac{1}{f} + \left(\frac{g_{m2}}{g_{m1}} \right)^2 \frac{K}{C_{ox}(LW)_2} \cdot \frac{1}{f} \quad [\text{V}^2/\text{Hz}]$$

$$\overline{v_{n,i}^2} \searrow \text{ if } g_{m1} \nearrow \text{ and } g_{m2} \searrow$$

Background 2

Diff Amp

 


Half circuit $\equiv$ CS amp

$$\overline{v_{n,i}^2} = 2 \times \left[4kT\gamma \frac{1}{g_{m1}} \left(1 + \frac{g_{m2}}{g_{m1}} \right) + \frac{K}{C_{ox}(LW)_1} \cdot \frac{1}{f} + \left(\frac{g_{m2}}{g_{m1}} \right)^2 \frac{K}{C_{ox}(LW)_2} \cdot \frac{1}{f} \right]$$

$\overline{v_{n,i}^2}|_{T_0}$ negligible (common mode rejection)


Cascode

 

$\overline{v_{n,o}^2}|_{T_2}$ negligible (degenerated CS: $\frac{v_o}{v_{pe}} \approx \frac{g_{m2}r_{op}}{1+g_{m2}r_{o1}} \approx \frac{r_{op}}{r_{o1}}$ close to 1)


$$\overline{v_{n,o}^2}|_{T_1} = \left(4kT\gamma \frac{1}{g_{m1}} + \frac{K}{C_{ox}(LW)_1} \cdot \frac{1}{f} \right) \left(\overbrace{g_{m1} (r_{op} \parallel g_{m2}(r_{on1}r_{on2}))}^{>> 1} \right)^2$$

Noise in Telescopic Amp.

 


- Give the main noise contributors
- Determine the input-referred noise $\overline{v_{n,i}^2}$
- Propose I_F (or V_{ov}) of the transistors to optimize the noise
- Discuss the resulted tradeoffs (noise vs offset, dynamic range and consumption)
- Propose a solution to optimize flicker noise

Noise in Folded cascode amp.

 

- Give the main noise contributors and compare with Telescopic
- Determine the input-referred noise $\overline{v_{n,i}^2}$
- Propose I_F (or V_{ov}) of the transistors to optimize the noise
- Discuss the resulted tradeoffs (noise vs offset, dynamic range and consumption)

Noise in Miler amp.

 

- Give the main noise contributors
- Determine the input-referred noise $\overline{v_{n,i}^2}$
- Propose I_F (or V_{ov}) of the transistors to optimize the noise
- Comment on V_{ov} of T_L
- Compare with the other topologies