 



Parameter		Value Extracted	Unit
K_p	PMOS	90	$\mu A/V^2$
	NMOS	220	
U_a	PMOS	10	$V/\mu m$
	NMOS	14	
V_{T0}		0.4	V
n	PMOS	1.25	-
	NMOS	1.2	
C_{ox}		13	$fF/\mu m^2$
C_{ov}		0.2	$fF/\mu m$

 1. Analyse the functionality of a comparator

Comparator with the internal positive feedback



Note the inverters are added at the output in order to ensure positive and negative saturation voltages equivalent to the logical one ($=V_{DD}$) and the logical zero ($=V_{SS}$) interpretable by digital circuits.



Describe in your own words how this comparator works taking into account the inverter transfer characteristics reported here and supposing a positive feedback factor $k=1$.

VOH	1.2 V
VOL	0 V
VM	0.6 V
VIH	~ 0.7 V
VIL	~ 0.5 V

.....

.....

.....

.....

.....

.....

.....

2. Size the comparator

- Create the schematic of the comparator and name it **COMP_FD**
 - Set the initial transistor sizes in order to minimize the parasitic capacitances by following the points listed below and explain briefly your calculations.
 - The bias transistor m_{BI} has to be sized to provide the differential pair tail current $I_0 = 4 \mu A$.
 - Choose the positive feedback factor $k = 1$;
- Set the size positive feedback transistors with minimum size $W=L= L_{min} = 65nm$;
- Size the differential pair transistors to operate in strong inversion ($I_F = 10$) and $L = 2L_{min}$.
 - Size the inverter with minimum size and to have $V_M = V_{DD}/2$

Check and save the schematic.

Transistor	W [μm]	L [μm]
M_{1,2}		
M_{3,6}		
M_{4,7}		
M_{BI}		

.....

.....

.....

.....


.....

.....

.....

3. Perform the DC analysis

Testbench_COMP_DC

 

The reference voltage connected to the negative input is equal to 0.6V.
The load capacitances correspond to the input parasitic capacitances of a D flip-flop, $C_L = 2\text{fF}$.

- Create the **Testbench_COMP_DC** cell.
- Choose **DC Analysis** and set the simulation parameters to sweep V_{in+} from 0 to V_{DD} .
- In order to plot the transfer curves, use the **vs** button and then choose in the schematic the corresponding node.

Note: The schematic has hierarchy, to visualize the transistors of the comparator you have to select the COMP_FD symbol in the schematic and descend into the transistor level view:

1 - First run

Perform the DC analysis for the initial transistor sizes. Descend to schematic view of the **COMP** cell and plot the following voltages: **vs (OUTn)**, **vs (OUTp)**, **vs (OUT+)**, **vs (OUT-)**.

If the comparator **does not switch the state**. Explain why:

.....

.....

.....

.....

.....

2 - Second run: Same current, different sizes

If necessary, resize the positive feedback transistors, keeping $I_0 = 4\text{ }\mu\text{A}$ and $k=1$, in order to correctly switch the states.

.....

.....

.....

$$(W/L) = \quad W_3 = W_4 = W_5 = W_6 = \quad \mu m, \quad L_3 = L_4 = L_5 = L_6 = \quad \mu m$$

Choose the positive (OUTp) or negative (OUTn) output to measure the positive and negative saturation voltage at the input of the inverter:

$$\mathbf{V}_{\text{SAT}+} = \mathbf{V}, \quad \mathbf{V}_{\text{SAT}-} = \mathbf{V}$$

If necessary, resize the bias transistor m_{BI} , keeping the minimal dimensions of feedback transistors, in order to correctly switch the states.

$(I_0)_{\min} = \underline{\hspace{1cm}} \mu\text{A}$ $W_{\text{mBI}} = \underline{\hspace{1cm}} \mu\text{m},$ $L_{\text{mBI}} = \underline{\hspace{1cm}} \mu\text{m}$

Choose the positive (OUTp) or negative (OUTn) output to measure the positive and negative saturation voltage at the input of the inverter:

$$V_{SAT+} = \frac{V_{SAT+}}{V_{SAT+}} V, \quad V_{SAT-} = \frac{V_{SAT-}}{V_{SAT-}} V$$

- Set the positive feedback transistors to minimal dimensions.**

.....


.....

.....

I_F diff pair	W/L diff pair	W diff pair
20		μm
10		μm
1		μm
0.1		μm

- Perform the transient analysis

Testbench_COMP_TRAN

 

- Create the **Testbench_COMP_TRAN** cell.
 - Choose Transient Analysis and set the simulation parameters.
 - Run the simulation.
 - In order to plot the transfer curves, use the vt button and then choose in the schematic the corresponding node.
- Determine large signal response delay:**

Set the pulse voltage source parameter **Voltage 1** to **0.2V** and **Voltage 1** to **1V**.
Perform transient analysis. Plot the following voltages: vt (IN+), vt (OUTn), vt (OUT+).

Fill in the table:

I_F diff pair	t_d (IN+, OUT+)	t_d (IN+, OUTn)	t_d (OUTn, OUT+)
20	ns	ns	ns
10	ns	ns	ns
1	ns	ns	ns
0.1	ns	ns	ns

Comment the results:

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

- **Determine small signal response delay:**

Set the pulse voltage source parameter **Voltage 1** to **0.59V** and **Voltage 2** to **0.61V**.
Perform transient analysis. Plot the following voltages: **vt (IN+)**, **vt (OUTn)**, **vt (OUT+)**.

Fill in the table:

I_F diff pair	t_d (IN+, OUT+)	t_d (IN+, OUTn)	t_d (OUTn, OUT+)
20	ns	ns	ns
10	ns	ns	ns
1	ns	ns	ns
0.1	ns	ns	ns

Comment briefly the results:

.....

.....

.....

- **Set the differential pair dimensions as calculated for $I_F = 1$ and $I_0 = 8 \mu A$.**

Set the pulse voltage source parameter **Voltage 1** to **0.2V** and **Voltage 2** to **1V**.
Compare the response delay for different I_0 values.

I_0	t_d (IN+, OUT+)	t_d (IN+, OUTn)	t_d (OUTn, OUT+)
8 μA	ns	ns	ns
16 μA	ns	ns	ns
32 μA	ns	ns	ns

Comment the results:

.....

.....

.....

.....

.....