 


LP Analog Design – Final Exam (Mock)

1. Fully differential folded cascode OTA: Procedural sizing

The purpose of this section is to provide the sizing procedure of the following OTA step-by-step. Starting by choosing circuit-level parameters (specifications) and propagating them to transistor level.



The technology used is CMOS 80nm 1.8V devices and their parameters are:

Parameter	Unit	
	Extracted	
K_p	PMOS	40
	NMOS	208
U_a	PMOS	16
	NMOS	5
n	PMOS	1.3
	NMOS	1.2
C_{ox}	8.3	fF/ μm^2

The OTA, have to meet the following specifications.

Parameter	Value		Unit
	Specification		
Open-loop gain	> 70		dB
GBW	60		MHz
Slew rate [SR]	50		V/ μs
Load capacitors [C_L]	100		fF

LP Analog Design – Final Exam (Mock)

1.1. Bias currents

	Parameter	Expression	Value	Unit	Guideline
Bias	I_o			μA	
	I_1	$1, 2 \times \frac{I_o}{2}$		μA	

1.2. Differential pair

Determine the transconductance, inversion factor and W/L ratio of the differential pair.

	Parameter	Expression	Value	Unit	Guideline
Differential pair	$g_{m1,2}$			μS	
	$I_{f1,2}$			-	
	$\frac{W_{1,2}}{L_{1,2}}$			-	

1.3. Folded cascode load

The 8 transistors composing the folded cascode stage will now be sized.

Determine the inversion factor and W/L ratio of these transistors to:

- Keep all saturation voltages of $m_{9,10}$, $m_{7,8}$, $m_{5,6}$ small
- Minimize the noise and offset contribution of m_3 and m_4
- For simplification, only two values will be chosen for the inversion factor: $I_F = 10$ or $I_F = 1$.

	Parameter	Expression	Value	Unit	Guideline
Folded	$\frac{W_5}{L_5}$				
	$\frac{W_7}{L_7}$				

LP Analog Design – Final Exam (Mock)

	$\frac{W_9}{L_9}$				
	$\frac{W_3}{L_3}$				

Calculate the output resistance necessary to meet the open-loop gain specification.

	Parameter	Expression	Value	Unit	Guideline
Rout	R_{out}			MΩ	

Neglecting the conductance of the differential pair (assume $g_{ds1} \approx 0.5g_{ds3}$), determine the conductance and length of all transistors so that:

- The specified open-loop gain is achieved
- The NMOS and PMOS resistances at the output node are balanced ($R_{up} = R_{down}$)
- The total area of the folded cascade stage is minimized (in the order of $85\mu\text{m}^2$)
 - m_7 and m_9 have the same length
 - The length of m_3 is two times the one of m_5

	Parameter	Expression	Value	Unit	Guideline
Rout	$n_{n,p} \times g_{m5,7}$			μS	
	R_{up}			MΩ	
	$L_7 \times L_9$			μm ²	
	L_9			nm	$L_7 = L_9$
	L_7			nm	$L_7 = L_9$
	R_{down}			MΩ	

LP Analog Design – Final Exam (Mock)

	$L_3 \times L_5$			μm^2	
	L_5			μm	$L_3 = 2L_5$
	L_3			μm	$L_3 = 2L_5$

Calculate the width of all transistors.

	Parameter	Expression	Value	Unit	Guideline
Rout	W_3	$\frac{W_3}{L_3} \times L_3$		μm	
	W_5	$\frac{W_5}{L_5} \times L_5$		μm	
	W_7	$\frac{W_7}{L_7} \times L_7$		μm	
	W_9	$\frac{W_9}{L_9} \times L_9$		μm	

1.4. Differential pair finalization & Current source

Find the length and the width of the differential pair.

Parameter	Expression	Value	Unit	Guideline
L_1			nm	$g_{ds1} \leq 0.5g_{ds3}$
W_1			μm	

Parameter	Expression	Value	Unit	Guideline
L_{B1}			nm	
W_{B1}			μm	

LP Analog Design – Final Exam (Mock)

1.5 Offset Estimation:

In case of the above folded cascade, give the expression of the input referred offset that include the contribution of Differential pair: $m_{1,2}$; Folded cascode: $m_{3,4}$ and Active load: $m_{9,10}$

$$\sigma_{V_{os}}^2 =$$

$$\sigma_{I_D(\beta, V_{T0})}^2 = \sigma_{\beta}^2 \left(\frac{\partial I_D}{\partial \beta} \right)^2 + \sigma_{V_{T0}}^2 \left(\frac{\partial I_D}{\partial V_{T0}} \right)^2$$

$$\text{Theoretical reminder: } \sigma_{V_G}^2 = \frac{\sigma_{I_D}^2}{g_m^2} = \sigma_{\beta}^2 \left(\frac{I_D}{\beta} \right)^2 + \sigma_{V_{T0}}^2 (g_m)^2$$

1.6 Common-mode feedback CMFB

Propose a CMFB circuit that use two differential pairs to tune the gate voltage of MB1 and set the common-mode output voltage to $V_{DD}/2$. Show how this CMFB circuit is connected to the fully differential cascode OTA (i.e. give the name of its input and output nodes):

CMFB schematic:

Family Name:

First Name:

Test

29/11/2019

8h15/10h45

LP Analog Design – Final Exam (Mock)

1.7 Propose and size an optimal biasing circuit for $V_{\text{Bias0-3}}$