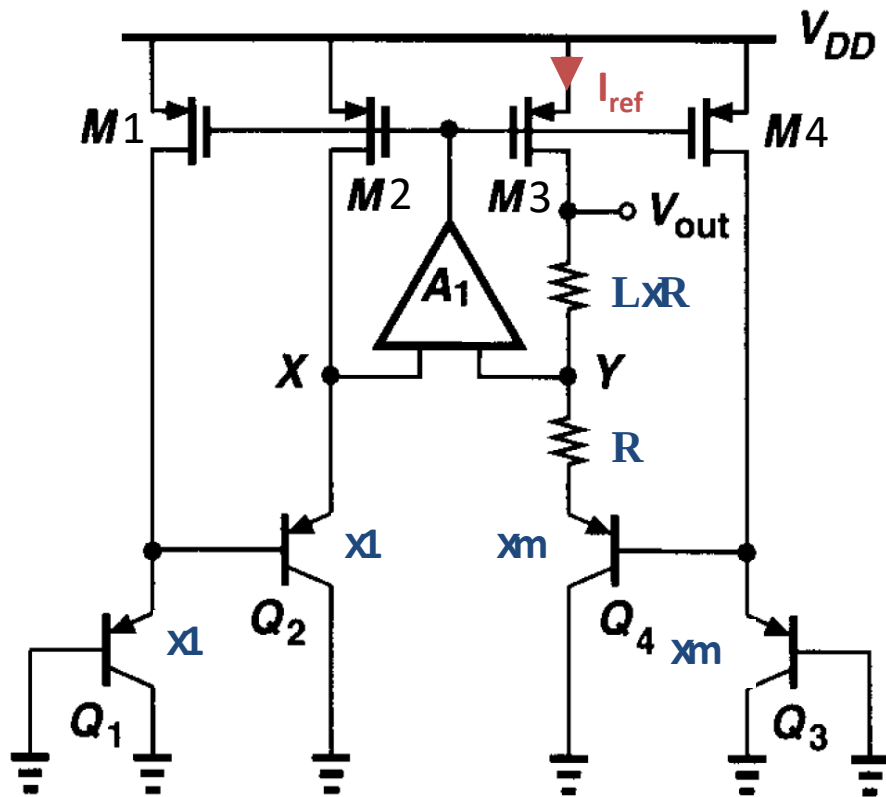


Bandgap reference



Neglect the channel modulation of the MOSFETS and the base currents of the BJTs. The OpAmp is supposed ideal. Q4 and Q3 are composed on m bipolars in parallel.

- 1- Show the inverting and non-inverting node of the OpAmp on the schematic and justify your choice.

Without loop V_Y is higher than V_X , due to the resistor R . the negative feedback at Y set lower V_Y and set it equal to V_X . Since the OpAmp drives an inverting stage (i.e. common source amp.), negative feedback at Y means non-inverting node is Y .

- 2- Give the expression of I_{ref} versus temperature. Is-it PTAT or CTAT?

$$I_{ref} = 2 n U_T \ln(m) / (R) = 2 n k T \ln(m) / (q R), \text{ PTAT if TCR is negative.}$$

- 3- Give the expression of V_{out} and $\partial V_{out} / \partial T$.

$$V_{out} = 2n (L+1) U_T \ln(m) + V_{eb4} + V_{eb3} \approx 2n (L+1) U_T \ln(m) + 2V_D$$

$$\partial V_{out} / \partial T = (85 \mu V / ^\circ C) 2n (L+1) \ln(m) + 2(-1.6 mV / ^\circ C)$$

- 4- Determine the value of L in order to have a bandgap reference (i.e. Temperature independent reference). (2pts)

$$L = 3,2 \cdot 10^3 / (170 \ln(m)) - 1$$

5- Numerical application: For $m = 8$, $T = 300K$ and $n = 1$

a. Determine: L , and V_{out} . (2pts)

$$L = 3,2 \cdot 10^3 / (170 \ln(8)) - 1 = 8$$

$$V_{out} = 2n (L+1)U_T \ln(m) + V_{eb4} + V_{eb3} = 2n (L+1)U_T \ln(m) + 2nU_T \ln(I_{ref}/mI_s)$$

We cannot calculate precisely V_{out} if we don't know the values of I_{ref} , m and I_s . We can only estimate its value by using the approximation:

$$V_{eb} = nU_T \ln(I_{ref}/mI_s) \approx 0.7V \text{ and thus:}$$

$$V_{out} \approx 2 (8+1) 26 \cdot 10^{-3} \ln(8) + 2 \times 0.7 \approx 2.37 V$$

6- Assume that bipolar transistors have a finite current gain β (i.e. we consider their base currents). Calculate the error in the output voltage V_{out} .

$$\begin{aligned} V_{out}^* &= 2n(L+1)U_T \ln(m) + V_{eb4} + V_{eb3} \\ &= 2n(L+1)U_T \ln(m) + nU_T \ln(I_{ref}/I_s) + nU_T \ln((I_{ref} + I_b)/I_s) \text{ avec } I_b = I_{ref}/\beta \\ &= 2n(L+1)U_T \ln(m) + 2nU_T \ln(I_{ref}/I_s) + nU_T \ln(1 + \beta^{-1}) \\ &= V_{out} + nU_T \ln(1 + \beta^{-1}) \end{aligned}$$

The error due to finite current gain β is $nU_T \ln(1 + \beta^{-1})$

7- Suppose that OpAmp has an offset voltage V_{os} (i.e. Voltage difference at the input of the OpAmp $V_+ - V_-$ is not zero but V_{os}). Calculate the error in the output voltage V_{out} . (2pts)

$$\text{Consider that } V_{os} = V_Y - V_X$$

$$\text{In this case } I_{ref} = 2n U_T \ln(m) / (R) + V_{os}/R$$

And

$$V_{out}^* = 2n (L+1)U_T \ln(m) + V_{eb4} + V_{eb3} + (L+1) V_{os}$$

The error due V_{os} is $(L+1) V_{os}$

8- Comment on the effect of the two BJT branches compared to the topology with only one BJT branch. (2pts)

Band gap with two BJTs allows for a higher V_{out} for while the effect of V_{os} remains the same.

9- Is this topology useful for a sub-1V bandgap?

No the minimum value of V_{out} is about 1,4 V due to the stack of the two BJTs.