

Microwaves

Series 3

Problem 1

A lossless transmission line is terminated with a $100\ \Omega$ load. If the SWR of the line is 1.5, find the two possible values for the characteristic impedance of the line

Problem 2

A radio transmitter is connected to an antenna having an impedance $80+j40\ \Omega$. with a $50\ \Omega$ coaxial cable. If the transmitter can deliver 30W to a $50\ \Omega$ load, how much power is delivered to the antenna ?

Problem 3

Use the Smith chart to find the following quantities for the transmission line circuit below :

- a) the SWR of the line
- b) the reflection coefficient at the load
- c) the load admittance
- d) the input impedance of the line

