
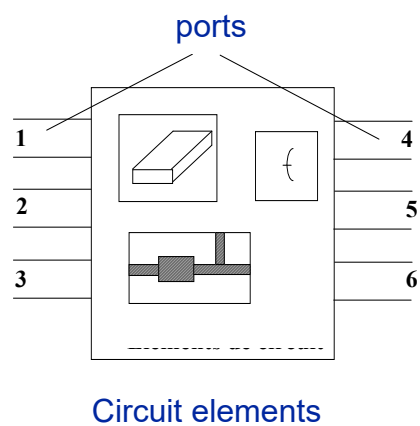


Microwave circuit characterization

Microwave component

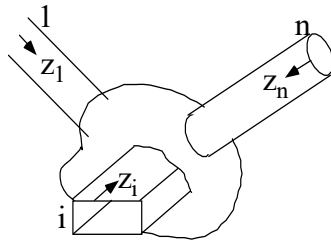

Reference planes



On each access line i of a component, a coordinate axis z_i is defined. The origin of this axis lies in the reference plane of the port i .


Assumptions :

- The transmission lines are lossless
- They support only the dominant mode
- The reference plane is distant enough from discontinuities to ensure that the Higher order modes are attenuated

Available models

- Kirchhoff
 - Currents and voltages ill defined
 - Well known from low frequency circuit analysis
 - Not adapted to system approach
- Scattering matrix
 - Based on signal and power
 - Well suited to microwaves
 - Not known from low frequency circuit analysis
 - Adapted to system analysis

Kirchhoff's model

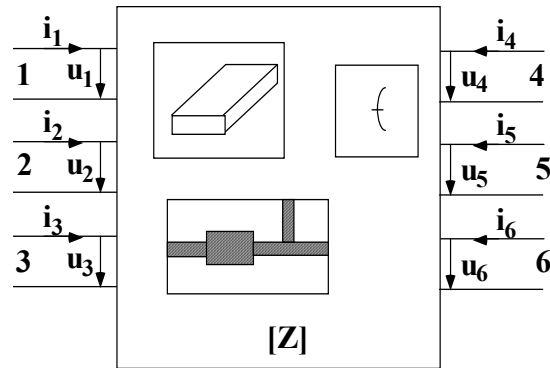


Current, voltages and impedances

Current voltages and impedances

- Easy to use
- Current and voltage difficult to measure
- Current and voltage not always uniquely defined

Example : TEM line

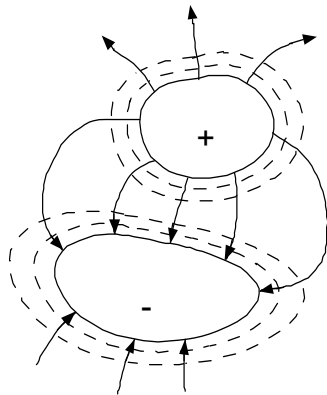

$$\mathbf{E} = -\nabla V$$

$$V = \int_+^- \mathbf{E} \cdot d\mathbf{l}$$

$$I = \oint_{C+} \mathbf{H} \cdot d\mathbf{l}$$

Characteristic impedance


$$Z_c = \frac{V}{I} = \sqrt{\frac{L}{C}}$$

Example : TEM line

- Univoque definition of voltage and current
- Fields identical to static fields
- Zero cutoff frequency
- Needs at least two separate conductors

Non-TEM line : the rectangular waveguide
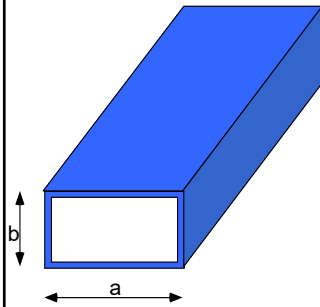
$$\mathbf{E} = -\nabla V - j\omega\mu\mathbf{A}$$



Example : mode TE₁₀ of a rectangular waveguide

$$E_y(x, y, z) = E_0 \frac{j\omega\mu a}{\pi} \sin \frac{\pi x}{a} e^{-j\beta z} = E_0 e_y(x, y) e^{-j\beta z}$$

$$H_x(x, y, z) = E_0 \frac{j\beta a}{\pi} \sin \frac{\pi x}{a} e^{-j\beta z} = E_0 h_y(x, y) e^{-j\beta z}$$

Thus

$$V = E_0 \frac{-j\omega\mu a}{\pi} \sin \frac{\pi x}{a} e^{-j\beta z} \int_y dy$$

Non TEM voltage and current definition

- Only defined for one mode
- The voltage is proportional to the transverse electric field
- The current is proportional to the transverse magnetic field
- The characteristic impedance is equal to U/I. We choose the characteristic impedance equal to the wave impedance
- The power flux is given by the product of the voltage and the current

Arbitrary line


$$\begin{aligned}
 \mathbf{E}_t(x, y, z) &= \mathbf{e}_t(x, y) \left(E_o^+ e^{-j\beta z} + E_o^- e^{j\beta z} \right) & V(z) &= V^+ e^{-j\beta z} + V^- e^{j\beta z} \\
 &= \frac{\mathbf{e}_t(x, y)}{C_1} \left(V^+ e^{-j\beta z} + V^- e^{j\beta z} \right) & I(z) &= I^+ e^{-j\beta z} - I^- e^{j\beta z} \\
 \mathbf{H}_t(x, y, z) &= \mathbf{h}_t(x, y) \left(E_o^+ e^{-j\beta z} - E_o^- e^{j\beta z} \right) & Z_c &= \frac{V^+}{I^+} = \frac{V^-}{I^-} = \frac{C_1 E_o^+}{C_2 E_o^-} = \frac{C_1}{C_2} \\
 &= \frac{\mathbf{h}_t(x, y)}{C_2} \left(I^+ e^{-j\beta z} - I^- e^{j\beta z} \right) & \frac{C_1}{C_2} &= Z_{\text{mod}}
 \end{aligned}$$

Different impedances

- Impedance of the medium : $Z_o = \sqrt{\frac{\mu}{\epsilon}}$
- Wave impedance : $Z_{\text{mod}} = \frac{|\mathbf{E}_t|}{|\mathbf{H}_t|}$
- Line characteristic impedance : $Z_c = \frac{V^+}{I^+} = \frac{V^-}{I^-} = \sqrt{\frac{L}{C}}$
- Impedance matrix of a circuit

Impedance matrix

Single port element

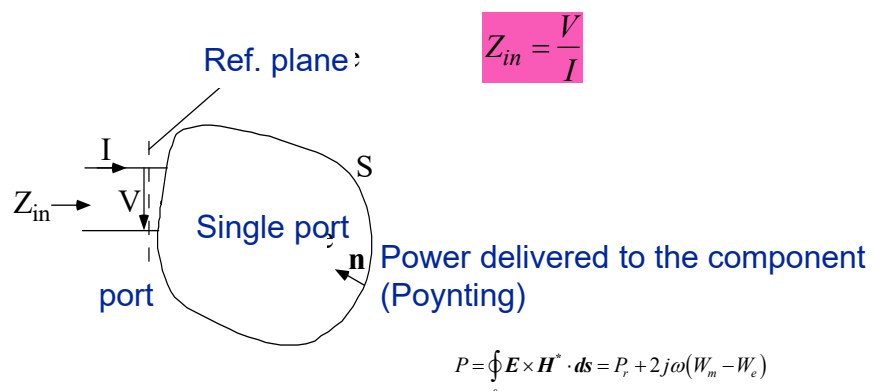

Single port element

Voltage and current :

$$\mathbf{E}_t(x, y, z) = V(z) \frac{\mathbf{e}_t(x, y)}{C_1} e^{-j\beta z}$$

$$\mathbf{H}_t(x, y, z) = I(z) \frac{\mathbf{h}_t(x, y)}{C_2} e^{-j\beta z}$$

with $\frac{1}{C_1 C_2} \int \mathbf{e}_t \times \mathbf{h}_t \cdot d\mathbf{s} = 1$ thus $P = \frac{1}{C_1 C_2} \int V I^* \mathbf{e}_t \times \mathbf{h}_t \cdot d\mathbf{s} = V I^*$

and


$$Z_{in} = R + jX = \frac{V}{I} = \frac{V I^*}{|I|^2} = \frac{P}{|I|^2}$$

$$= \frac{(P_r + 2j\omega(W_m - W_e))}{|I|^2}$$

Single port element

- R is proportional to the real power dissipated in the system (Losses)
- X is proportional to the mean reactive stored energy in the system

Impedance and admittance matrix

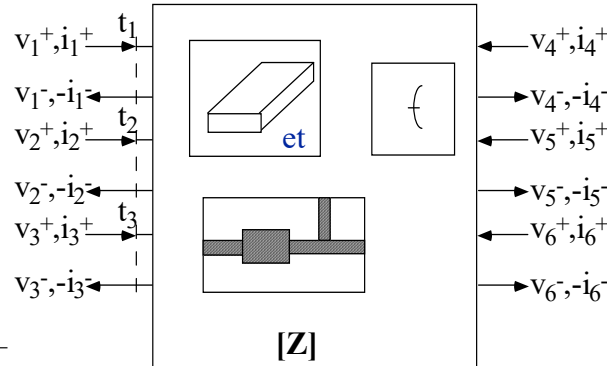

$$V_n = V_n^+ + V_n^-$$

$$I_n = I_n^+ - I_n^- \quad \text{At each port } t_i$$

Impedance and admittance matrix

$$[V] = [Z][I]$$

$$[I] = [Y][V]$$

$$Z_{ij} = \left. \frac{V_i}{I_j} \right|_{I_k=0 \text{ pour } k \neq j}$$

$$Y_{ij} = \left. \frac{I_i}{V_j} \right|_{V_k=0 \text{ pour } k \neq j}$$


- Impedance matrix is obtained in open circuit conditions
- Admittance matrix is obtained in short circuit conditions

EPFL Properties of the impedance and admittance matrix

- Reciprocity : $Y_{ij} = Y_{ji}$
 $Z_{ij} = Z_{ji}$
- Lossless circuit : $\text{Re}\{Z_{mn}\} = 0$

19 A. Skrivervik, MAG

EPFL Example : transmission line

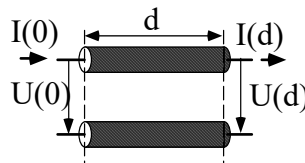


$$U_1 = U(0), I_1 = I(0),$$

$$U_2 = U(d), I_2 = -I(d)$$

$$U(z) = U_+ e^{-\gamma z} + U_- e^{+\gamma z}$$
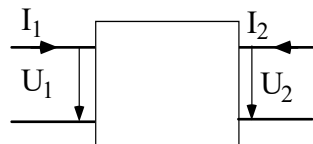
$$I(z) = I_+ e^{-\gamma z} + I_- e^{+\gamma z}$$




$$U(0) = U_+ + U_- \quad U(d) = U_+ e^{-\gamma d} + U_- e^{+\gamma d}$$


$$I(0) = I_+ + I_- \quad I(d) = I_+ e^{-\gamma d} + I_- e^{+\gamma d}$$

20 A. Skrivervik, MAG

Example : transmission line

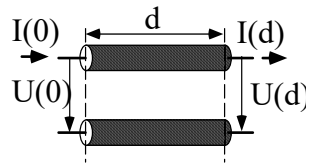

$$\begin{bmatrix} U_1 \\ U_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

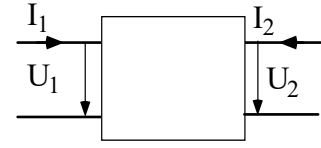
$$= Z_c \begin{bmatrix} \coth(\gamma d) & \frac{1}{\sinh(\gamma d)} \\ \frac{1}{\sinh(\gamma d)} & \coth(\gamma d) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$


$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} U_1 \\ U_2 \end{bmatrix}$$

$$= Y_c \begin{bmatrix} \coth(\gamma d) & \frac{-1}{\sinh(\gamma d)} \\ \frac{-1}{\sinh(\gamma d)} & \coth(\gamma d) \end{bmatrix} \begin{bmatrix} U_1 \\ U_2 \end{bmatrix}$$

21 A. Skrivervik, MAG


EPFL Equivalent T circuit of a reciprocal two-port
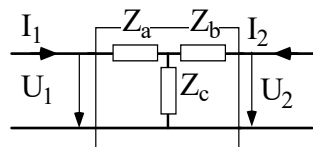
$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{12} & Z_{22} \end{bmatrix}$$


$$\begin{aligned} Z_a &= Z_{11} - Z_{12} \\ Z_b &= Z_{22} - Z_{12} \\ Z_c &= Z_{12} \end{aligned}$$

22 A. Skrivervik, MAG

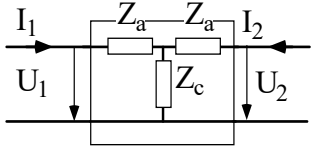EPFL Equivalent T circuit of a transmission line



$$Z_a = Z_{\text{caract}} \left(\coth(\gamma d) - \frac{1}{\sinh(\gamma d)} \right)$$


$$= Z_{\text{caract}} \left(\frac{\cosh(\gamma d) - 1}{\sinh(\gamma d)} \right) = Z_{\text{caract}} \tanh\left(\frac{\gamma d}{2}\right)$$

$$Z_c = \frac{Z_{\text{caract}}}{\sinh(\gamma d)}$$

23 A. Skrivervik, MAG

EPFL Equivalent Π circuit of a reciprocal two-port
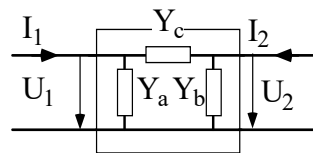
$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{12} & Y_{22} \end{bmatrix}$$




$$Y_a = Y_{11} + Y_{12}$$

$$Y_b = Y_{22} + Y_{12}$$

$$Y_c = -Y_{12}$$

24 A. Skrivervik, MAG

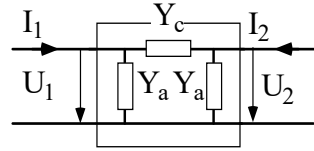Equivalent Π circuit of a transmission line



$$\begin{aligned}
 Y_a &= Y_{caract} \left(\coth(\gamma d) - \frac{1}{\sinh(\gamma d)} \right) \\
 &= Y_{caract} \left(\frac{ch(\gamma d) - 1}{\sinh(\gamma d)} \right) = Y_{caract} \tanh\left(\frac{\gamma d}{2}\right) \\
 Y_c &= \frac{Y_{caract}}{\sinh(\gamma z)}
 \end{aligned}$$

Scattering parameters

EPFL Normalized wave amplitudes : definition

Normalized wave amplitudes

$$a_i = \frac{v_i + Z_{ci} i_i}{2\sqrt{Z_{ci}}} , \quad b_i = \frac{v_i - Z_{ci} i_i}{2\sqrt{Z_{ci}}} \quad [W^{1/2}]$$

Inverse relation

$$v_i = \sqrt{Z_{ci}}(a_i + b_i) , \quad i_i = \frac{(a_i - b_i)}{\sqrt{Z_{ci}}}$$

27 A. Skrivervik, MAG

EPFL Normalized wave amplitudes : properties

Transmission lines

$$\begin{aligned} v_i &= v_i^+ e^{-j\beta z} + v_i^- e^{+j\beta z} \\ i_i &= i_i^+ e^{-j\beta z} + i_i^- e^{+j\beta z} \end{aligned} \quad \longrightarrow \quad \begin{aligned} a_i &= \frac{v_i^+}{\sqrt{Z_{ci}}} e^{-j\beta z} \\ b_i &= \frac{v_i^-}{\sqrt{Z_{ci}}} e^{+j\beta z} \end{aligned}$$

a_i : progressive wave
 b_i : retrograde wave


28 A. Skrivervik, MAG

Power at one component port

$$P_i = \operatorname{Re}[v_i i_i^*] = \operatorname{Re}[(a_i + b_i)(a_i^* - b_i^*)] = |a_i|^2 - |b_i|^2$$

$|a_i|^2$: power entering port
 $|b_i|^2$: power leaving port

Signal model

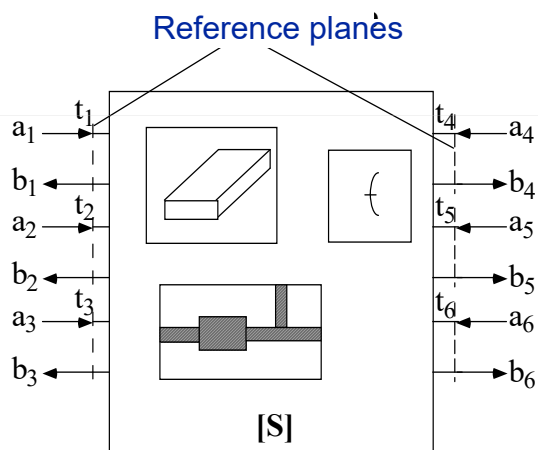

$$[b] = [S][a]$$

$$s_{ij} = \left. \frac{b_i}{a_j} \right|_{a_k=0, k \neq j}$$

Scattering matrix : definition

Normalized wave amplitude

Inverse relation

$$a_i = \frac{v_i + Z_{ci}i_i}{2\sqrt{Z_{ci}}} \quad , \quad b_i = \frac{v_i - Z_{ci}i_i}{2\sqrt{Z_{ci}}} \quad v_i = \sqrt{Z_{ci}}(a_i + b_i) \quad , \quad i_i = \frac{(a_i - b_i)}{\sqrt{Z_{ci}}}$$

Scattering matrix

$$[b] = [S][a] \quad s_{ij} = \left. \frac{b_i}{a_j} \right|_{a_k=0, \quad k \neq j}$$

Signal model

- Advantages :
 - Signals are easy to measure
 - Well suited to a system approach (transfer functions)
- Drawbacks :
 - Not known at low frequencies

Scattering matrix : properties

- S_{ij} : transfert function from port j to port i
- Depends on the component and its properties
- To change the connecting lines implies to change the scattering matrix
- The scattering matrix is obtained termiating the ports by matched loads

Reciprocity

Passive, linear, isotropic circuit



The circuit is reciprocal



$$Z_{ij} = Z_{ji}$$



$$S_{ij} = S_{ji}$$

Lossless circuit

$$\sum |a_i|^2 = \sum |b_i|^2 \longrightarrow [\tilde{a}][a] - [\tilde{b}][b] = 0 \quad \text{With } [\tilde{a}] = [a^*]^t$$

Moreover


$$\begin{aligned} [b] &= [S][a] \\ [\tilde{b}] &= [\tilde{a}][\tilde{S}] \end{aligned} \longrightarrow \begin{aligned} [\tilde{a}][a] - [\tilde{a}][\tilde{S}][S][a] &= 0 \\ [\tilde{a}]\{[1] - [\tilde{S}][S]\}[a] &= 0 \\ [\tilde{S}][S] &= [1] \end{aligned} \longrightarrow$$

$$\sum_{i=1}^N s_{ij}^* s_{ik} = \delta_{jk} \quad \delta_{jk} = \begin{cases} 1 & \text{si } j = k \\ 0 & \text{si } j \neq k \end{cases}$$

Matched circuit

$$S_{ii} = 0$$

Change of reference plane

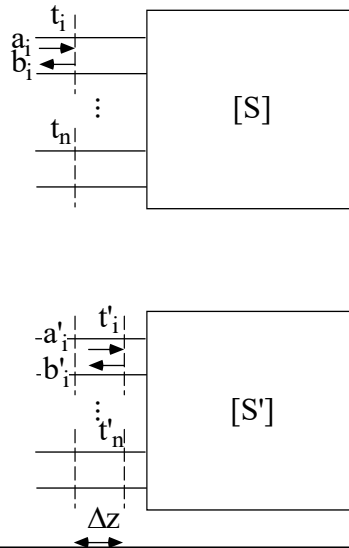

37 A. Skriversvik, MAG

Change of reference plane

$$a'_i = a_i e^{-j\varphi_i}$$

$$b'_i = b_i e^{j\varphi_i}$$

$$\varphi_i = -\beta_i \Delta z_i$$

thus

$$s'_{ii} = s_{ii} e^{j2\varphi_i}$$

And in general

$$[a] = [\text{diag } e^{j\varphi}] [a']$$

$$[a'] = [\text{diag } e^{-j\varphi}] [a]$$

$$[b] = [\text{diag } e^{-j\varphi}] [b']$$

$$[b'] = [\text{diag } e^{j\varphi}] [b]$$

$$[\text{diag } e^{j\varphi}] = \begin{bmatrix} e^{j\varphi_1} & 0 & \dots & 0 \\ 0 & e^{j\varphi_2} & & \vdots \\ \vdots & & & \\ 0 & \dots & & e^{j\varphi_n} \end{bmatrix}$$

38 A. Skriversvik, MAG

Change of reference plane

$$[b'] = \begin{bmatrix} \text{diag } e^{j\varphi} \end{bmatrix} [S] \begin{bmatrix} \text{diag } e^{j\varphi} \end{bmatrix} [a']$$

$$[S'] = \begin{bmatrix} \text{diag } e^{j\varphi} \end{bmatrix} [S] \begin{bmatrix} \text{diag } e^{j\varphi} \end{bmatrix}$$

$$s'_{ij} = s_{ij} e^{j(\varphi_i + \varphi_j)}$$

Passive circuits : questions

1. Linearity
2. Reciprocity
3. Losslessness
4. Matched
5. Symmetry

[S] → [Z]

$$\begin{aligned} \underline{[b]} &= \underline{[S]} \underline{[a]} & \underline{a_i} &= (\underline{U_i} + Z_{ci} \underline{I_i}) / 2 \sqrt{Z_{ci}} & \underline{U_i} &= \sqrt{Z_{ci}} (\underline{a_i} + \underline{b_i}) \\ \underline{[U]} &= \underline{[Z]} \underline{[I]} & \underline{b_i} &= (\underline{U_i} - Z_{ci} \underline{I_i}) / 2 \sqrt{Z_{ci}} & \underline{I_i} &= (\underline{a_i} - \underline{b_i}) / \sqrt{Z_{ci}} \end{aligned}$$

We define two auxiliary matrices

$$[G] = [\text{diag}(Z_{ci})]$$

$$[F] = [\text{diag}(1/2\sqrt{Z_{ci}})]$$

And we can write

$$\begin{aligned} \underline{[a]} &= [F] \{ \underline{[U]} + [G] \underline{[I]} \} \\ \underline{[b]} &= [F] \{ \underline{[U]} - [G] \underline{[I]} \} \end{aligned}$$

$$\begin{aligned} (\underline{[a]} + \underline{[b]}) &= 2 [F] \underline{[U]} \\ (\underline{[a]} - \underline{[b]}) &= 2 [F] [G] \underline{[I]} \end{aligned}$$

[S] → [Z]

$$\underline{[a]} = [F] \{ \underline{[U]} + [G] \underline{[I]} \} \rightarrow \underline{[a]} = [F] \{ \underline{[Z]} + [G] \} \underline{[I]}$$

$$\rightarrow \underline{[I]} = \{ \underline{[Z]} + [G] \}^{-1} [F]^{-1} \underline{[a]}$$

$$\underline{[b]} = [F] \{ \underline{[U]} - [G] \underline{[I]} \} \rightarrow \underline{[b]} = [F] \{ \underline{[Z]} - [G] \} \underline{[I]}$$

$$\rightarrow \underline{[b]} = [F] \{ \underline{[Z]} - [G] \} \{ \underline{[Z]} + [G] \}^{-1} [F]^{-1} \underline{[a]} = \underline{[S]} \underline{[a]}$$

$$\text{Thus: } \underline{[S]} = [F] \{ \underline{[Z]} - [G] \} \{ \underline{[Z]} + [G] \}^{-1} [F]^{-1}$$

$$\text{In one dimension, we have } \underline{\rho} = \underline{S}_{11} = (\underline{Z}_t - Z_c) / (\underline{Z}_t + Z_c)$$

[Z] → [S]

$$([a] + [b]) = 2 [F] [U] \rightarrow [U] = (2 [F])^{-1}([a] + [b]) = (2 [F])^{-1}([1] + [S]) [a]$$

$$([a] - [b]) = 2 [F] [G] [U] = ([1] - [S]) [a] \rightarrow [a] = ([1] - [S])^{-1} 2 [F] [G] [U]$$

regrouping, we obtain:

$$[U] = (2 [F])^{-1}([1] + [S]) ([1] - [S])^{-1} 2 [F] [G] [U] = [Z] [U]$$

Et on en tire: $[Z] = ([F])^{-1}([1] + [S]) ([1] - [S])^{-1} [F] [G]$

For a single access component, we have


$$\underline{Z}_t = Z_c(1 + \underline{r})/(1 - \underline{r})$$

Flow charts


The scattering parameters (reflection and transfer functions) are represented as arrows




Flow charts

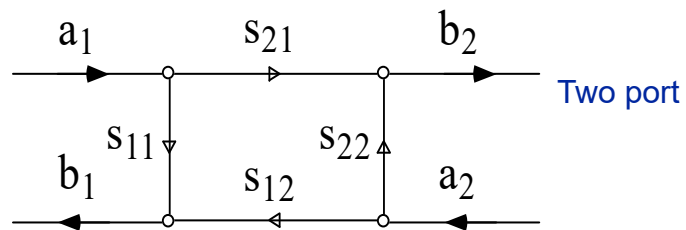

Flow charts

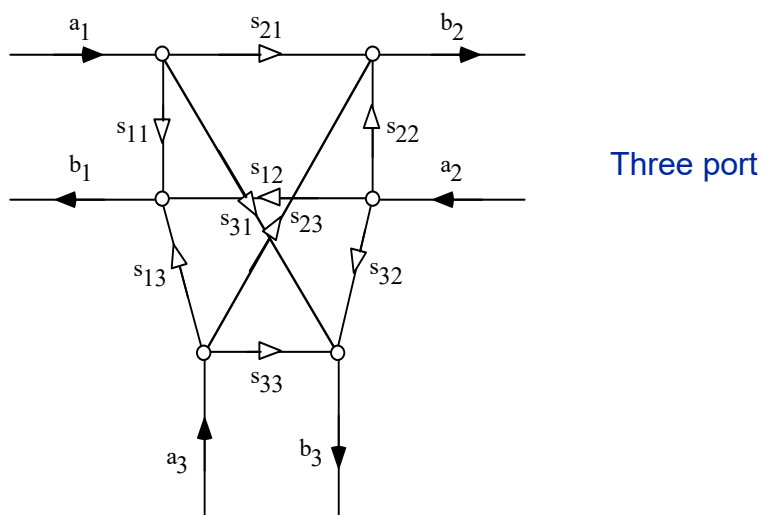


Flow charts

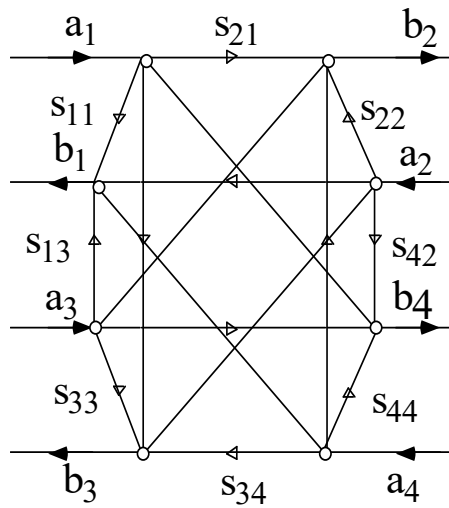

4-port


Flow chart reduction rules

1) multiplication

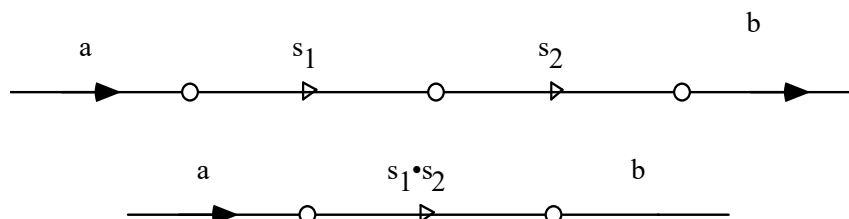

Flow chart reduction rules


2) addition

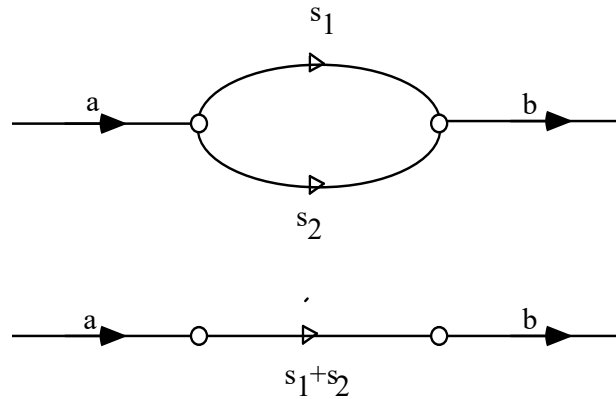

49 A. Skriversvik, MAG


Flow chart reduction rules

3) retroaction

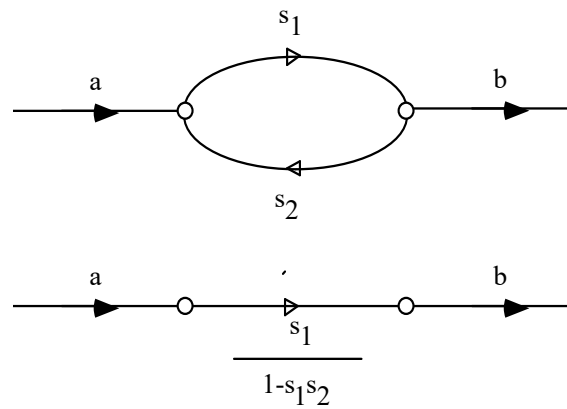


50 A. Skriversvik, MAG


Example

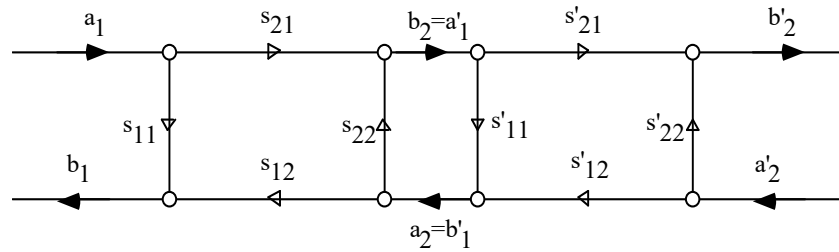


Example

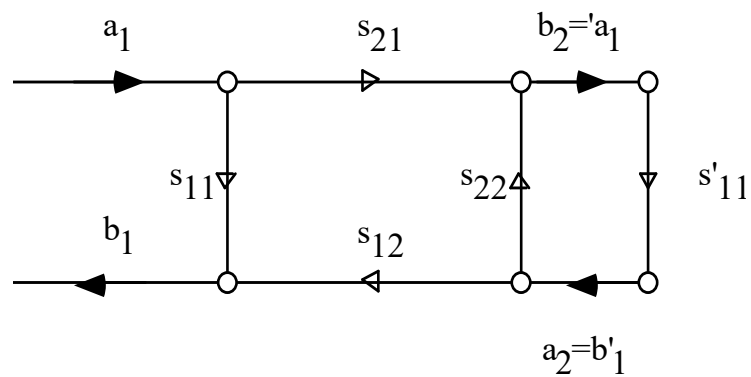


Example

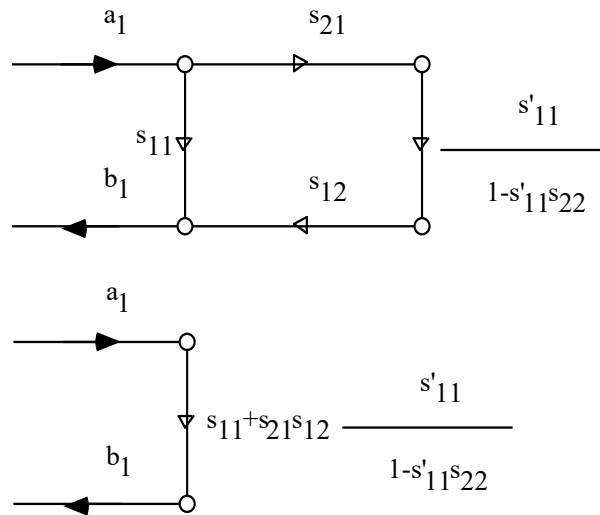


Example

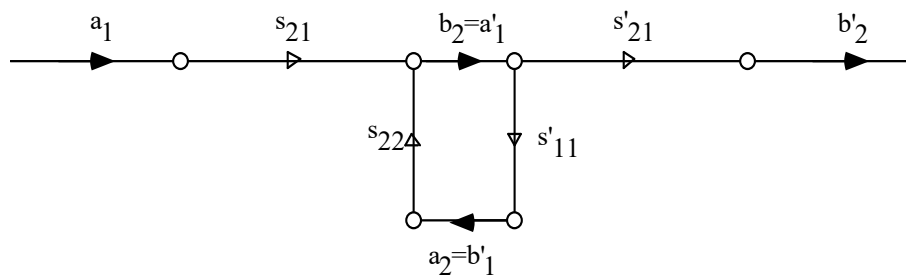


Example

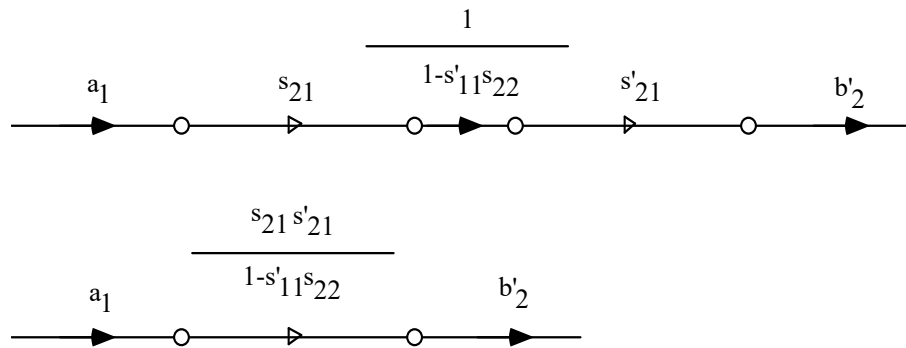


Example

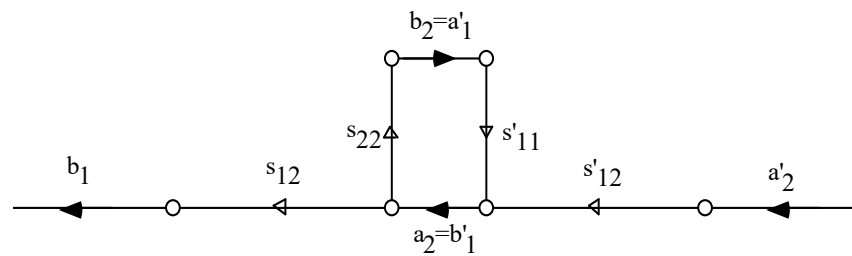

Example

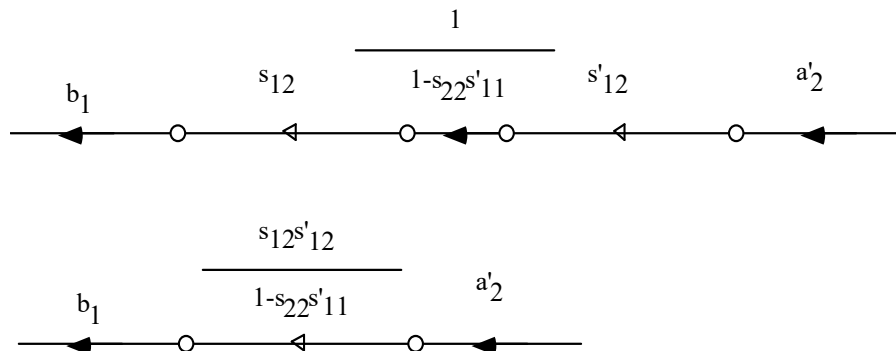

Example

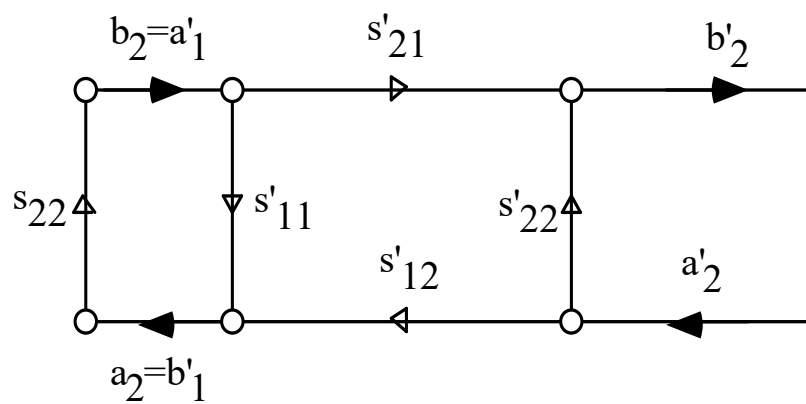

Example

