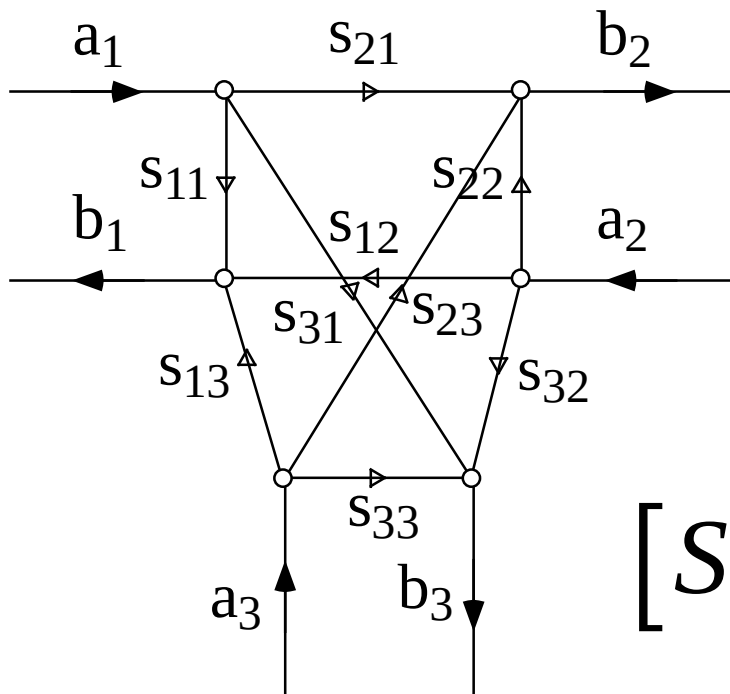


Three port components

Main application : power division and combination

Three port components



$$[S] = \begin{bmatrix} s_{11} & s_{12} & s_{13} \\ s_{21} & s_{22} & s_{23} \\ s_{31} & s_{32} & s_{33} \end{bmatrix}$$

Reciprocal

$$[S] = \begin{bmatrix} s_{11} & s_{21} & s_{31} \\ s_{21} & s_{22} & s_{32} \\ s_{31} & s_{32} & s_{33} \end{bmatrix}$$

Matched

$$[S] = \begin{bmatrix} 0 & s_{12} & s_{13} \\ s_{21} & 0 & s_{23} \\ s_{31} & s_{32} & 0 \end{bmatrix}$$

Lossless

$$\sum_{i=1}^3 s_{ij}^* s_{ik} = \delta_{ik} \quad j, k = 1, 2, 3$$

Lossless, matched and reciprocal

$$[S] = \begin{bmatrix} 0 & s_{21} & s_{31} \\ s_{21} & 0 & s_{32} \\ s_{31} & s_{32} & 0 \end{bmatrix}$$

$$\begin{bmatrix} 0 & s_{21}^* & s_{31}^* \\ s_{21}^* & 0 & s_{32}^* \\ s_{31}^* & s_{32}^* & 0 \end{bmatrix} \begin{bmatrix} 0 & s_{21} & s_{31} \\ s_{21} & 0 & s_{32} \\ s_{31} & s_{32} & 0 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$$

Lossless, matched and reciprocal

Thus

$$|s_{12}|^2 + |s_{13}|^2 = 1$$

$$|s_{12}|^2 + |s_{23}|^2 = 1$$

$$|s_{13}|^2 + |s_{23}|^2 = 1$$

$$s_{13}^* s_{23} = 0$$

$$s_{12}^* s_{23} = 0$$

$$s_{12}^* s_{13} = 0$$

suppose :

$$s_{13} \neq 0 \Rightarrow s_{23} = 0 \text{ and } s_{12} = 0$$

incompatible with

$$|s_{12}|^2 + |s_{23}|^2 = 1$$

A three port cannot be lossless, matched and reciprocal at the same time

Lossless, matched at 2 ports and reciprocal

$$[S] = \begin{bmatrix} 0 & s_{21} & s_{31} \\ s_{21} & 0 & s_{32} \\ s_{31} & s_{32} & s_{33} \end{bmatrix}$$

$$\begin{bmatrix} 0 & s_{21}^* & s_{31}^* \\ s_{21}^* & 0 & s_{32}^* \\ s_{31}^* & s_{32}^* & s_{33}^* \end{bmatrix} \begin{bmatrix} 0 & s_{21} & s_{31} \\ s_{21} & 0 & s_{32} \\ s_{31} & s_{32} & s_{33} \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$$

Lossless, matched at 2 ports and reciprocal

Thus

yields :

$$|s_{12}|^2 + |s_{13}|^2 = 1$$

$$|s_{12}|^2 + |s_{23}|^2 = 1$$

$$|s_{13}|^2 + |s_{23}|^2 + |s_{33}|^2 = 1$$

$$s_{13}^* s_{23} = 0$$


$$s_{12}^* s_{23} + s_{13}^* s_{33} = 0$$

$$s_{12}^* s_{13} + s_{23}^* s_{33} = 0$$

$$s_{13} = 0 \Rightarrow s_{12} = 1 \text{ and } s_{23} = 0, \text{ thus } s_{33} = 1$$

$$s_{23} = 0 \Rightarrow s_{12} = 1 \text{ and } s_{13} = 0, \text{ thus } s_{33} = 1$$

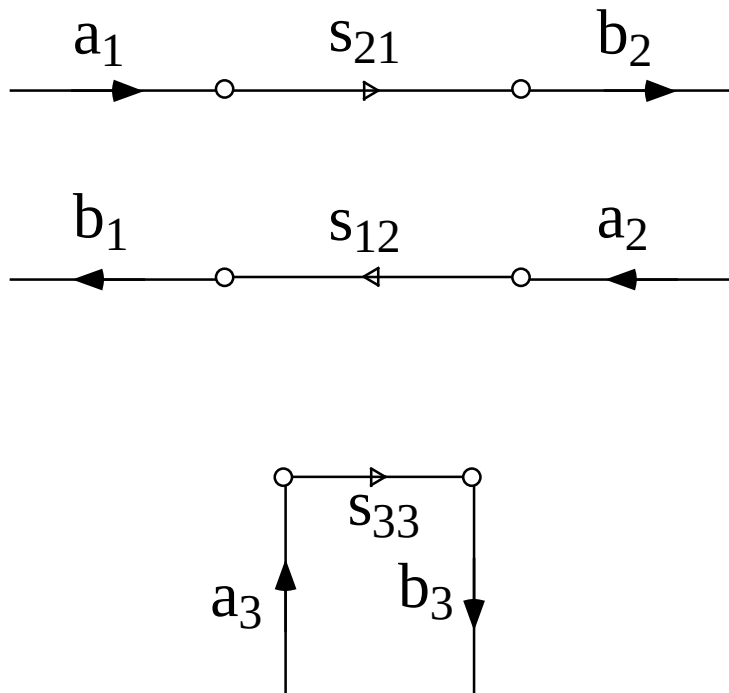Lossless, reciprocal and matched at two ports



two decoupled components

Three port "nearly" matched at two ports

scattering matrix

$$[S] = \begin{bmatrix} \varepsilon & s_{21} & s_{31} \\ s_{21} & \varepsilon & s_{32} \\ s_{31} & s_{32} & s_{33} \end{bmatrix} \quad \varepsilon \ll 1$$

Ref. planes at ports 1 and 2 selected to have ε real

$$\varepsilon^2 + |s_{12}|^2 + |s_{13}|^2 = 1$$

$$\Rightarrow |s_{13}| = |s_{23}|$$

$$\varepsilon^2 + |s_{12}|^2 + |s_{23}|^2 = 1$$

Three port "nearly" matched at two ports

$$\varepsilon \left(s_{12} + s_{12}^* \right) + s_{13} s_{23}^* = 0$$

and


$$\varepsilon s_{13} + s_{12}^* s_{23} + s_{13}^* s_{33} = 0$$

$$|s_{13}| = \sqrt{2\varepsilon \operatorname{Re}(s_{12})} \sim \sqrt{\varepsilon}$$

Thus

$$\begin{aligned} |s_{12}| &= \sqrt{1 - 2\varepsilon \operatorname{Re}(s_{12}) - \varepsilon^2} \\ &\cong 1 - \varepsilon \operatorname{Re}(s_{12}) \approx 1 \end{aligned}$$

Three port "nearly" matched at two ports

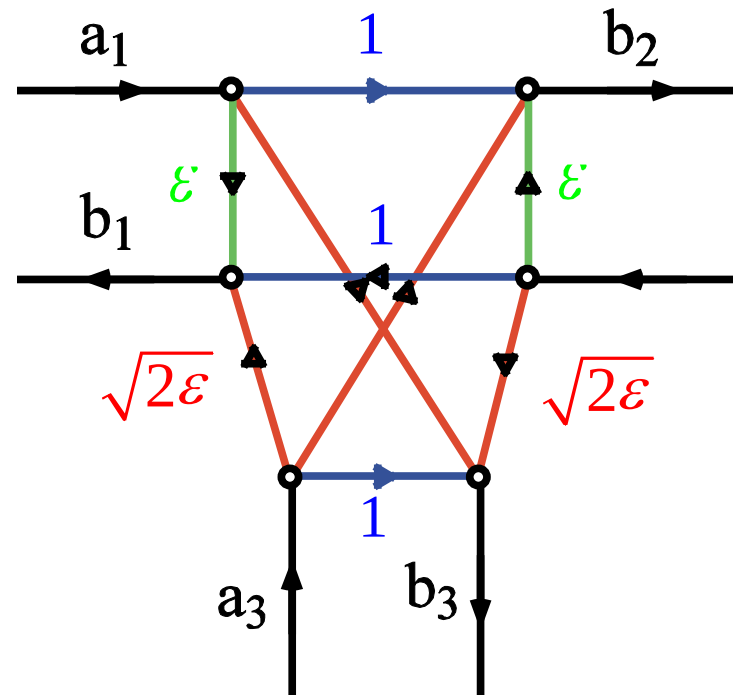

Matched and Lossless three port circuits

$$|s_{21}|^2 + |s_{31}|^2 = 1$$

$$|s_{12}|^2 + |s_{32}|^2 = 1$$

$$|s_{23}|^2 + |s_{13}|^2 = 1$$

$$s_{12}^* s_{13} = 0$$


$$s_{21}^* s_{23} = 0$$

$$s_{31}^* s_{32} = 0$$


$$\begin{aligned} s_{13} \neq 0 &\Rightarrow s_{12} = 0 \Rightarrow |s_{32}| = 1 \Rightarrow s_{31} = 0 \\ &\Rightarrow |s_{21}| = 1 \Rightarrow s_{23} = 0 \Rightarrow |s_{13}| = 1 \end{aligned}$$

Circulator
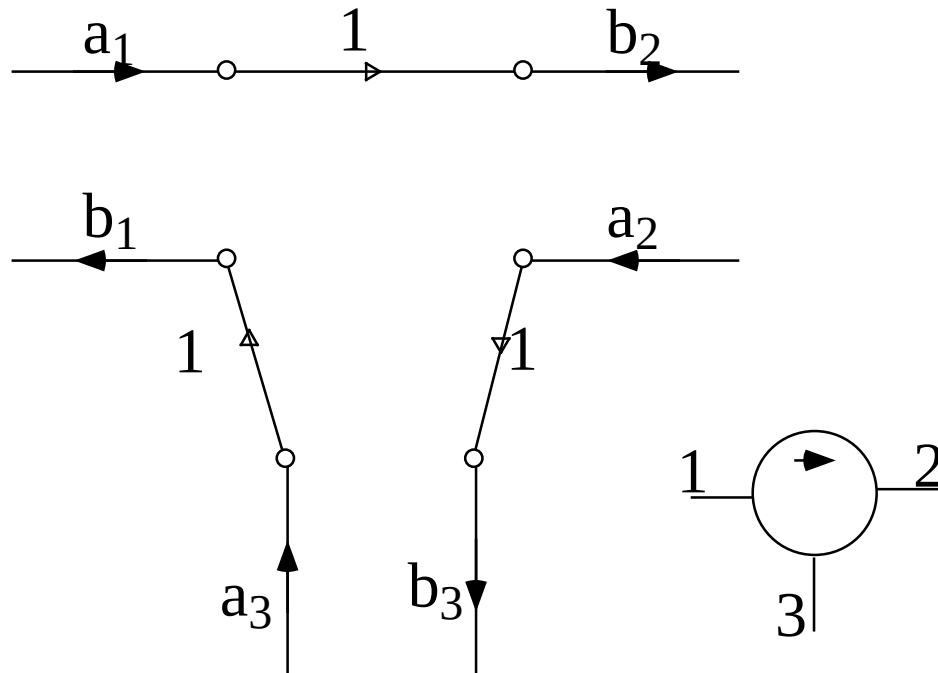
$$[S] = \begin{bmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{bmatrix}$$



Y Junction

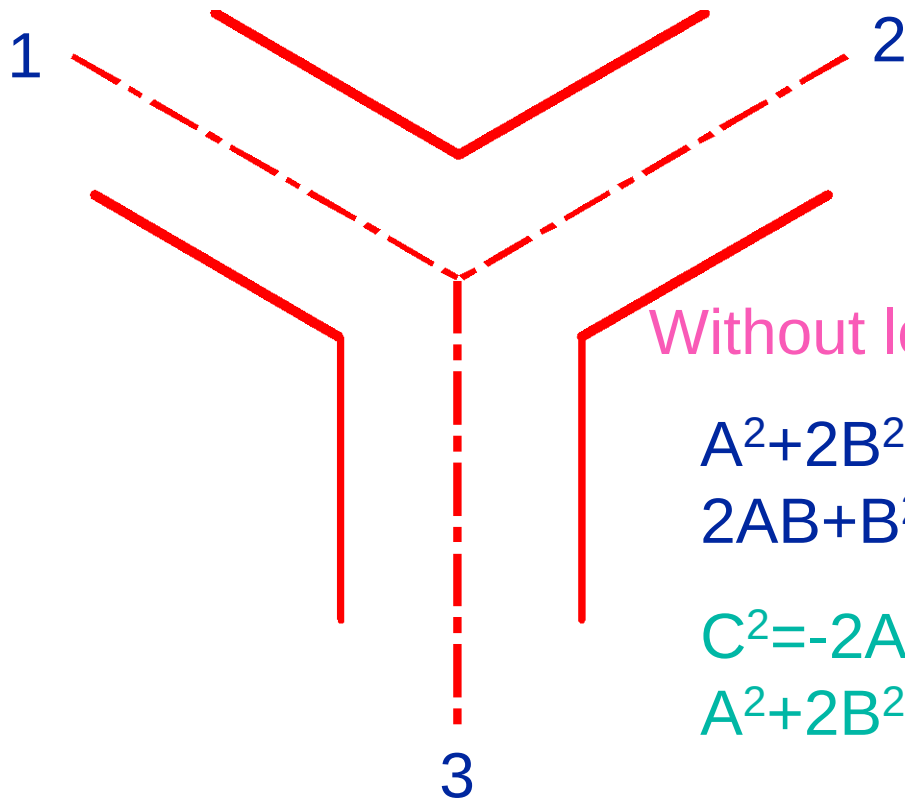

$$S_{11}=S_{22}=S_{33}=A$$

$$S_{12}=S_{21}=S_{13}=S_{31}=S_{32}=S_{23}=B+jC$$

Without losses :

$$A^2+2B^2+2C^2=1 \quad (\text{ellipsoid})$$


$$2AB+B^2+C^2=0$$

$$C^2=-2AB-B^2 \Rightarrow AB<0$$

$$A^2+2B^2-4AB-2B^2=1$$


$$B=1/4(A-1/A) \quad A=2B \pm (4B^2+1)^{1/2}$$

Y-junction

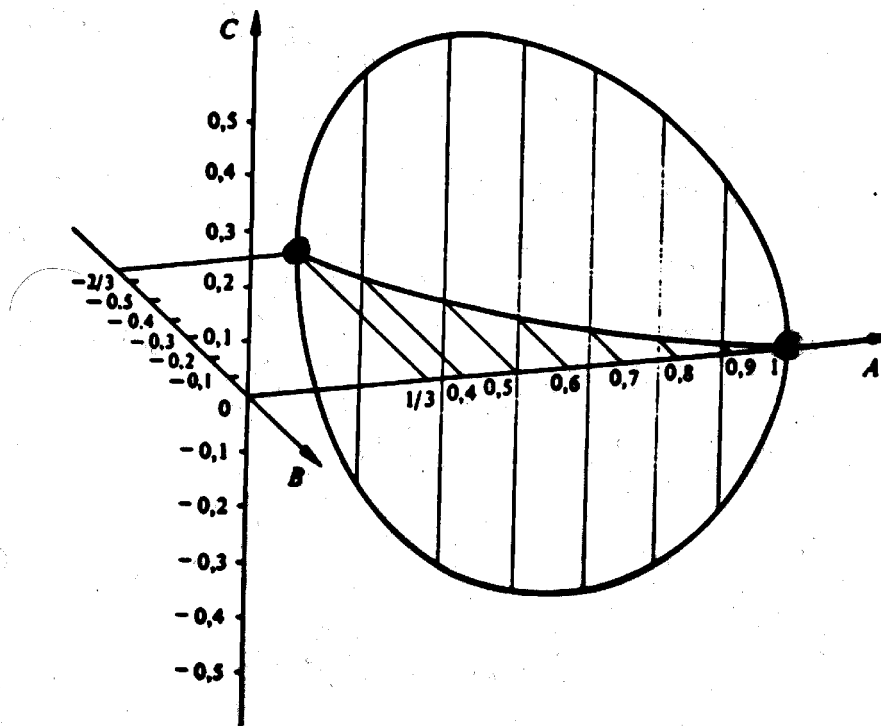

Ellipsoid

Lossy three ports : resistive divider

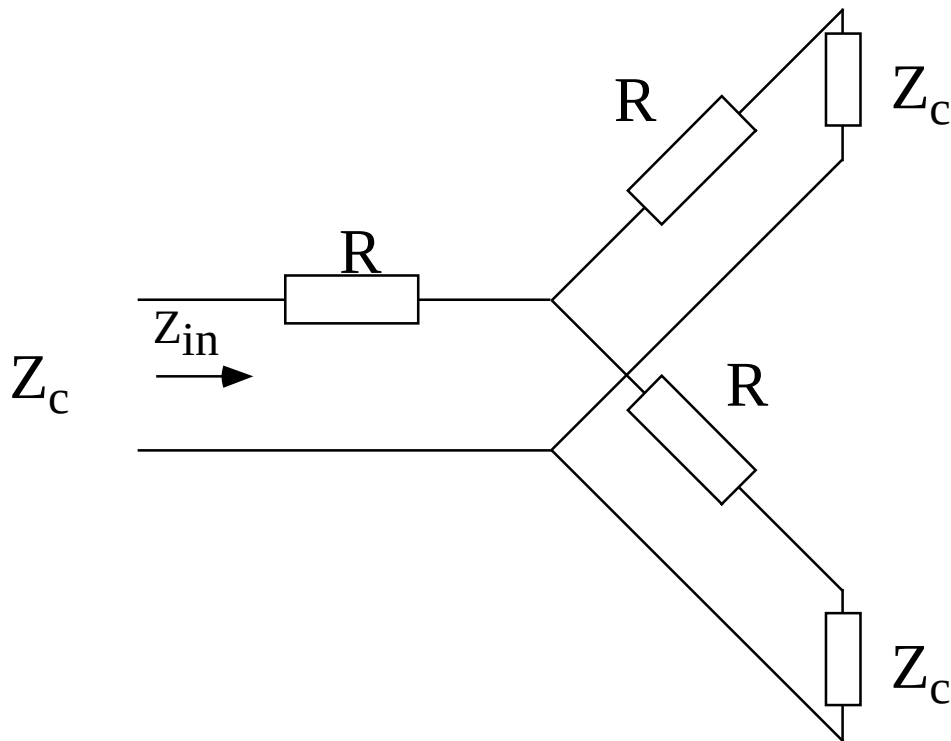

Match

$$Z_{in} = Z_c$$


$$Z_{in} = \frac{3}{2}R + \frac{Z_c}{2}$$

$$R = \frac{1}{3}Z_c$$


$$[S] = \frac{1}{2} \begin{bmatrix} 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \end{bmatrix}$$

Wilkinson divider

Example in microstrip line

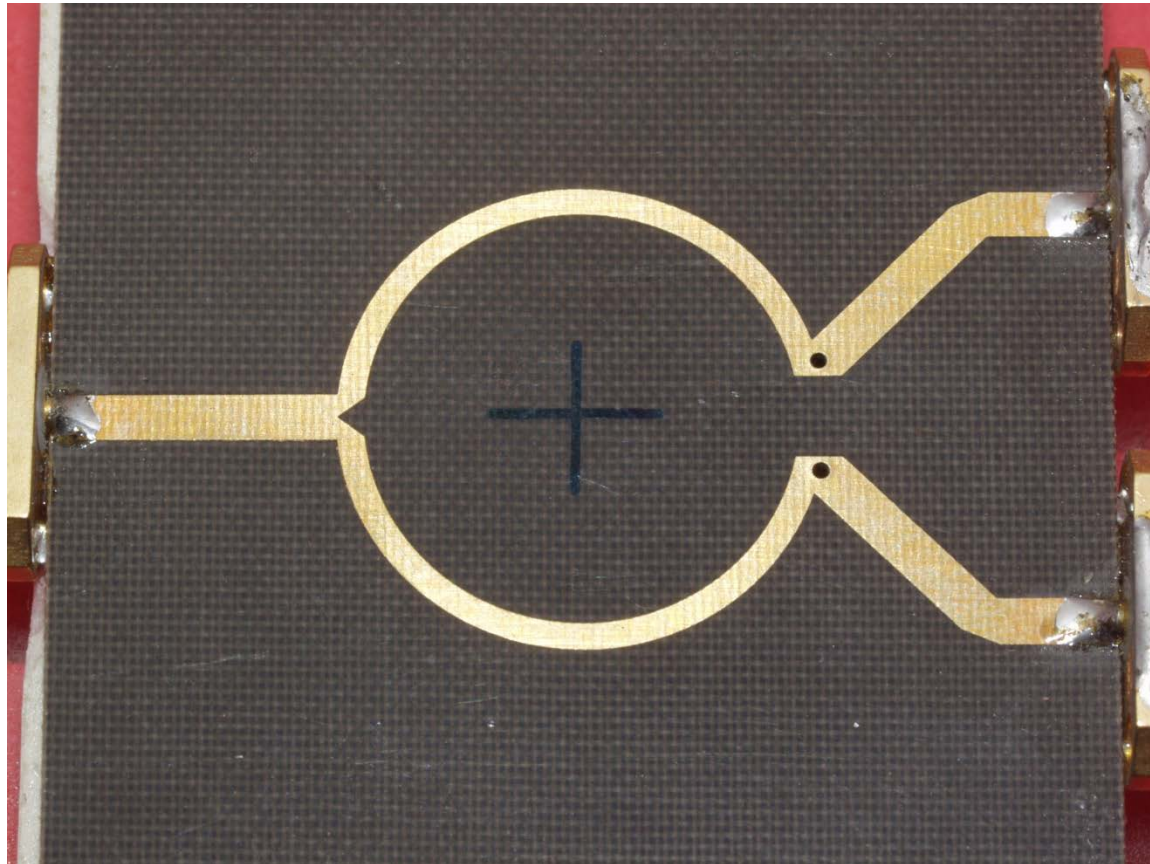


Wilkinson

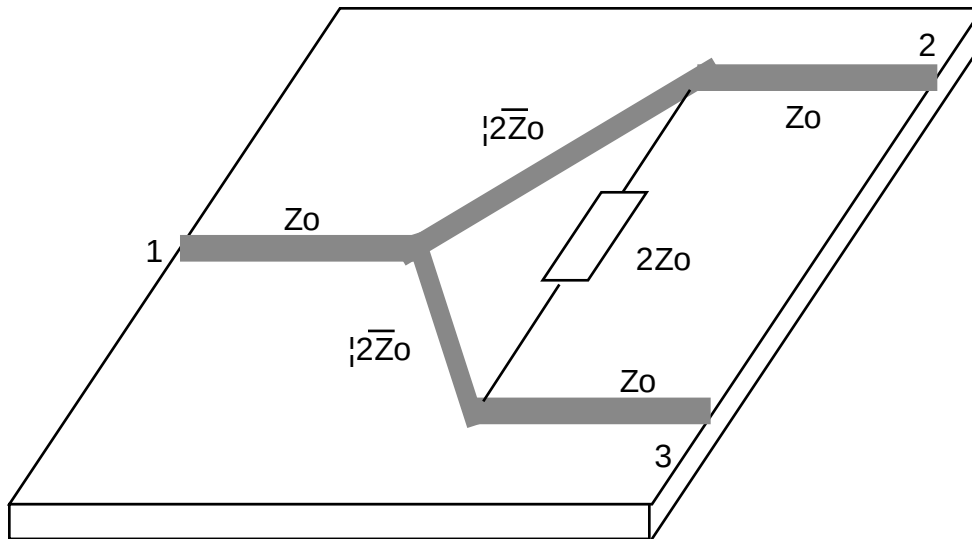


We want :
3 ports matched
port 2 and 3 isolated


Equivalent network

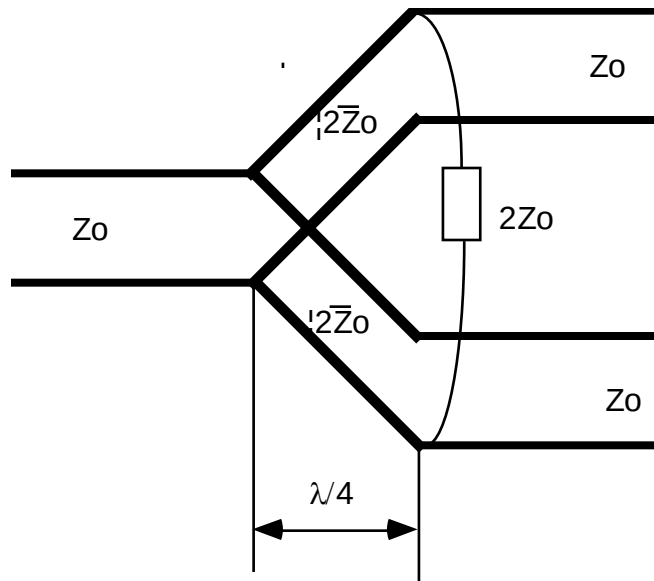

Symmetry

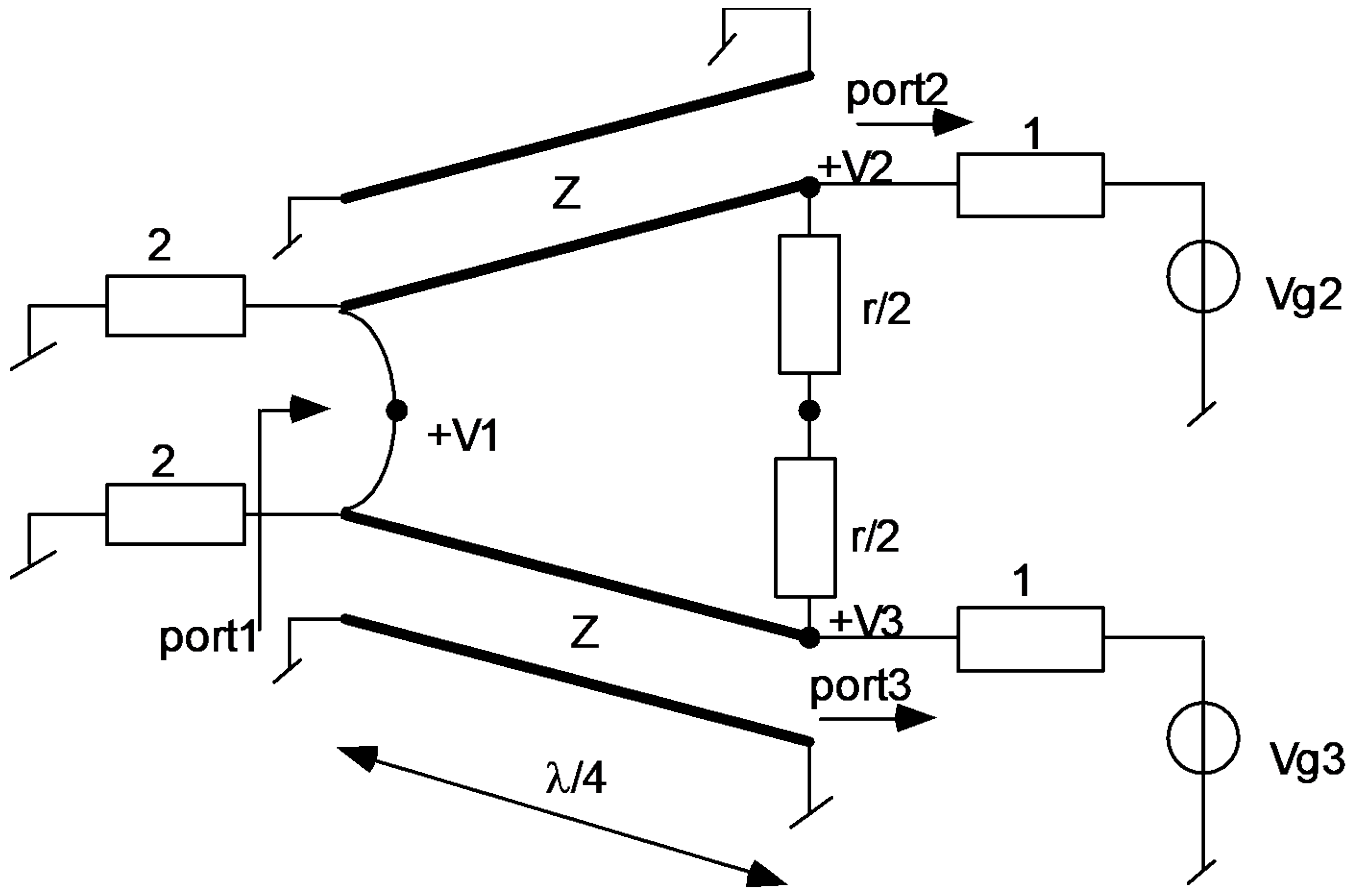

Symmetric excitation

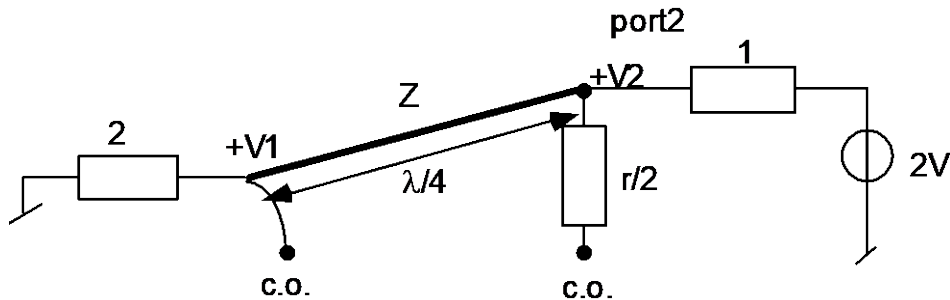

Looking into port 2 2:

$$Z_{in}^e = \frac{Z^2}{2}$$

We obtain :

$$Z = \sqrt{2}$$

Symmetric excitation

Computation of s_{21} :

$$V(x) = V^+ \left(e^{-j\beta x} + \Gamma e^{j\beta x} \right)$$

$$V(0) = V^+ (1 + \Gamma) = V_2 = V$$

$$V_1 = V(\lambda / 4) = jV^+ (1 - \Gamma) = jV \frac{\Gamma - 1}{\Gamma + 1}$$



$$V_1 = jV \frac{-1}{\sqrt{2}}$$

where Γ is the reflexion seen at port 1
looking towards resistor 2

$$\Gamma = \frac{2 - \sqrt{2}}{2 + \sqrt{2}}$$

Symmetric excitation


Thus

$$S_{12} = S_{21} = \frac{V_1}{V_2} = \frac{-j}{\sqrt{2}} = -j0.707$$

By symmetry

$$S_{13} = S_{31} = \frac{V_1}{V_2} = \frac{-j}{\sqrt{2}} = -j0.707$$

Asymmetric excitation

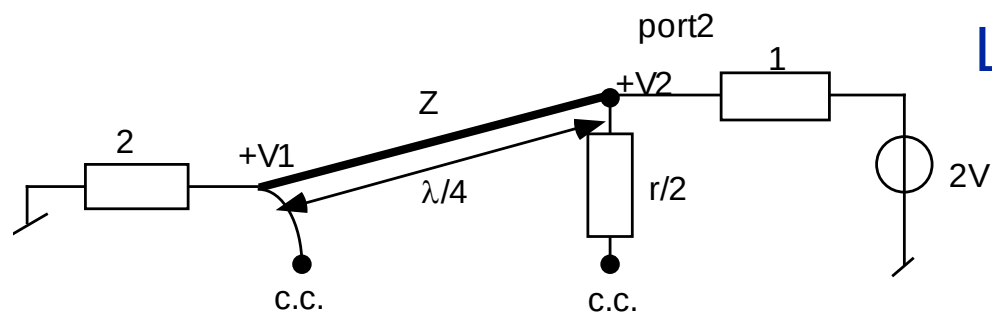

Looking into port 2:

$$Z_{in}^e = \frac{r}{2}$$

We get

$$r = 2$$

In summary


$s_{33} = s_{22} = 0$ (ports 2 and 3 are matched for both excitations)

$s_{12} = s_{21} = -j0.707$ (The component is reciprocal)

$s_{13} = s_{31} = -j0.707$ (The component is reciprocal)

$s_{23} = s_{32} = 0$ (Because of the short circuit or open circuit on the symmetry axis)

Match at port 1

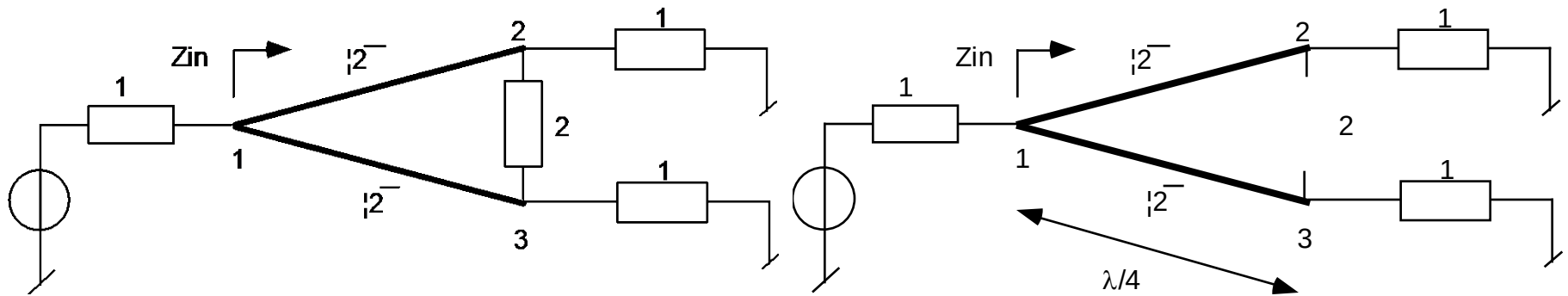

$$Z_{in} = \frac{1}{2} \frac{(\sqrt{2})^2}{1} = 1$$

Thus

$$S_{11} = 0$$