

### Problem 1

Consider a sensing platform that outputs two signals  $V_1(t)$  and  $V_2(t)$ . Design a circuit based on operational amplifiers that integrates the difference of these two signals. Make sure that the integrator does not saturate during operation.

The design specifications are listed hereunder:

- $-0.5\text{ V} \leq V_1(t) \leq 0.5\text{ V}$  and  $-0.5\text{ V} \leq V_2(t) \leq 0.5\text{ V}$
- *Operational amplifiers*: ideal, rail-to-rail with symmetric supply voltages  $V_{cc} = 2.5\text{ V}$
- *Digital clock*:  $f_{clk} = 10\text{ kHz}$
- *Resistances*:  $R_{min} = 10\text{ k}\Omega$

### Problem 2

Design a circuit that takes two voltages  $V_1(t)$  and  $V_2(t)$  as inputs and computes the weighted sum

$$V_{out}(t) = \frac{3}{4}V_1(t) + \frac{5}{4}V_2(t)$$

Use ideal operational amplifiers and resistors.

### Problem 3

Consider an electrochemical cell in a three-electrode configuration, involving a *Working Electrode* (WE), a *Reference Electrode* (RE), and a *Counter Electrode* (CE). Design a circuit that applies  $650\text{ mV}$  between WE and RE while converting the faradaic current in the WE-CE path into a voltage.

Use ideal operational amplifiers and resistors.