

EE-517: Bio-Nano-Chip Design

Exercises 13: Bio-CMOS circuits for DNA detection

December 8, 2020

Problem 1

Consider a *Charge-Based Capacitance Measurement* (CBCM) circuit. Evaluate the range of capacitance that could be sensed at the Bio/CMOS interface by a CBCM front-end designed with the hereunder specifications.

- *Square wave signal applied at the Bio/CMOS interface:*
 $V_{\text{step}} = 100\text{mV}$ $\text{duty_cycle} = 50\%$ $f \in [10\text{Hz}; 10\text{MHz}]$
- *Resistance of the bio layer:* $R_{\text{bio}} = 5\text{M}\Omega$
- *Detectable current range:* $I_{\text{avg}} \in [3.3\mu\text{A}; 3.3\text{mA}]$

Problem 2

Assume that the integration stage of the CBCM is implemented with an RC opamp-based integrator with DC gain control. Design this circuit block such that it could measure Bio/CMOS interface capacitance in the range of frequency $[10\text{Hz}; 100\text{kHz}]$.

Problem 3

A circuit front-end for label-free DNA detection is considered. The sensing electrodes consist of two interdigitated gold electrodes bio-modified by covalent binding of single-stranded DNA probes. Hybridization events of complementary DNA strands (probe/target molecules) is detected by the variation of the interface capacitance. A capacitance-to frequency converter is implemented in Figure. 1.

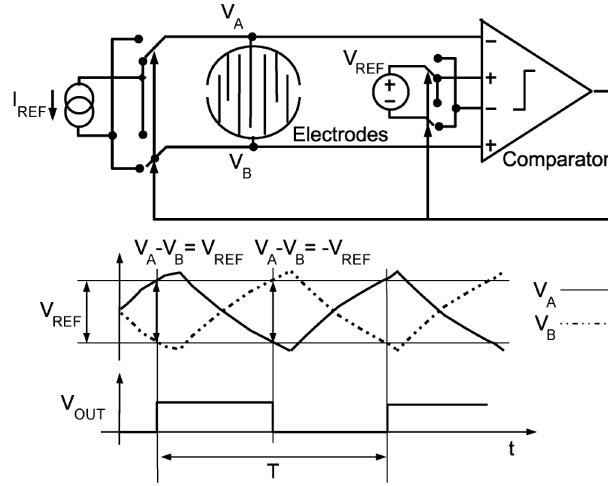


Figure 1: Capacitance-to-Frequency measurement circuit [1].

A periodic current excitation I_{REF} polarizes the electrodes. The electrodes respond to the stimulus by changing their voltage difference $V_C = V_A - V_B$, in a transient waveform which time constant is dominated by the capacitive elements of the electrode-solution impedance. The comparator inverts the polarization current when V_C reaches the threshold values $\pm V_{REF}$. Therefore, the width of the pulsed signal V_{OUT} at the output of the comparator encodes the interfacial capacitance.

(a) Demonstrate that the period of the square signal V_{OUT} could be expressed as

$$T = 2RC \ln \left(\frac{1}{1 - \frac{V_{REF}}{R I_{REF}}} \right),$$

where R and C represent the contribution of the interface resistance and capacitance, respectively, of both electrode/solution interface. Neglect the solution resistance and the geometrical two-plates capacitance formed by the two electrodes.

(b) Evaluate the range of frequency at which the comparator switches its state, with the specifications listed hereunder:

- Resistance of the bio-layer: $R_{bio} \in [5 \text{ M}\Omega; 15 \text{ M}\Omega]$
- Capacitance of the bio-layer: $C_{bio} \in [20 \text{ nF}; 40 \text{ nF}]$
- Reference current driving the cell: $I_{REF} = 3 \mu\text{A}$
- Threshold value of the comparator: $V_{REF} = 200 \text{ mV}$

Problem 4

What is the relative error made in the computation of the switching frequency of the comparator of problem 3, when assuming that $\frac{V_{ref}}{R_{bio} I_{ref}} \rightarrow 0$?

References

- [1] C. Stagni, C. Guiducci, L. Benini, B. Riccò, S. Carrara, B. Samorí, C. Paulus, M. Schienle, M. Augustyniak, and R. Thewes, “CMOS DNA sensor array with integrated A/D conversion based on label-free capacitance measurement,” *IEEE Journal of Solid-State Circuits*, vol. 41, no. 12, pp. 2956–2963, 2006.