

EE-517: Bio-Nano-Chip Design

Exercises 11: Current-to-frequency converters, Amperometric detection, Temperature measurement November 24,

November 24, 2020

Problem 1

A *Current-to-Frequency Converter* (I-to-F converter) is implemented for the amperometric detection of a glucose biosensor. An electrochemical cell in a three-electrodes configuration is used, where the *Working Electrode* (WE) is functionalized with glucose oxidase enzyme. Fig. 1 represents the front-end circuit, including the potentiostat that controls the electrochemical cell potentials, and the I-to-F converter that readouts the faradaic current encoded as a pulse width-modulated signal.

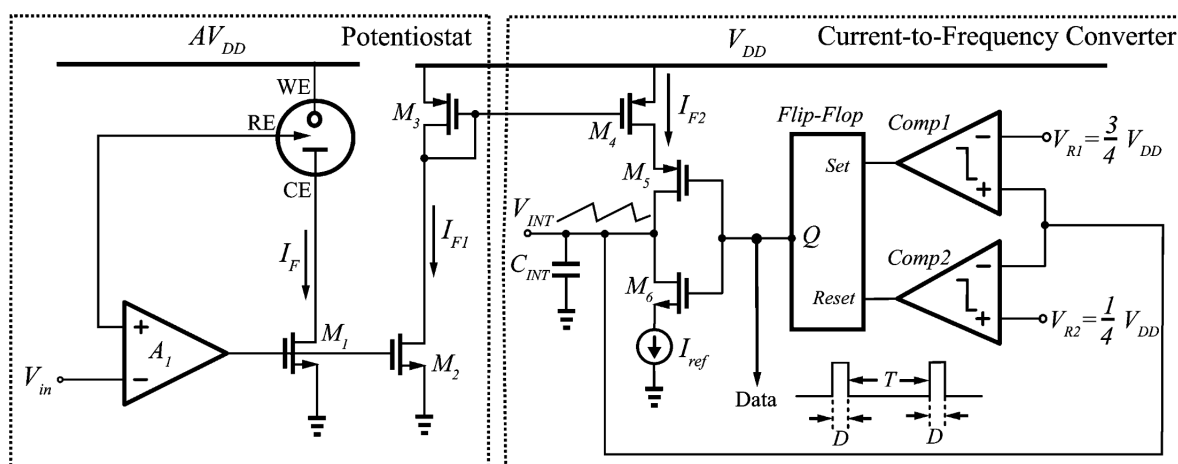


Figure 1: Simplified schematic of potentiostat and current-to-frequency conversion of oxidation currents.

The design specifications are listed hereunder:

- *Oxidation currents:* $I_f \in [1\text{nA}; 1\mu\text{A}]$
- *Supply voltages:* $V_{\text{dd}} = 1.8\text{V}$, $V_{\text{dd}} = 1.8\text{V}$
- *Reference current:* $I_{\text{ref}} = 1\mu\text{A}$
- *Maximum resolvable frequency of the pulsed signal:* $f_{\text{max}} = 100\text{kHz}$

- (a) Describe the functional blocks of the front-end circuitry. Explain how the faradaic current is encoded.
- (b) Size the capacitor C_{INT} to comply with the design specifications.
- (c) Implement circuit modifications to measure reduction currents.

Problem 2

The amperometric measurement of *Cyclophosphamide* and *Dextromethorphan* is considered. These exogenous metabolites are sensed with two *Working Electrodes* (WEs), both functionalized with carbon nanotubes and cytochrome P450 enzyme. An additional WE is functionalized only with carbon nanotubes in order to remove the common-mode capacitive current.

Design a circuit that monitors selectively the two metabolites. Use a three-electrodes electrochemical cell in a grounded-WE configuration. Classical current-to-voltage converters are used. Justify your design choices.

A glucometer usually comprises a temperature sensor for calibration purposes. We consider a *Proportional To Absolute Temperature* (PTAT) circuit implemented with a beta-multiplier topology (see Fig. 2) . Size the transistors operating in weak inversion such that they comply with the design constraints listed hereunder:

- *Operating temperature:* $T = 300\text{K}$
- *Sensing resistor:* $R_s = 100\text{k}\Omega$ at $T = 300\text{K}$
- *Reference bias current:* $I_{\text{ref}} = 1\mu\text{A}$

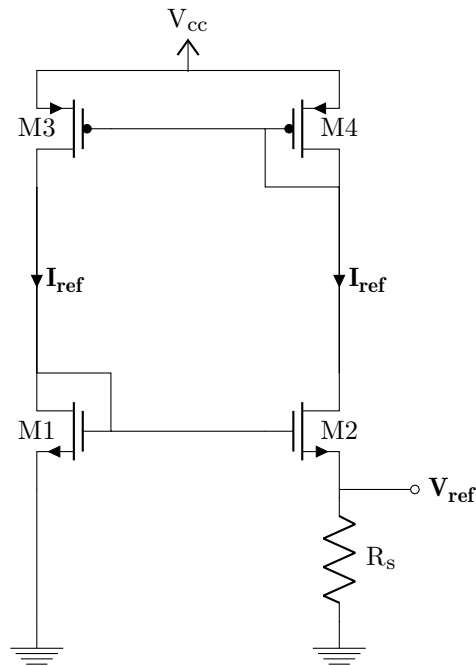


Figure 2: Beta-multiplier implemented for temperature measurement.