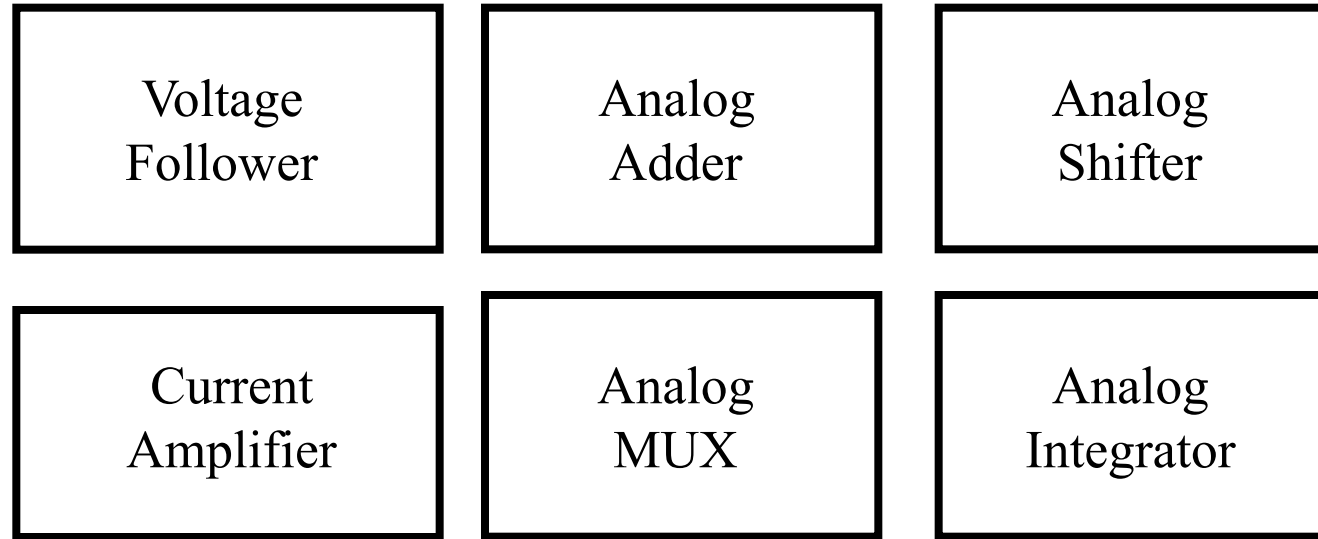


Lecture #10

CMOS Building Blocks:

Addendum on Basic Configurations of Operational Amplifiers

Required Building Blocks




Basic Configurations of Operational Amplifiers

(Book Bio/CMOS: Appendix B)

What's an Op. Amp.?

DIFFERENTIAL AMPLIFIER

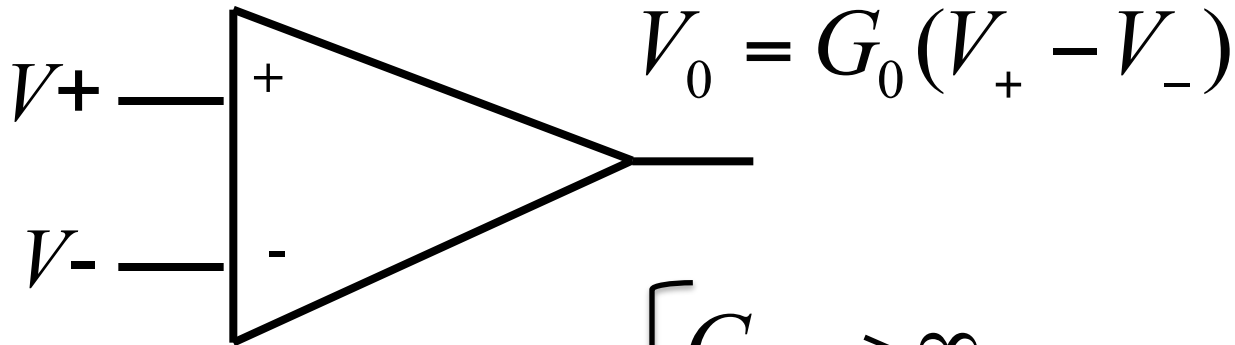

$$V_o = G_o (V_+ - V_-)$$

IDEAL CHARACTERISTICS
Op-amp

$$G_o \rightarrow \infty$$


$$R_i \rightarrow \infty \rightarrow I_i \cong 0$$

$$R_o \cong 0 \rightarrow V_o \neq f(R_L)$$

Basic Configurations with Op. Amp.

- 1. Comparator**
- 2. Inverter Amplifier**
- 3. Non-inverter Amplifier**
- 4. Analog Adder**
- 5. Analog Shifter**
- 6. Analog Integrator/Differentiator**

1. Comparator

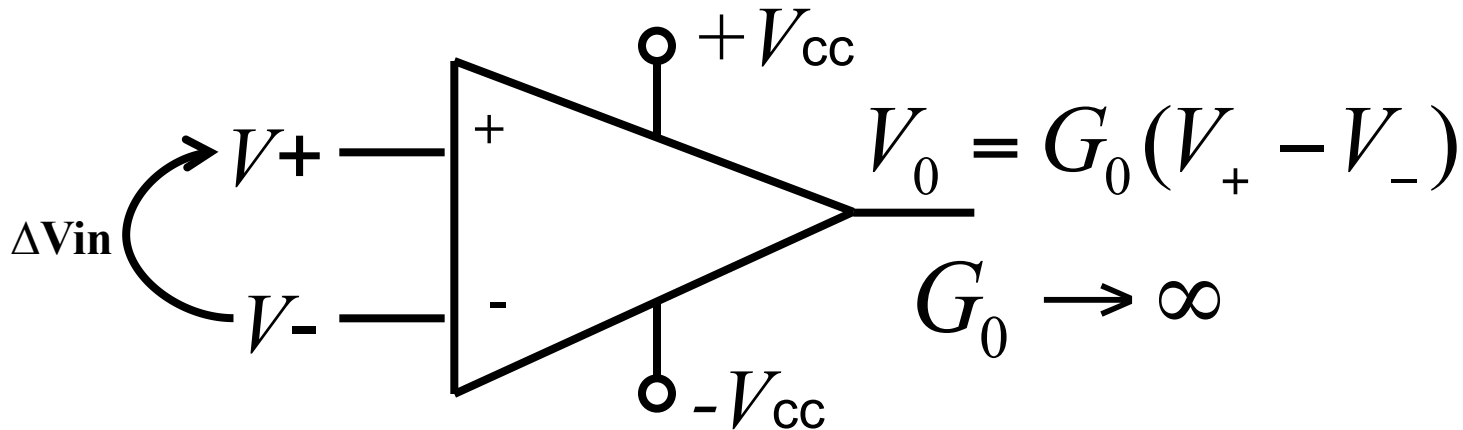


$$\text{if } V_+ > V_- \rightarrow V_0 \rightarrow \infty \rightarrow V_o = +V_{CC}$$

$$\text{if } V_+ < V_- \rightarrow V_0 \rightarrow -\infty \rightarrow V_o = -V_{CC}$$


$$\text{if } V_o \neq \pm V_{cc} \rightarrow \Delta V_{in} = V_+ - V_- \equiv \frac{V_o}{G_0} \cong 0$$

$$\text{Then: } V_- \cong V_+ = 0$$

2. Inverter Amplifier

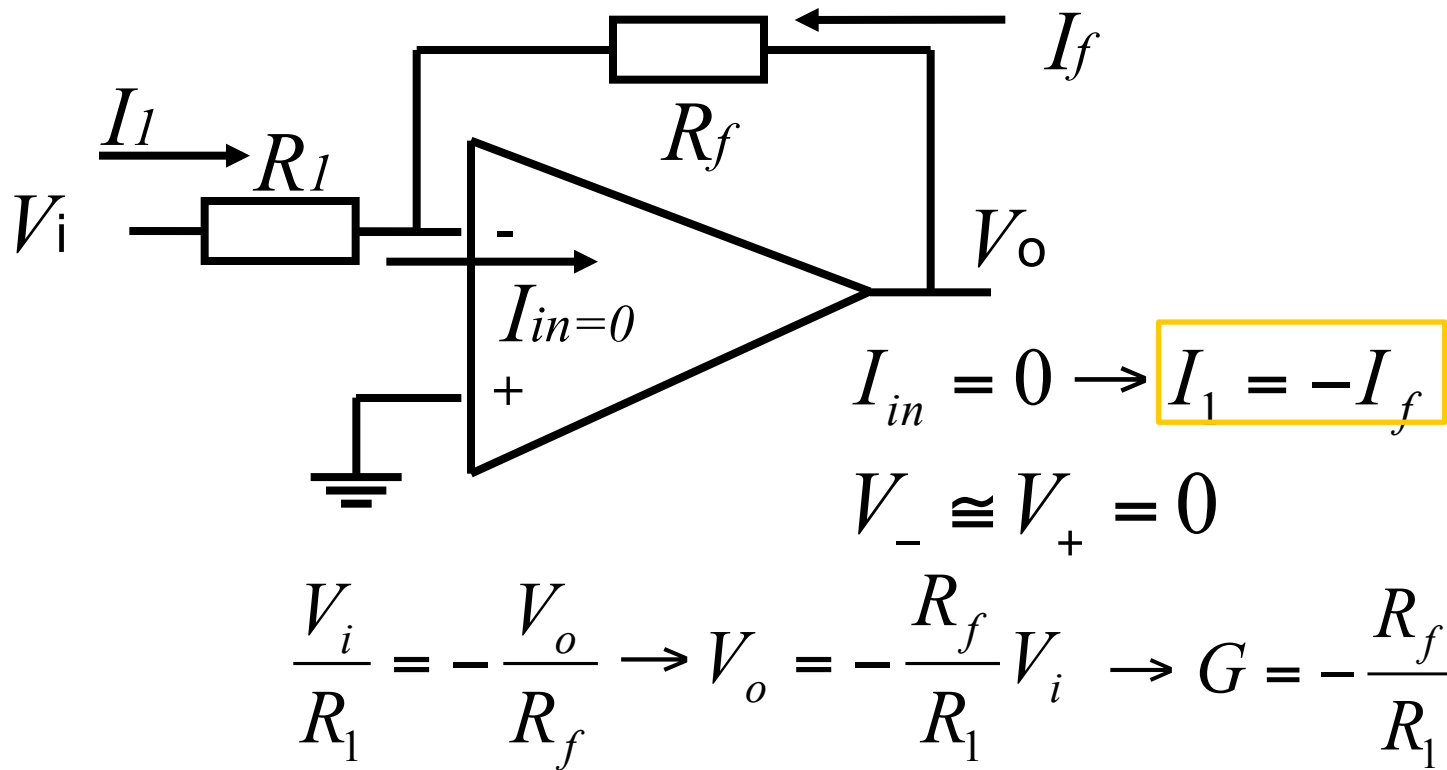


3. Non-Inverter Amplifier

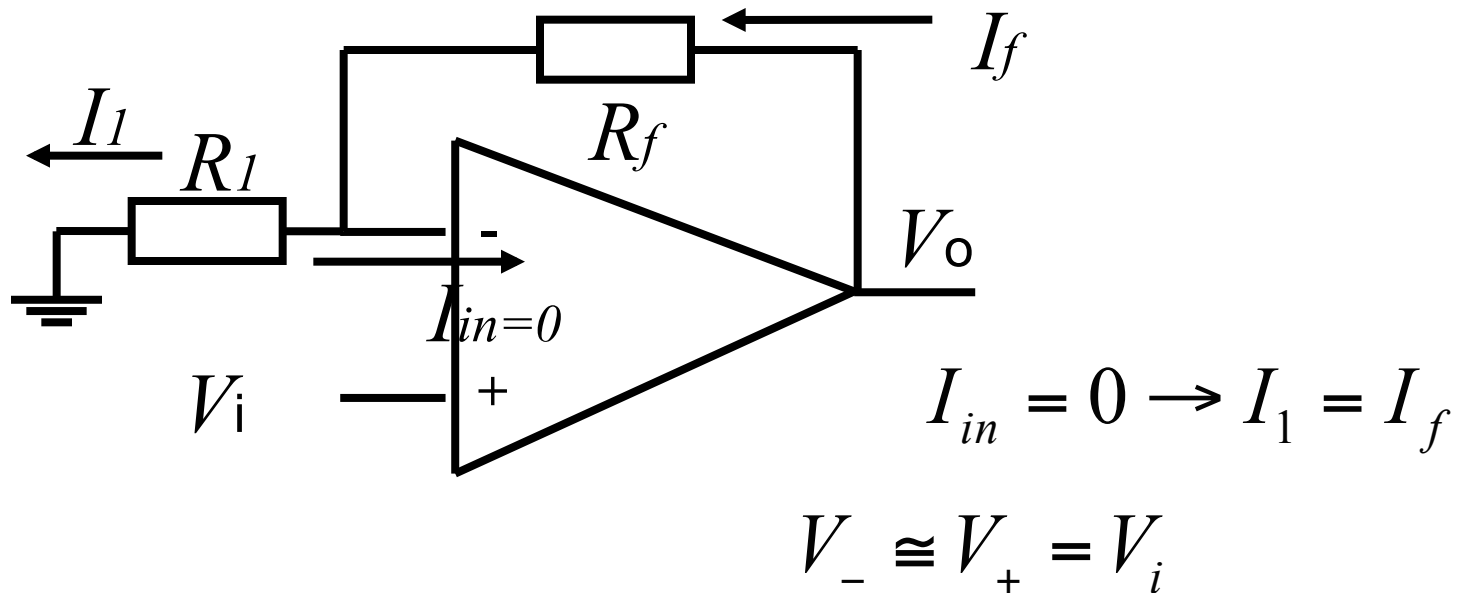

$$\frac{V_i}{R_1} = \frac{V_o - V_i}{R_f} \rightarrow V_o = \frac{R_1 + R_f}{R_1} V_i \quad G = 1 + R_f / R_1$$


4. Voltage Follower

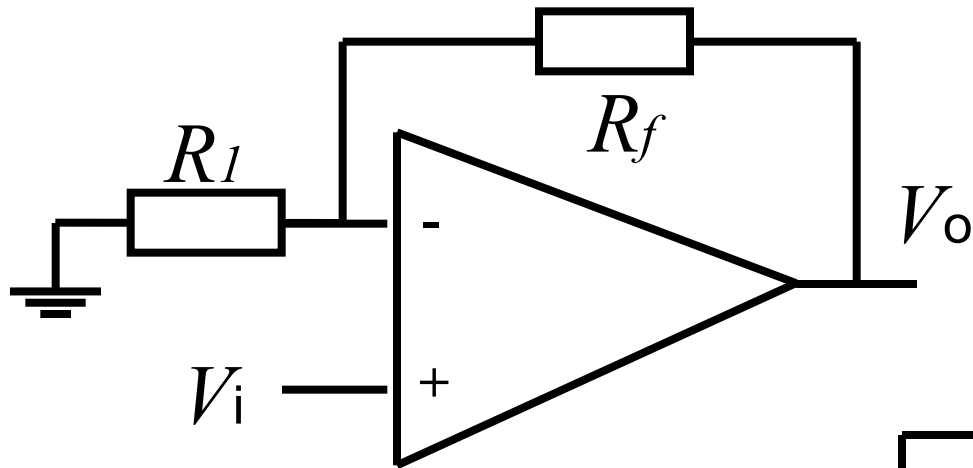


$$R_1 \rightarrow \infty$$

$$R_f = 0$$

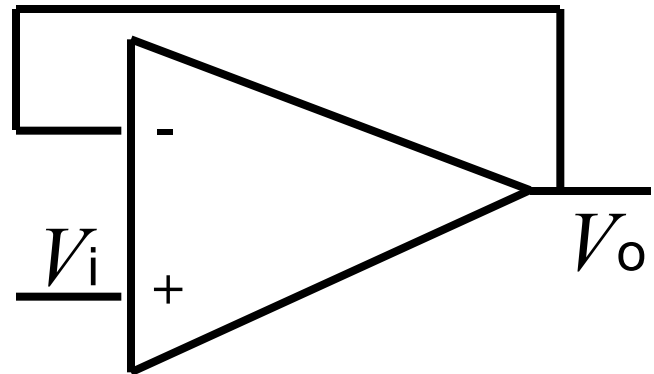
$$V_o = \frac{R_1 + R_f}{R_1} V_i \rightarrow V_o = V_i$$



5. Weighted Analog Adder

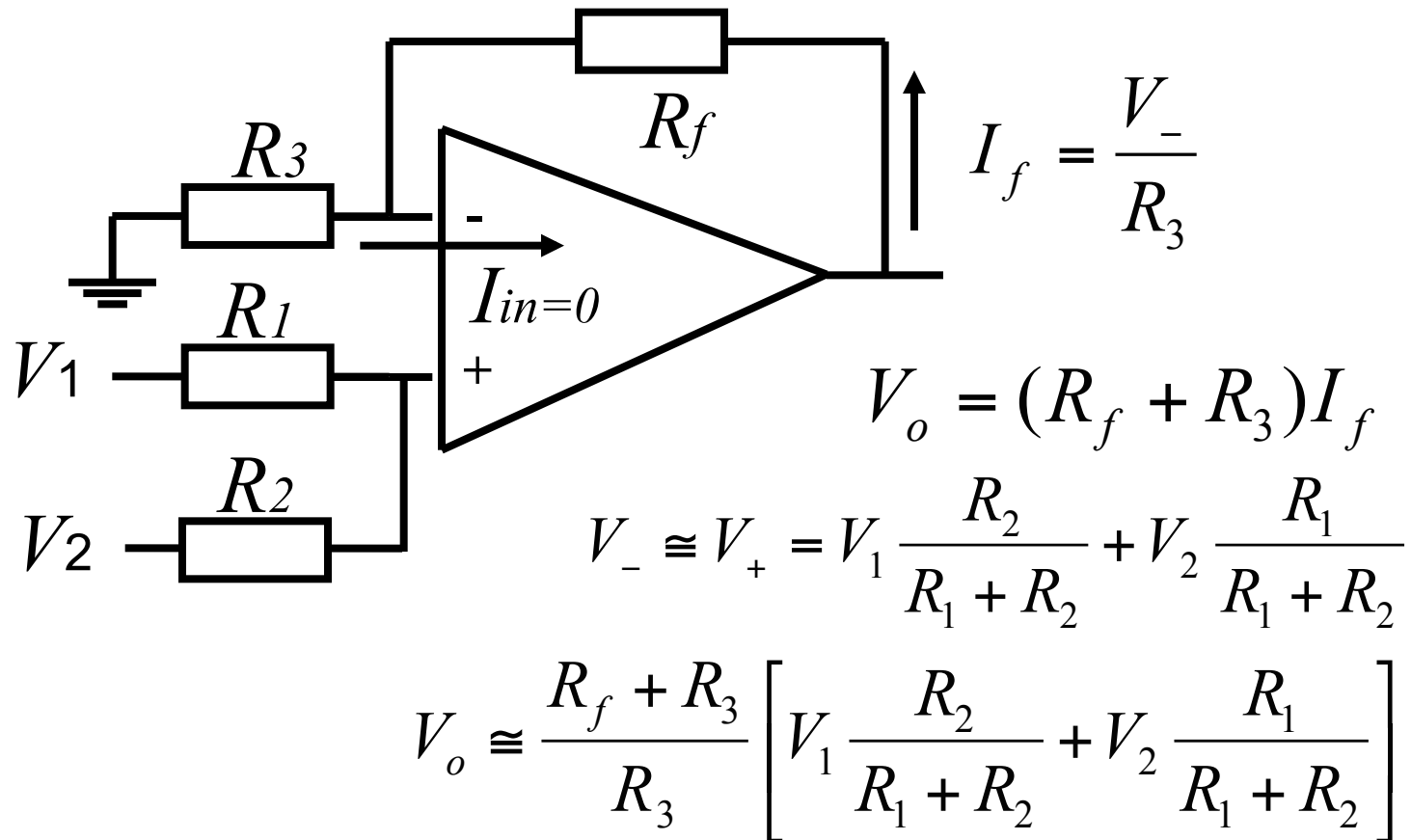


The “pure” Analog Adder

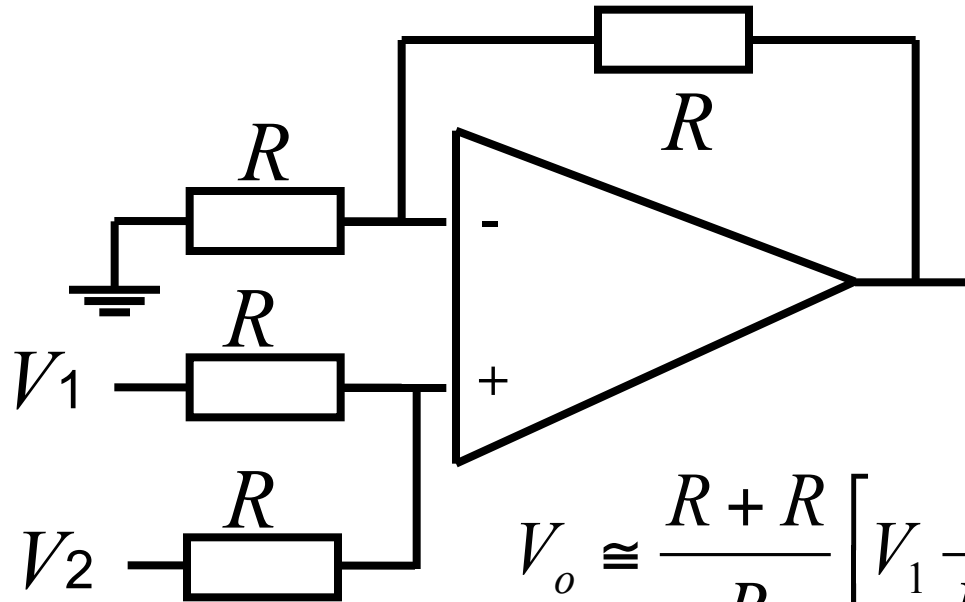

$$V_o \cong \frac{R + R}{R} \left[V_1 \frac{R}{R + R} + V_2 \frac{R}{R + R} \right]$$


$$V_o \cong 2 \left[V_1 \frac{1}{2} + V_2 \frac{1}{2} \right] = V_1 + V_2$$

5. Analog Shifter

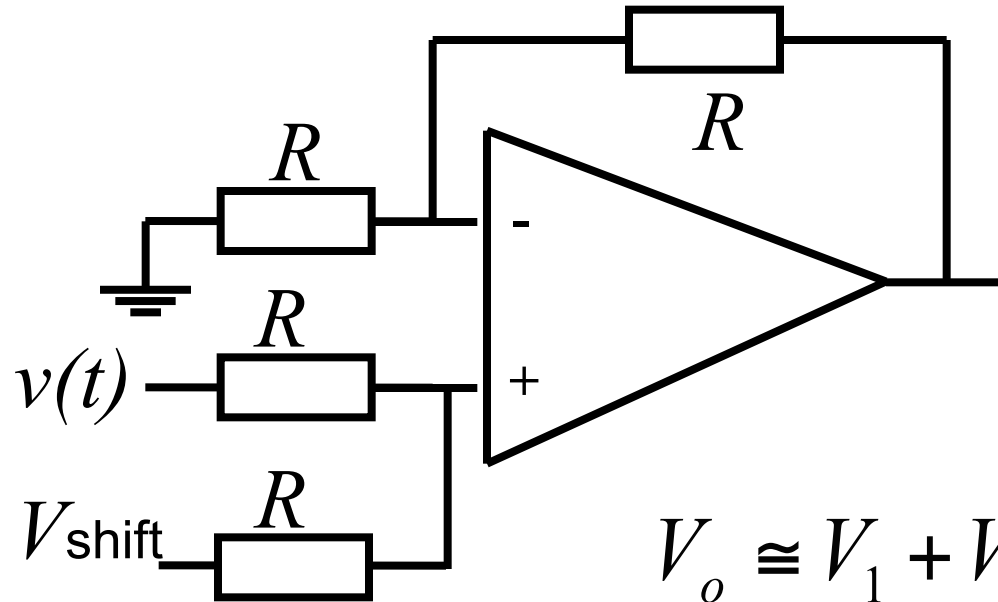


$$V_o \cong V_1 + V_2 = v(t) + V_{\text{Shift}}$$

6. Analog Integrator

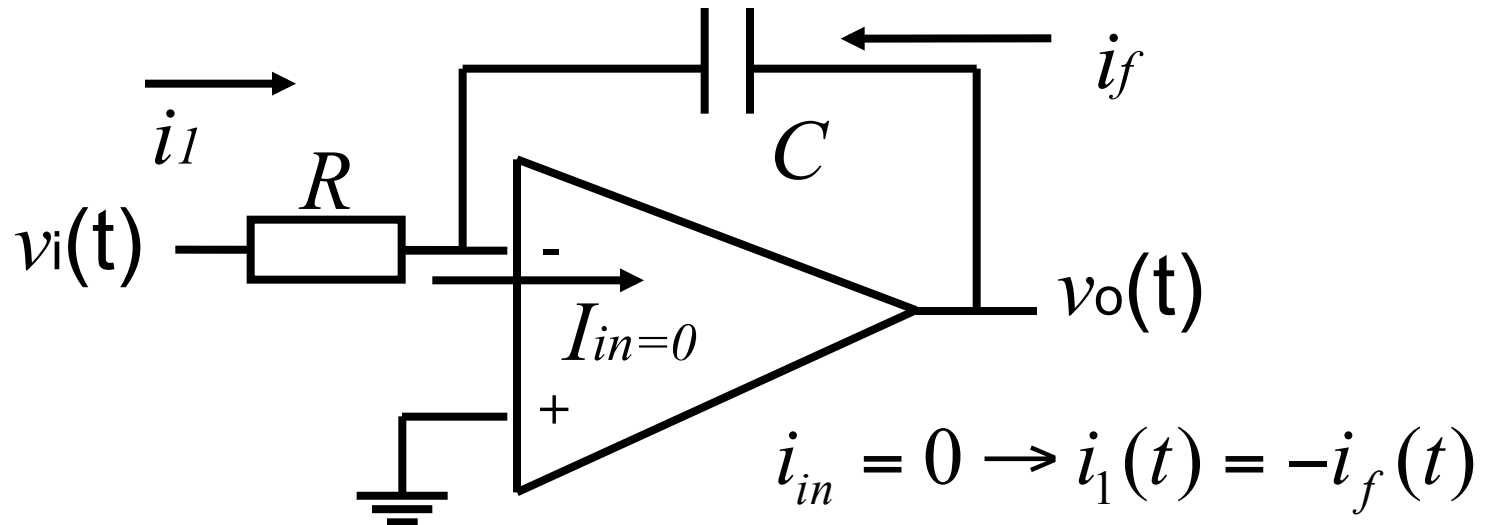


$$\frac{v_i(t)}{R} = -i_f(t) = -\frac{dq}{dt} \overset{\substack{\uparrow \\ q=Cv_o(t)}}{=} -\frac{Cdv_o(t)}{dt} \rightarrow \frac{dv_o(t)}{dt} = -\frac{1}{RC}v_i(t)$$

6. Analog Integrator

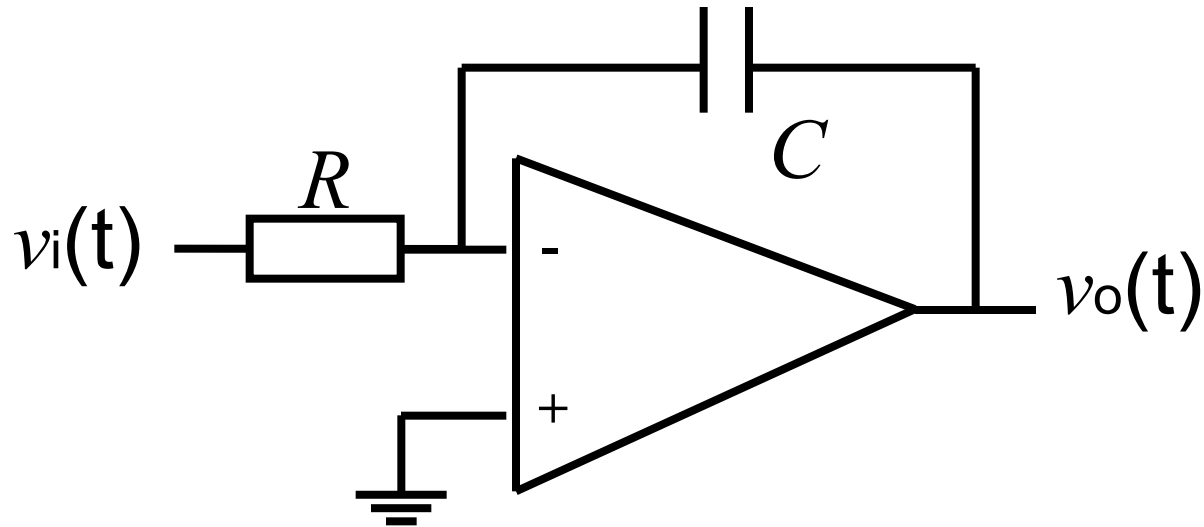


$$\frac{dv_o(t)}{dt} = -\frac{1}{RC} v_i(t) \rightarrow v_o(t) = -\frac{1}{RC} \int_0^t v_i(\tau) d\tau$$

6. Inverting Differentiator

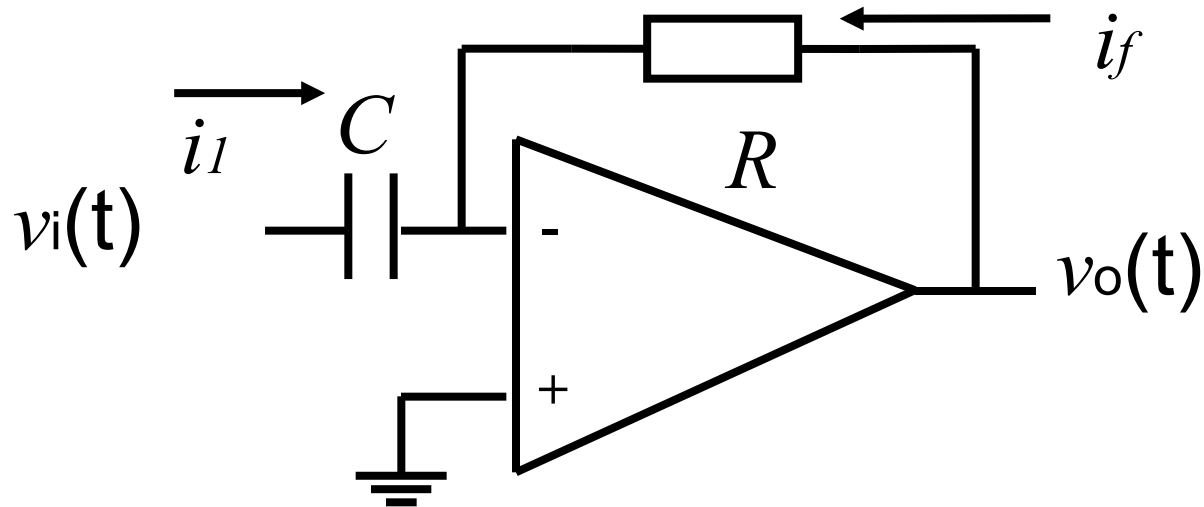

$$\left. \begin{array}{l} i_l = dq/dt \\ i_f = v_o / R \end{array} \right\} \quad i_l = -i_f \quad \rightarrow d[C v_i] / dt = -v_o / R \quad \rightarrow v_o = -RC \, dv_i / dt$$

Required Building Blocks

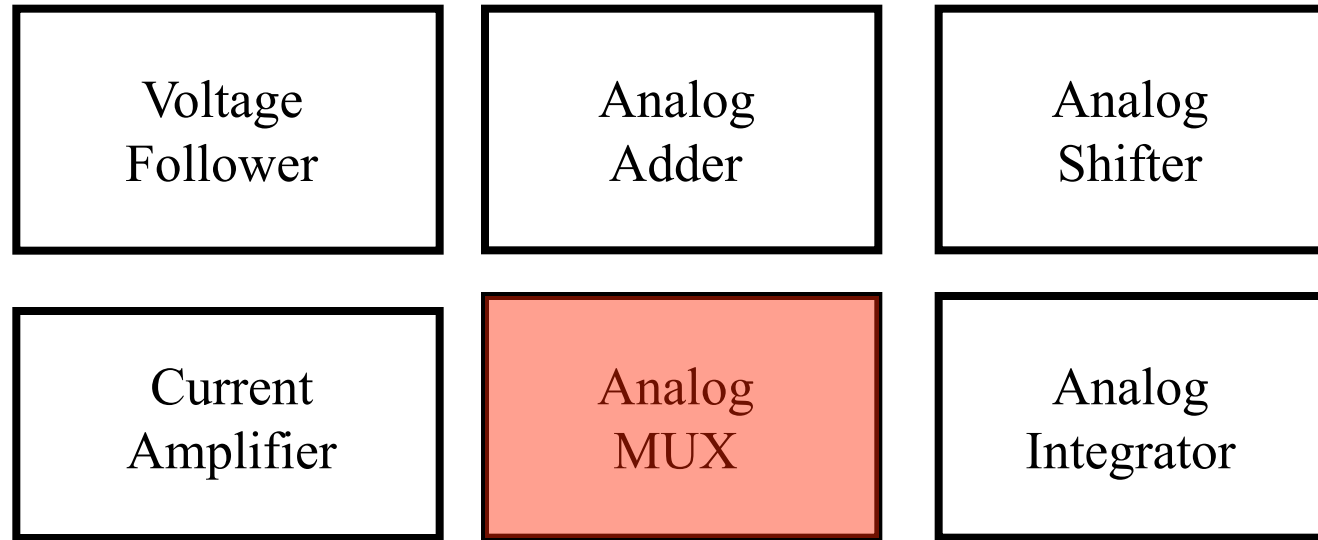

CMOS Operational Amplifiers (OpAmp)

An Analog MUX

