

Addendum


Closed-box and vented-box formulations

H. Lissek

December 21, 2016

Closed-box: definitions

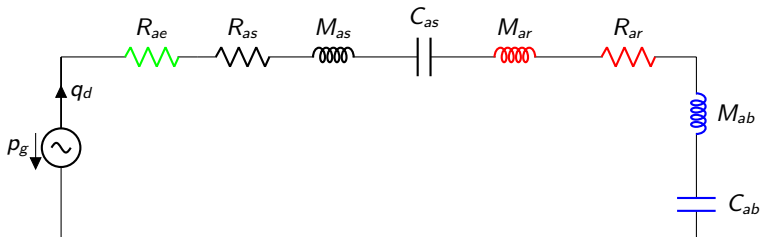Analogue acoustical circuit of a loudspeaker + closed cabinet (Volume V_b) system:



Closed-box: definitions

The components of the analogue scheme are:

Electrical parts	
$p_g = \frac{B\ell U_g}{S_d R_e}$ $R_{ae} = \frac{(B\ell)^2}{S_d^2 R_e}$	source pressure analogue to the source electrical voltage U_g acoustic resistances analogue to R_e, DC resistance of the coil (we neglect here the output resistance of voltage source U_s, as well as the electrical inductance of the coil L_e)
Mechanical parts	
$R_{as} = \frac{R_{ms}}{S_d^2}$ $M_{as} = \frac{M_{ms}}{S_d^2}$ $C_{as} = S_d^2 C_{ms}$	acoustic resistance corresponding to the mechanical resistance of the loudspeaker acoustic mass corresponding to the mechanical mass of the loudspeaker acoustic compliance corresponding to the mechanical compliance of the loudspeaker
Acoustic parts	
$M_{ar} = \frac{8}{3\pi} \frac{\rho a}{S_d}$ $R_{ar} \approx \frac{\rho c}{S_d} \frac{(ka)^2}{4}$ $M_{ab} \approx M_{ar} \approx \frac{8}{3\pi} \frac{\rho a}{S_d}$ $C_{ab} = S_d^2 C_{ms}$	radiation mass of a piston of radius $a = \sqrt{S_d/\pi}$ mounted on a screen radiation resistance of a "pulsating" source of radius a (solid angle 4π) radiation mass inside the cabinet (deformation of particle velocity in the cabinet) acoustic compliance equivalent to the cabinet volume V_b

Closed-box: response in flow velocity

The closed-box loudspeaker is assimilated to a small semi-monopolar (in 2π steradians) source of radius a (radiation resistance $R_{ar} = 2\pi\rho\frac{f^2}{c}$) and flow velocity q_d .

The radiated power is then: $P_a = R_{ar}|q_d|^2$

The power can be derived by expressing q_d as a function of voltage U_g .

Since: $q_d = \frac{p_g}{Z_{ac}}$, where $Z_{ac} = R_{ac} + j\omega M_{ac} + \frac{1}{j\omega C_{ac}}$ with:

$R_{ac} = R_{ae} + R_{as} + R_{ar}$: total losses of the closed-box loudspeaker

$M_{ac} = M_{as} + M_{ar} + M_{ab}$: total acoustic mass

$C_{ac} = \frac{C_{as}C_{ab}}{C_{as} + C_{ab}}$: total acoustic compliance

Then $q_d = \left(\frac{BlU_g}{S_d R_e} \right) \frac{j\omega C_{ac}}{(j\omega)^2 M_{ac} C_{ac} + j\omega R_{ac} C_{ac} + 1}$

Closed-box: response in flow velocity

$$q_d = \left(\frac{B\ell U_g}{S_d R_e} \right) \frac{j\omega C_{ac}}{(j\omega)^2 M_{ac} C_{ac} + j\omega R_{ac} C_{ac} + 1}$$

Defining: $\omega_c = \frac{1}{\sqrt{M_{ac} C_{ac}}}$ and $Q_{tc} = \frac{1}{\omega_c R_{ac} C_{ac}}$ the acoustic resonator's resonance frequency and quality factor, we show that:

$$C_{ac} = \frac{1}{\omega_c R_{ac} Q_{tc}}$$

$$M_{ac} C_{ac} = \frac{1}{\omega_c^2}$$

$$R_{ac} C_{ac} = \frac{1}{\omega_c Q_{tc}}$$

$$\text{And then } q_d = \left(\frac{B\ell U_g}{S_d R_e} \right) \frac{1}{Q_{tc} R_{ac}} \frac{\left(\frac{j\omega}{\omega_c} \right)}{\left(\frac{j\omega}{\omega_c} \right)^2 + \frac{1}{Q_{tc}} \left(\frac{j\omega}{\omega_c} \right) + 1}$$

$$\text{Since } \frac{B\ell}{S_d R_e} = \frac{S_d R_{ae}}{B\ell}, \text{ then we can define } q_c = \frac{B\ell U_g}{S_d R_e Q_{tc} R_{ac}} = \frac{S_d}{B\ell Q_{tc}} U_g$$

$$\text{and finally } q_d = q_c \frac{\left(\frac{j\omega}{\omega_c} \right)}{\left(\frac{j\omega}{\omega_c} \right)^2 + \frac{1}{Q_{tc}} \left(\frac{j\omega}{\omega_c} \right) + 1}$$

Closed-box: response in power



$$P_a = R_{ar} |q_d|^2 = 2\pi\rho \frac{f_c^2}{c} q_c^2 \left| \frac{\left(\frac{j\omega}{\omega_c}\right)}{\left(\frac{j\omega}{\omega_c}\right)^2 + \frac{1}{Q_{tc}} \left(\frac{j\omega}{\omega_c}\right) + 1} \right|^2$$

$$\text{Then } P_a = P_{ac} \left| \frac{\left(\frac{j\omega}{\omega_c}\right)^2}{\left(\frac{j\omega}{\omega_c}\right)^2 + \frac{1}{Q_{tc}} \left(\frac{j\omega}{\omega_c}\right) + 1} \right|^2$$

$$\text{where } P_{ac} = \frac{2\pi\rho}{c} f_c^2 q_c^2$$

Vented-box loudspeaker: definitions

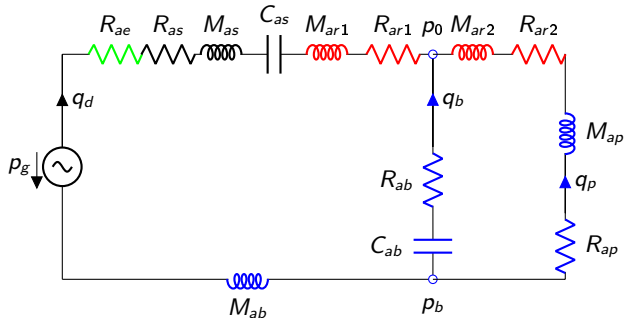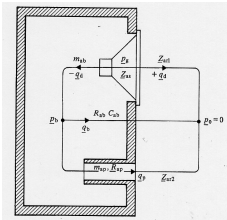Analogue acoustic circuit of a vented-box + loudspeaker system (bass-reflex):



Vented-box loudspeaker: definitions

In the analogue acoustic representation of the vented-box loudspeaker:

- the electrical voltage U_g applied to the loudspeaker terminals is replaced by the equivalent pressure $p_g = \frac{B\ell}{S_d R_e} U_g$.
- the total acoustic impedance of the loudspeaker (excluding the Helmholtz resonator of the vented box) becomes:

$$Z'_{as} = (R_{ae} + R_{as} + R_{ar}) + j\omega (M_{as} + M_{ab} + M_{ar}) + \frac{1}{j\omega C_{as}}$$


$$\approx R_{ae} + R'_{as} + j\omega M'_{as} + \frac{1}{j\omega C_{as}}$$

- the equivalent acoustic impedance of the Helmholtz resonator constituted with volume V_b (acoustic compliance $C_{ab} = \frac{V_b}{\rho c^2}$, we neglect the resistance R_{ab}) and the port of length l_p and cross-section s_p (acoustic mass $M'_{ap} = M_{ap} + M_{ar2} = \rho \frac{a_p + 2\Delta L}{s_p}$, with ΔL the termination correction accounting for the acoustic radiation at each sides of the port $\Delta L \approx \frac{8a}{3\pi}$) reads:

$$Z_{ab} = \frac{j\omega M'_{ap}}{(j\omega)^2 M'_{ap} C_{ab} + 1} = \frac{j\omega M'_{ap}}{\left(\frac{j\omega}{\omega_p}\right)^2 + 1}, \text{ with } \omega_p = \frac{1}{\sqrt{M'_{ap} C_{ab}}}$$

Vented-box loudspeaker: acoustic radiation

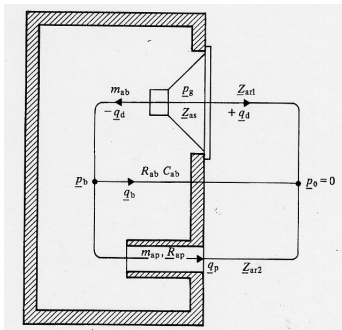The radiated sound power is due to the combination of both the loudspeaker diaphragm and the port radiations. Then, we can consider the flow velocity $q_s + q_p = -q_b$ to process the radiated power, and consider the loudspeaker as a semi-monopole $R_{ar} = \frac{2\pi\rho}{c} f^2$.



The radiated power then writes:
 $P_a = R_{ar} |q_b|^2$,
 and can be derived by analyzing the
 analogue acoustic circuit of the system.

Vented-box loudspeaker: acoustic radiation

We can derive q_b in the analogue acoustic circuit as $q_b = j\omega C_{ab} p_b$, where p_b is the pressure inside the cabinet of volume V_b .

Pressure p_b can be simply deduced by analyzing the “pressure divider”:

$p_b = \frac{Z_{ab}}{Z_{ab} + Z'_{as}} p_g$, then:

$$q_b = \frac{B\ell U_g}{S_d R_e} \frac{j\omega C_{ab} Z_{ab}}{Z_{ab} + Z'_{as}} = \frac{B\ell U_g}{S_d R_e} \frac{(j\omega)^2 C_{ab} M'_{ap}}{\left[\left(\frac{j\omega}{\omega_p} \right)^2 + 1 \right] \left[j\omega M'_{as} + R'_{as} + \frac{1}{j\omega C_{as}} \right] + j\omega M'_{ap}}$$

$$= \frac{B\ell U_g \omega_s}{S_d R_e M'_{as} \omega_s} \frac{(j\omega)^3 C_{ab} M'_{ap} C_{as} M'_{as}}{(j\omega)^4 M'_{as} C_{as} M'_{ap} C_{ab} + (j\omega)^3 M'_{ap} C_{ab} (R_{ae} + R_{as}) C_{as} + (j\omega)^2 [M'_{ap} C_{ab} + M'_{as} C_{as} + M'_{ap} C_{as}] + (j\omega) C_{as} (R_{ae} + R'_{as}) + 1}$$

Reminding $\omega_s = \frac{1}{\sqrt{M'_{as} C_{as}}}$ and $Q_{ts} = \frac{1}{\omega_s R'_{as} C_{as}}$, as well as $\omega_p = \frac{1}{\sqrt{M'_{ap} C_{ab}}}$ it comes:

$$q_b = \frac{B\ell U_g}{S_d R_e M'_{as} \omega_s} \frac{\left(\frac{j\omega}{\omega_s} \right)^3 \frac{\omega_s^2}{\omega_p^2}}{\left(\frac{j\omega}{\omega_s} \right)^4 \frac{\omega_s^2}{\omega_p^2} + \left(\frac{j\omega}{\omega_s} \right)^3 \frac{1}{Q_{ts}} \frac{\omega_s^2}{\omega_p^2} + \left(\frac{j\omega}{\omega_s} \right)^2 \left[\frac{\omega_s^2}{\omega_p^2} + 1 + \frac{C_{as}}{C_{ab}} \frac{\omega_s^2}{\omega_p^2} \right] + \left(\frac{j\omega}{\omega_s} \right) \frac{1}{Q_{ts}} + 1}.$$

Vented-box loudspeaker: acoustic radiation

$$q_b = \frac{B\ell U_g}{S_d R_e M'_{as} \omega_s} \frac{\left(\frac{j\omega}{\omega_s}\right)^3 \frac{\omega_s^2}{\omega_p^2}}{\left(\frac{j\omega}{\omega_s}\right)^4 \frac{\omega_s^2}{\omega_p^2} + \left(\frac{j\omega}{\omega_s}\right)^3 \frac{1}{Q_{ts}} \frac{\omega_s^2}{\omega_p^2} + \left(\frac{j\omega}{\omega_s}\right)^2 \left[\frac{\omega_s^2}{\omega_p^2} + 1 + \frac{C_{as}}{C_{ab}} \frac{\omega_s^2}{\omega_p^2} \right] + \left(\frac{j\omega}{\omega_s}\right) \frac{1}{Q_{ts}} + 1}.$$

Introducing $\alpha = \frac{C_{as}}{C_{ab}}$ et $h = \frac{\omega_p}{\omega_s}$, it comes:

$$q_b = \frac{B\ell U_g}{S_d R_e M'_{as} \omega_s} \frac{\left(\frac{j\omega}{\omega_s}\right)^4 h^{-2}}{\left(\frac{j\omega}{\omega_s}\right)^4 h^{-2} + \left(\frac{j\omega}{\omega_s}\right)^3 \frac{h^{-2}}{Q_{ts}} + \left(\frac{j\omega}{\omega_s}\right)^2 [1 + h^{-2}(1 + \alpha)] + \left(\frac{j\omega}{\omega_s}\right) \frac{1}{Q_{ts}} + 1}.$$

Vented-box loudspeaker: response in power

$$\begin{aligned}
 P_a &= \frac{2\pi\rho}{c} f^2 \left(\frac{B\ell U_g}{S_d \text{Re} M'_{as} \omega_s} \right)^2 \left| \frac{\left(\frac{j\omega}{\omega_s} \right)^3 h^{-2}}{\left(\frac{j\omega}{\omega_s} \right)^4 h^{-2} + \left(\frac{j\omega}{\omega_s} \right)^3 \frac{h^{-2}}{Q_{ts}} + \left(\frac{j\omega}{\omega_s} \right)^2 [1 + h^{-2}(1 + \alpha)] + \left(\frac{j\omega}{\omega_s} \right) \frac{1}{Q_{ts}} + 1} \right|^2 \\
 &= \frac{2\pi\rho}{c} f_s^2 \left(\frac{B\ell U_g}{S_d \text{Re} M'_{as} \omega_s} \right)^2 \left| \frac{\left(\frac{j\omega}{\omega_s} \right)^4 h^{-2}}{\left(\frac{j\omega}{\omega_s} \right)^4 h^{-2} + \left(\frac{j\omega}{\omega_s} \right)^3 \frac{h^{-2}}{Q_{ts}} + \left(\frac{j\omega}{\omega_s} \right)^2 [1 + h^{-2}(1 + \alpha)] + \left(\frac{j\omega}{\omega_s} \right) \frac{1}{Q_{ts}} + 1} \right|^2 \\
 &= P_{ao} \left| \frac{\left(\frac{j\omega}{\omega_s} \right)^4 h^{-2}}{\left(\frac{j\omega}{\omega_s} \right)^4 h^{-2} + \left(\frac{j\omega}{\omega_s} \right)^3 \frac{h^{-2}}{Q_{ts}} + \left(\frac{j\omega}{\omega_s} \right)^2 [1 + h^{-2}(1 + \alpha)] + \left(\frac{j\omega}{\omega_s} \right) \frac{1}{Q_{ts}} + 1} \right|^2
 \end{aligned}$$