

Chapter V-2 - Loudspeakers

Laboratory of Signal Processing LTS2


Fall 2014

Exercise 1. Measurement of loudspeaker small-signal parameters (Thiele-Small)


Let's consider a loudspeaker of unknown small-signal parameters. We will consider in the following only the low-frequency parameters, with small signal excitation.

a . Loudspeaker on a screen

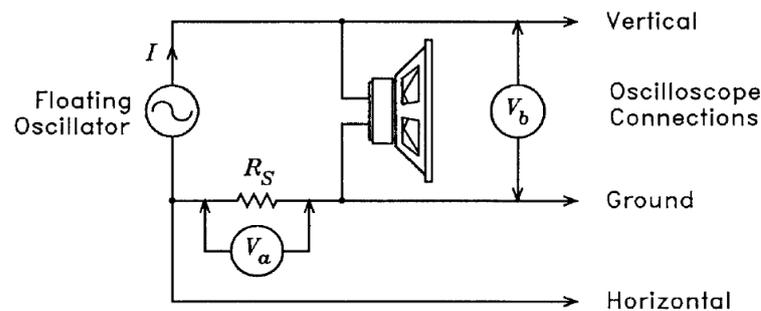Let's first consider the loudspeaker mounted on a screen. We measure the input electrical impedance Z_{hp} at its terminals, as illustrated in the following measurement installation :



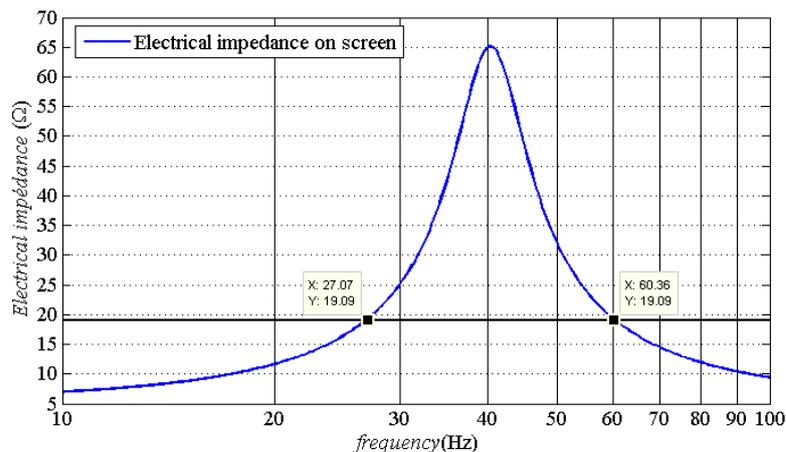The input impedance is deduced from the known measurement resistance $R_s = 1\Omega$, as $\hat{Z}_{hp} = R_s \frac{V_b}{V_a}$ and gives the following result :



- Derive the expression of the input electrical impedance Z_{hp} of the loudspeaker as a function of the DC electrical impedance R_e , the mechanical impedance Z_{ms} (R_{ms} , M_{ms} , C_{ms}) and the force factor $B\ell$.
- Remind the equivalent acoustical scheme of the wall-mounted loudspeaker, and then the equivalent electrical scheme.

- Express the electrical input impedance as a function of the electrical resistances R_e and $R_s = \frac{(Bl)^2}{R_{ms}}$, the resonance frequency $\omega_s = \frac{1}{\sqrt{M_{ms}C_{ms}}}$ and the mechanical quality factor $Q_{ms} = \frac{1}{\omega_s C_{ms} R_{ms}}$.

The measurement of the DC asymptote of \hat{Z}_{hp} gives 5.6Ω .

- What is the value of R_e ?

We also observe that the maximum of \hat{Z}_{hp} occurs at f_s , with a value of 65Ω .


- What is the expression of \hat{Z}_{hp} at its maximum? Is it possible to retrieve a parameter from this measurement ?

We now will derive the value of the mechanical, electrical and total quality factors Q_{ms} , Q_{es} , Q_{ts} . Let's denote $r_0 = \frac{\hat{Z}_{hp,max}}{R_e}$, and introduce $r_1 = \sqrt{r_0}$. We observe on that the curve crosses the line $Z_{hp} = r_1 R_e$ at two frequencies, that we denote f_1 and f_2 .

- Show that $\sqrt{f_1 f_2} = f_s$. Give the values of r_0 and r_1 .
The measurement gives $f_1 = 27Hz$ and $f_2 = 60.4Hz$.

- Determine f_s
- Show that $Q_{ms} = r_1 \frac{f_s}{f_2 - f_1}$
- Show that $Q_{es} = \frac{Q_{ms}}{r_0 - 1}$
- Give the values of Q_{ms} , Q_{es} , and Q_{ts} .

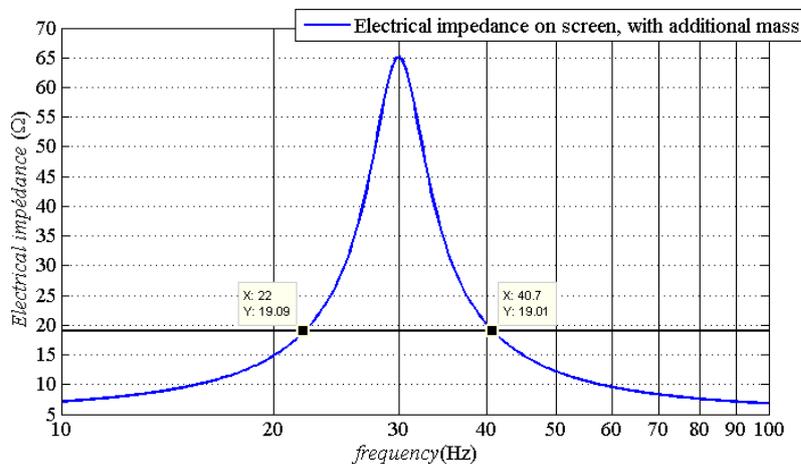- b . Loudspeaker with an additional mass Now we add a mass $M_{add} = 9 \text{ g}$ on the diaphragm, and repeat the same protocol. It gives the following measurement.




The measurement gives the two new frequencies $f'_1 = 22Hz$ and $f'_2 = 40.7Hz$.

- What is the value of the new resonance frequency f'_s
- Show that $\frac{f_s^2}{f'^2_s} = 1 + \frac{M_{add}}{M_{ms}}$
- Deduce M_{ms} and C_{ms}
- Can you deduce R_{ms} and Bl now ?

The remaining parameter is S_d . We should derive it from another measurement.

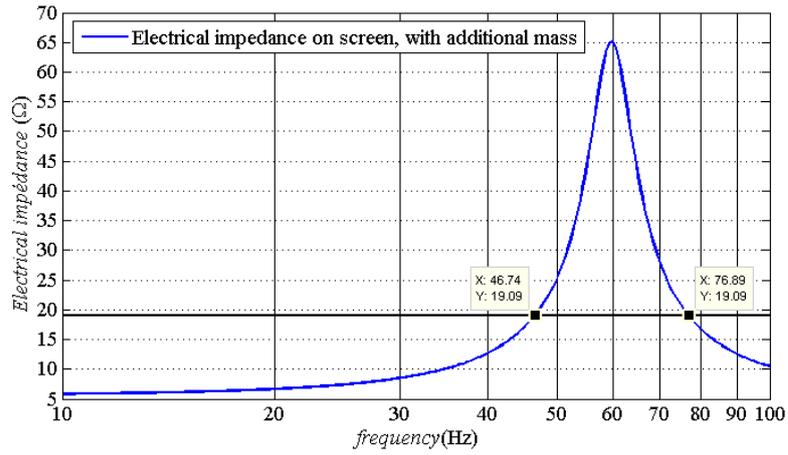- c . Loudspeaker with a closed-box cabinet We now remove the masse M_{add} and close the rear face of the loudspeaker with a sealed cabinet of volume $V_b = 20 \text{ L}$. We do once again the same measurement, which gives :



We introduce the compliance factor $\alpha = \frac{C_{as}}{C_{ab}}$, where $C_{ab} = \frac{V_b}{\rho c^2}$

- Show that the new resonance frequency $f_c \approx \sqrt{1 + \alpha} f_s$
- Show that the new electrical quality factor is $Q_{ec} \approx \sqrt{1 + \alpha} Q_{es}$
- Express α as a function of f_c , Q_{ec} , f_s , Q_{es} . Deduce the value of V_{as}
- Deduce the value of S_d

Numerical values : $\rho = 1.18 \text{ kg.m}^{-3}$, $c = 343 \text{ m.s}^{-1}$