

Exercise 1:

Consider an alkaline water electrolysis cell with a manganese (Mn) coated nickel (Ni) anode and a platinum (Pt) coated Ni cathode submerged in a KOH solution and separated by a porous diaphragm.

Assume the following values:

$$R_{cat} = 0.2 \Omega \text{ cm}^2 \text{ for the cathodic resistance}$$

$$R_{an} = 2 \Omega \text{ cm}^2 \text{ for the anodic resistance}$$

$$R_s = 1 \Omega \text{ cm}^2 \text{ for the serial resistance composed of the diaphragm and the KOH electrolyte}$$


$$C_{cat} = 10 \mu\text{F cm}^{-2} \text{ for the cathodic capacitance}$$

$$C_{an} = 1 \text{ mF cm}^{-2} \text{ for the anodic capacitance}$$

- Construct the equivalent circuit of the electrolysis cell.
- Using the assumed parameters, formulate the total impedance of the system Z_{tot} .
- Using the formula developed in part b, Plot the Nyquist and Bode diagrams for the frequencies ranging from 1 MHz to 10 mHz (use Excel/MATLAB).
- Assume the anode was replaced by a NiFeO_x anode, and the anodic capacitance and resistance are now changed to $C_{an} = 100 \mu\text{F cm}^{-2}$ and $R_{an} = 2 \Omega \text{ cm}^2$ respectively. Replot the Nyquist and Bode diagrams and conclude.

Solution:

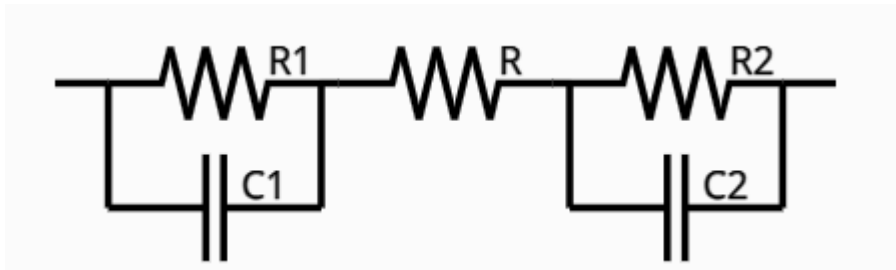- The equivalent circuit is represented as 3 components in a series configuration: anode, cathode and resistance. Both electrodes are each represented as a resistor and a capacitor in parallel, while the KOH solution and the diaphragm are represented as the serial resistance as shown the figure below.



- Let f be the frequency in Hz, then $\omega = 2\pi f$

The capacitive impedance is $Z_C = \frac{1}{i\omega C}$


For the parallel RC circuit of each electrode, $\frac{1}{Z_{RC}} = \frac{1}{Z_C} + \frac{1}{R}$

$$Z_{RC} = \frac{RZ_C}{R+Z_C} = \frac{R \frac{1}{i\omega C}}{R + \frac{1}{i\omega C}} = \frac{1}{\frac{1}{R} + i\omega C}$$


The total impedance of the electrolysis cell is $Z_{tot} = Z_{R_1C_1} + R_s + Z_{R_2C_2}$

$$\text{Therefore } Z_{tot} = \frac{1}{\frac{1}{R_1} + i\omega C_1} + R_s + \frac{1}{\frac{1}{R_2} + i\omega C_2}$$

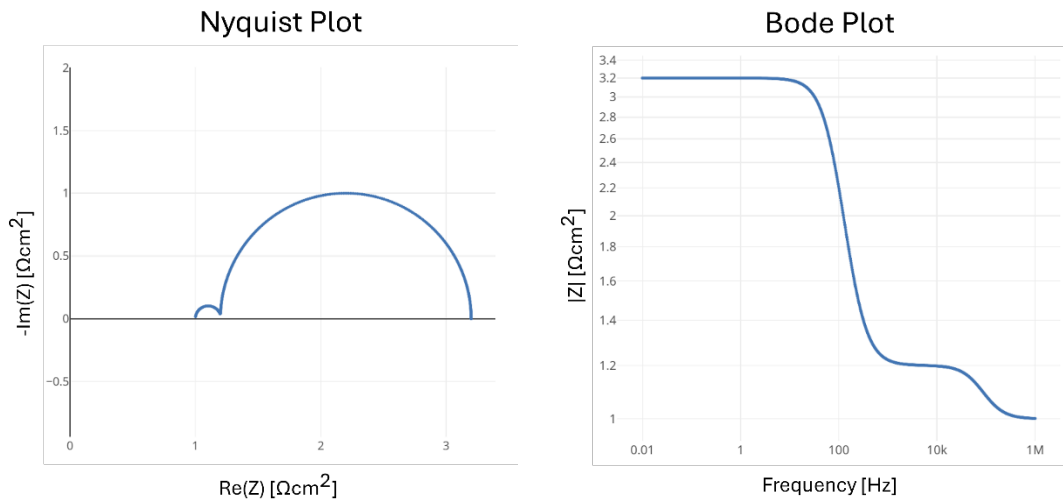- Calculating the impedance over a large range of frequencies, the Nyquist and Bode plots are represented as follows:



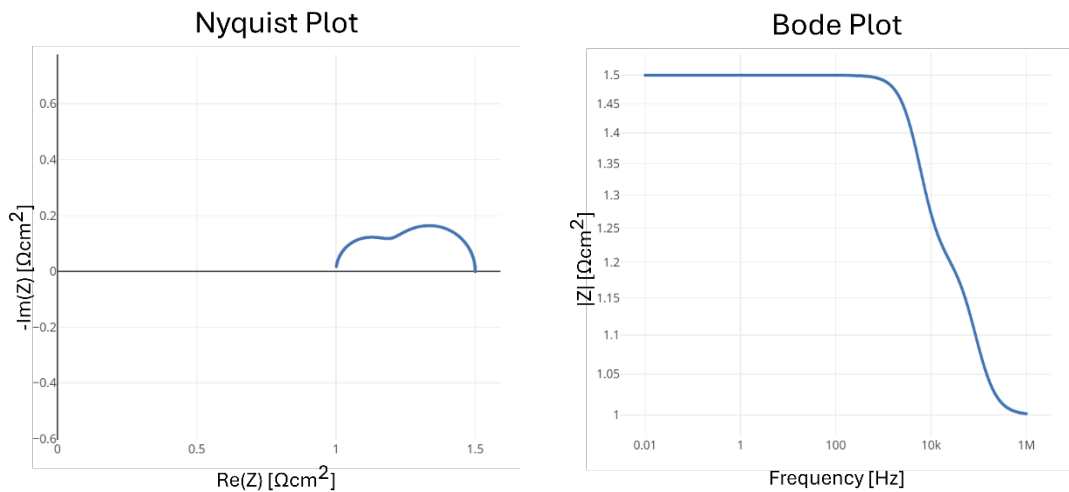d) Changing the anode material results in changes in the anodic capacitance and resistance, therefore the new Nyquist and Bode plots are shown as:



By comparing the Nyquist plots of the two different cells, it can be concluded that when the time constants of the 2 RC circuits are different enough (case 2), the 2 semi-circles are distinct, but when the time-constants are close (case 1), the semi-circles overlap.

Exercise 2:

Exercise about charge/energy density, comparison fuel cell with battery.

- Compute the energy density of a portable polymer electrolyte fuel cell (PEFC), weighing 100 g, including a 30 ml metal-hydride tank which stores 3 g of hydrogen (molar mass $H_2 = 2 \text{ g/mol}$). The working discharge voltage of the fuel cell is admitted to be constant throughout at 0.6 V.
- Same computation as before, but this time with a 30 ml methanol storage tank instead of hydrogen (LHV MeOH = 5 kWh/L).
- If we run a portable electronic device from this fuel cell, consuming on average 10 We, for how long can it run until full discharge from H_2 , respectively methanol, before a refill is necessary ?
- compare to a 100 g battery with an energy density of 200 Wh/kg.

Solutions:

a)

$3 \text{ g H}_2 = 1.5 \text{ mole H}_2$, 2 e^- per mole of H_2 , total 3 mole e^- transferred

Capacity = $3 \text{ mole e}^- \times 96485 \text{ C/mole} = 289455 \text{ C} = 80.4 \text{ A}\cdot\text{h}$

Energy = Capacity \times Voltage = $80.4 \text{ A}\cdot\text{h} \times 0.6 \text{ V} = 48.24 \text{ W}\cdot\text{h}$

Energy density = $48.24 \text{ W}\cdot\text{h} / 100 \text{ g} = 482 \text{ W}\cdot\text{h/kg}$

b)

Energy = $30 \text{ ml} \times 5 \text{ kW}\cdot\text{h} / \text{L} = 0.15 \text{ kW}\cdot\text{h}$

Energy density = $0.15 \text{ kW}\cdot\text{h} / 100 \text{ g} = 1500 \text{ W}\cdot\text{h/kg}$

c)

H_2 : Time = Energy/Power = $48.24 \text{ W}\cdot\text{h} / 10 \text{ W} = 4.82 \text{ hours}$

MeOH : Time = Energy/Power = $0.15 \text{ kW}\cdot\text{h} / 10 \text{ W} = 15 \text{ hours}$

d)

Battery:

Energy = $100 \text{ g} \times 200 \text{ W}\cdot\text{h} / \text{kg} = 20 \text{ W}\cdot\text{h}$

Time = Energy/Power = $20 \text{ W}\cdot\text{h} / 10 \text{ W} = 2 \text{ hours}$