


Neural Interfaces

Mahsa Shoaran
IEM and Neuro-X Institutes





Recap: Neural Amplifier: OTA architecture

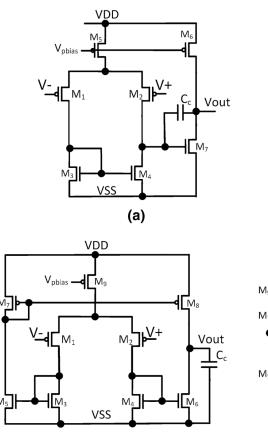- a) 2-stage
- b) Current mirror
- c) Telescopic cascode
- d) Folded cascode



(b)

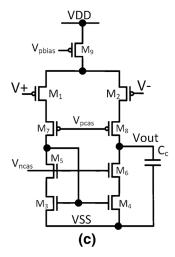

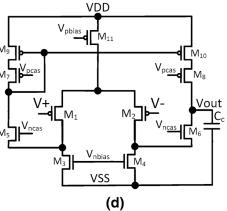






Recap: Noise basics

Thermal noise:

Flicker (1/f) noise:

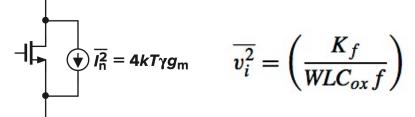

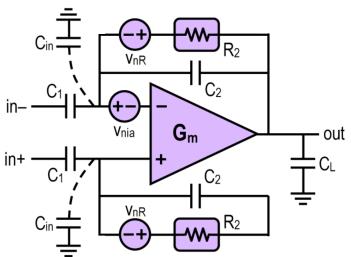

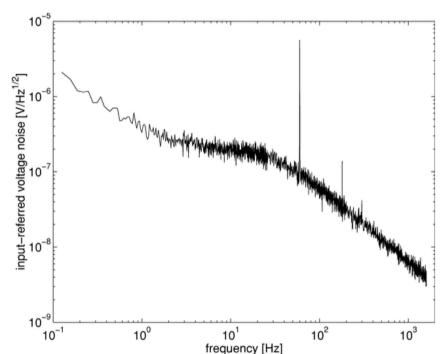


EPFL

Noise Efficiency Factor (NEF)


- V_{rms,in}: The total input-referred noise
- I_{tot}: The total current drain
- V_t: The thermal voltage
- BW: The 3-dB bandwidth of the system
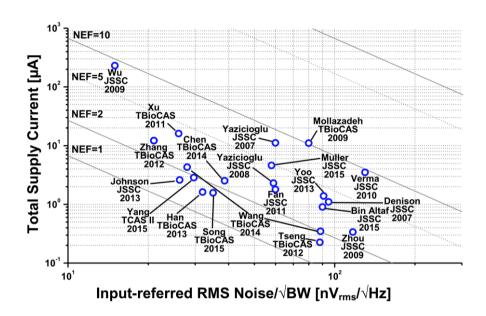
$$NEF = V_{rms,in} \sqrt{\frac{2I_{tot}}{\pi V_t \cdot 4kT \cdot BW}}$$






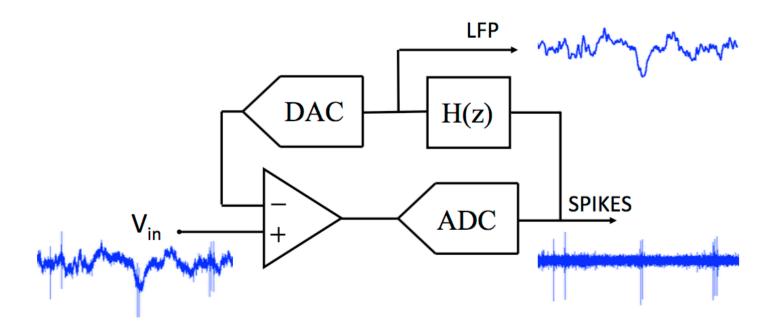DC Offset Cancellation with DC-Coupled Amplifier






Spike and LFP Measurements

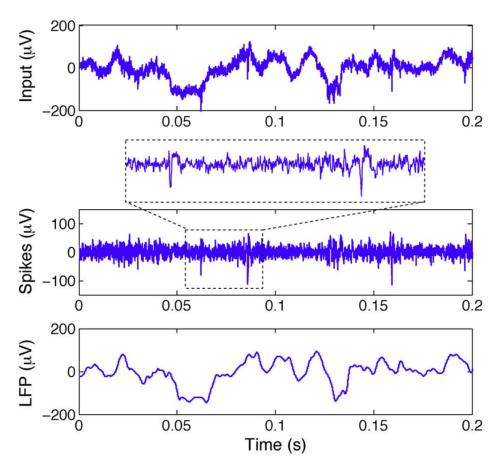




Amplifier gain and input-referred noise

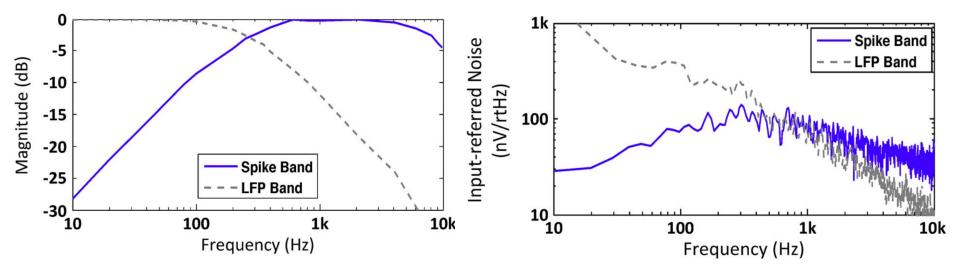



Die photo and performance smmary

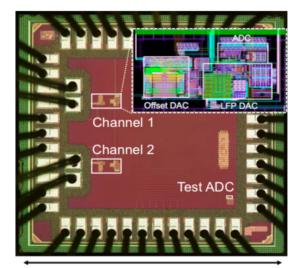


1.2mm

	Power	Area
Merged Amplifier-DAC	4.13μW	0.0037mm ²
Summing Amplifier & DAC	0.66μW	0.0045mm ²
ADC	0.24μW	0.0018mm²
Digital Filters	0.1μW*	0.0017mm ²

	JSSC '09	[4] JSSC '07	[6] BioCAS '07	[7] ISSCC '10	[24] VLSI '11	This Work
Power (µW)	15	42.2	7.56	0.64	43	5.04
IRNoise (μV), Spike	7.0	5.1	3.06	14	2.2	4.9
Spike Bandwidth	5kHz	5kHz	5.3kHz	6.2kHz	10kHz	10kHz
NEF	4.6	9.8	2.67	6.5	5	5.99
NEF ² •V _{DD}	63.48	316.9	20	33.8	30	17.96
IRNoise (μV), LFP	-	-	1.66*	-	14	4.3
LFP Bandwidth	-	-	300Hz*	-	100Hz	300Hz
CMRR (dB)	-	-	66	59	-	75
PSRR (dB)	-	-	75	71	-	64
V _{DD} (V)	3	3.3	2.8	0.8	1.2	0.5
Area (mm²)	0.04	0.16	0.16	0.4**	0.2**	0.013
Technology	0.35µm	0.5µm	0.5µm	0.13µm	0.13µm	65nm
Blocks included in comparison	LNA, BPF	LNA, BPF	LNA, BPF	LNA, BPF	LNA, BPF, ADC	LNA, BPF, ADC



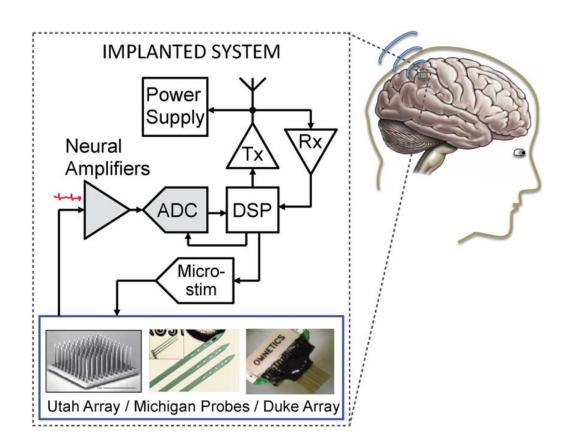
Circuit Block Diagram of a Neural Interface: ADC





Neural Interface: ADC and Compression

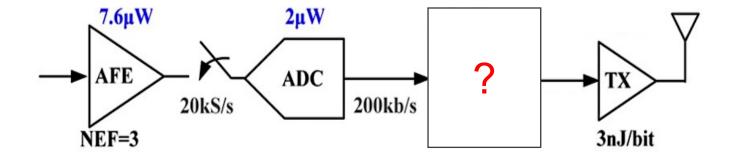
 The typical circuit blocks used in sensors for medical monitoring and their associated energy cost and power consumption





Neural Interface: ADC and Compression

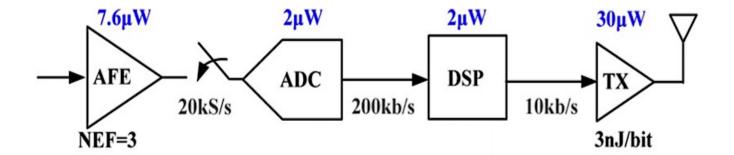
 The typical circuit blocks used in sensors for medical monitoring and their associated energy cost and power consumption




EPFL

Analog to Digital Conversion

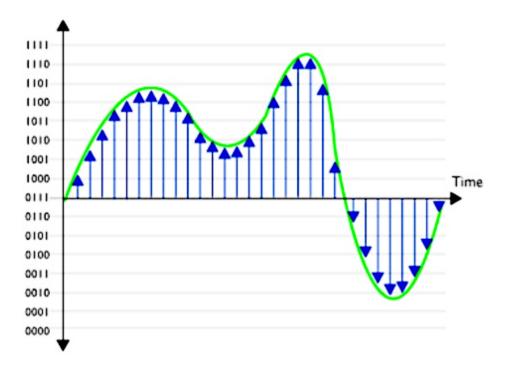After amplification and filtering, signal is digitized (sampled at a fixed rate)



Analog and Digital Signals

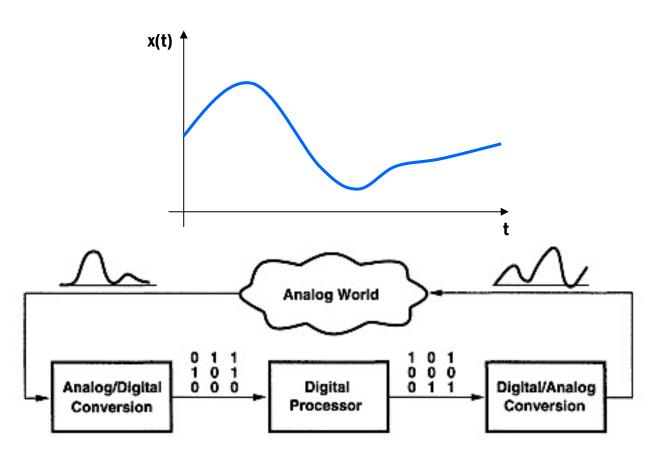



Digital Data Acquisition

Foundation: Shannon/Nyquist sampling theorem




"if you sample densely enough (at the Nyquist rate), you can perfectly reconstruct the original analog data"



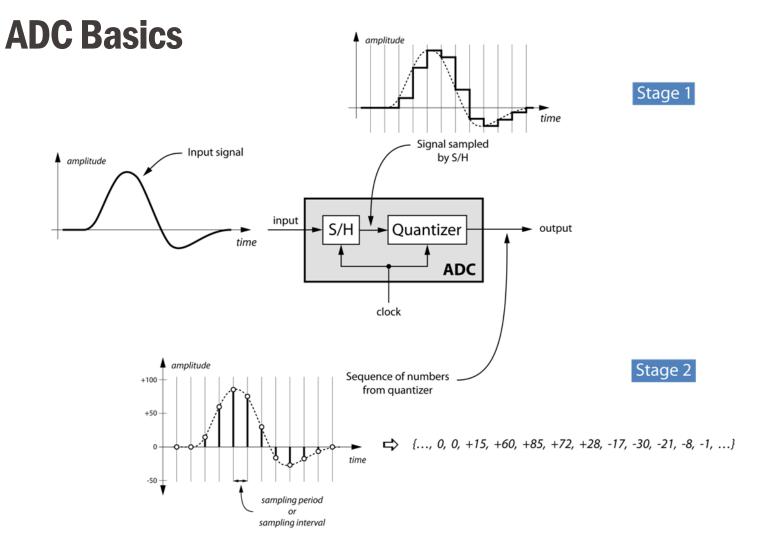A bandlimited analog signal can be perfectly reconstructed from a sequence of samples if the sampling rate fs exceeds 2f_{max} samples per second, where f_{max} is the highest frequency in the original signal.







EPFL

ADC Operation

Sampling and Holding

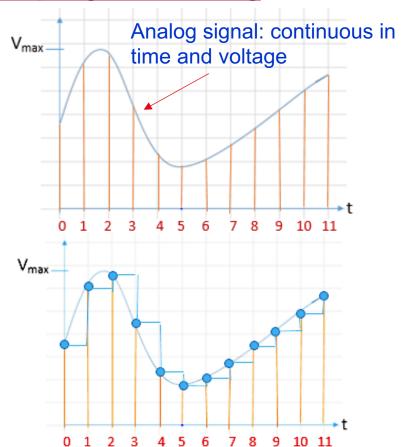


Quantization and Encoding

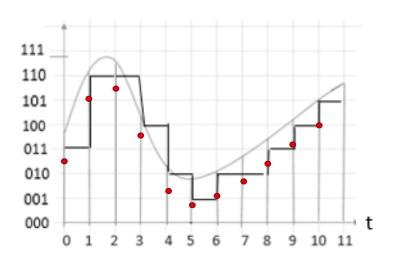

Sequence of digital codes: 011, 110, 110, 100, 010, 001, 001, 010, 011, 100, 101, ...




The least significant bit (LSB)

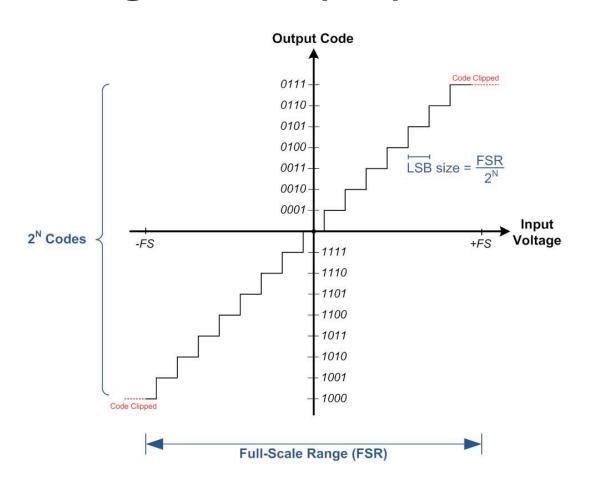



3-bit flash (parallel) ADC

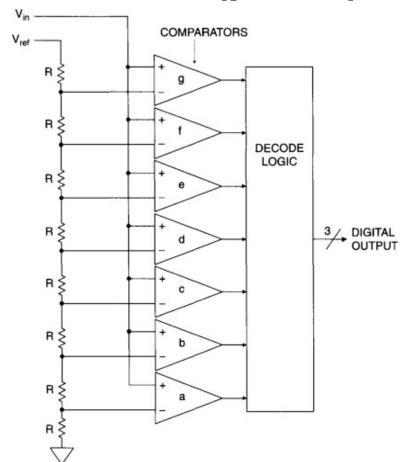

- An n-bit flash ADC uses 2ⁿ-1 comparators, 2ⁿ resistors and a decode logic.
- Pros: the fastest type of ADC.
- Cons: limited resolution, expensive, large power consumption and low accuracy
- Applications: Data acquisition, sampling oscilloscope and highdensity disk drives.



Successive-approximation-register (SAR) ADC

